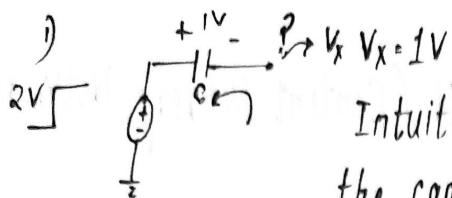


NETWORK ANALYSIS

lecture - 9a Analysis of Capacitor ckt. with current inputs



Intuitively we can say that there is no path for the capacitor to get charged/discharged.

$\frac{1}{I_0} \Rightarrow \frac{1}{0}$: Potential across the capacitor is constant.


Charge transferred from the voltage source is zero.

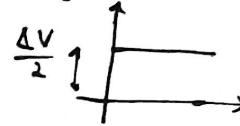2)


$$\begin{aligned} Q &= CV \\ Q &= (0)(V) = 0 \end{aligned}$$



Steady state voltages in the presence of an application of an impulse current.



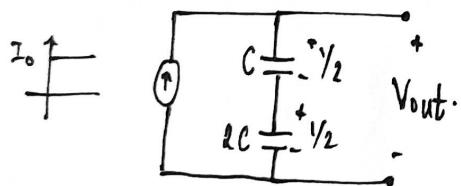3) Behavior of Capacitor voltages on constant current



$$V(t) = V(0) + \int_0^t i(t) dt$$

$$V_C = \frac{1}{2} + \int_0^t \frac{I_0}{C} dt$$


$$= \frac{1}{2} + \frac{I_0}{C} t$$

$$V_{2C} = \frac{1}{2} + \frac{I_0}{2C} t$$


$$V_{out} = V_C + V_{2C}$$

$$= 1 + I_0 t \left(\frac{1}{C} + \frac{1}{2C} \right)$$
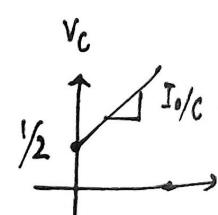
$$\boxed{V_{out} = 1 + \frac{I_0 t}{(C_{eq})}}$$



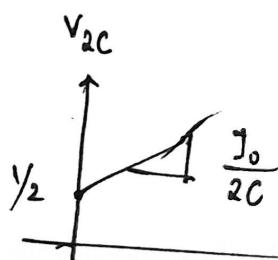
$$\frac{I_0}{C_{eq}} = \frac{I_0(3)}{2C}$$




4) find steady state Voltage across capacitors.

Apply superposit:


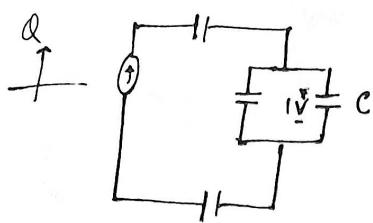


- i) Find how the 1V will distribute across other caps.
- ii) Then find effect of current.


(1)

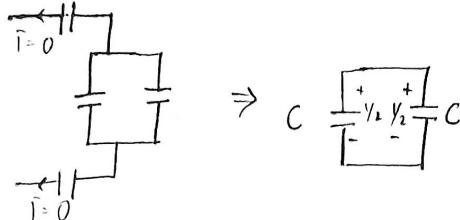

(2)

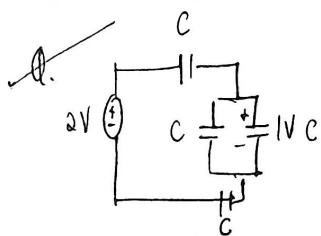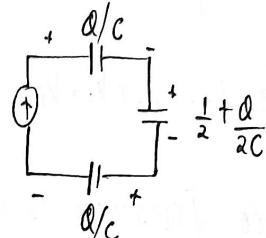

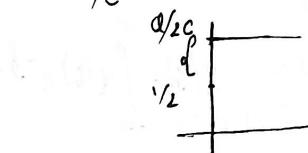
$$\frac{1}{2} + \frac{\Delta V}{2} = 0.8$$



$$\frac{\Delta V}{2} = \frac{3}{2} \quad \boxed{\Delta V = 0.6}$$

Lecture 10:- 1st order systems & Frequency domain analysis of capacitors.

Suppose I/P is step

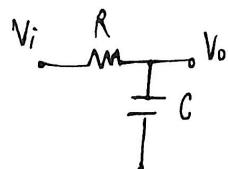

$$C \frac{dV_o}{dt} = \frac{V_i - V_o}{R}$$

$$C \frac{dV_o}{dt} + V_o = V_x u(t)$$

$$RC \frac{dV_o}{dt} + V_o = V_i$$

$$V_{f0}(t) = V_o(\infty) (1 - e^{-t/\tau}) u(t)$$

$$C \frac{dV_o}{dt} + V_o = V_i$$

$$V_o(t) = V_o(\infty) (1 - e^{-t/\tau}) + V_o(0) e^{-t/\tau}$$

$$V_i = 0$$

$$V_o(t) = V_o(\infty) + (V_o(0) - V_o(\infty)) e^{-t/\tau}$$

$$C \frac{dV_o}{dt} + V_o = 0$$





$$V_o(t) = V_o e^{-t/\tau} \rightarrow \text{Natural response}$$

$$V_{no}(t)$$

(without I/P)

$V_{fo}(t) \rightarrow$ Forced

$$V_o(t) = V_{no}(t) + V_{fo}(t)$$

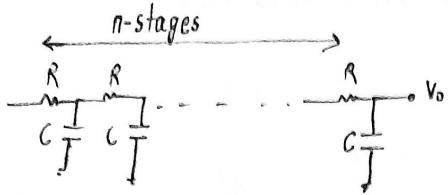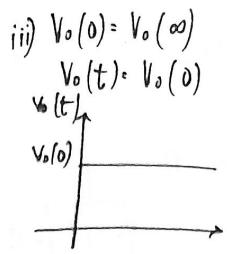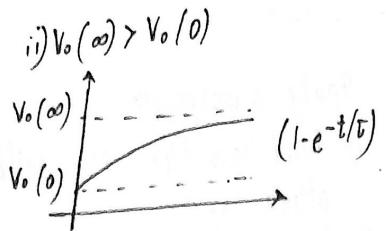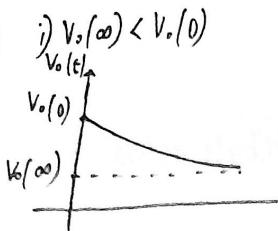

$$\frac{d^n V_o}{dt^n} + \dots + V_o = V_i$$

Laplace Transform is used

$$X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$

$$x(t) \rightarrow X(s)$$

$$f(t) \rightarrow 1$$

$$f'(t) \rightarrow sX(s)$$

$$u(t) \rightarrow 1/s$$

$$\int x(t) dt \rightarrow \frac{X(s)}{s}$$

$$e^{-at} u(t) \rightarrow \frac{1}{s+a}$$

$$T \frac{dV_o}{dt} + V_o = V_i$$

$$Ts V_o(s) + V_o(s) = V_i(s)$$

$$V_i = V_x u(t)$$

$$\boxed{V_o(s) = \frac{1}{(1+sT)} V_i(s)}$$

$$V_o(s) = \frac{1}{(1+sT)} \frac{V_x}{s}$$

$$= V_x \left[\frac{1}{s} - \frac{1}{1+sT} \right]$$

$$= V_x \left[\frac{1}{s} - \frac{1}{s+T} \right]$$

$$= V_x \left[u(t) - e^{-t/T} u(t) \right]$$

$$\boxed{V_o(t) = V_x u(t) [1 - e^{-t/T}]}$$

$$\frac{V_o(s)}{V_i(s)} =$$

$$T \frac{dV_o}{dt} +$$

$$(sT+1)$$

$$\frac{V_o}{V_i}$$

$$\boxed{\frac{V_x}{V_i}}$$

$$20.$$

$$V_x$$

$$\frac{V_o(s)}{V_i(s)} = H(s) = \frac{1}{1+sT}$$

$$H(s)|_{s=w_p} \rightarrow \infty$$



$$H(s)|_{s=w_2} \rightarrow \infty$$

poles should lie on LHS of s-plane

$$T \frac{dV_o}{dt} + V_o = \frac{1}{w_c} \frac{dV_i}{dt} + V_i$$

$$(sT+1)V_o(s) = (1+s/w_2)V_i(s)$$
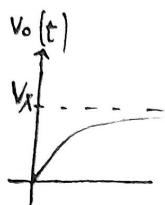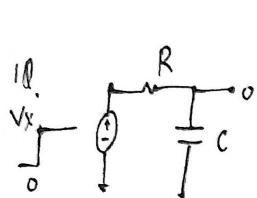
$$\frac{V_o}{V_i} = \frac{(1+s/w_2)}{(sT+1)} \quad s = -w_2 \\ s = -1/T$$




$$i = \frac{V_x - V_o(t)}{R}$$

$V_o(t)$ gradually rises, so the slope of current decs. At $t=0$; Cap. behaves as short ckt.

At $t=\infty$; Cap. \rightarrow open ckt.

$$\text{Also, } H(s) = \frac{1}{1+sT}$$

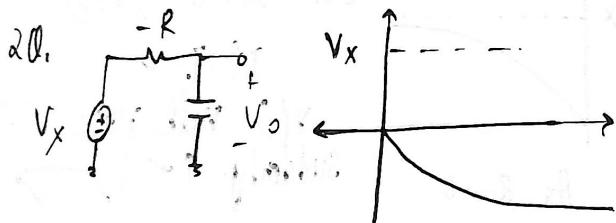$\therefore s_p = -1/T \rightarrow \text{Stable.}$



$$i = -\frac{(V_x - V_o)}{R}$$

As V_o rises, $V_i \rightarrow -\infty$.

Hence, unstable $s_p = 1/T$

$$\frac{V_o}{V_i} = H(s)$$

$$V_o(t) = V_o(\infty) (1 - e^{t/T})$$

$$V_o = H(s) V_i \rightarrow \boxed{V_o = H(s)}$$

Fourier Transform

$$x(t) = \sum c_k e^{jk\omega_0 t}$$

D.C.

$$\omega = 0 \rightarrow |Z_c(\omega)| \rightarrow \infty$$

Open ckt.

$$x(t) = \int_{-\infty}^{\infty} x(f) e^{j2\pi f t} df$$

$$\omega = \infty \Rightarrow |Z_c(\omega)| \rightarrow 0.$$


$$H(j\omega) = A(\omega) e^{j\phi(\omega)}$$

Short ckt


For a sudden step I/P, capacitor behaves as short circuit.

Lecture II - Energy loss in charging and discharging of capacitor cts.

$$\frac{1}{T} e^{-t/T} u(t)$$

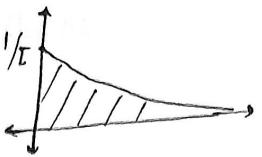

$$T \rightarrow T/2$$

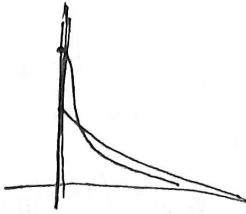


$$-\infty \int \frac{1}{T} e^{-t/T} u(t) dt$$

$$\frac{1}{T} \int_{-\infty}^{\infty} e^{-t/T} u(t) dt = 1.$$

$$T \rightarrow 0 \Rightarrow \text{Impulse}$$

$$\frac{1}{T} e^{-t/T} u(t) \rightarrow \delta(t) \text{ as } T \rightarrow 0$$

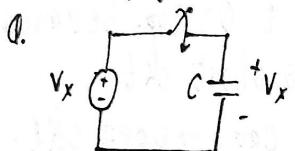
Charging of capacitors:- W.D. by Voltage source:-



$$V_x Q = V_x^2 (C)$$


$$\text{Energy stored in capacitor} = \frac{1}{2} C V_x^2$$

Assume finite resistance of switch R.

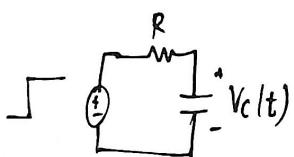

$$V_c(0) = 0$$

$$V_c(\infty) = V_x$$

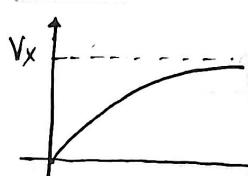

$$V_c(t) = V_x (1 - e^{-t/T}) u(t)$$

$$\text{If } T = 0$$

V_c will rise
Suddenly \uparrow

As $R \rightarrow 0$

$$P_R(t) = \frac{1}{2} C V_x^2 \frac{2}{T} e^{-2t/T} u(t)$$

$$P_R(t) = \frac{1}{2} C V_x^2 \delta(t) \quad \rightarrow \text{Energy will be finite}$$

$$V_R(t) = V_x u(t) - V_x (1 - e^{-t/T}) u(t)$$

$$= V_x e^{-t/T} u(t)$$

$$i_R(t) = \frac{V_x e^{-t/T} u(t)}{R}$$

$$P_R(t) = \frac{V_x^2}{R} e^{-2t/T} u(t) \rightarrow \text{Decays twice as fast}$$

$$P_R(t) = \frac{1}{2} \frac{V_x^2}{RC} e^{-2t/T} u(t)$$

$$E = \int P_R(t) dt$$

Current in the resistor is an impulse.


$$\frac{1}{2} C V_x^2$$

Impulse of power is dissipated across the resistor.

$$\frac{1}{2} C V_x^2$$

ET
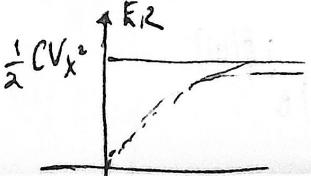
$$= \frac{1}{2} C V_x^2 \frac{2}{T} e^{-2t/T} u(t)$$



$$= \frac{1}{2} C V_x^2$$

Discharging

$$V_x + \frac{1}{C} \int u(t) dt$$

$$V_x$$

& Charge s

$$F = \frac{1}{2} C V^2$$

$$V_x + \frac{1}{C} \int u(t) dt$$

$$V_1(0) = V$$

$$V_1(\infty) = V$$


$$\frac{I^2}{V_x} \frac{V}{\frac{V_x}{2}}$$

$$E_P =$$



Even power

Discharging of capacitors:-

$$V(0) = V_x \quad V(\infty) = 0.$$

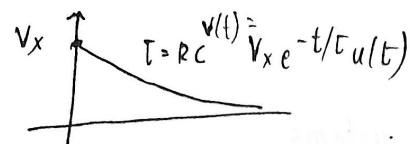

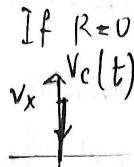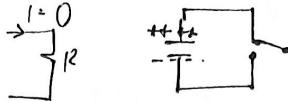Steady state \Rightarrow Capacitor behaves as an open ckt.



$\frac{1}{2} CV_{x_0}^2$
At $t=0 \rightarrow$ When switch is turned ON, it goes to 0.
Energy is $\frac{1}{2} CV_x^2$
and suddenly it is lost to 0.

& Charge sharing betw 2 capacitors:-

$$E = \frac{1}{2} CV_x^2$$

$$\Rightarrow \frac{V_x}{2} + \frac{1}{C} \frac{1}{R} \frac{1}{t} = \frac{V_x}{2}$$

$$CV_x = 2CV_1$$


$$V_1 = \frac{V_x}{2}$$

$$V_1(0) = V_x$$

$$V_2(0) = 0$$

$$V_1(\infty) = V_2(\infty) = \frac{V_x}{2}$$

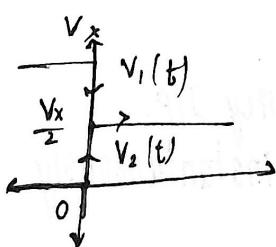
If $R \rightarrow 0 \quad T \rightarrow 0$



$$E_p = \frac{1}{4} CV_x^2$$

Assume finite resistance of switch.
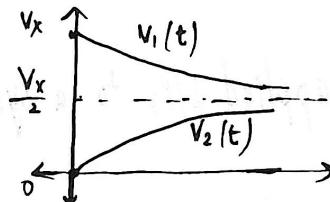
$$\frac{1}{C} \frac{1}{R} \frac{1}{t} = \frac{RC}{2}$$



$$V_2(t) = \frac{V_x}{2} [1 - e^{-t/T}] u(t)$$

$$V_1(t) = \left(\frac{V_x}{2} + \frac{V_x e^{-t/T}}{2} \right) u(t)$$

$$= \frac{V_x}{2} [1 + e^{-t/T}] u(t)$$

$$V_R(t) = V_1 - V_2$$

$$= V_x e^{-t/T} u(t)$$

$$T = \frac{RC}{2}$$

$$i_R(t) = \frac{V_x}{R} e^{-t/T} u(t)$$

Even if the switch resistance is 0,
power dissipated will become ∞ .

$$P_R(t) = \frac{V_x^2}{R^2} e^{-2t/T} u(t)$$


$$= \frac{1}{4} CV_x^2 \left[\frac{2}{T} e^{-2t/T} u(t) \right]$$

Lecture 12 a :- Time Domain Analysis of first order systems for various I/Ps

2) Ste

$$T \frac{dV_o}{dt} + V_o = V_i$$

$$V_o(t) = V_x (1 - e^{-t/T}) u(t)$$

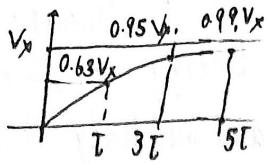

$t_s \rightarrow$ settling time

$t_s \approx \infty$ for many systems

95%.

$$V_o(t_s) = 0.95 V_x$$

99%.

$$t_s = 5T$$

$$0.95 V_x = V_x (1 - e^{-t/T})$$

$$e^{-t/T} = 0.05$$

$$t_s \approx 3T$$

Area = 1.

1) Impulse



3 most commonly applied I/Ps to a system:-

2) Step



3) Ramp

$$r(t) = tu(t)$$

i) Unit Impulse

$$\delta(t) \xrightarrow{\text{FOS}} \boxed{f(t)}$$

FOS will see the I/P as a very high frequency I/P.

$\frac{1}{R} \frac{C}{I} \frac{1}{t} + V_o$ So, the capacitor voltage won't change instantaneously.
 \therefore Voltage drop only across resistor.


$i = \frac{1}{R} \delta(t) \rightarrow$ This current flows into the capacitor.

$$\therefore V_o(0^+) = \frac{1}{C} \int_0^t \frac{1}{R} \delta(t) dt$$

The next moment $t = 0^+$, impulse drops down to 0.

$$= \frac{1}{R} \rightarrow V_c \text{ suddenly rises to } \frac{1}{R}$$

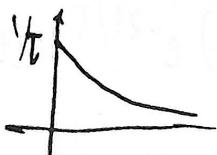
$$R \left\{ C \frac{1}{I} + \frac{1}{t} \right\}$$



$$\delta(t) \rightarrow \frac{1}{t} e^{-t/R} u(t)$$

3) Ra

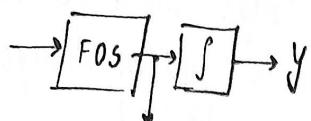
2) Step Response $u(t) = \int_{-\infty}^t g(t)dt$



$$\text{Impulse response } e^{-t/T} u(t)$$


$$\therefore y = \int_0^t \frac{1}{T} e^{-t/T} dt$$

$$\boxed{y = (1 - e^{-t/T}) u(t)}$$

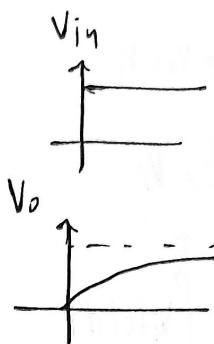

3) Ramp Response

$$y(t) = \int_{-\infty}^t u(t) dt$$

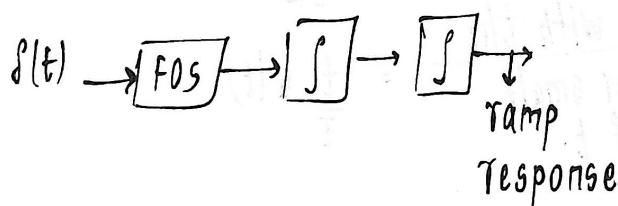


$$y = \int_{-\infty}^t (1 - e^{-t/\tau}) dt$$



$$\boxed{y = t u(t) - T(1 - e^{-t/\tau}) u(t)}$$

$$t \rightarrow \infty$$
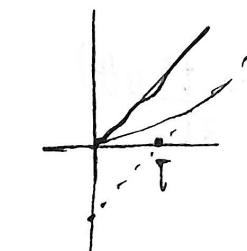
$$\textcircled{3} \quad \boxed{y = u(t)(t - \tau)} \quad \# \text{ Delayed ramp fn.}$$


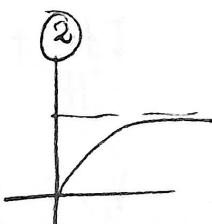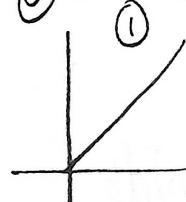
$$\textcircled{3} = \frac{\textcircled{1} - \textcircled{2}}{\textcircled{1}}$$



$V_{in} - V_o = T u(t) \rightarrow \text{Steady State Error}$
bet: I/P & O/P.

Lecture 12b.: Initial and steady state response


$$\begin{aligned} t=0 & \quad V_o(\infty) \\ \text{Know: } -V_o(0) & \\ \text{Want: } V_o(t) \Big|_{t=0} & \quad V_o(t) \Big|_{t=\infty} \end{aligned}$$

$$T \frac{dV_o}{dt} + V_o = V_i$$

$$\frac{T dV_o}{dt} = V_i$$

$$V_o = \frac{1}{T} \int_{-\infty}^t V_i(t) dt$$

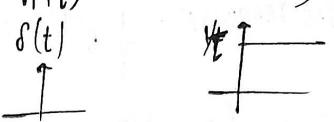
1st order systems doesn't change instantaneously respond to sudden changes to the input $V_o(t)$



When there is a sudden change in the I/P

At $t=0$, FOS is behaving like a pure integrator
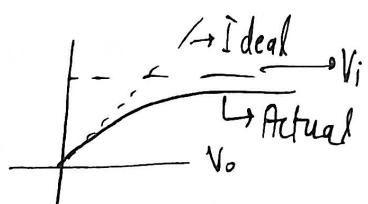
$$\begin{aligned} \text{For Step I/P: } y &= (1-e^{-t/\tau})u(t) \\ e^{-\alpha} \approx 1-\alpha & \quad \xrightarrow{\text{Match with the}} V_o(t) = \frac{1}{T} \int_{-\infty}^t V_i(t) dt \\ \therefore (1-e^{-t/\tau}) \approx t/\tau & \quad \text{actual O/P for small values of } t. \end{aligned}$$




$$y = t u(t) - T (1 - e^{-t/T}) u(t)$$

$$\begin{aligned} \rightarrow \frac{t^2}{2T} u(t) & \quad e^{-\alpha} \approx 1-\alpha + \frac{\alpha^2}{2!} \quad \alpha = \frac{t}{T} \\ t u(t) - T \left(\frac{t}{T} + \frac{-t^2}{2T^2} \right) & \end{aligned}$$

$$\begin{aligned} T \frac{dV_o}{dt} + V_o &= V_i \\ V_o &= \frac{1}{T} \int_{-\infty}^t (V_i - V_o) dt \end{aligned}$$
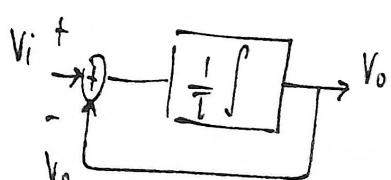
$$\begin{aligned} t u(t) - T \left(\frac{t}{T} + \frac{-t^2}{2T^2} \right) & \\ t u(t) + t + \frac{t^2}{2T} & \\ \rightarrow \frac{t^2}{2T} u(t) & \end{aligned}$$



$$\begin{aligned} V_i - V_o &= T \frac{dV_o}{dt} \\ \approx T A V_o & \end{aligned}$$




$$V_i = V_o \text{ at } t=0$$

$$V_i - V_o = T$$

$$e = V_i - V_o = T \tan(\theta)$$

$$V_i = \frac{b}{2} u(t)$$

$$(V_i - V_o) d\left(\frac{dV_i}{dt}\right) / \text{steady state}$$

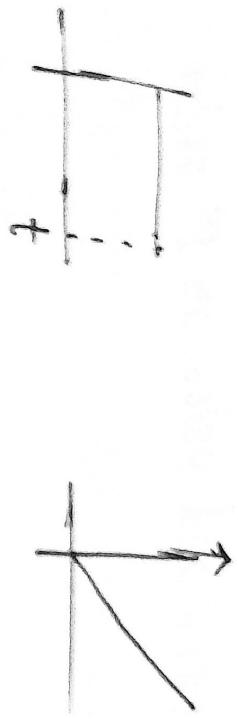

Lecture 15 - Laplace transforms and effects of zeroes and poles on 1st order systems.

$$s = \sigma + j\omega$$

$$x(t) \xrightarrow{\text{Laplace}} X(s)$$

$$X(s) = \int_{-\infty}^t x(t) e^{-st} dt$$

$$f(t) \rightarrow 1. \quad f(t) = \frac{d u(t)}{dt} = s \cdot \frac{1}{s} = 1$$

$$u(t) \rightarrow 1/s$$

$$\gamma(t) \rightarrow 1/s^2$$

$$\frac{dx(t)}{dt} \rightarrow sX(s)$$

$$e^{-at} u(t) \rightarrow \frac{1}{s+a}$$

$$\int x(t) dt \rightarrow \frac{X(s)}{s}$$

$$e^{at} u(t) \rightarrow \frac{1}{s-a}$$

$$[\frac{dV_o}{dt} + V_o = V_i]$$

$$sT V_o(s) + V_o(s) = V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{sT+1} = H(s)$$

$$h(t) \rightarrow H(s)$$


↑
Impulse
Response

$$b_n \frac{d^n V_o}{dt^n} + \dots + b_0 = a_M \frac{d^M V_i}{dt^M} + \dots + a_0$$

$$H(s) = \frac{\sum_{i=0}^M a_i s^i}{\sum_{i=0}^N b_i s^i} = \frac{N(s)}{D(s)}$$

$$H(s) \xrightarrow{s \rightarrow 0} 0 \quad H(s) \xrightarrow{s \rightarrow \infty} \infty$$

↳ max. power of s : order of the ckt.

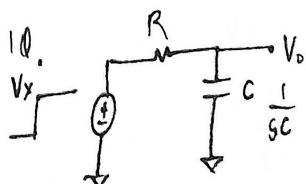

$$\frac{V_o}{V_i} = \frac{1}{1+sRC} = \frac{1}{1+sT} = \frac{1}{1+s/w_p}$$

$w_p = 1/T$ → Pole is inverse of time constant in a 1st order system.


$$H(s) = \frac{(1+s/w_z)}{(1+s/w_p)}$$

$$w_z = 0$$

$$w_p = -w_p \\ = -1/T$$

Q7

$$V_o(s) = V_x(s) H(s)$$

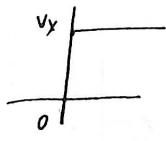

$$V_o(s) = \frac{V_x}{s} \cdot \frac{1}{1+s/w_p}$$

$$= V_x \left[\frac{1}{s} - \frac{1/w_p}{1+s/w_p} \right]$$

$$\boxed{V_o(s) = V_x \left[\frac{1}{s} - \frac{1}{s+w_p} \right]}$$

$$V_o(t) = V_x \left[1 - e^{-w_p t} \right] u(t)$$

Ex:- $H(s) = \frac{(1+s/w_2)}{(1+s/w_p)}$

$$V_o(s) = \frac{V_x}{s} \frac{\left(1+s/w_2\right)}{\left(1+s/w_p\right)}$$

$$= \frac{V_x}{s} \cdot \frac{1}{(1+s/w_p)} + \left(\frac{s}{w_2}\right) \left[\frac{V_x}{s} \cdot \frac{1}{1+s/w_p} \right]$$


$$= V_x \left[1 - e^{-w_p t} \right] u(t) + \frac{1}{w_2} \frac{d}{dt} \left[V_x \left(1 - e^{-w_p t} \right) u(t) \right]$$

$$= V_x \left[1 - e^{-w_p t} \right] u(t) + V_x \frac{w_p}{w_2} e^{-w_p t} u(t)$$




$$w_p < w_2.$$

$$\text{Resultant} = ① + ②$$

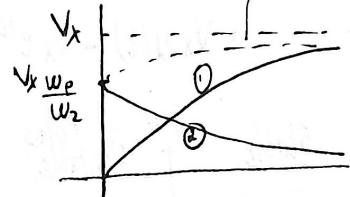Effect of adding zero is equivalent to adding initial condition.





If $w_p = w_2$

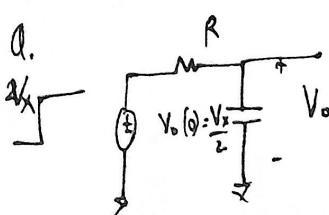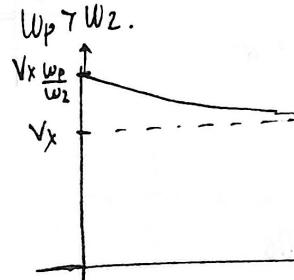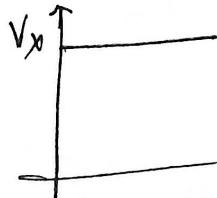

$$H(s) = \frac{1}{1+sRC} \quad w_p = 1/RC$$

$$s_p = -1/RC$$

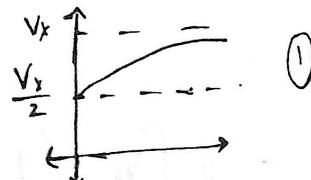

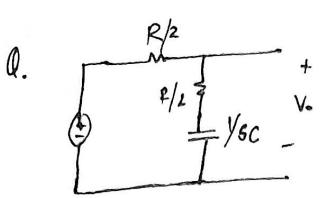




$$H(s) = \frac{R/2 + j\omega C}{R + j\omega C}$$

$$= \frac{1 + j\omega RC}{1 + sRC}$$

$$\omega_2 = \frac{2\pi}{RC}$$

$$\omega_p = \frac{1}{RC}$$
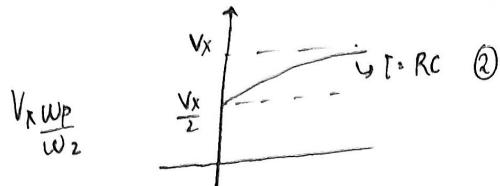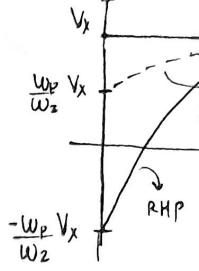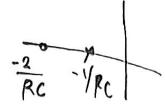
$$\frac{\omega_p}{\omega_2} = \frac{1}{2}$$



① & ② same \rightarrow depicts effect of zeroes

$$\frac{1}{1+s/\omega_p} = \frac{\omega_p}{s+\omega_p} \Rightarrow h(t) = \omega_p e^{-\omega_p t} u(t)$$

$$\frac{1}{1-s/\omega_p} = \frac{\omega_p}{s-\omega_p} \Rightarrow h(t) = -\omega_p e^{\omega_p t} u(t)$$




Ex:-

$$H(s) = \frac{V_x}{s} \cdot \frac{1}{(1-s/\omega_p)} = V_x \left[\frac{1}{s} + \frac{1/\omega_p}{1-s/\omega_p} \right]$$


$$= V_x \left[\frac{1}{s} - \frac{1}{s-\omega_p} \right]$$

$$= V_x u(t) - V_x e^{\omega_p t} u(t)$$

When the pole is in the right pole, the impulse response goes down to ∞ , which makes it unstable.

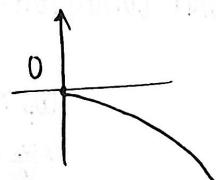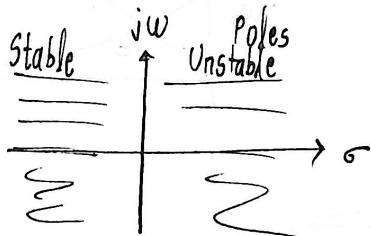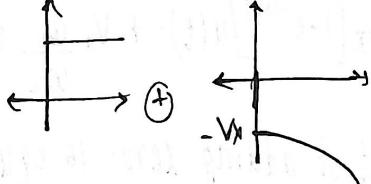

Lecture 1b - 5

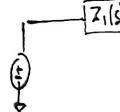


$$H(s) =$$

Ex:- A zero in the right of s-plane


$$H(s) = \frac{(1-s/\omega_2)}{(1+s/\omega_p)}$$

$$V_o(s) = \frac{V_x}{s} \cdot \frac{(1-s/\omega_2)}{(1+s/\omega_p)} = \frac{V_x}{s} \cdot \frac{1}{1+s/\omega_p} - \frac{s}{\omega_2} \left[\frac{V_x}{s} \cdot \left(\frac{1}{1+s/\omega_p} \right) \right]$$
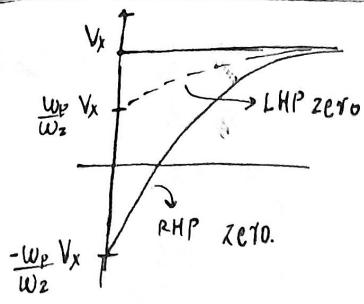
$$= V_x (1 - e^{-\omega_p t}) u(t) - \frac{\omega_p}{\omega_2} V_x e^{-\omega_p t} u(t)$$



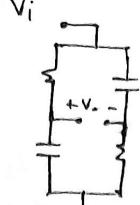For settling time \rightarrow Not desired.
In case of RHP zero




$$0 \frac{1}{1+sRC} - \frac{R}{R+1/sC}$$




$$\frac{1-sRC}{1+sRC}$$

$$H(s) = \frac{w_i}{s}$$

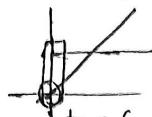
If V_x is given as step I/P
Output will be Ramp ($\frac{1}{s} \rightarrow t$) O/P: 0



$$H(s) = \frac{s}{w_D}$$

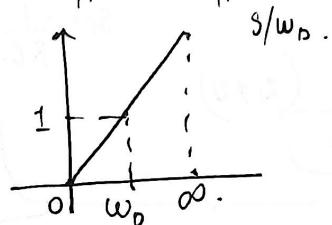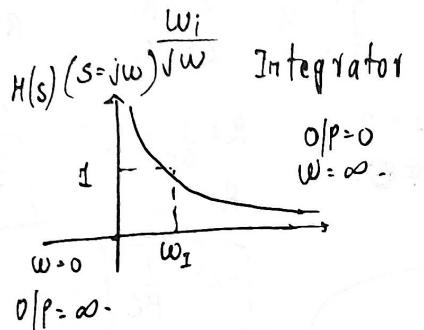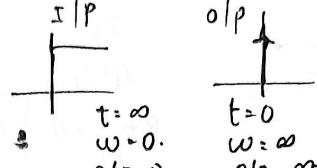

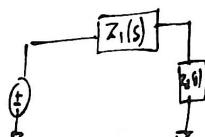Lecture 1b - Simple & Intuitive tricks to find poles & zeroes in 1st order RC ckt.






$$i) \text{ Poles} : - z_1 + z_2 = 0 \Rightarrow z_1(s) = -z_2(s)$$

$$\& z_1(s) = z_2(s) \neq 0.$$

$$H(s) = \frac{z_2(s)}{z_1(s) + z_2(s)}$$

$$ii) \text{Zeroes} : - z_2(s) = 0 \quad (z_1(s) \neq 0)$$
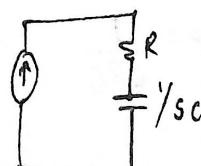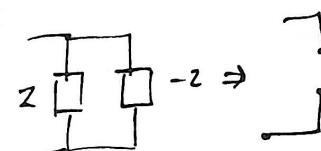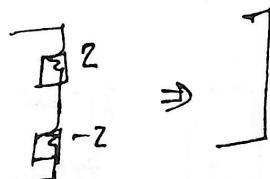
$$z_1(s) = \infty \quad (z_2(s) \neq \infty)$$



$$R = -\frac{1}{sC} \Rightarrow s_z = -\frac{1}{RC}$$

$$\frac{1}{sC} = \infty \Rightarrow s_p = 0$$

Lecture 17:- Frequency

F-T. tells about

$$H(\omega) = A(\omega)$$


$$\frac{1}{1+s/\omega_p} \rightarrow h$$

$$\frac{s/\omega_p}{1+s/\omega_p}$$

$$H(0) \rightarrow DC$$


$\frac{\omega_p H(0)}{s}$
Integator (D.C. g)
Can't be real

⇒ Q.H.

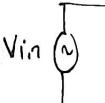

$$H(s) = \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{R}{RC}$$

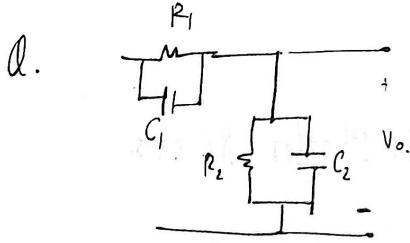


$$H(s) = \frac{Z_2}{Z_1 + Z_2}$$

$$= \frac{R_2}{SR_2 C_2 + 1}$$

$$= \frac{R_1}{SR_1 C_1 + 1} + \frac{R_2}{SR_2 C_2 + 1}$$

V
-
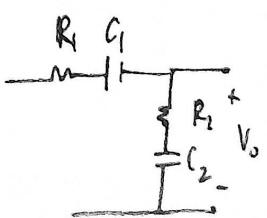
$$= \frac{R_2 (SR_1 C_1 + 1)}{R_1 (SR_2 C_2 + 1) + R_2 (SR_1 C_1 + 1)}$$



$$S_p = -\frac{1}{(G_1 C_1)(R_1 + R_2)}$$

$$S_2 = \frac{1}{R_1 C}$$

$$S_Z = -\frac{1}{R_1 C}$$

$$S_p = -\frac{1}{(1+C_2)(Z_1 || R_2)}$$

≠ No zeroes in the C



$$Z_1 = \omega$$

$$S_2 = 0$$

$$\frac{1}{SC} + R = -R$$

$$S_p = -\frac{1}{2RC}$$

$$S_p = -\frac{1}{(1+C_2)(Z_1 || R_2)}$$

$$\frac{1}{SC} = -R$$

$$S_p = -\frac{1}{RC}$$

Q2.



$$Z_2 = R$$

$$Z_1 = -Z_2$$

$$S_p = -\frac{1}{RC}$$


$$\frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = \infty$$

$$\frac{1}{SC} = \infty$$

$$S_Z = 0$$

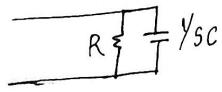For ZDIO:-
 $\frac{1}{SC} = 0 \Rightarrow S_Z = \infty$



$$\frac{Z_2}{Z_1 + Z_2}$$

$$R + \frac{1}{SC} = 0$$

$$S_p = -\frac{1}{RC}$$

$$Z_2 = 0, (Z_1 \neq 0)$$

$$S_Z = \infty$$

$$H(s) = \frac{1}{1+SCRC}$$

$$Z_2 = R + \frac{1}{SC}$$

$$Z_1 = R$$

$$Z_1 = -Z_2$$

$$R + \frac{1}{SC} = R$$

$$2R = -\frac{1}{SC}$$

$$R = -\frac{1}{2SC}$$

$$S_Z = -\frac{1}{RC}$$

$$Z_2 = 0$$

$$Z_1 \neq 0$$

$$R + \frac{1}{SC} = 0$$

$$R = -\frac{1}{SC}$$

$$S_Z = -\frac{1}{2RC}$$

$$H(s) = \frac{R + \frac{1}{SC}}{R + R + \frac{1}{SC}} = \frac{RCSH}{2RCSH}$$

$$H(s) = \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{R}{RC}$$

$$Z_1 = \frac{R_1}{SR_1 C_1 + 1}$$

$$Z_1 = \frac{1}{T(C_1 + C_2)}$$

For pole:-
 $Z_1 = -Z_2$

$$Z_1 = \frac{1}{T(C_1 + C_2)}$$

$$Z_1 = \omega$$

$$S_2 = 0$$

$$\frac{1}{SC} + R = -R$$

$$S_p = -\frac{1}{2RC}$$

$$S_p = -\frac{1}{(1+C_2)(Z_1 || R_2)}$$

≠ No zeroes in the C

Lecture 17:- Frequency response of 1st order systems and bode plots.

F.T. tells about the distribution of energy of the signal across frequencies.

$$H(\omega) = A(\omega)$$

$$\frac{1}{1+s/w_p} \rightarrow \text{lpt}$$

$$\frac{s/w_p}{1+s/w_p} \rightarrow \text{lpt}$$


$$20 \log\left(\frac{1}{\sqrt{2}}\right) = -3 \text{ dB}$$

For high frequencies, the plot is same for a lpt as well as an integrator.

$$H(0) \rightarrow \text{DC gain.}$$

$$\int \frac{w_p H(0)}{s} \quad \text{Integrator (D.C. gain is } \infty)$$

Can't be realized using RC ckt.

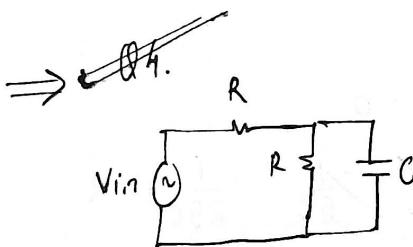

$$Z_2 = \frac{Z_1 + Z_2}{Z_1} = \frac{R + \frac{1}{sC}}{R + \frac{1}{sL}} = \frac{RCS}{RCs + 1}$$

$$H(s) = \frac{\frac{RCS}{RCs+1}}{\frac{RCS}{RCs+1} + R} = \frac{RCS}{RCs + R^2Cs + R} = \frac{Cs}{Cs + RCS} \Rightarrow$$

$$Z_2 = 0 \quad (Z_1 \neq 0)$$

$$Z_1 = -Z_2$$

$$SC = 0 \\ G_L = 0$$

$$\frac{R}{RCs+1} = -j$$

$$S_L = \infty$$

$$1 = -RCs - 1$$


$$RCs = -2$$

$$1 + RCS = -1$$


$$s(RC + C) = -1$$

$$s_p = -\frac{1}{C(RH)}$$

$$G_p = -\frac{2}{RC}$$

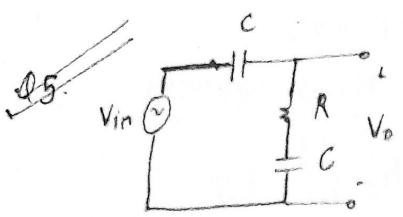

For pole:-
short the I/P.

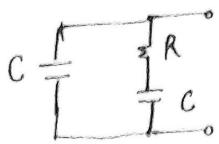

$$R + \frac{1}{sC} = -\frac{1}{sC}$$

$$-\frac{1}{sC} = R$$

$$\boxed{s_p = -\frac{1}{2RC}}$$

$$Z_2 = 0$$

$$Z_1 = \infty$$

$$R + \frac{1}{sC} = 0$$


$$\frac{1}{sC} = \infty$$

$$\boxed{\frac{s}{2} = -\frac{1}{RC}}$$

$$\boxed{S_2 = 0.} \times$$

$$H(s) = \frac{R + \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{RCs + 1}{RCs + 2}$$

46.

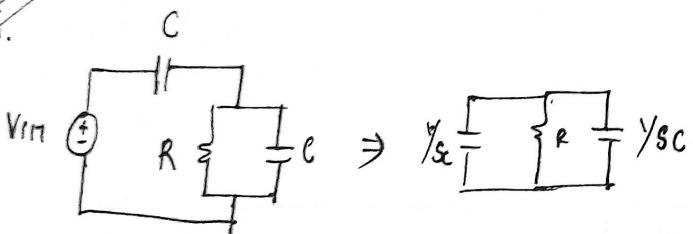

$$Z_1 + Z_2 = 0$$

$$R + \frac{1}{sC} = -\frac{1}{sC}$$

$$\frac{1}{2sC} = -R$$

$$R = -\frac{1}{2sC}$$

$$\boxed{s_p = -\frac{1}{2RC}}$$

$$Z_2 = 0.$$

$$R + \frac{1}{sC} = 0$$

$$\boxed{S_2 = \infty} \times \Rightarrow Z_1 = 0.$$

$$Z_1 \rightarrow \infty.$$

$$\frac{1}{sC} = \infty.$$

$$\boxed{S_2 = 0}$$

$$H(s) = \frac{\frac{R}{1+sRC}}{\frac{R}{1+sRC} + \frac{1}{sC}} = \frac{sRC}{1+s^2CR}$$

We al

H(

20 lug

Lecture 17

$H(s)$


$S = j\omega$

$H(\omega)$

$|H(\omega)|$



Consider

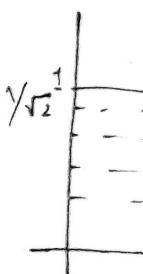

$\log_{10}(*)$

←

We al

H(

20 lug

L

Lecture 1+ - Frequency Response of 1st order systems and Bode plots

$$H(s) = \frac{1}{1+s/w_p}$$

$$s = j\omega$$

$$H(\omega) = \frac{1}{1+j\omega/w_p}$$

$$|H(\omega)| = \frac{1}{\sqrt{1+(\omega/\omega_p)^2}}$$



$$\phi(\omega) = -\tan^{-1}(\omega/\omega_p)$$

$$\omega = 0 \Rightarrow 1$$


$$\omega = \omega_p \Rightarrow 1/\sqrt{2}$$

$$\omega = \infty \Rightarrow 0$$
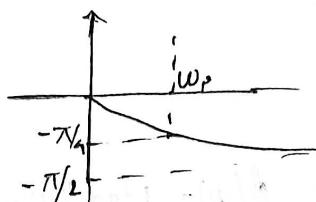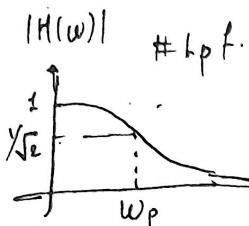
$$\cos \omega_p t \Leftrightarrow \frac{1}{\sqrt{2}} \cos(\omega_p t - \pi/4)$$




Consider 3 more pts.

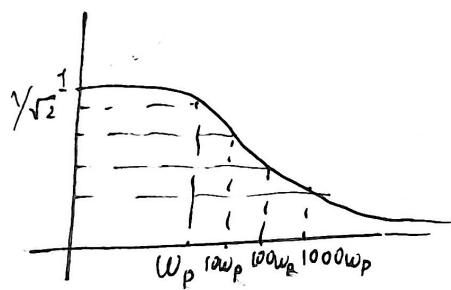

$$\text{For } \omega > \omega_p \Rightarrow \left(\frac{\omega_p}{\omega}\right) \approx 0.1 \text{ for } 10\omega_p \\ = 0.01 \text{ for } 100\omega_p \\ = 0.001 \text{ for } 1000\omega_p$$

$$0.1 - 0.01 \approx 0.1$$

$$0.01 - 0.001 \approx 0.01$$


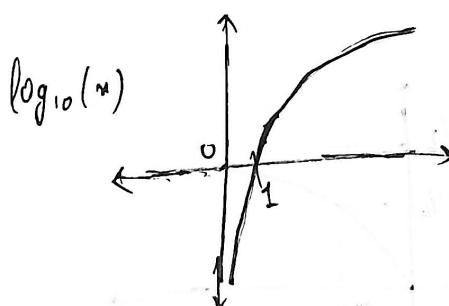


We always plot $20 \log |H(\omega)|$

$$H(\omega) = \frac{1}{\sqrt{1+(\omega/\omega_p)^2}}$$

$$LH(\omega)$$
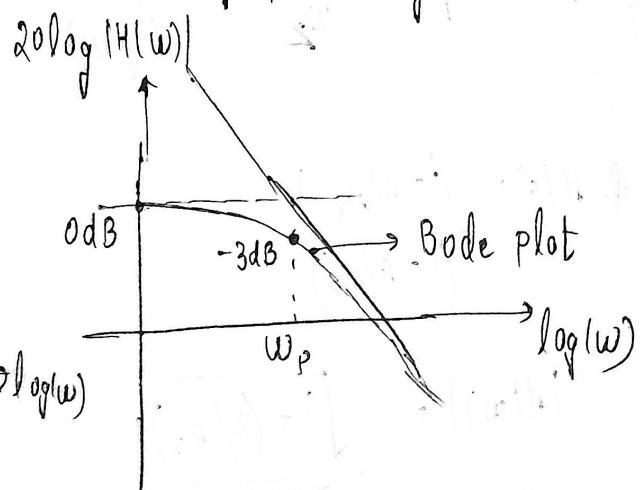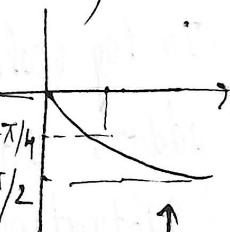
$$20 \log \left(\frac{1}{\sqrt{1+(\omega/\omega_p)^2}} \right)$$



If $\omega \ll \omega_p \Rightarrow 20 \log(1) = 0$. O/P lags the I/P

$\omega \gg \omega_p \Rightarrow 20 \log \omega_p - 20 \log(\omega) \rightarrow 0$

$$20 \log \left(\frac{1}{\sqrt{2}} \right) = -3 \text{ dB}$$

$$20 \log |H(w)| = 20 \log(w_p) - 20 \log(w)$$

At $w = 10w_p$

$$\Rightarrow 20 \log\left(\frac{w_p}{10w_p}\right) = -20$$

At $w = 100w_p$

$$\Rightarrow 20 \log\left(\frac{w_p}{100w_p}\right) = -40$$

\therefore Slope is -20 dB/decade



$$\text{Ex: } H(s) = 1 + \frac{s}{w_2}$$

$$H(w) = 1 + \frac{w}{w_2}$$

$$|H(w)| = \sqrt{1 + (w/w_2)^2}$$

$$20 \log |H(w)| = 20 \log \left(\sqrt{1 + (w/w_2)^2} \right)$$
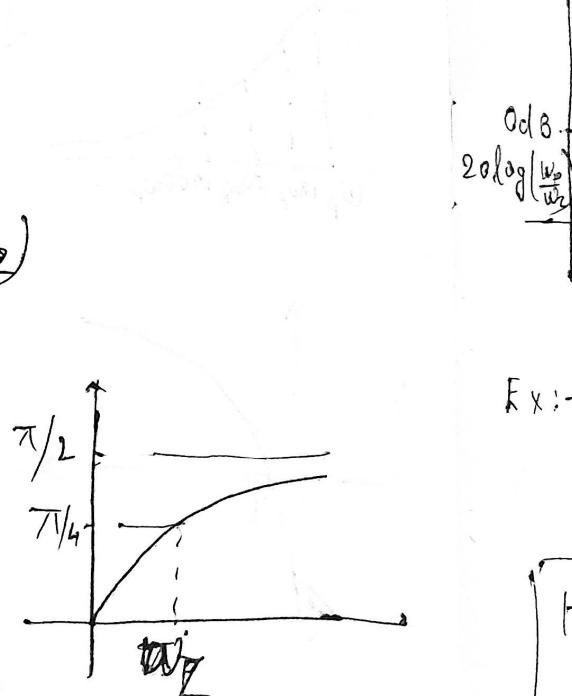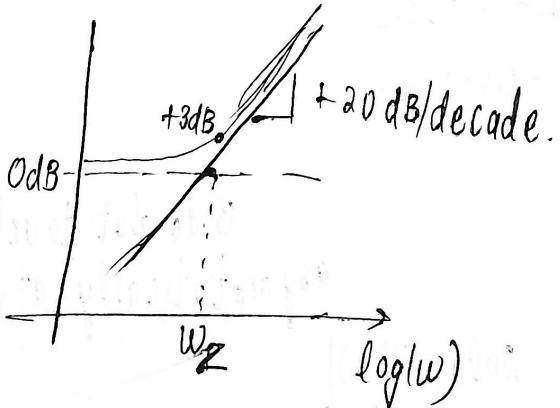
$$\text{For } w > w_p \Rightarrow 20 \log(w) - 20 \log(w_2)$$




$$\text{Q. } H(s) = \frac{(1+s/w_2)}{(1+s/w_p)}$$

$$|H(w)| = \frac{\sqrt{1 + (w/w_2)^2}}{\sqrt{1 + (w/w_p)^2}}$$

In log scale, multiplication becomes addition and division becomes subtraction.


1) $w_p > w_2$.

Encounter zero before a pole.

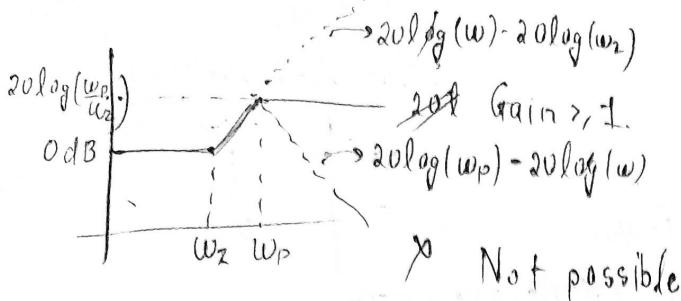

$$\phi(w) = \tan^{-1}\left(\frac{w}{w_2}\right) - \tan^{-1}\left(\frac{w}{w_p}\right)$$

Map: $\pi/2$ $-\pi/2$

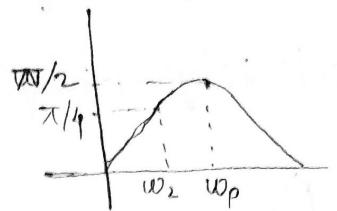

I/P
coss w₀t

O/P
 $\frac{w_p}{w_2} \cos w_0 t$


Not possible

For $w >> w_p, w_2$

$$H(w) = \frac{(w/w_2)}{(w/w_p)} = \frac{w_p}{w_2}$$

2) $w_p < w_2$.




$$H(\omega) = H(0) \frac{w_p}{w_2}$$

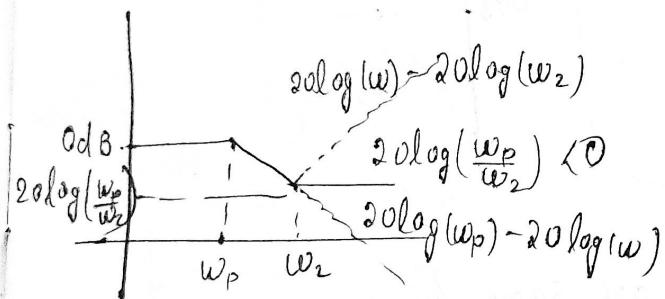

Ex :- $H(s) = \frac{s/w_p}{(1+s/w_p)}$ # High pass filter

$$H(w) = \frac{w/w_p}{\sqrt{1+(w/w_p)^2}}$$
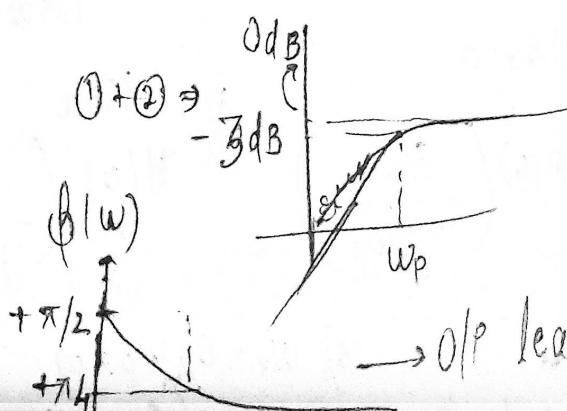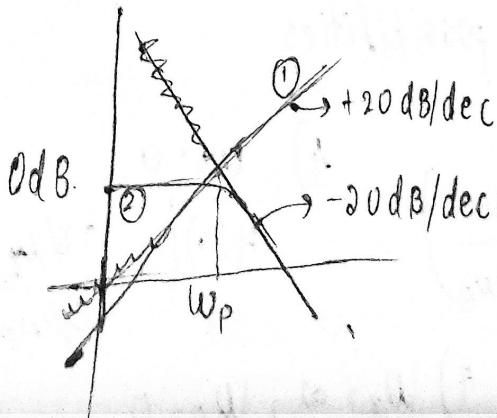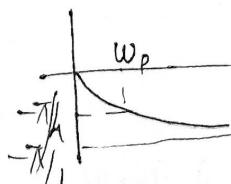
$$\phi(w) = \frac{\pi}{2} - \tan^{-1}\left(\frac{w/w_p}{jw/w_p}\right)$$



\rightarrow O/P leads the I/P

H Ideal Differentiator


H Ideal Integrator

$$H(s) = \frac{1}{s} \quad \omega_i = \frac{\omega_0}{s} \quad \phi = -\pi/2$$

$$20\log|H(w)| = 20\log(\omega_i) - 20\log(w)$$



$$H(s) = \frac{1}{s} \quad \frac{\omega_p}{s} \quad \frac{s}{\omega_0}$$

$$20\log(\omega) - 20\log(\omega_0)$$

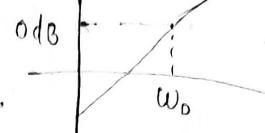


$$j + H(s) = \frac{1}{1 + s/w_p}$$

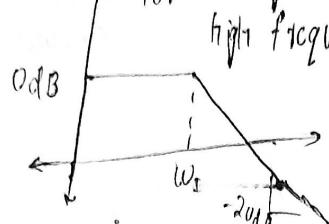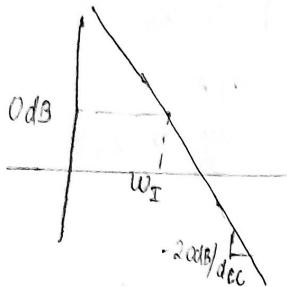For a single-pole system,
high frequency phase ϕ is $s - \pi/2$



For $w > w_i$; the frequency response
of an integrator is same as that
of a 1st order low pass filter.
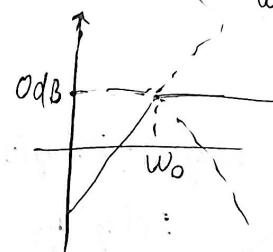
$$H(s) = \frac{1}{s} \quad \left(1 + \frac{s}{\omega_0}\right)$$




1st order hpf & a differentiator are same for $w < w_i$.

(5) & (6) are not
Only (1), (2) & (3)
(3) \rightarrow only (1)
For passive C

$$\frac{1}{2\pi} \int_{-\infty}^{\infty} |Y(j\omega)|^2 d\omega$$

For a pas

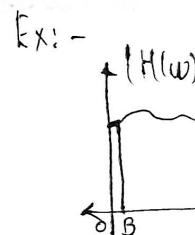

For an in

\therefore It

Lecture 18:- Realizable 1st order transfer f: using passive R/C ckt.

H General 1st order transfer f:

$$H(s) = H(0) \left(\frac{1 + s/w_2}{1 + s/w_p} \right)$$

D.C. gain

$$H(s)|_{s=0} = H(0)$$

$$s_2 \quad \omega_2 = 0, \omega_2, \infty$$

$$s_p \quad \omega_p = 0, \omega_p, \infty$$

(0,0), (\infty, \infty) \rightarrow Not possible

Total 7 possibilities.

1) $w_2 = \infty$

2) $w_2 = 0$

$$\left(\frac{H(0)}{1 + s/w_p} \right)$$

$$H(0) \left(\frac{s/w_2}{1 + s/w_p} \right)$$

3) Finite

$$H(0) \left(\frac{1 + s/w_2}{1 + s/w_p} \right)$$

4) $w_p = 0$

$$H(0) \left(\frac{i + s/\omega_2}{s/w_2} \right)$$

5) $w_p = \infty$

$$H(0) \left(\frac{1 + s/w_2}{1 + s/w_p} \right)$$

6) $w_2 = 0; w_p \neq \infty$

$$H(0) \left(\frac{s}{w_2} \right)$$

7) $w_2 = \infty; w_p = 0$

$$H(0) = \frac{H(0)w_2}{s}$$


integrator

(5) & (6) are not 1st order systems because they don't have a pole.

Only (1), (2) & (3) are realizable.

(3) → only under certain conditions.

For passive ckt's; $H(0) \leq 1$ $|H(\omega)|^2 \leq 1$

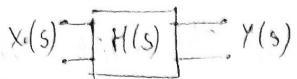

$$Y(s) = H(s)X(s)$$

$$|Y(\omega)| = |H(\omega)X(\omega)|$$



$$\frac{1}{2\pi} \int_{-\infty}^{\infty} |Y(\omega)|^2 d\omega = \frac{1}{2\pi} \int_{-\infty}^{\infty} |H(\omega)|^2 |X(\omega)|^2 d\omega.$$

$$E_y = \frac{1}{2\pi} \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$$

For a passive system; energy at the O/P is lesser than that at the I/P.

$$E_y \leq E_x.$$

Ex:-

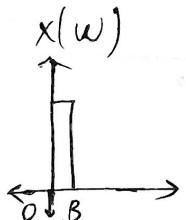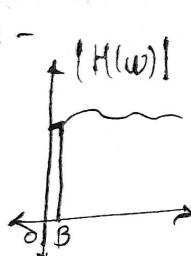

$$E_y = \frac{1}{2\pi} \int_{-\infty}^{\infty} |H(0)|^2 |X(\omega)|^2 d\omega$$

$$E_y = E_x |H(0)|^2 \ll E_x$$

For an integrator; DC gain is ∞ ($\omega_2 = \infty$)

∴ It can't be realized using a passive RC ckt.

(4) It has a pole at D.C. ∴ D.C gain is ∞ .

$$H(s) = \frac{s/w_2}{1+s/w_p} \approx \frac{s/w_2}{s/w_p} = \frac{w_p}{w_2}$$


$$w_p \ll w_2 \quad (H(0) \ll 1)$$

→ Integrator

$$\textcircled{1} H(s) = \frac{1}{1+s/w_p}$$

$$\textcircled{2} H(s) = \frac{s/w_2}{1+s/w_p} \approx \frac{s/w_2}{s/w_p} = \frac{w_p}{w_2}$$

$\therefore w_p < w_2$

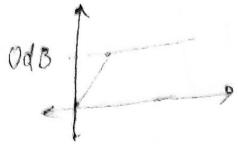

If $w_p < w_2 \geq 0 \text{ dB}$

$$20\log\left(\frac{w_p}{w_2}\right)$$

The slope with which the graph rises has to be smaller than the slope with which it is going to fall after w_p .

$$H(s) = H(0)$$

If $s_2 > 0$



$$H(s) = H(0)$$

For $s_2 = 0$; D.

We need to know

$$\textcircled{3} H(s) = \frac{(1+s/w_p)}{(1+s/w_2)}$$



$$w_p < w_2$$

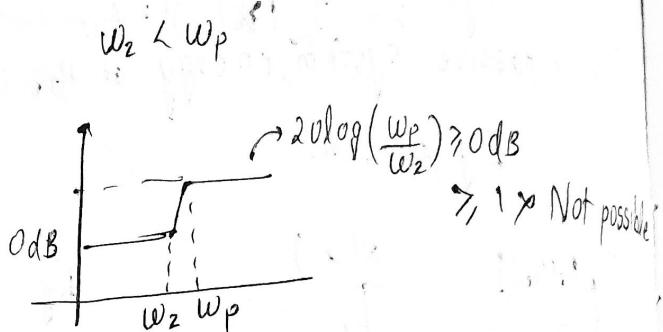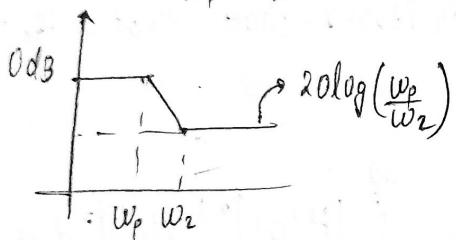

$\therefore \textcircled{3}$ is realizable only if $w_p < w_2$.


Once the

the val
(only +ve)

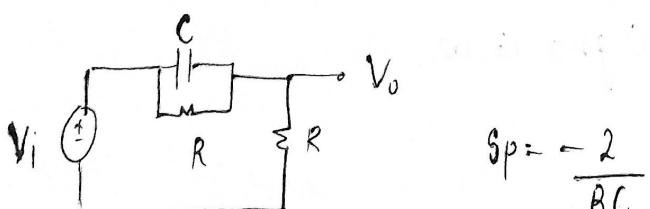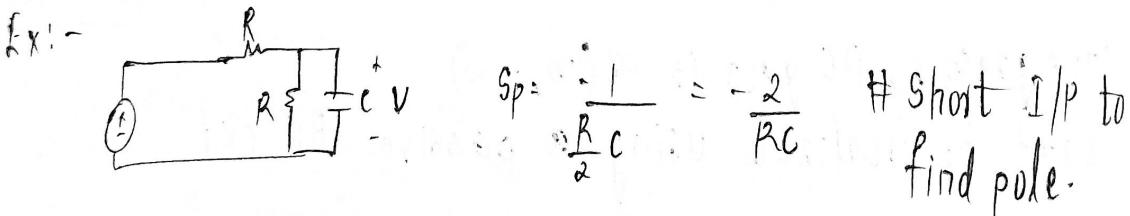

D.C. gain for this fil is $\textcircled{1/2}$, $s_2 = -\frac{1}{RC}$
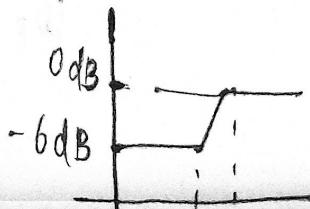
$$20\log\left(\frac{w_p}{w_2}\right) = 20\log(2) = 6 \text{ dB}$$



$$H(s) = H(0) \left(\frac{1+s/w_2}{1+s/w_p} \right)$$

If $s_z = 0$

$$H(s) = H(0) \left(\frac{s/w_2}{1+s/w_p} \right)$$

For $s_z = 0$; D.C-gain ($H(0)$) = 0.

We need to know the slope, i.e., the way it behaves for low frequencies

$\textcircled{1} \quad H(s) = H(0) \frac{s}{w_2}$ # for low frequencies.

Step / Impulse responses \Rightarrow Sudden I/Ps ($t=\infty$)

$$H(\omega) = H(0) \left(\frac{1+j\omega/w_2}{1+j\omega/w_p} \right)$$

$$\boxed{H(\infty) = H(0) \left(\frac{w_p}{w_2} \right)}$$

Once the I/P attains a steady state ($t=\infty$)




the value of the O/P at $t=\infty$.

(only true for steady state I/Ps)

Steady state is like D.C.

$$\boxed{y(\infty) = H(0) x(\infty)}$$


$$\boxed{y(0^+) = H(\infty) x(0)}$$

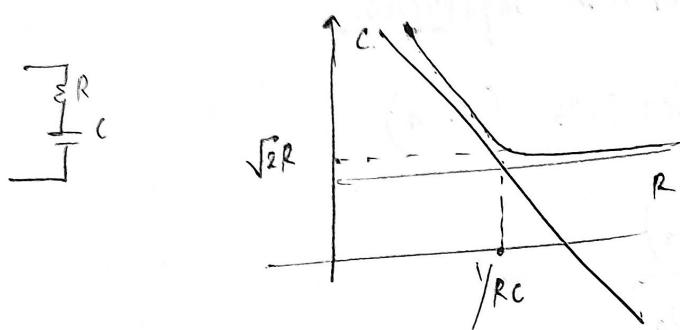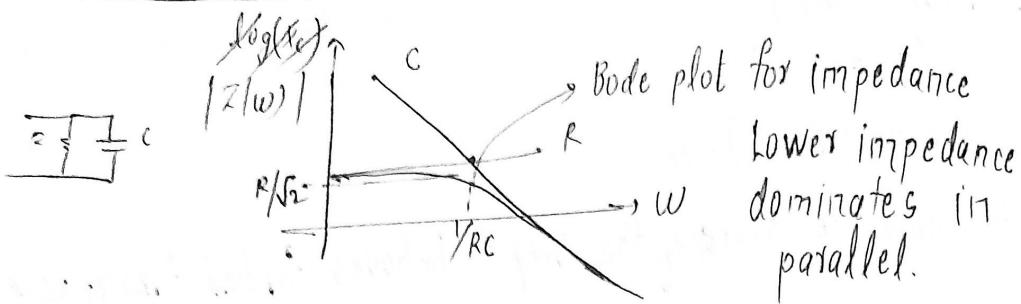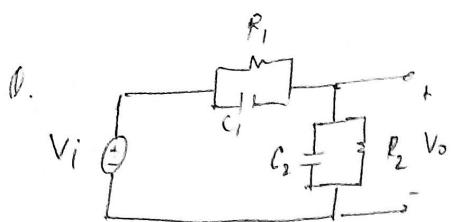

To find transfer fn; 3 things are needed:- DC gain, pole, zero
No need of high frequency gain.

For DC gain $s=0$.
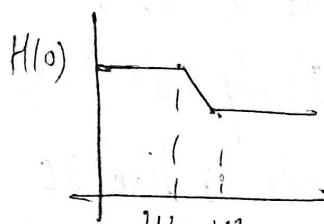
$$\frac{V_1}{V_i} = \frac{R_2}{R_f + R_2}$$



$$-w_p = \frac{1}{(R_1 || R_2)(C_1 + C_2)}$$


$$-w_2 = \frac{1}{R_1 C_1} \quad (Z_1 \text{ should blow up})$$

$$\therefore H(s) = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{1 + s R_1 C_1}{1 + s (R_1 || R_2)(C_1 + C_2)} \right)$$

For Very

$$\left(\frac{R_2}{12 + \gamma w} \right)$$

Ex :- To f

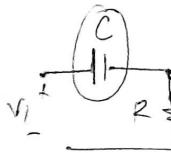


At low

$$\frac{V_i}{V_o}$$

At hi

Lecture

For very high frequencies; $X_C \ll R$

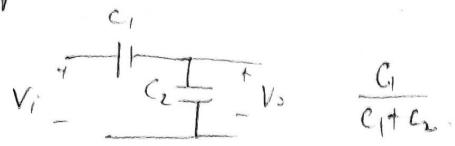

$$\left(\frac{R^2}{1+SR_2} \right) \left(\frac{1+SR_1 C_1}{S(R_1+R_2)(1+C_2)} \right) = \frac{C_1}{C_1 + C_2}$$

Ex:- To find transfer f. of system where it has zero at D.C.

$s_k = 0$. $H(s) = \frac{sk}{1+sR_2 C} = \frac{sRC}{1+2sRC}$

At low frequencies:- This ckt. behaves like a differentiator.

$V_i(sC) R = V_o$.

$$\frac{V_o}{V_i} = sRC$$

At high freq:-

$$\frac{V_o}{V_i} = \frac{1}{2}$$

$$\frac{sk}{2sRC} = \frac{1}{2}$$

$k = RC$.

Lecture 19:-

$$Sp = -\frac{2}{RC}$$

$$H(0) = 1/2$$

$$= \frac{1}{2} \left(\frac{1}{1 + \frac{sRC}{2}} \right)$$

Q.

$$At s=0 \rightarrow It \text{ is an open circuit}$$

$$S_p = 0$$

$$S_L = 0$$


$$S_p = -\frac{1}{9RC}$$

$$H(s) = \frac{s\alpha}{(1+s9RC)}$$

$$\alpha = 4RC$$

$$H(s) = \frac{4SRC}{1+s9RC}$$

At low freq.


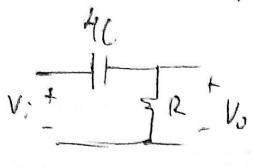


$$V_i(4SC) R = V_o$$

$$\frac{V_o}{V_i} = 4SRC$$

$$H(s) = \frac{4}{9}$$

At high freq

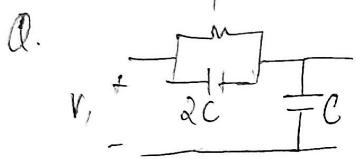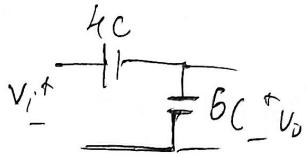

At $s=0$

$$S_p = -\frac{1}{3RC}$$

$$V_o = V_i$$



$$H(0) = 1$$

$$S_L = -\frac{1}{2RC}$$

$$H(s) = \frac{1}{(1+2sRC)} \left(\frac{1+2sRC}{1+3sRC} \right)$$

At high f

$$H(s) = \frac{2}{3}$$

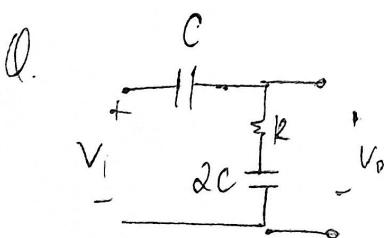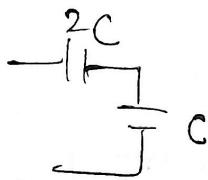


$$S_L = -\frac{1}{2RC}$$



$$H(s) = \frac{1}{3} \frac{(1+s2RC)}{\left(1+\frac{2}{3}sRC\right)}$$

$$S_p = -\frac{3}{2RC}$$

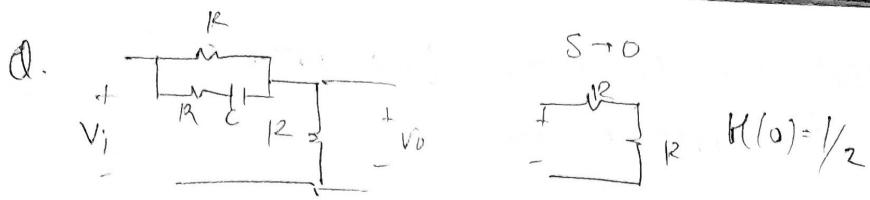

$$S \rightarrow 0$$

$$H(0) = \frac{1}{2}$$


$$R = -R - \frac{1}{SC}$$

$$S_2 = -\frac{1}{2RC}$$

$$\frac{1}{SC} + R = -R/2$$

$$Sp = -\frac{2}{3RC}$$
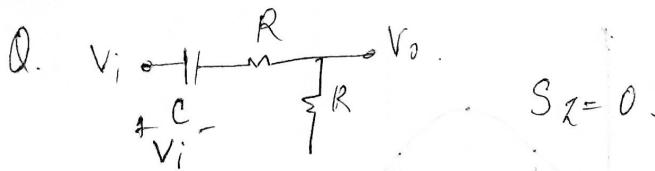
$$H(s) = \frac{\frac{1}{2}(1+2SRC)}{(1+\frac{3}{2}SRC)} \approx \frac{1}{3}$$




$$S_2 = 0$$

$$Sp = -\frac{1}{2RC}$$

$$\frac{S(RC)}{1+S2RC} = \frac{Vi(sC)}{1/2} Vi(sC)$$

High freq. gain

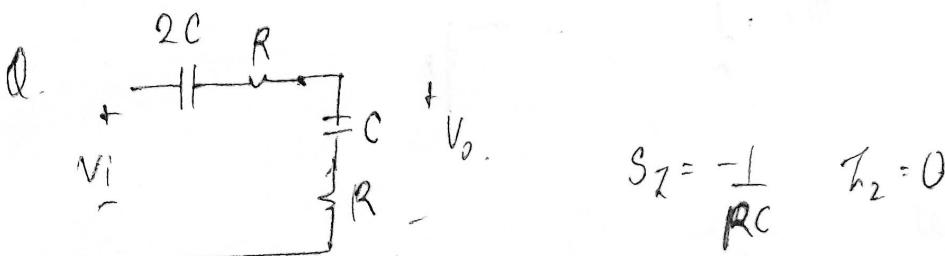

$$S_2 = -\frac{1}{RC} \quad Z_2 = 0$$


$$Sp = -\frac{1}{\frac{4}{3}RC}$$

$$\frac{2C}{1+C} \quad \frac{2}{3}$$


$$\frac{2}{3} \left(\frac{1+SRC}{1+\frac{4}{3}SRC} \right)$$

Lecture 20 - Relation betw frequency & time domain response of first order system


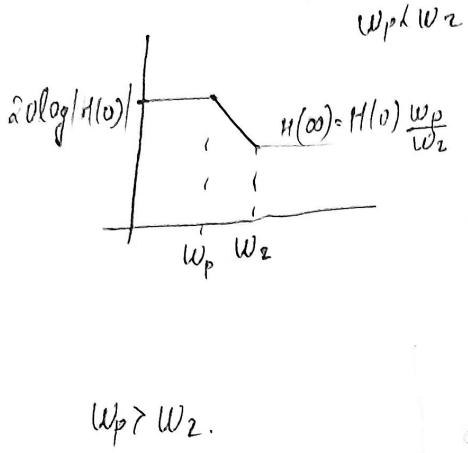
$$H(s) = H(0) \frac{(1+s/w_2)}{(1+s/w_p)}$$



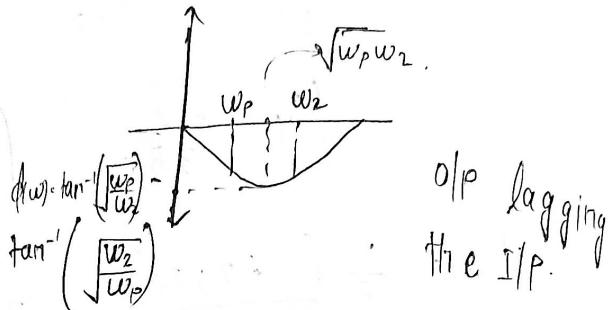
$$\phi(\omega) = \tan^{-1}(w/w_2) - \tan^{-1}(w/w_p)$$


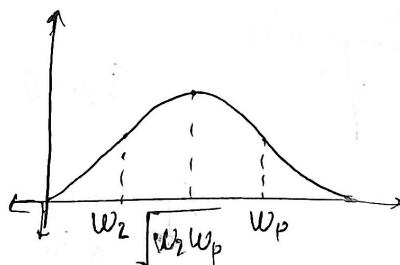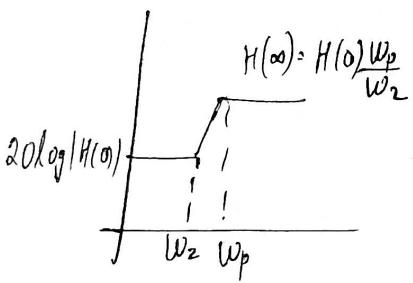
$$\phi(\omega) = \tan^{-1}(w/w_2) - \tan^{-1}(w/w_p)$$



Step F/P
v_x

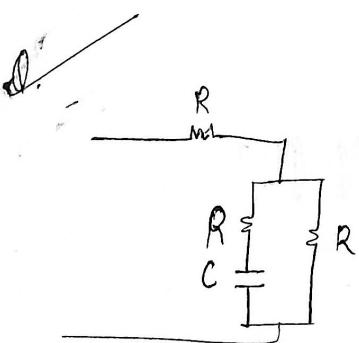

D.C. at gain (low freq.)

$$H(0) = \frac{1}{2}$$



When

For zero; $Z_2 = 0 / Z_1 = 0$.

$$Z_2 = R \parallel \left(R + \frac{1}{sC} \right)$$

$$= \frac{R \left(R + \frac{1}{sC} \right)}{2R + \frac{1}{sC}}$$

$$\frac{R(RCs+1)}{\frac{2RCs+1}{sC}}$$

$$\text{For } Z_2 = 0 \rightarrow R = 0 / R + \frac{1}{sC} = 0.$$


$$R = -\frac{1}{sC}$$

$$s_z = -\frac{1}{RC}$$

$\frac{V_x}{2}$
 $\frac{V_x}{3}$

Be
Vi


$$G_p = \frac{2}{3RC}$$

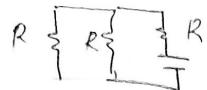

$$\frac{R}{2} + R = \frac{3R}{2}$$


$$H(s) = \frac{1}{2} \left(\frac{1 + sRC}{1 + \frac{3}{2}sRC} \right)$$
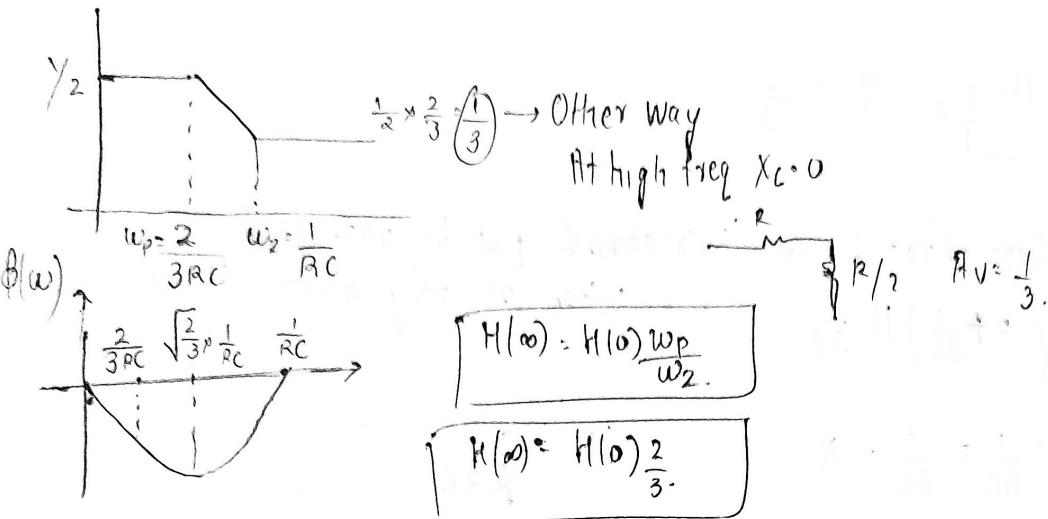
$$\omega_p = \frac{2}{3}RC ; \omega_x = \frac{1}{RC}$$



When step I/P is given; assume cap. is short

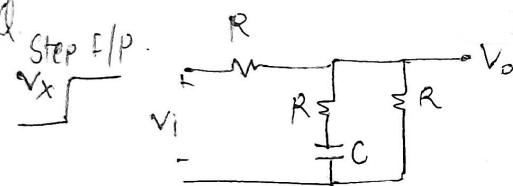
$$\text{As } t \rightarrow 0 ; f \rightarrow \infty ; X_C = \frac{1}{2\pi f C} = 0.$$




$$\begin{aligned} &\text{I/P} - V_x \\ &0/I/P - V_x/3. \end{aligned} \quad \text{This is at } t=0.$$

$$\text{When } t \rightarrow \infty / s \rightarrow 0, \quad X_C = \frac{1}{2\pi f C} = \infty.$$

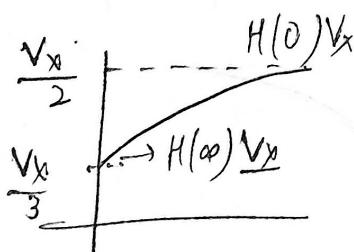
$$\frac{R}{2} \quad H(0) = \frac{1}{2} \cdot \frac{V_x}{2}.$$



If there were no poles:-

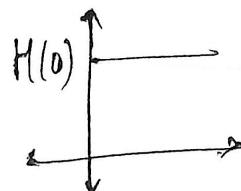

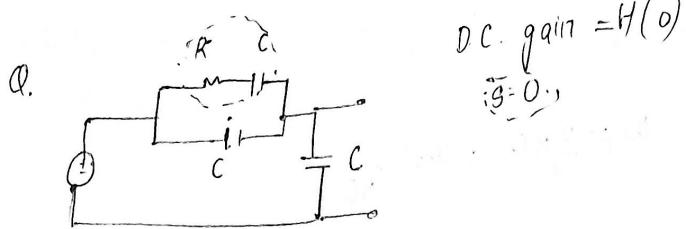Because of presence of poles; if (the I/P) tries to catch up with the steady state value ($H(0)$)



$$\frac{2C}{R} \parallel \frac{1}{C} \quad H(0) = \frac{2}{3}$$

$S_2 = 0$ Zero when $Z_2 \in \infty$. (This should just be non-zero)
 $Z_2 = (R + \frac{1}{SC}) \parallel \frac{1}{SC}$ $\therefore Z_2 \in \infty$ only when $f = 0$.

$$\frac{1}{SC} = \frac{1}{SC} + R$$

$$S_p = -\frac{3}{R^2 C}$$

$$R = -\frac{2}{SC}$$

$$S_p = -\frac{3}{2RC}$$

$$S = -\frac{2}{RC}$$



$$\omega_x = \frac{2}{RC}$$

$$\omega_p = \frac{3}{2RC}$$


$$s \rightarrow \omega$$


$$\frac{1}{1 + \frac{1}{C}} H(0) = \frac{1}{2}$$
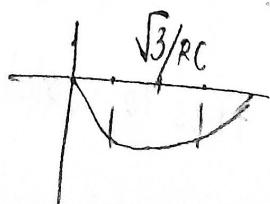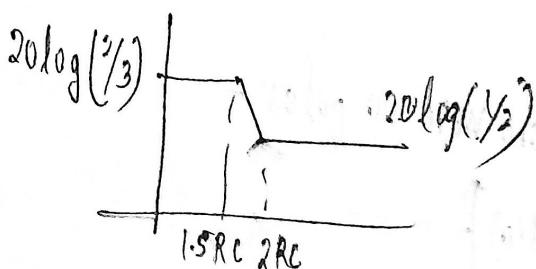
$$H(s) = \frac{2}{3} \cdot \frac{\left(1 + \frac{s}{RC}\right)}{\left(1 + \frac{2}{3}sRC\right)}$$



In case of step response:-

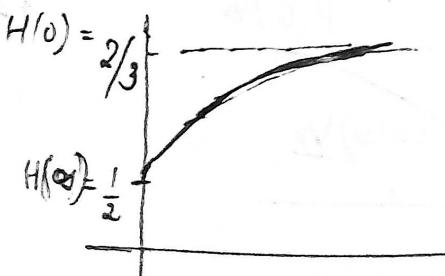

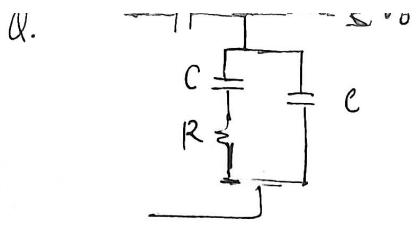

ω_2 as well

$\therefore s=0$ is not a zero.

Check if $\omega_1 = 0$

$$H(0) = Y_3.$$

$s=0.$

$$R + \frac{1}{sC} = 0$$

$$\boxed{s_C = -\frac{1}{RC}}$$



$$\frac{1}{s^2 + \frac{1}{RC}} = Y_3$$

$$\boxed{s_p = -\frac{3}{2RC}}$$




$$H(\infty) = Y_2$$

$$\frac{1}{s^2}$$

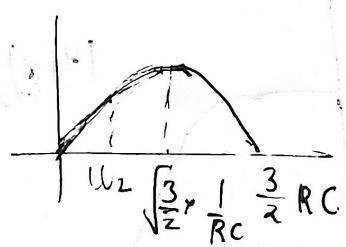
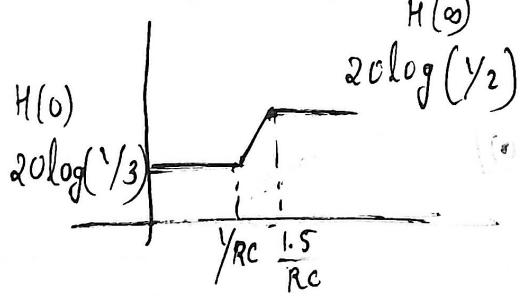
$$H(s) = \frac{1}{3} \frac{(1+sRC)}{\left(1+\frac{2}{3}sRC\right)}$$




In case of a step I/P:-

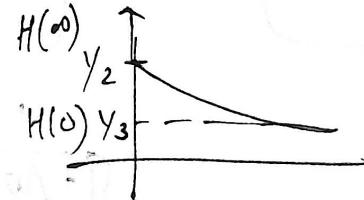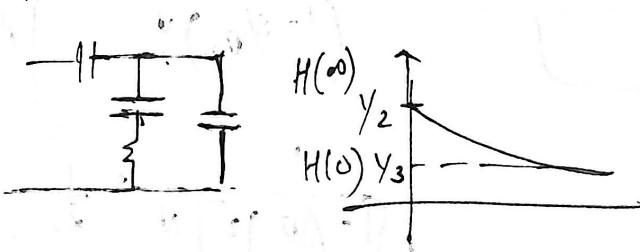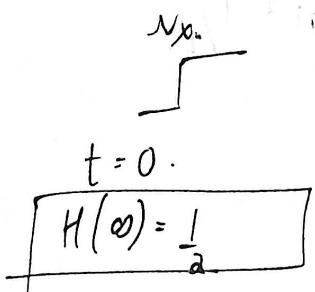
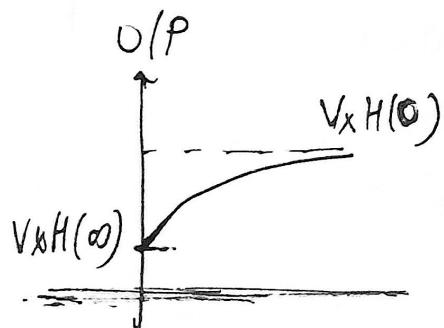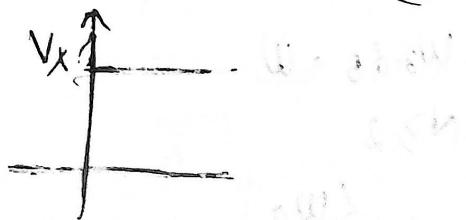
$$H(s) = H(0) \frac{1+s/\omega_L}{(1+s/\omega_P)}$$


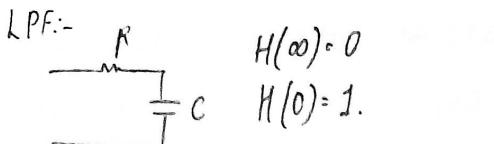
$$V_{out}(t) = V_x H(\infty) e^{-\omega_P t} + V_x H(0) (1 - e^{-\omega_P t})$$



$$H(\infty) = 0$$

$$H(0) = 1.$$

$$V_o(t) = V_x (1 - e^{-\omega_p t})$$

HPF:-

$$H(\infty) = 1$$

$$H(0) = 0$$

$$V_o(t) = V_x e^{-\omega_p t}$$


$H(\omega)$ depends on zero.

$$\boxed{H(\omega) = H(0) \frac{\omega_p}{\omega_2}}$$

$H(0) \rightarrow$ ckt dependent parameter.

$$V_o(t) = V_x H(0) \frac{\omega_p}{\omega_2} e^{-\omega_p t} + V_x H(0) (1 - e^{-\omega_p t})$$

LPF

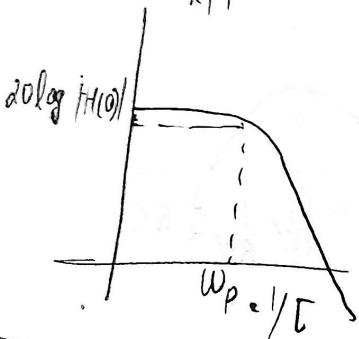

$$|H(j\omega)|_{dB} = \frac{|H(0)|}{\sqrt{2}}$$

$$\boxed{\omega_{3-dB} = \omega_p}$$

$$\left(1 + \frac{s}{\omega_p}\right)^N$$

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

$$|H(0)|^2 = \frac{1}{2}.$$


$$\left[1 + \left(\frac{\omega}{\omega_p}\right)^2\right]^N = \frac{1}{2}$$

$$\boxed{\omega_{3-dB} = \omega_p \sqrt{2^{1/N} - 1}}$$

$$\textcircled{a} N=1$$

$$\omega_{3-dB} = \omega$$

$$N > 2$$

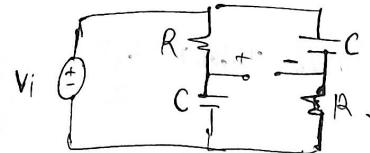

$$I/P - V_p \cos(\omega_p t + \phi)$$

$$\boxed{\omega_p = \frac{1}{RC}}$$


Mag. response

$$\frac{\sqrt{1+(\omega RC)^2}}{\sqrt{1+(\omega_p RC)^2}} = 1$$


$$RC = 1/\omega_p$$

$$\phi(\omega) = -\alpha \tan^{-1}(\omega/\omega_p)$$

$$\begin{aligned} O/P - & V_p \cos(\omega_p t + \phi - \pi/2) \\ & = V_p \sin(\omega_p t + \phi) \end{aligned}$$

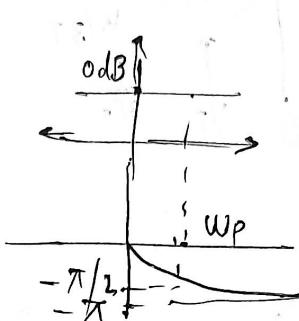

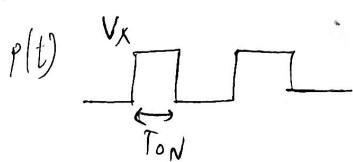Lecture 21:- Pulse response of 1st order RC ckt's.



$$|P(f)| = V_x T_{ON} \operatorname{sinc}(\pi f T_{ON})$$

$$T_{ON} + T_{OFF} = T$$

$$\left| \frac{P(k/T)}{T} \right| = V_x \frac{T_{ON}}{T} \operatorname{sinc}(\pi f T_{ON})$$

$$P(f) = V_x T_{ON} \operatorname{sinc}(\pi f T_{ON})$$

$$x(t) = \sum_{k=-\infty}^{\infty} p(t-kT)$$

$$X(f) = \frac{1}{T} |P(f)| \sum_{k=-\infty}^{\infty} \delta(f - \frac{k}{T})$$

$$= \frac{|P(k/T)|}{T} \sum_{k=-\infty}^{\infty} \delta(f - \frac{k}{T})$$

$\uparrow P(0/T)$


$$\boxed{D = 1/2} \quad \frac{V_x T_{ON}}{T} \frac{\sin(\pi f T_{ON})}{T(k)(\frac{T_{ON}}{T})}$$

$$= DV_x \frac{\sin(\pi k D)}{\pi k D}$$


$$= \frac{V_x}{2} \frac{[\sin(\pi k/2)]}{(\pi k/2)} \rightarrow \begin{cases} 1 & \text{for odd } k \\ 0 & \text{for even } k \end{cases}$$

$$\frac{|P(k/T)|}{T} = \begin{cases} \frac{V_x}{\pi k} & \text{for odd } k \\ 0 & \text{for even } k \end{cases}$$

Total power = $\frac{V_x^2}{2}$

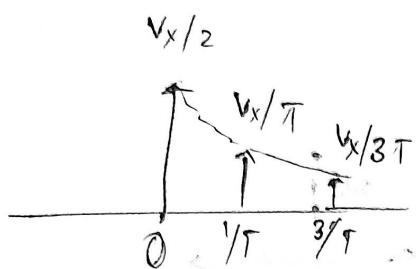

Q.

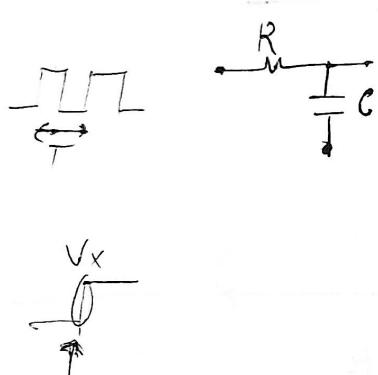

① $T_L < T$

② $T_c \gg T$

The O/P will settle
within 5 time constants ($5T$)

$5T < T/2$

At this pt., the system will think of it as a Step I/p.

At $t = T/2$ Cap. stores a charge of V_x

After the falling, capacitor discharges
thru' the resistor:


$$V_x(1 - e^{-t/T}) \rightarrow t = T/2 \Rightarrow V_x$$

$$V_x e^{-t/T} \rightarrow t = T/2 \Rightarrow 0$$

There are no sudden transitions (S.T. \Rightarrow high frequency)

High frequency changes are all eliminated

② $t \gg T$

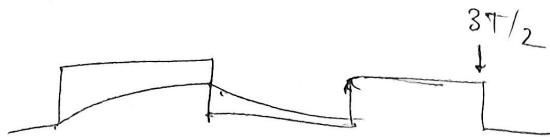

$$V_x \left(1 - e^{-T/2T}\right) \cdot e^{-T/2T} > 0$$

At $t = T/2$

At $t = T$

At $t = 3T/2$

$$\boxed{V_x \left(1 - e^{-T/2T}\right) + V_x \left(1 - e^{-T/2T}\right) e^{-T/2T} \cdot e^{-T/2T}}$$

$$e^{-T/2T} = x$$

$$V_x \left(1 - x\right) + V_x \left(1 - x\right) x^2$$

$$V_x \left(1 - x + x^2 - x^3 + \dots\right)$$


At $t = nT/2$

$$V_x \left(1 - x + x^2 - x^3 + \dots\right) \quad |x| \leq 1$$


$$V_x \cdot \frac{1}{1+x}$$

$$\frac{q}{1+r} \quad r = -x$$

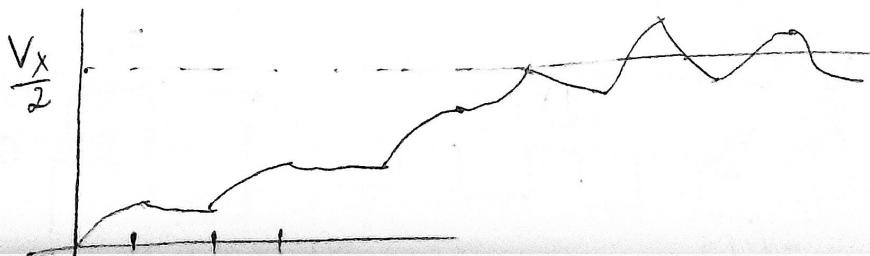
$$\frac{V_x}{1 + e^{-T/2T}} = \frac{V_x}{1+1} = \frac{V_x}{2}$$



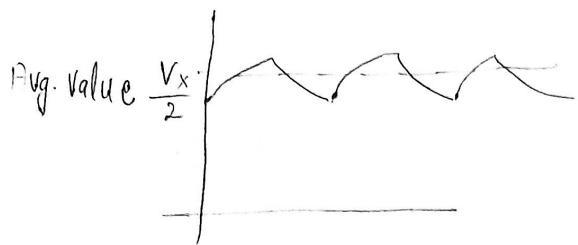Applicati:- To generate a constant D.C. voltage by applying pulse I/p.



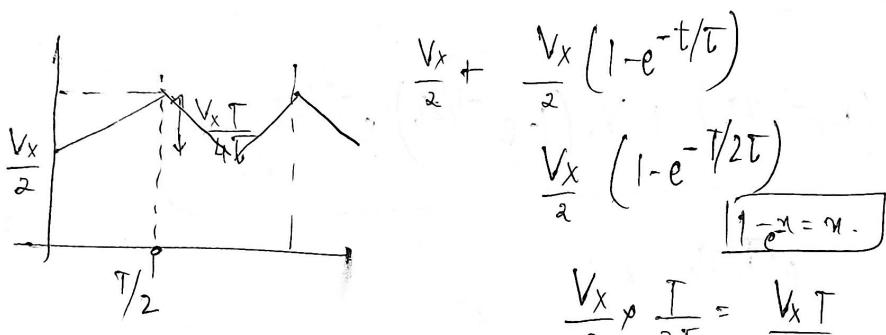Assume Initial Voltage on capacitor $\approx \frac{V_x}{2}$.






In (-)ve half-cycles:-

$$\frac{V_x}{2} \left(1 - \frac{T}{2\tau}\right) = \frac{V_x}{2} - \frac{V_x T}{4\tau}$$

$$\therefore \text{Ripple Value} = \frac{V_x T}{4\tau}$$

This everything was in time domain.

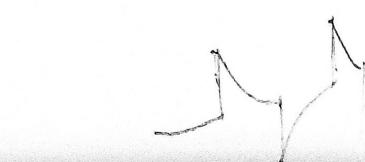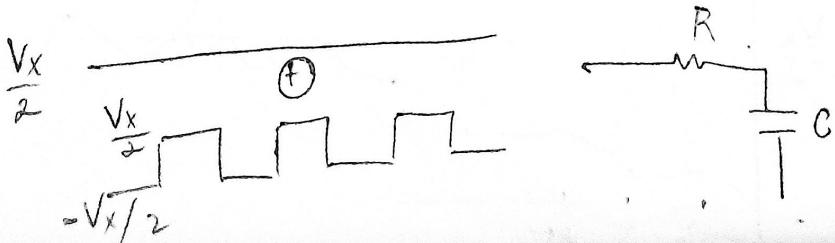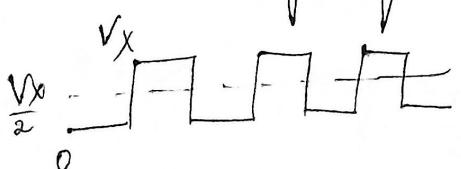

D.C. &

0dB

Steady

$\frac{V_x}{2}$


Hpf:-

I/P


O/P

$-V_x$



$T/2$

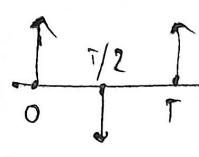


D.C gain of a 1st order system is 1.

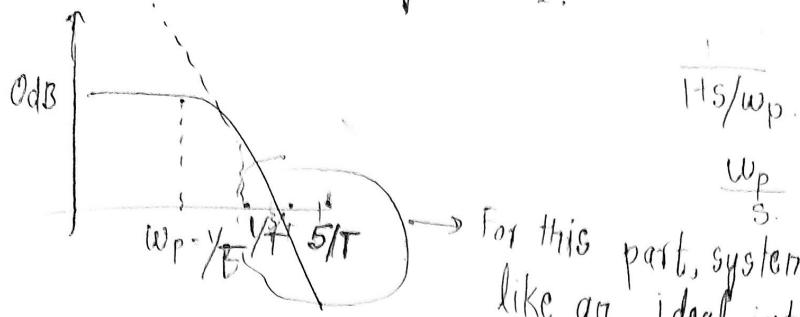


Steady State Transient O/P:-

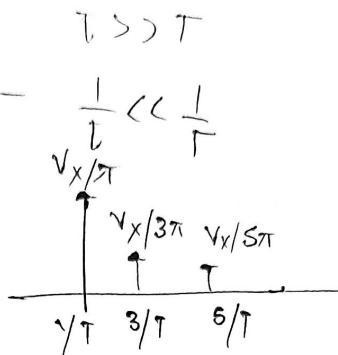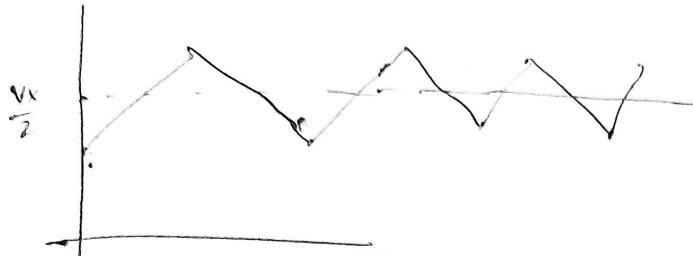

H_{PT}:-

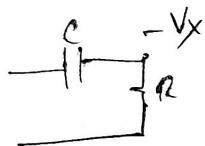

T << T

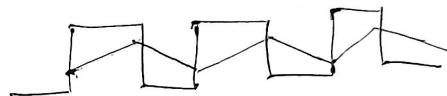

I/P




O/P








-Vx

$$\frac{S/w_p}{1+Ts/w_p}$$

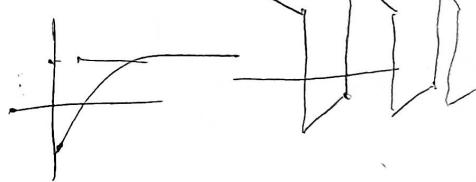

$$T \gg T$$

$$V_R(t) = V_i(t) - V_c(t)$$

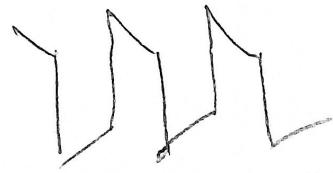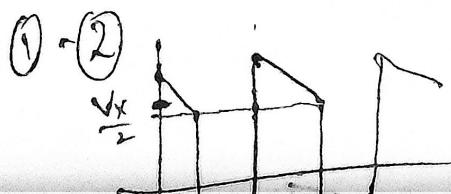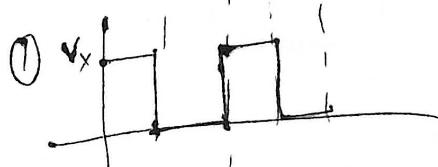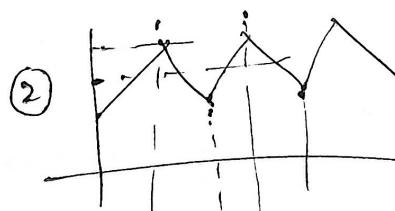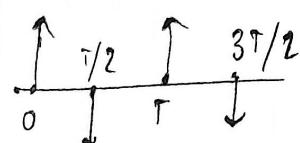

Lecture 22:- Step Response of first order RC ckt.


$$H(s) = \frac{H(0)}{(1+s/w_p)}$$

$$\boxed{|H(0)| \leq 1}$$

$$H(0)V_x(1 - e^{-w_p t}) u(t)$$


$$w_p = \frac{1}{L}$$

$$\frac{H(\infty)(s/w_p)}{(1+s/w_p)}$$

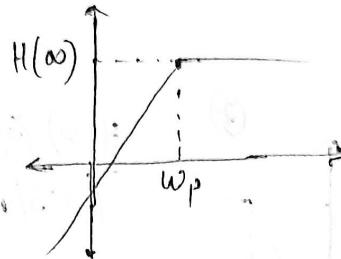


$$H(\infty)V_x e^{-w_p t} u(t)$$


$$\frac{H(0)(1+s/w_2)}{(1+s/w_p)}$$

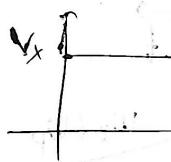



$w_p < w_2$
lagging phase

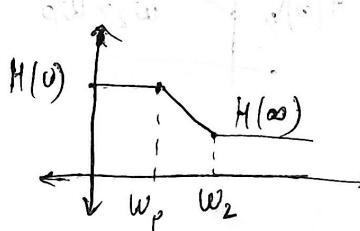




$$H(\infty) < H(0)$$

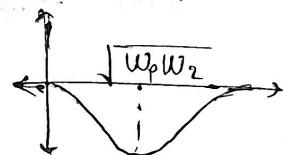

$w_p > w_2$.
leading phase

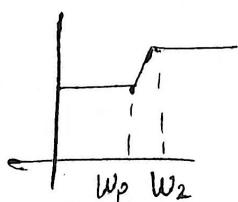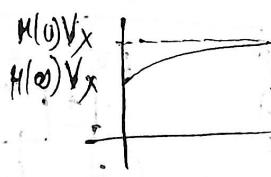


$$H(\infty) > H(0)$$

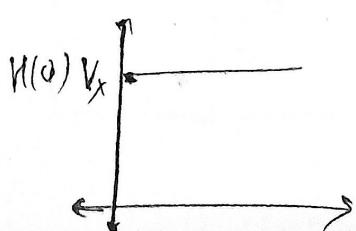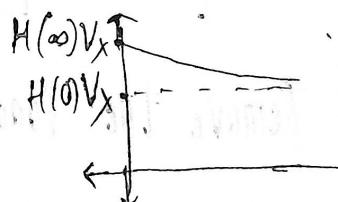
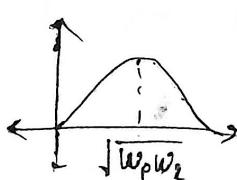


$$H(s) \frac{(1-s/w_2)}{(1+s/w_p)}$$

Phase is always lagging.


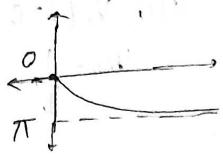


① - ② gives:-

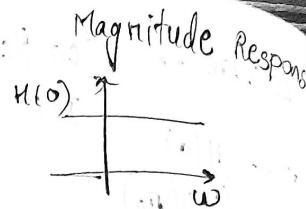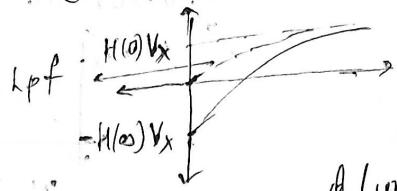


To find

$$\phi(w) = -2 \tan^{-1}(w/w_p)$$

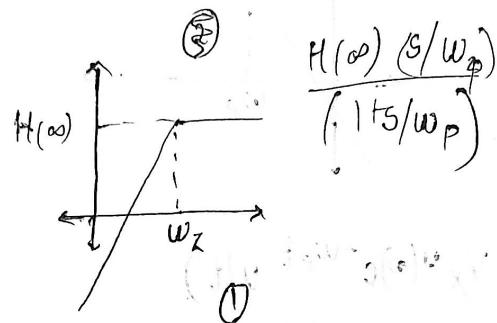
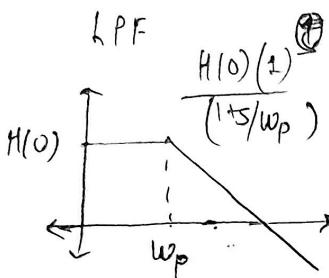


$$\frac{H(0)(1+s/w_2)}{(1+s/w_p)}$$

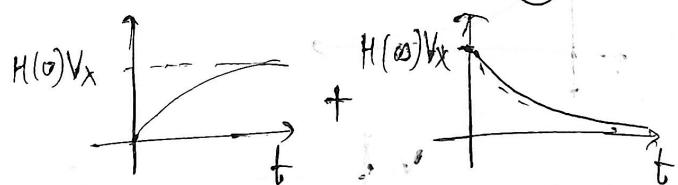


$$H(\omega) = H(0) \frac{w_p}{\omega}$$
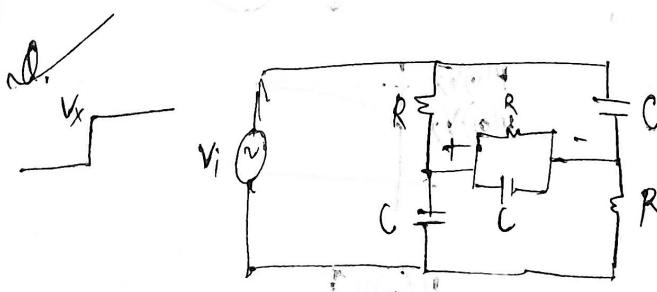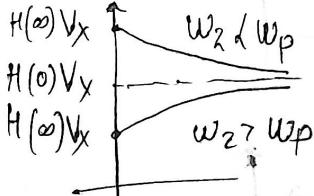
$$H(\omega) = H(0) \frac{w_p}{\omega} \cdot \frac{s}{\omega_2}$$





Remove the load.

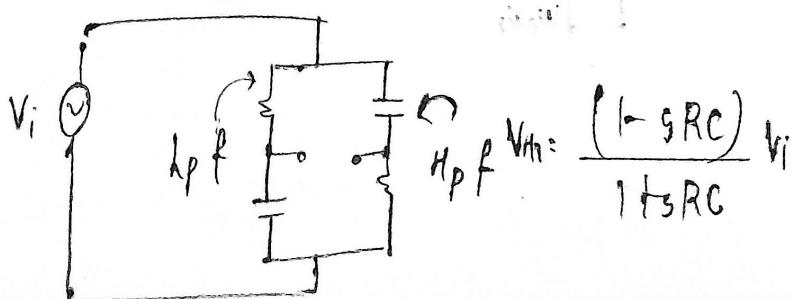

$$H_{pf} V_{in} = \frac{(1 - sRC)}{1 + sRC} V_i$$

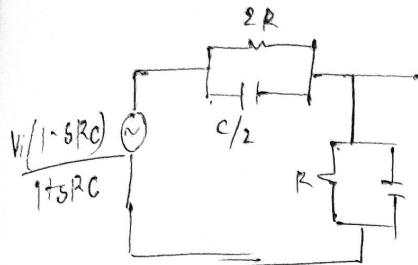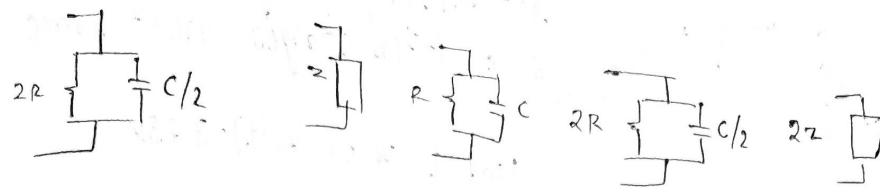
Magnitude response. To find R_{th}, short the I/P



$$\frac{V_o}{V_1} = \frac{2}{k+1} \quad k = \frac{1}{2}$$

$$\frac{V_o}{V_1} = \frac{1}{3}$$
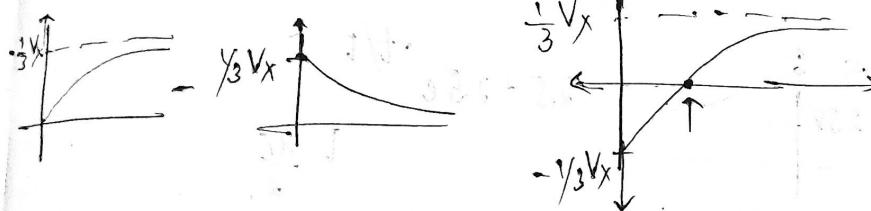
$$V_o = \frac{1}{3} \left(\frac{1-sRC}{1+sRC} \right) V_1$$





$$\frac{1}{3} V_x (1 - e^{-t/T}) \rightarrow \frac{1}{3} V_x e^{-t/T}$$

$$V_o(t) = \frac{1}{3} V_x (1 - 2e^{-t/T})$$

To find response at $t=0$.

$$2.5 + 7.5 e^{-w_p t}$$

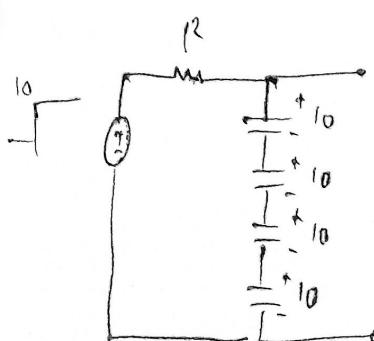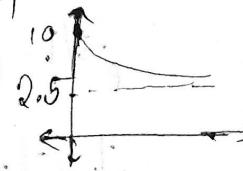

Find t when $V_o = 2.5V$.

$$V_o(\infty) = 10V \quad V_o(0) = 40V$$

$$V_o(t) = 10 + (40-10)e^{-w_p t}$$

$$T = RC/4 \quad V_o(t) = 10 + 30e^{-w_p t}$$

$$40 + 40\Delta V = 10$$


$$4\Delta V = -30$$

$$\Delta V = -7.5V$$

$$10V$$


15

$$\therefore t = T/\ln 2$$

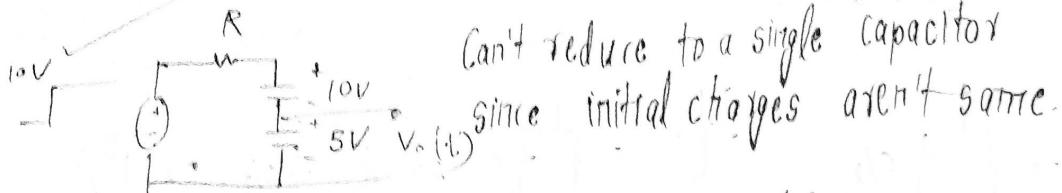

Can't reduce to a single capacitor since initial charges aren't same.



Find t when $V_o(t) = 3.25V$

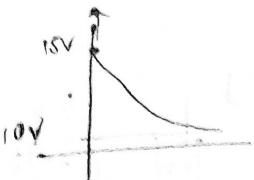

In steady state, ignore resistor

$$\frac{1}{T} \cdot \frac{10+5V}{5V} = 15 + 2\Delta V = 10 \\ 2\Delta V = 5 \\ \Delta V = 2.5$$

$$V(\infty) = 7.5V \\ V(0) = 2.5V$$

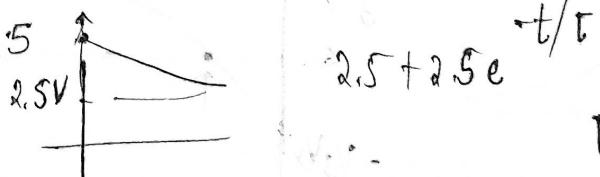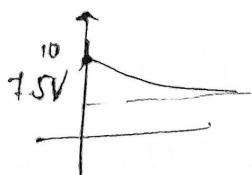

$$T = \frac{RC}{2}$$

$$2.5 + 2.5e^{-t/T} = 3.25$$


$$2.5e^{-t/T} = 0.75$$

$$e^{-t/T} = 0.3$$

$$\frac{t}{T} = -\ln(0.3)$$

$$-\frac{t}{T} = \ln(0.3)$$



$$t = 1.2T$$

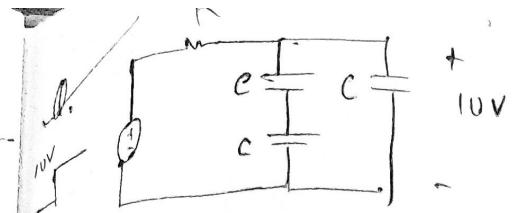

$$c/2 \parallel \frac{V_o(0)}{C}$$


$$V_o(0) \cdot \frac{3C}{2} = 10C$$

$$\boxed{V_o(0) = 6.67V}$$

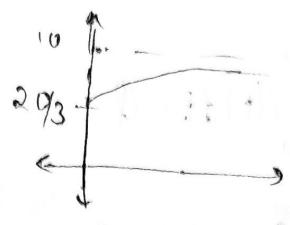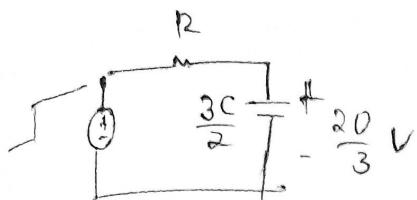


$$20 + \frac{10}{3}(1 - e^{-t/\tau})$$
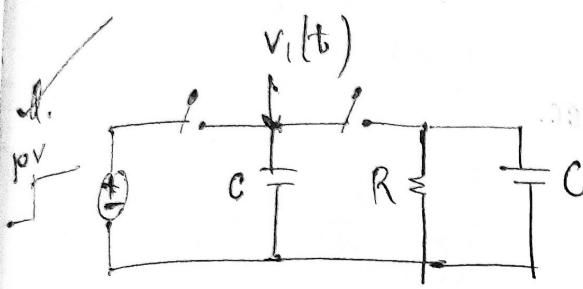
$$V(t) = \boxed{10 - \frac{10}{3}e^{-t/\tau}}$$




$$10V \quad t=0 \quad 0$$


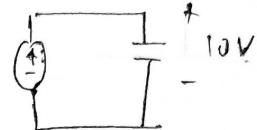


After 10s


$$10 - \frac{10}{3}e^{-10/\tau}$$

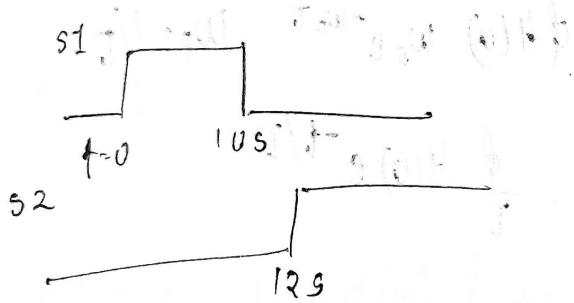

After 10s

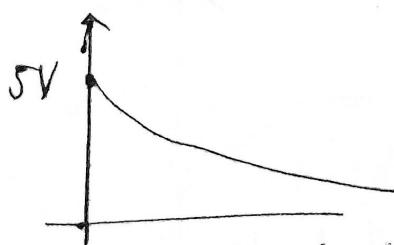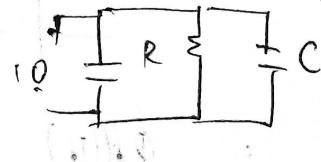


$$2C \parallel \frac{1}{S}V$$

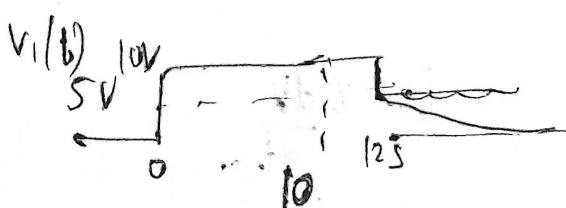

Lecture 23: - Impulse Response

$$\delta(t) \quad \int_{-\infty}^{\infty} \delta(t) dt = 1$$


$t=0$

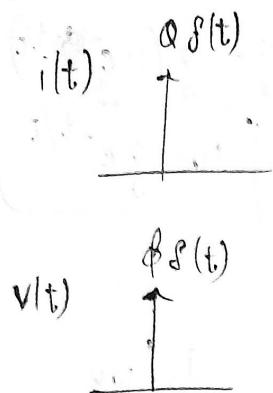


$$\int_{-\infty}^{\infty} i(t) dt = \phi$$

$$\int_{-\infty}^{\infty} v(t) dt = \phi$$

ϕ = Voltage sec.

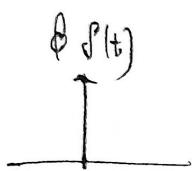

$$\frac{H(0)}{1+s/w_p}$$

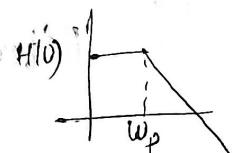

$$\phi H(0) w_p e^{-w_p t} \quad w_p = 1/T$$


$$\frac{\phi}{T} H(0) e^{-t/T}$$

$$\int_{-\infty}^{\infty} x(t) dt = X(0)$$

$$\int = \phi H(0)$$

When impulse is applied, Cap. will behave as short ckt.

LPF: -

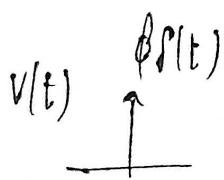


$$i_C = \frac{1}{C} \frac{dV}{dt}$$

$$V = \int \frac{i_C}{C} dt$$

$$V_C = \frac{\phi}{RC} u(t) \quad \text{at } t=0$$

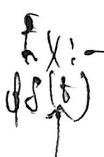And then the I/P goes to 0.
So, cap. will start discharging.



Cap
Cur

Th




$$\phi = V_x T$$


$$V_x e^{-t/T} u(t)$$

HPF:-
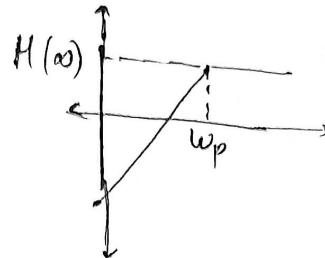
$$H(s) = \frac{H(\infty) (s/w_p)}{1 + s/w_p}$$



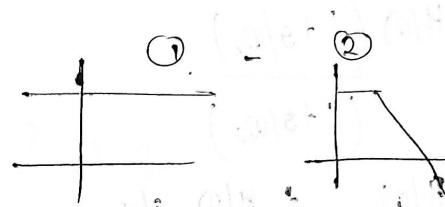
$$H(\infty) \left(1 - \frac{1}{(fs/w_p)} \right)$$




$\phi s(t)$
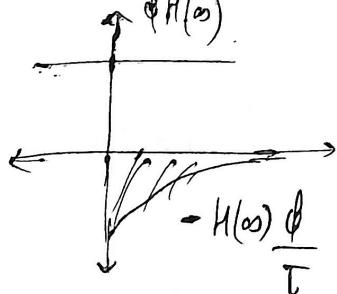
$$\phi H(\infty) s(t) = H(\infty) \phi w_p e^{-w_p t} u(t)$$


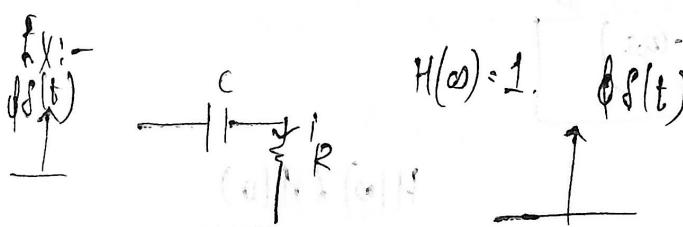
$$\phi H(\infty) + \left[-\frac{H(\infty)\phi}{T} \right] t + \phi H(\infty) = 0. \quad \text{D.C. gain is } 0 \text{ for HPF.}$$



Cap. is short $t=0$.


Current flows thru resistor.

i. $\phi s(t)$

This i^R sets up voltage in the cap


$$V_C = \frac{\phi}{T}$$

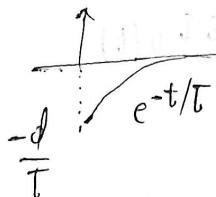s/p is 0 O/P will go to $-\frac{\phi}{T}$



$$\phi = V_x T$$

$$\frac{V_x H(\omega)}{T} \delta(t)$$

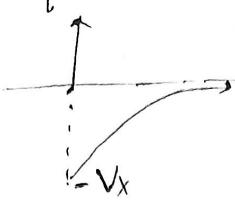


Ex:- General f.

$$H(0) \frac{(1+s/w_p)}{(1+s/w_z)}$$

$$H(\omega) = H(0) \frac{w_p}{w_z}$$

$$\frac{H(0)}{1+s/w_p} + H(0) \frac{s/w_z}{(1+s/w_p)}$$

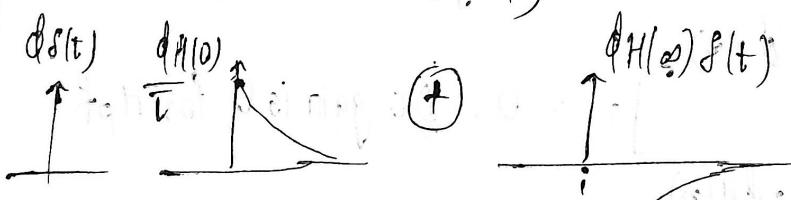
$$\frac{H(0)}{(1+s/w_p)} + H(\omega) \frac{(s/w_p)}{(1+s/w_p)}$$



$$\boxed{w_p \phi H(0) e^{-w_p t} + H(\omega) \phi (s(t) - w_p e^{-w_p t})}$$




$$H(\omega) > H(0)$$



$$w_z < w_p$$

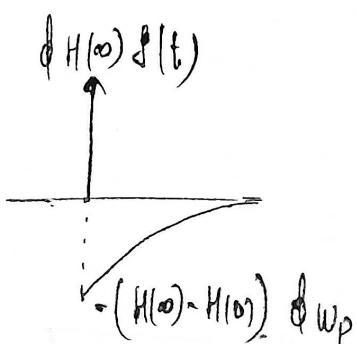

$$H(\omega) < H(0)$$

$$w_p < w_z$$

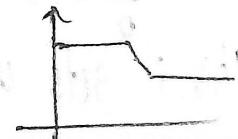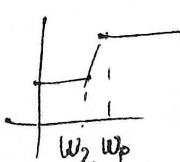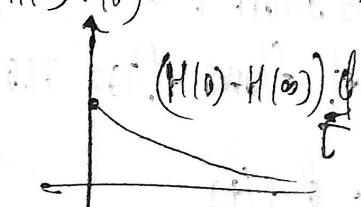

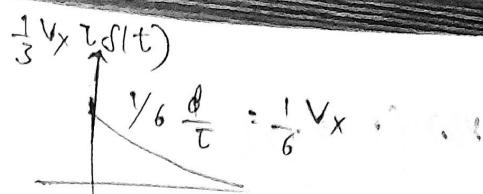
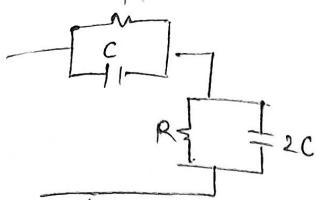


$$H(\infty) = \frac{1}{3}$$

$$H(0) > H(\infty)$$

$$H(0) = \frac{1}{2}$$

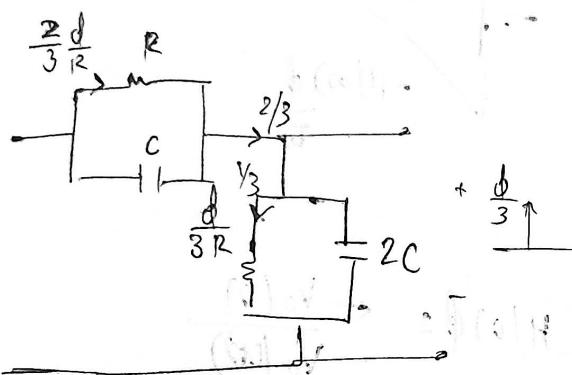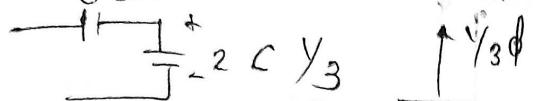When impulse $\frac{2}{3}\delta$ is applied, resistors can be ignored



$$\text{Remaining Current} = \frac{1}{3} \frac{\delta}{R} \delta(t)$$

will split betw 2 capacitors

Cdi

$$\therefore i_{2C} = \frac{2}{3} \times \frac{1}{3} \times \frac{\delta}{R} \delta(t)$$


$$V_{2C} = \int \frac{1}{2C} \left(\frac{2}{3} \times \frac{1}{3} \frac{\delta}{R} \delta(t) \right)$$

$$= \frac{1}{9} \frac{\delta}{T} u(t)$$

$$\boxed{V_{2C} = \frac{\delta}{9T} = \frac{V_x}{9}}$$

$$\omega_p = \frac{2}{3RC}$$

$$\omega_z = \frac{1}{RC}$$


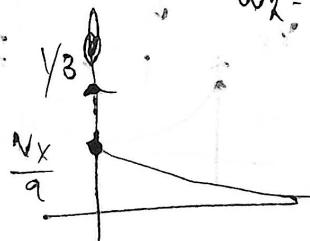


$$\boxed{\omega_p \ll \omega_z}$$

$$\frac{H(0)}{1+s/w_p} \left(1 - s/w_p\right)$$

$$\frac{H(0)}{1+s/w_p} - H(\infty) \frac{s/w_p}{(1+s/w_p)}$$



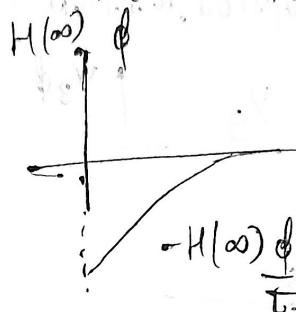
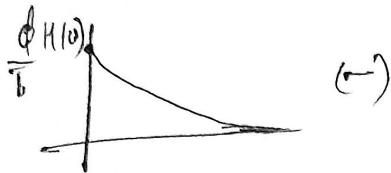
$$H(0) w_p e^{-w_p t} u(t) - H(\infty) \phi(s(t) - w_p e^{-w_p t} u(t))$$



$$\begin{aligned} & \frac{\phi(H(0))}{t} \\ & \downarrow \\ & \frac{\phi(H(0) + H(\infty))}{t} \\ & \downarrow \\ & -H(\infty) \phi(s(t)) \end{aligned}$$

$$H(0) \phi = \frac{V_o(0)}{V_o(\infty)}$$

$$\phi: V_x T$$

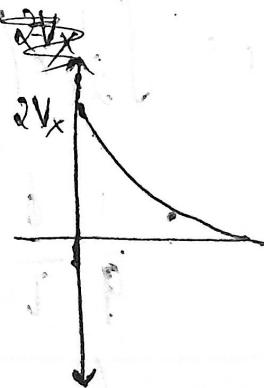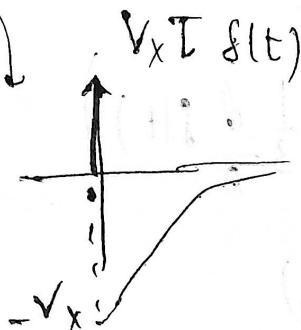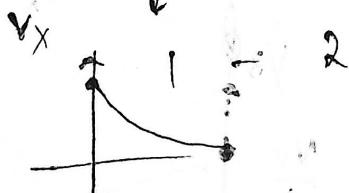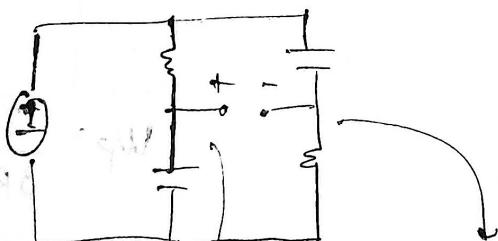

$$-V_x t \delta(t)$$

Lecture 24: - Ramp response of 1st order ckt's

$$v(t) = mt u(t)$$

$$\text{L.T. } [v(t)] = \frac{m}{s^2}$$

LPF :-

$$H(s) = \frac{H(0)}{(1+s/\omega_p)}$$

$$V_i H(s) = \frac{m H(0)}{s^2} \frac{1}{(1+s/\omega_p)}$$

$$= H(0)m \frac{1}{s^2} \left[\frac{1}{s} - \frac{1}{1+s/\omega_p} \right]$$

$$= m H(0) \frac{1}{s^2} \left[\frac{1}{s} - \frac{\omega_p}{1+s/\omega_p} \right]$$






$$= m H(0) \left[\frac{1}{s^2} - \left(\frac{1}{\omega_p} \right) \left[\frac{1}{s} - \frac{\omega_p}{1+s/\omega_p} \right] \right]$$


\downarrow
ILT

$$m H(0) \left[t u(t) - T \left(1 - e^{-\omega_p t} \right) u(t) \right] \rightarrow ①$$

If $H(0)=1$ & $t \gg T$

$$m H(0) \left[(t - T) u(t) \right]$$

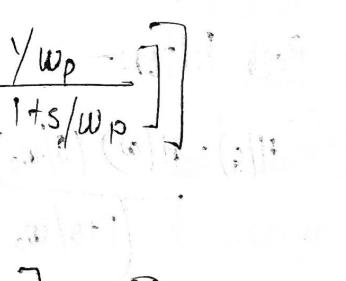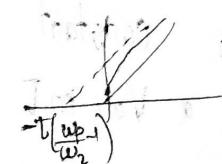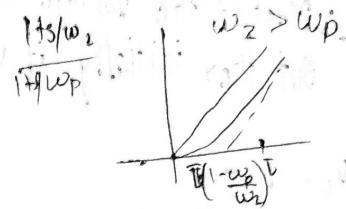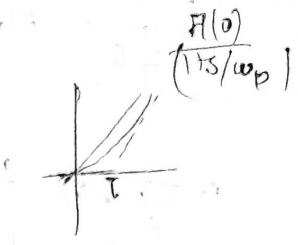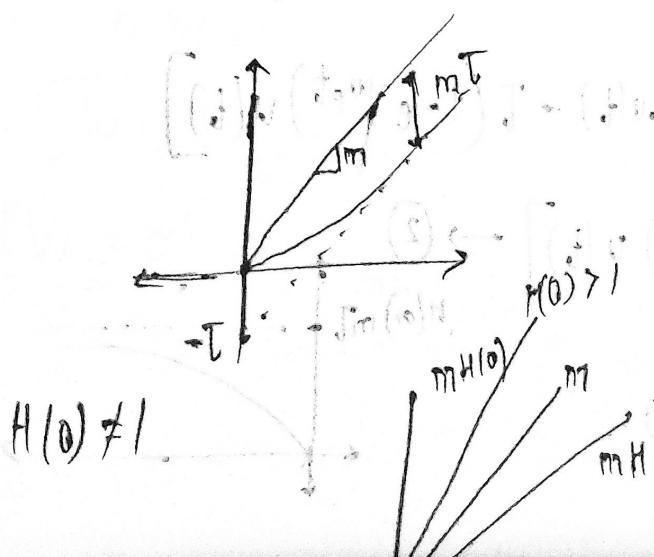

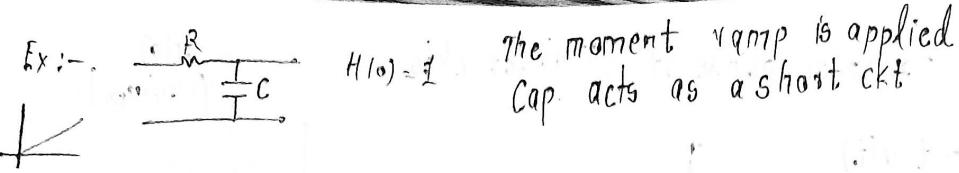

$\frac{m}{R} u(t)$ flows across R & C .

For small values of t , $\frac{1}{C}$ behaves like an integrator

At steady state, Cap. Z_{imp} becomes very large

: Most of the voltage would appear across the capacitor.

But then initially, it was taking time to build that voltage.

$$V_C = \text{ramp}$$

$$i_C = \text{step (constant)}$$

\therefore this constant current i_C flows through R generating

$$\text{a } V_R = mT$$

* High Pass Filter:-

$$H(s) = H(\infty) \frac{(s/w_p)}{(1+s/w_p)}$$



$$H(\infty) \left[1 - \frac{1}{(1+s/w_p)^2} \right]$$

$$\frac{m}{s^2}$$

From ①

$$mH(\infty) \left[mtu(t) - \left[mtu(t) - T \left(1 - e^{-w_p t} \right) u(t) \right] \right]$$
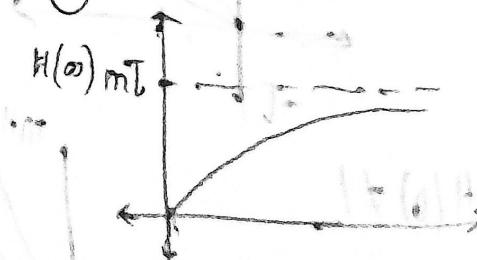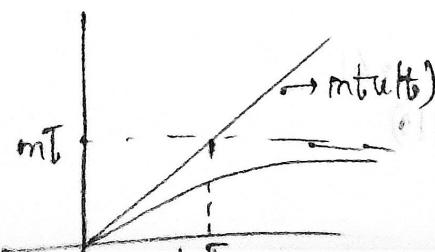
$$H(\infty) \left[mT \left(1 - e^{-w_p t} \right) u(t) \right] \rightarrow ②$$



$$H(s) = \frac{1}{1+s/w_p} \quad (\text{Assume})$$

$$\boxed{\frac{s/w_p}{1+s/w_p} \approx 1} \quad \text{At } t=0.$$

$\therefore V_o = V_i$

At $t \gg T$ (steady state)

$$\frac{s/w_p}{1+s/w_p} \approx \frac{s/w_p}{s/w_p + sT} = sT \quad (\text{Ideal differentiator})$$

$$\frac{d}{dt} (m t u(t)) = T \quad \frac{du}{dt} = mT$$

D.C. gain is 0 for a hpf.

Ex:-



$$H(s) = \frac{SRC}{1+sRC}$$

At $t=0$; when ramp is applied; C is short and voltage appears across R


$$V_o = V_i \text{ at } t=0$$

At time Tes ; $V_c = \text{ramp}$ and $i_p = \text{constant}$
 $v = mtu(t)$

$$i = mCu(t)$$

$$V_R = mRCu(t)$$

$$V_R = mT$$

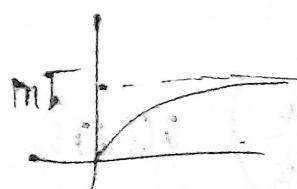

General Transfer f:-

i) Finite zero & a pole

$$\frac{H(0)(1+s/w_2)}{(1+s/w_p)}$$

$$H(0) \cdot \frac{w_p}{w_2} \times \frac{s}{w_p} = H(\infty)$$

$$= \frac{H(0)}{1+s/w_p} + \frac{H(0)s/w_2}{1+s/w_p}$$

$$= \underbrace{\frac{H(0)}{1+s/w_p}}_{L_p f} + \underbrace{\frac{H(\infty)s/w_p}{(1+s/w_p)}}_{H_p f}$$

From (1) & (2):-


$$= H(0) m[t u(t) - T(1 - e^{-w_p t}) u(t)] + H(\infty) m[T(1 - e^{-w_p t}) u(t)]$$

$$= H(0) m t u(t) - m T [H(0) - H(\infty)] (1 - e^{-w_p t}) u(t)$$

$$= H(0) m \left[t u(t) - \underbrace{\left(1 - \frac{w_p}{w_2}\right)}_{-T} \cdot T (1 - e^{-w_p t}) u(t) \right]$$

For a 1st order system ($L_p f$) $w_2 \rightarrow \infty$.

Here; w_2 is at a finite frequency

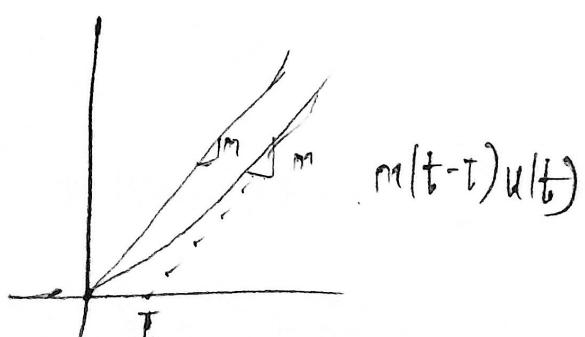

Factor of $\left(1 - \frac{w_p}{w_2}\right)$ occurs.

a) w_p
logging

Stea

b) w_p

(1 -

m

- $T\left(\frac{w_p}{w_2}\right)$


0.

H(0)

w_p

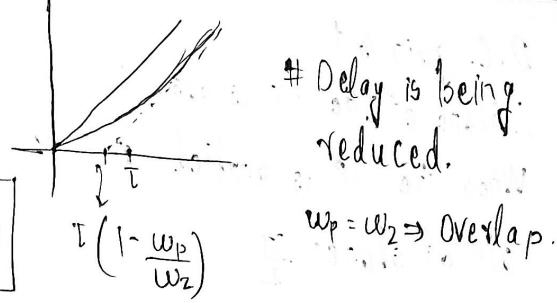a) $w_p < w_2 \Rightarrow \left(1 - \frac{w_p}{w_2}\right) < 1$
lagging phase
 $t = \pi \frac{1}{\omega_p}$


Steady state error = $m t \left(1 - \frac{w_p}{w_2}\right)$



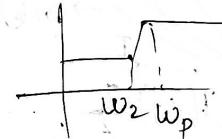
b) $w_p > w_2$

$$\left(1 - \frac{w_p}{w_2}\right) \quad \text{Assume } H(0) = 1 \quad \therefore H(\infty) > 1$$


$$m(t u(t)) = \left(1 - \frac{w_p}{w_2}\right) t \left(1 - e^{-w_p t}\right) u(t)$$


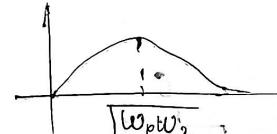
$$m(t u(t)) + \left(\frac{w_p}{w_2} - 1\right) t \left(1 - e^{-w_p t}\right) u(t)$$


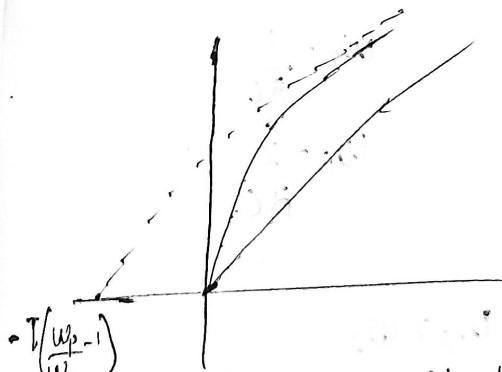
$$m(t + t \left(\frac{w_p}{w_2} - 1\right))$$




At $t=0 \Rightarrow$ The O/P rises faster.

$$2 = -\frac{s}{RC}$$


Steady state error = $m t \left(\frac{w_p}{w_2} - 1\right) \quad s = -2RC$

$$\frac{1}{1 + \frac{1}{RCST}}$$

$$\frac{RCSH}{RCST + 2}$$

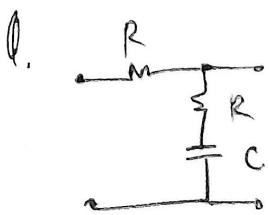
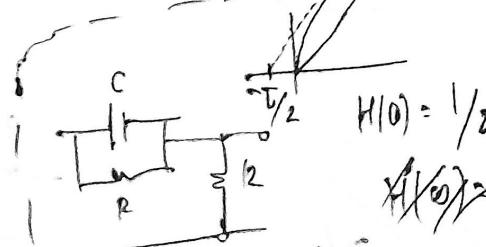
$$H(0) = 1, \quad H(\infty) = \frac{1}{2}$$



$$H(0) = \frac{1}{2}, \quad H(\infty) = 0$$

$$\frac{R}{2 + \frac{R}{RCST}}$$

$$R(RCST)$$

$$w_p (w_2) \frac{1 + sRC}{1 + 2sRC}$$

$$H(\infty) = H(0) \frac{w_p}{w_2}$$

$$w_2 > w_p$$

$$\frac{w_p}{w_2} = \frac{1}{2}$$




$$w_2 = -\frac{1}{RC} \quad w_p > w_2$$

$$w_p = -\frac{2}{RC}$$

H(s)


D.C. gain is 1.

∴ Slope of the O/P is also 1.

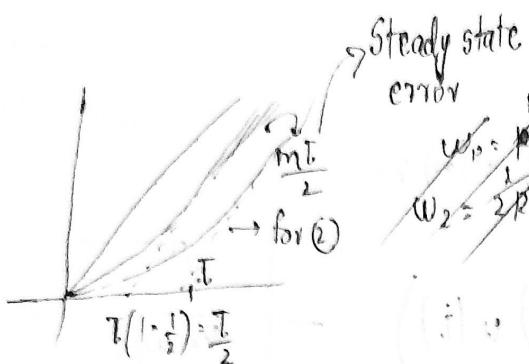When the T/P is applied at + ω_0 ckt will becomeO/P of slope: $\frac{m}{2}$ 

$$w_p = \frac{1}{2RC}$$


$$w_2 = \frac{1}{RC}$$

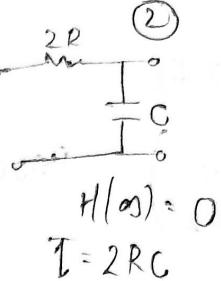

$$H(\omega) = 0$$

$$T = 2RC$$

Q.

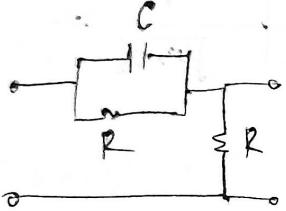


$$\text{D.C. gain} = H(0) = \frac{1}{2}$$

$$\frac{1}{2} \left(\frac{1+sRC}{1+s\frac{RC}{2}} \right)$$


$$w_2 = \frac{1}{RC}$$

$$w_p = \frac{2}{RC}$$

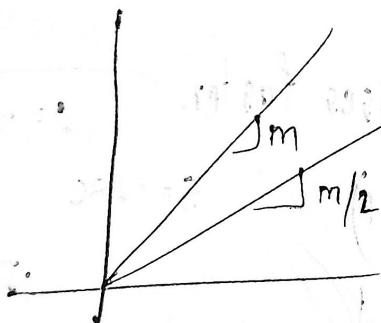

$$w_p > w_2$$


$$T = \frac{RC}{2}$$

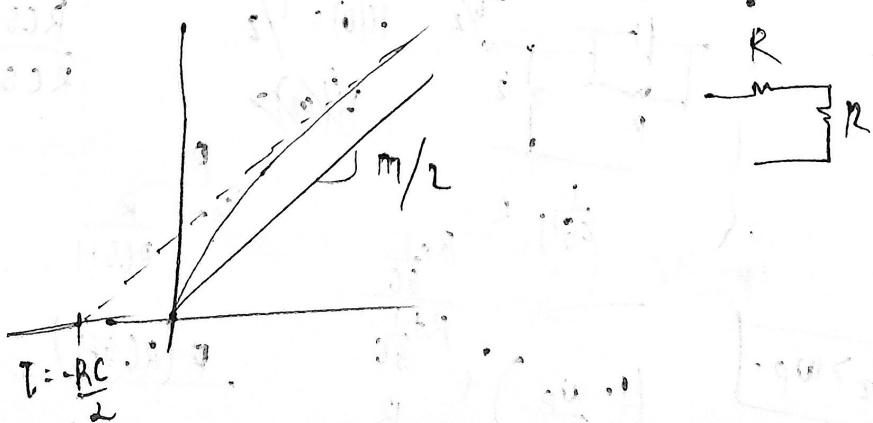


$$T = \frac{RC}{2}$$

$$\frac{H(0)}{(1+s/\omega_p)}$$
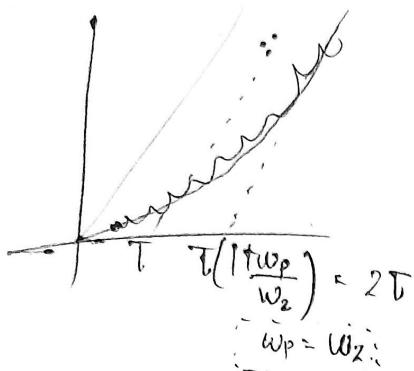
$$mH(0) \left[t u(t) - \left(\frac{1}{1+s/\omega_p} \right) t (1 - e^{-\omega_p t}) u(t) \right]$$




"Extra Delay" occurs.

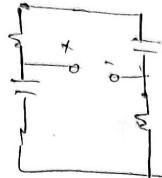

Here, slope of O/P doesn't rise parabolically, instead it rises linearly or same as the I/p.

$$\frac{1}{1+s(2\zeta)}$$


For a 1st order system; $H(\infty) = 0$.

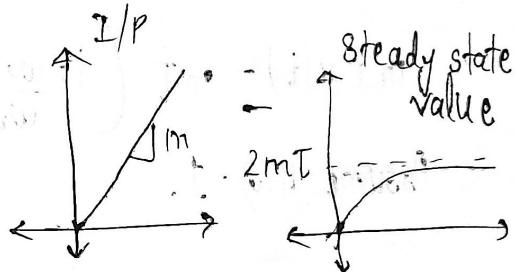

$$t u(t) = 2T (1 - e^{-\omega_p t}) u(t)$$

$$t u(t) = 2T \left(\frac{t}{T} \right) u(t)$$


$$-t u(t)$$

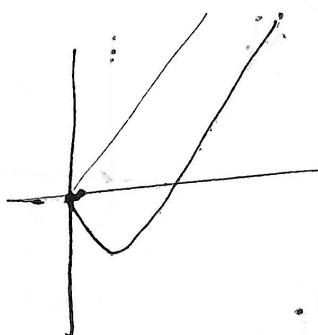

Lecture 24a! - Ramp response of 1st order systems with right half plane zero.

$$H(s) = H(0) \frac{(1-s/w_2)}{(1+sw_p)} \quad \boxed{H(\infty) = H(0) \frac{w_p}{w_2}}$$


$w_p < w_2$

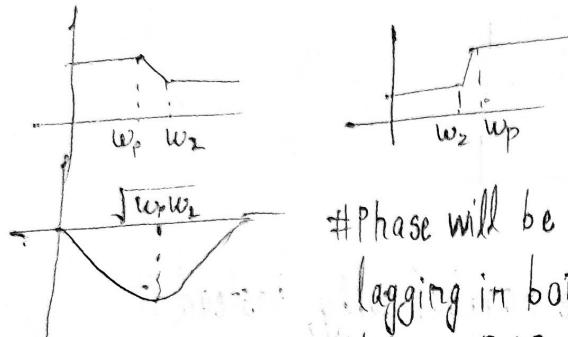

Phase will be lagging in both cases as it is a RHP zero.



$$m t u(t) = m T \left(1 + \frac{w_p}{w_2} \right) \left(1 - e^{-w_p t} \right) u(t)$$

Assume $H(0) = 1$.

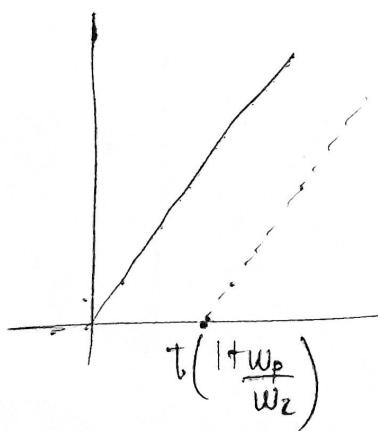

$$m \left[t - T \left(1 + \frac{w_p}{w_2} \right) \right] \rightarrow m(t - 2T)$$
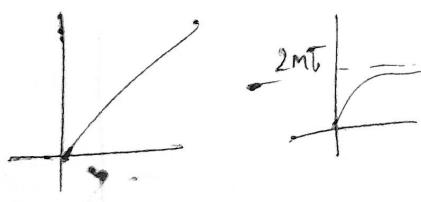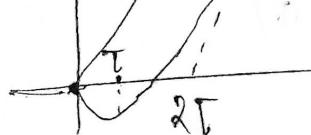
$$\times m(t - 2T \left(1 - e^{-w_p t} \right))$$



$$\frac{1 - s/w_2}{1 + s/w_p} \approx -\frac{(s/w_2)}{s/w_p} = -\frac{w_p}{w_2}$$

2/P

$$m t u(t) \rightarrow m t \underline{w_p} u(t)$$

At $t = 2T$

I/p is at $2mT$







This will reach $2mT$ at $t = \infty$.

(X) at $t = 2T$ is a (+)ve value for

Ex-

this o/p rises parabolically.

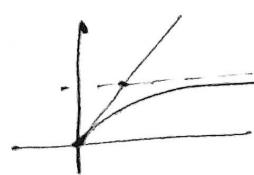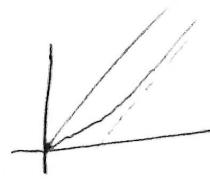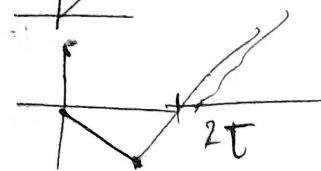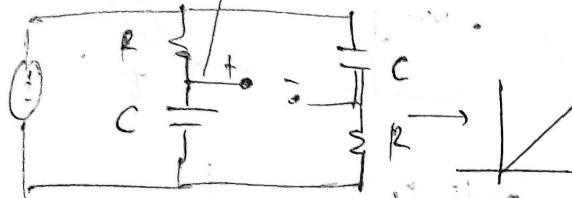

$$m(t+2T) - T(1 - e^{-\omega_p t}) = m(T(1 - e^{-\omega_p t}))$$

$$m(t + 2T)(1 - e^{-\omega_p t})$$



Pulse Response:-



i) $T \gg t$





ii) $t \gg T$ $V_c(t)$

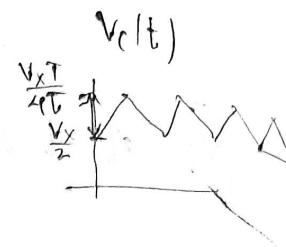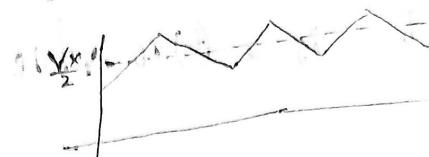



Q. 8.



Ramp Response:-

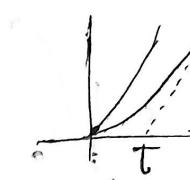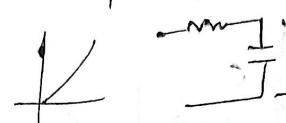

$$i) V_r(t) = V_i(t) - V_c(t)$$

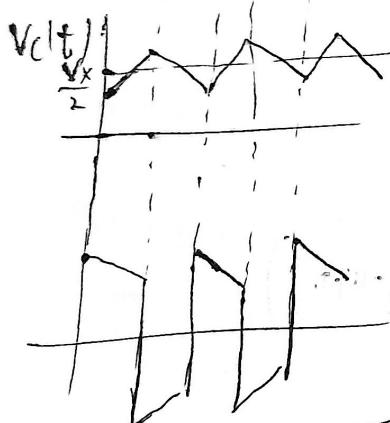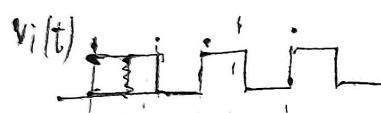




$$\frac{(1+s/w_p)}{(1+s/w_z)}$$

$$mH(0) \left[t u(t) - t \left(1 - \frac{w_p}{w_z} \right) \left(1 - e^{-w_p t} \right) u(t) \right]$$

$$\frac{w_p}{w_z} < 1$$

$$\frac{w_p}{w_z} > 1$$

$$\frac{(1-s/w_z)}{(1+s/w_p)}$$

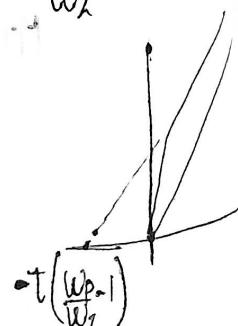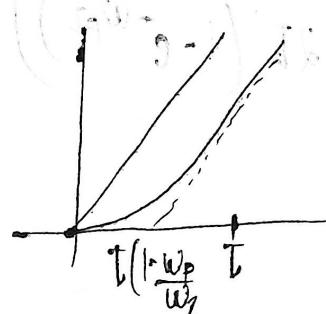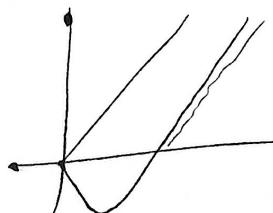

Q. 9.