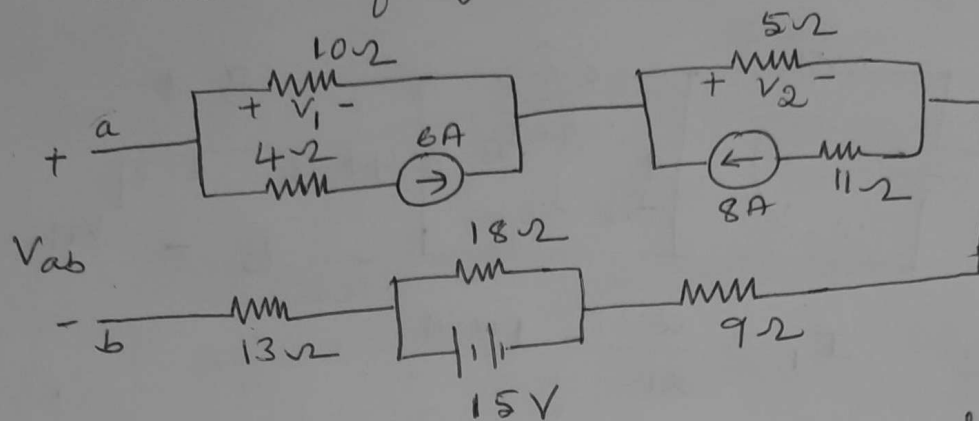


Ex: Determine the v/g drop V_{ab} across the open ckt in the ckt of Fig



Solution: No current flows in the 9Ω and 13Ω resistors \therefore zero volts across each of them.


same 6A source current flows through the 10Ω resistor and $^{\text{same}}$ 8A current flows through 5Ω resistor.

$$V_1 = -6 \times 10 = -60V, \quad V_2 = 8 \times 5 = 40V$$

$$V_{ab} = V_1 + V_2 - 15 = -60 + 40 - 15 = -35V$$

$$\boxed{V_{ab} = -35V}$$

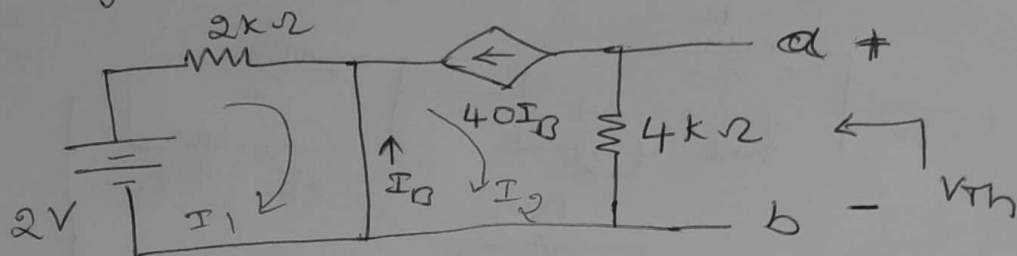Ex: Find the Thevenin equivalent ckt shown in Fig at the terminal a-b



Solution: $I_1 = \frac{2}{2K} = 1\text{mA}$

$$I_2 = -40 I_B$$

$$I_B = I_2 - I_1 = -40 I_B - 1\text{m}$$

$$I_B + 40 I_B = -1\text{m}$$

$$41 I_B = -1\text{m}$$

$$I_B = \frac{-1\text{m}}{41} = -0.0243\text{mA}$$


~~$V_{th} = 4K(-40 I_B)$~~

$$V_{th} = 4K I_2 = 4K(-40 I_B)$$


$$V_{th} = (4K)(-40)(-0.0243\text{mA})$$

$$V_{th} = 3.88\text{V} \approx 3.9\text{V}$$

To find I_{SC}

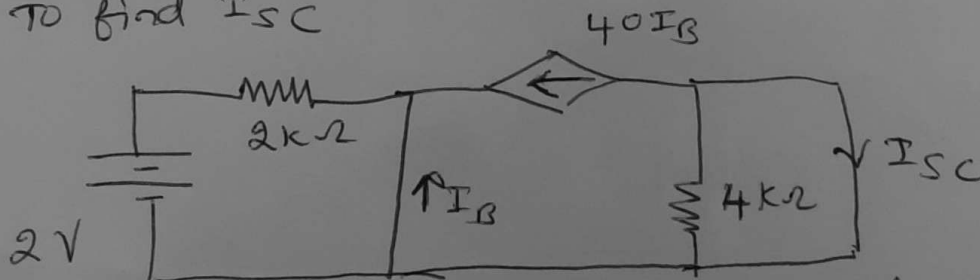

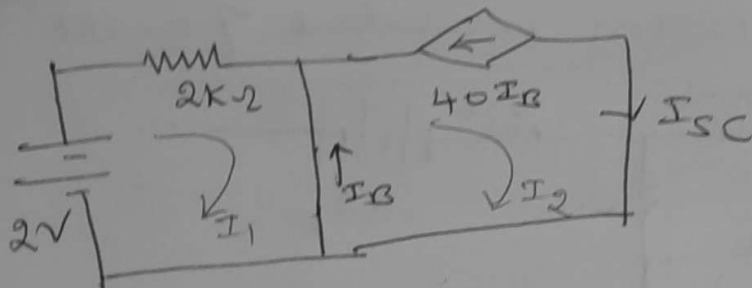Current through $4k\Omega = 0$ \because node $V_B = 0$ since of short ckt



$$I_1 = \frac{2}{2k} = 1mA$$

$$I_2 = I_{sc} = -40I_1$$

$$I_1 = I_2 - I_1 = -40I_1 - 1mA$$

$$41I_1 = -1mA$$


$$I_1 = -0.0243mA$$

$$I_2 = I_{sc} = -40(-0.0243mA)$$


$$I_{sc} = 0.972mA$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{3.9}{0.972} \approx 4k$$


$$R_{th} = 4k$$

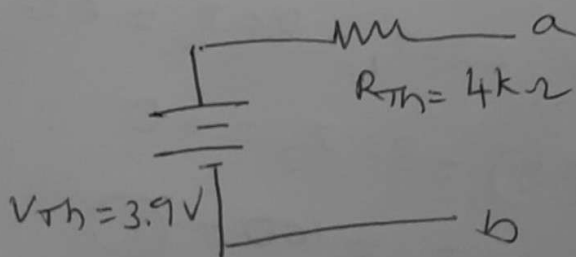

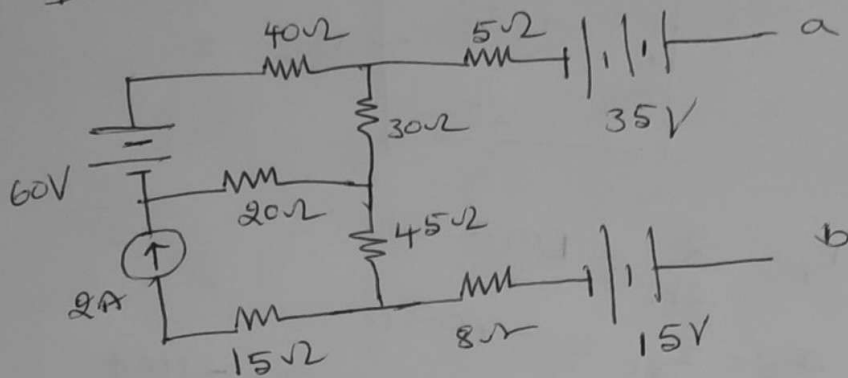Ex: Determine Norton equivalent of the ckt



Solution Find I_N (I_{sc})

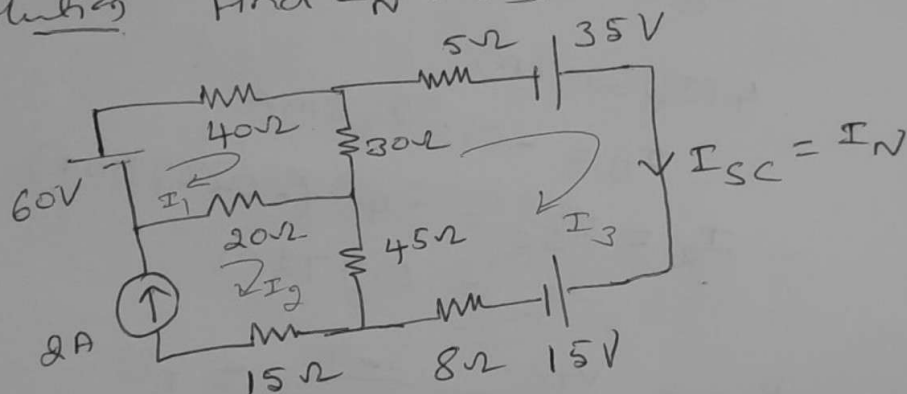

KVL to mesh 1

$$40I_1 + 30(I_1 - I_3) + 20(I_1 - I_2) = 60$$

$$I_2 = 2A$$

$$40I_1 + 30I_1 - 30I_3 + 20I_1 - 20I_2 = 60$$

$$90I_1 - 20(2) - 30I_3 = 60$$

$$90I_1 - 30I_3 = 100 \quad (1)$$

KVL to mesh 3

$$5I_3 - 35 + 15 + 8I_3 + 45(I_3 - I_2) + 30(I_3 - I_1) = 0$$

$$5I_3 - 20 + 8I_3 + 45I_3 - 90 + 30I_3 - 30I_1 = 0$$

$$-30I_1 + 88I_3 = 110 \quad (2)$$

*3


solving eqn ① and ②

$$I_1 = 1.724, I_3 = 1.837A$$

$$I_N = I_{SC} = I_3 = 1.837A$$

To find R_N

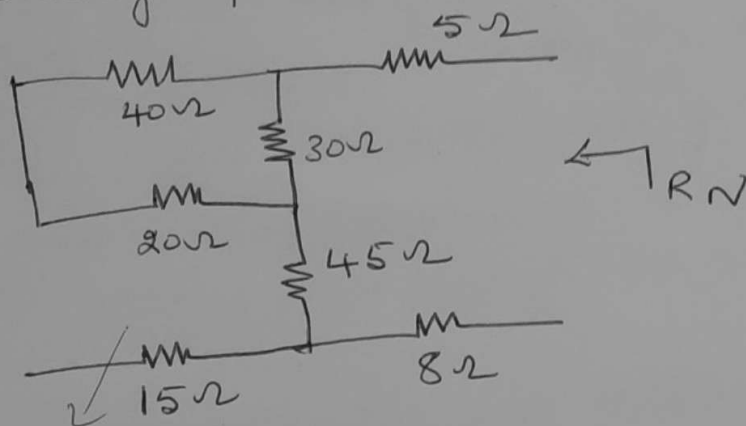Replace Vg source by short and current source by open circuit



not to consider.

$$\cancel{(40 \parallel 20)} + 30 =$$

$$(40 + 20) \parallel 30 = 20 \Omega$$

$$20 \Omega + 5 + 45 + 8 = 78 \Omega$$

$$R_N = 78 \Omega$$

