

unit 2  
tutorial sheet

## Elements of Electronics Engineering [22EC13]

## Tutorial 2

- An enhancement type NMOS transistor with  $V_t = 0.8V$  and  $k = 2mA/V^2$ , find the drain current for each of the following cases:  
 $\cancel{a) V_{GS} = 5V \text{ and } V_{DS} = 1V.}$   $\cancel{b) V_{GS} = 2V \text{ and } V_{DS} = 1.2V.}$   
 $\cancel{c) V_{GS} = 0.6V \text{ and } V_{DS} = 0.2V.}$   $\cancel{d) V_{GS} = V_{DS} = 3V.}$
- An N-channel enhancement type MOSFET with  $V_{th} = 1V$  conducts a current  $I_D = 100\mu A$  when  $V_{GS} = V_{DS} = 1.5V$ . Find the value of  $I_D$  for  $V_{GS} = 2.5V$  and  $V_{DS} = 4V$ . Also calculate the value of  $r_{DS}$  for small values of  $V_{DS}$ , when  $V_{GS} = 3V$ .
- An n-channel MOSFET is used as an amplifier with a drain resistance of  $20k\Omega$ . It is biased such that  $V_{GS} = 4V$  and  $V_{DS} = 5V$ . If  $V_{th} = 0.8V$  and  $k = 1.5mA/V^2$  for the MOSFET, determine the transconductance,  $g_m$ , and the voltage gain.
- An N-channel enhancement type MOSFET with  $V_{th} = 0.7V$ ,  $I_D = 100\mu A$  when  $V_{GS} = V_{DS} = 1.2V$ . Find  $I_D$  and  $g_m$  when  $V_{GS} = 1.5V$  and  $V_{DS} = 3V$ .
- Find  $t_{db}$  for the small value of  $V_{DS}$  when  $V_{th} = 0.7V$ ,  $V_{GS} = 3.2V$  and  $k = 2mA/V^2$ .
- A voltage amplifier needs  $10mV$  input to give a certain output. When negative feedback is provided to this amplifier, it needs  $4V$  to deliver the same output. If the closed loop gain of the amplifier is  $40dB$ , determine the open loop gain of the amplifier and the feedback factor.
- An amplifier with an open loop gain of  $1000$  delivers a certain output power at  $10\%$  harmonic distortion when the input signal is  $10mV$ . If  $40dB$  negative voltage series feedback is provided to this amplifier, determine the required input signal so that the output power remains the same and also find the new % harmonic distortion.
- An amplifier has a gain of  $40dB$ , bandwidth of  $300kHz$ , distortion of  $15\%$ , input impedance of  $10k\Omega$  and an output impedance of  $1k\Omega$ . If voltage series negative feedback of  $3.9\%$  is given to this amplifier, calculate the gain, input impedance, output impedance, bandwidth and distortion of the amplifier with negative feedback.

open loop  $\rightarrow A$   
closed loop  $\rightarrow A_f$

Course Co-ordinator Name

Course Co-ordinator Signature

1)  $V_{GS} = V_{GS} - V_t$   
 $1.5 > 1.5 - 1$   
 $\Rightarrow$  saturation  
 $I_D = \frac{k}{2} (V_{GS} - V_t)^2$   
 $100\mu = \frac{k}{2} (1.5 - 1)^2$   
 $k = 800\mu A = 0.8mA$

2)  $V_{GS} = V_{GS} - V_t$   
 $4 > 4 - 1$   
 $\Rightarrow$  saturation  
 $I_D' = \frac{k}{2} (V_{GS} - V_t)^2$   
 $= \frac{800\mu}{2} (2.5 - 1)^2$   
 $= \frac{800\mu}{2} \times \frac{9}{4}$   
 $= 900\mu A$   
 $I_D' = 0.9mA$

3)  $g_m = \frac{1}{r_{DS}} = \frac{1}{k(V_{GS} - V_t)}$   
 $= \frac{1}{1.5m(4 - 0.8)}$   
 $= \frac{1}{1.5m \times 3.2}$   
 $g_m = 4.8m$   
 $r_{DS} = \frac{1}{g_m} = \frac{1}{4.8m} = 0.21k$   
 $A_v = -g_m R_D$   
 $= -4.8m \times 20k$   
 $A_v = -96$

4)  $V_{GS} = V_{GS} - V_t$   
 $1.2 > 1.2 - 0.7 = 0.5$   
 $\Rightarrow$  saturation  
 $I_D = \frac{k}{2} (V_{GS} - V_t)^2$   
 $100\mu = \frac{k}{2} (0.5)^2$   
 $k = 800\mu A$   
 $I_D = \frac{k}{2} (V_{GS}' - V_t)^2$   
 $= \frac{800\mu}{2} (1.5 - 0.7)^2$   
 $= 400\mu \times 0.8^2$   
 $= 400\mu \times 0.64$   
 $I_D = 0.256mA$   
 $g_m = k(V_{GS}' - V_t)$   
 $= 800\mu (1.5 - 0.7)$   
 $= 800\mu (0.8)$   
 $= 0.64mA$

5)  $r_{DS} = \frac{1}{g_m} = \frac{1}{k(V_{GS} - V_t)}$   
 $= \frac{1}{1.5m(4 - 0.8)}$   
 $= \frac{1}{1.5m \times 3.2}$   
 $r_{DS} = 0.2k$

6)  $V_{in} = 10mV$ ;  $A_{f, dB} = 40dB$   
 $V_{inf} = 4V$   $A_f$   $B_f$   
 $A_f = \frac{V_{of}}{V_{inf}}$ ,  $A = \frac{V_o}{V_{in}}$   
 $V_{of} = V_o$   
 $A_f V_{inf} = A V_{in}$   
 $100(4) = A(0.01)$   
 $A = 40k$   
 $A_f = \frac{A}{1 + A\beta}$   
 $100 = \frac{40k}{1 + 40k(\beta)}$   
 $1 + 40k(\beta) = 400$   
 $40k(\beta) = 399$   
 $\beta = 9.975 \times 10^{-3}$   
 $= 0.009975$

⑧  $A = 40dB$   
 $A = 100$   
 $BW = 300kHz$   
 $D = 15\%$   
 $Z_i = 10k\Omega$   
 $Z_o = 1k\Omega$   
 $\beta = 3.9\%$   
 $= 0.039$   
 $\rightarrow Z_{if} = \frac{1k}{4.9}$   
 $= 204.08\Omega$   
 $40 = 20 \log(A)$   
 $A = 100$   
 $1 + A\beta = 1 + (100)(0.039)$   
 $= 4.9$   
 $\rightarrow A_f = \frac{A}{1 + A\beta} = \frac{100}{4.9} = 20.4$   
 $\rightarrow BW_f = BW(1 + A\beta)$   
 $= 1.47MHz$   
 $\rightarrow D_f = \frac{15\%}{4.9} = 3.06\%$   
 $\rightarrow Z_{if} = \frac{(10k)(4.9)}{4.9} = 49k\Omega$

⑦  $A = 1000$   
 $D = 10\%$   
 $V_{in} = 10mV$   
 $1 + A\beta = 40dB = 100$   
 $40 = 20 \log(A\beta)$   
 $A\beta = 100$   
 $A_f = \frac{A}{1 + A\beta} = \frac{1000}{100}$   
 $A_f = 10$   
 $A \times V_{in} = A_f \times V_{inf}$   
 $1000 \times 10m = 10 \times V_{inf}$   
 $V_{inf} = 1V$   
 $D_f = \frac{D}{1 + A\beta} = \frac{10\%}{100} = 0.1\%$

$D_f = \frac{D}{1 + A\beta} = \frac{10\%}{100} = 0.1\%$