

Subject:

Tutorial 4

- In the voltage follower circuit, op amp used is ideal in all respects, except it has a finite gain, A. Determine V_o/V_{in} . If A is equal to 1000, calculate the error of the gain from that of the voltage follower with an ideal op amp.
- Draw the summer circuit, using two ideal op amps, and calculate the different resistor values to obtain $V_o = 2V_1 - 4V_2 + 6V_3$, for $V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$, where V_1, V_2, V_3, V_4, V_5 and V_6 are the available inputs.
- The output signal of an op amp with a slew rate of $2.5V/\mu s$, has a peak to peak value of $18V$. Find the maximum frequency for undistorted output voltage.
- An op amp has a differential gain of 2×10^4 and a CMRR of $86dB$. Determine the output, if the differential input is $10\mu V$ and the common mode input is $10mV$.
- In the circuits of Figs 7, 8 and 9, determine the output voltage, V_o . Assume the op amps to be ideal.

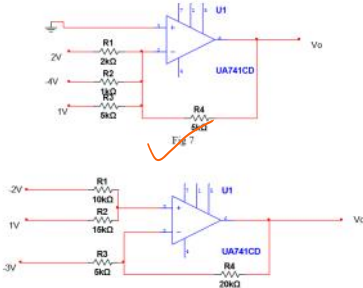


Fig 8

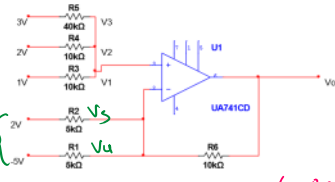


Fig 9

$$V_{o1} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$= -10k \left(\frac{2}{5k} + \frac{-4}{1k} + \frac{1}{10k} \right)$$

$$V_{o1} = 6V$$

$$V_o = V_{o1} + V_{o2}$$

① $A = 1000$

$$\frac{V_o}{V_{in}} = A_v = \frac{A}{1+A}$$


$$= \frac{1000}{1+1000}$$

$$A_v = 0.99$$

$$e_{gain} = 1 - A_v$$

$$= 0.01$$

② a) $V_o = 2V_1 - 4V_2 + 6V_3$

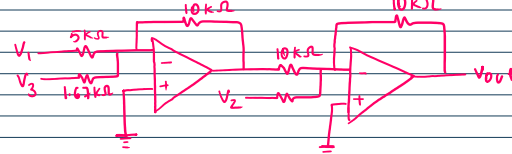

Assuming $R_f = 10k\Omega$,

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$V_o = - \left[\frac{R_f}{R_2} V_2 \right]$$

$$\frac{R_f}{R_1} = 2$$

$$R_1 = \frac{10k}{2} = 5k\Omega$$


$$\frac{R_f}{R_2} = 4$$

$$R_2 = \frac{10k}{4} = 2.5k\Omega$$

$$\frac{R_f}{R_3} = 6$$

$$R_3 = \frac{10k}{6} = 1.67k\Omega$$

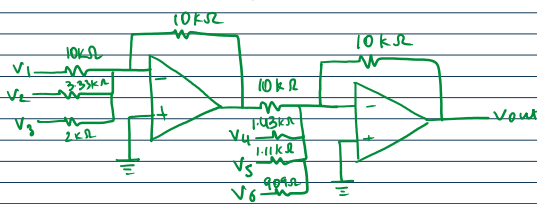b) $V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$



Assuming $R_f = 10k\Omega$

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 + \frac{R_f}{R_5} V_5 + \frac{R_f}{R_6} V_6 \right]$$

$$V_o = - \left[\frac{R_f}{R_4} V_4 + \frac{R_f}{R_5} V_5 + \frac{R_f}{R_6} V_6 \right]$$

$$\frac{R_f}{R_1} = 1 \Rightarrow R_1 = \frac{10k}{1} = 10k\Omega$$

$$\frac{R_f}{R_2} = 3 \Rightarrow R_2 = \frac{10k}{3} = 3.33k\Omega$$


$$\frac{R_f}{R_3} = 5 \Rightarrow R_3 = \frac{10k}{5} = 2k\Omega$$

$$\frac{R_f}{R_4} = 7 \Rightarrow R_4 = \frac{10k}{7} = 1.43k\Omega$$

$$\frac{R_f}{R_5} = 9 \Rightarrow R_5 = \frac{10k}{9} = 1.11k\Omega$$

$$\frac{R_f}{R_6} = 11 \Rightarrow R_6 = \frac{10k}{11} \approx 0.91k\Omega$$

5) Fig 7

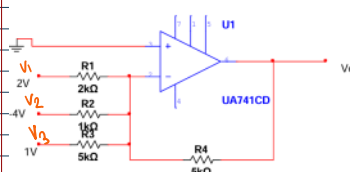

$$V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$= -5k \left(\frac{2}{2k} + \frac{-4}{1k} + \frac{1}{5k} \right)$$

$$= -5(1 - 4 + 0.2)$$

$$= -5(-2.8)$$

5) Fig 8

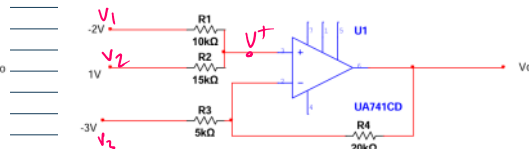


Fig 8

$$V_{o2} = \left(1 + \frac{R_4}{R_3} \right) V^+$$


$$= \left(1 + \frac{20k}{5k} \right) \left(\frac{-4}{5} \right)$$

$$V^+ = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

$$= \frac{3}{15k} \times (-2) + \frac{10k}{15k} \times (1)$$

$$\begin{aligned}
 &= -5K \left(\frac{2}{2K} + \frac{-4}{1K} + \frac{1}{5K} \right) \\
 &= -5 \left(1 - 4 + 0.2 \right) \\
 &= -5 \left(-2.8 \right) \\
 &= 14V
 \end{aligned}$$

5) fig 9

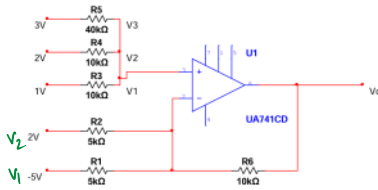

$$\begin{aligned}
 V_{o2} &= \left(1 + \frac{R_4}{R_3} \right) V^+ \\
 &= \left(1 + \frac{10K}{5K} \right) \left(\frac{-4}{5} \right) \\
 V_{o2} &= -4V \\
 V_{o1} &= -R_4 \left(\frac{V_1}{R_1} \right) \\
 &= -10K \left(\frac{-5}{5K} \right)
 \end{aligned}$$

$$\begin{aligned}
 V^+ &= \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2 \\
 &= \frac{5K}{10K + 5K} \times (-2) + \frac{10K}{10K + 5K} \times (1) \\
 &= \frac{-6}{5} + \frac{2}{5} = \frac{-4}{5} \\
 V_{o1} &= 12V
 \end{aligned}$$

$$\begin{aligned}
 V_{o1} &= 12V \\
 \rightarrow V_o &= V_{o1} + V_{o2} \\
 &= 12 - 4 \\
 V_o &= 8V
 \end{aligned}$$

$$\begin{aligned}
 &\begin{matrix} 10 & 10 & 40 \\ 1 & 2 & 3 \end{matrix} \quad \frac{10K \parallel 10K}{10K + 10K} = \frac{5K}{10K} = 0.5K \\
 &\quad \frac{10K \parallel 40K}{10K + 10K + 40K} = \frac{10K \cdot 40K}{60K} = \frac{40K}{6} \approx 6.67K
 \end{aligned}$$

$$\begin{aligned}
 V_{o1} &= -R_4 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \\
 &= -10K \left(\frac{-5}{5K} + \frac{2}{5K} \right) \\
 &= -2(-3) \\
 &= 6V
 \end{aligned}$$

$$\begin{aligned}
 V_{o2} &= \left(1 + \frac{R_4}{R_3} \right) V^+ \\
 &= \left(1 + \frac{10K}{5K} \right) \frac{5}{3} \\
 &= (1 + 2) \frac{5}{3} \\
 &= 5 \times \frac{5}{3} \\
 &= \frac{25}{3} \\
 &= 8.33
 \end{aligned}$$

$$\begin{aligned}
 V^+ &= \frac{R_2 \parallel R_5}{R_3 + R_4 \parallel R_5} V_1 + \frac{R_3 \parallel R_5}{R_4 + R_3 \parallel R_5} V_2 + \frac{R_3 \parallel R_4}{R_5 + R_3 \parallel R_4} V_3 \\
 &= \frac{10K \parallel 40K}{10K + 10K \parallel 40K} \times 1 + \frac{10K \parallel 40K}{10K + 10K \parallel 40K} \times 2 + \frac{10K \parallel 10K}{40K + 10K \parallel 10K} \times 3 \\
 &= \frac{8K}{18K} + \frac{8K}{18K} \times 2 + \frac{5K}{45K} \times 3 \\
 &= \frac{8K}{18K} \times 3 + \frac{1}{3} \\
 &= \frac{4}{3} + \frac{1}{3} = \frac{5}{3}
 \end{aligned}$$

$$V_o = 14.33$$