
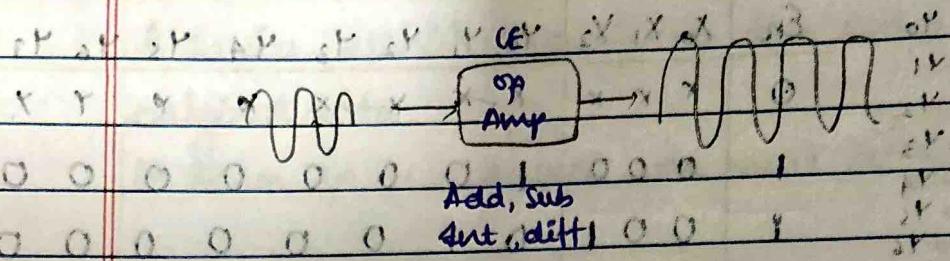


UNIT 3: OPERATIONAL AMPLIFIER

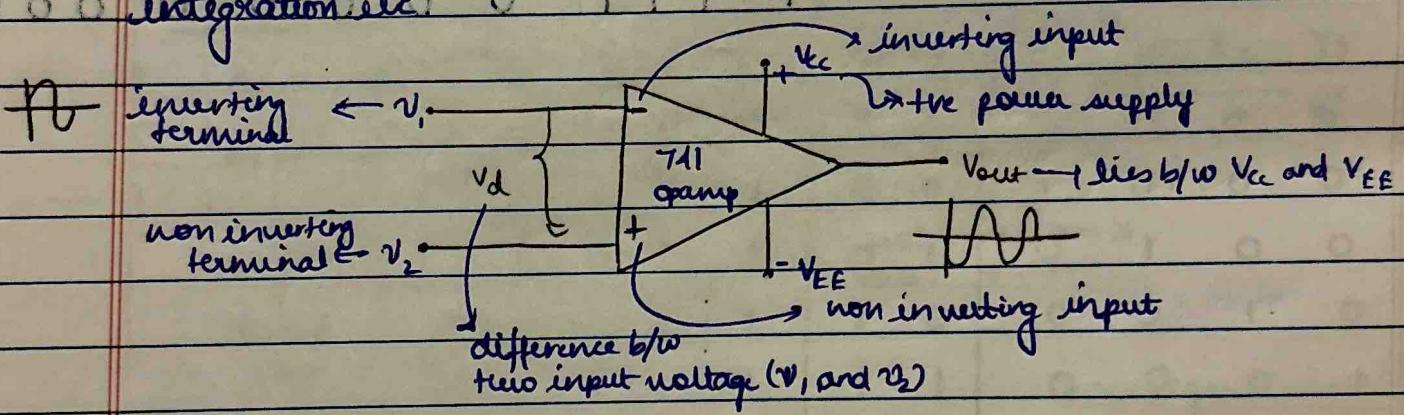

An operational amplifier is a multistage cascaded or coupled amplifier with an extremely (very high) gain.

Its behaviour can be controlled by adding a suitable feedback (negative). OPamps are mainly used for performing mathematical operations such as addition, subtraction, differentiation, integration etc.



CASE 1: Supplying the input signal/voltage to V_1 ; $V_2 \rightarrow$ grounded

$$\boxed{V_{out} = A V_{in}}$$

$\rightarrow 10^5 - 10^6$

$$V_d = V_2 - V_1$$

$$V_{out} = A (V_2 - V_1)$$

$\therefore A(-V_1) = -AV_1 \rightarrow$ phase shift takes place

CASE 2: Give input to the 2nd terminal V_2 and find the output voltage $V_1 \rightarrow$ grounded.

$$V_{out} = A V_{in}$$

$$V_d = V_2 - V_1$$

$$\boxed{V_{out} = A(V_2)}$$

PROPERTIES OF IDEAL OPAMP:

- (1) Input impedance is infinite
- (2) Output impedance is 0.
- (3) Voltage gain is infinity
- (4) Bandwidth $\rightarrow \infty$.
- (5) When equal voltages are applied to both the inputs of opamp then the output voltage is 0.
- (6) Characteristics of an opamp do not change with temperature.
- (7) CMRR = Common mode rejection ratio $= \infty$
- (8) slew rate $= \infty$
- (9)

TYPICAL SPECIFICATIONS OF GENERAL PURPOSE OPAMP

| PARAMETER | IDEAL VALUE | TYPICAL VALUE |
|--------------------------------|---|-----------------------------|
| (1) Voltage gain | $A = \infty$ | 2×10^5 |
| (2) Output impedance | 0Ω | 75 Ω |
| (3) Input impedance | ∞ | 2 M Ω |
| (4) CMRR | 0 dB | 90 dB |
| (5) Slew rate | $0.5 \text{ V/}\mu\text{s}$ | $0.5 \text{ V/}\mu\text{s}$ |
| (6) Bandwidth | ∞ | 1 MHz |
| (7) PSRR | 0 | 30 V/V |
| (Power supply rejection ratio) | $V_{DD} = 15 \text{ V}, V_{SS} = -15 \text{ V}$ | |

APPLICATION OF OPAMP:

- (1) Inverting operational amplifier
- (2) Non inverting operational amplifier
- (3) Summing amplifier (summer)
- (4) Voltage follower
- (5) Integrator
- (6) Differentiator
- (7) Instrumentation amplifier

(8) Schmidt trigger

(1) inverting opamp

structure of multivibrator

of multivibrator

principle of inverting action

as per definition

need to provide 10 times gain at threshold i.e. open-loop gain needed.

$V_{out} = -A \cdot V_{in}$

input resistance $R_{in} = \frac{V_B}{I}$ is very large so $V_{in} \approx 0$

output resistance $R_{out} = \frac{V_{out}}{I}$ is very small

$$(eg) A = 10^5; V_{out} = 10V$$

$$V_{out} = A \cdot V_{in}$$

$$R_{in} = \frac{V_B}{I} = 10^5 \Omega \cdot 10^{-1} = 100 \mu\text{V}$$

$$V_{in} = V_2 - V_1 = 100 \mu\text{V}$$

value cannot be measured or taken as 0

Principle

$$V_2 - V_1 = 0$$

A

inverting action

i.e. $V_2 = V_1$

$$V_2 = V_1 \Rightarrow V^+ = V^-$$

virtual ground

AMC

so

;

multivibrator

Since input impedance $\approx \infty \rightarrow$ no current flows through the opampso whatever current will flow, will flow through R_F willdue to virtual ground $\Rightarrow I_B = I_A$

$I = I_F$ since current flows through R_F only

$$KVL \Rightarrow V_{in} - V_A = V_A - V_{out}$$

$$R_I \quad R_F$$

$$A_V = \frac{V_{out}}{V_{in}} = -\frac{R_F}{R_I} \rightarrow 180^\circ \text{ phase shift}$$

$V_{in} < V_A$ \rightarrow R_I charges positive

$V_{in} > V_A$ \rightarrow R_I discharges negative


(unstable) stability is ensured

number of options

interactions

initial effect

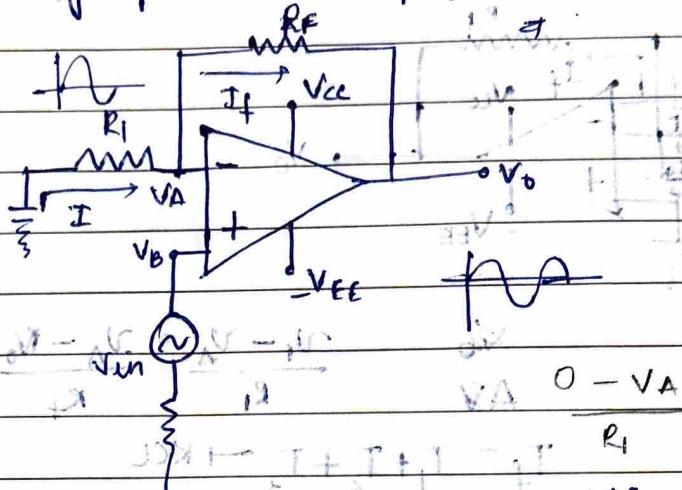Non inverting operational amplifier \rightarrow Vin \rightarrow positive terminal



$$\text{Virtual short: } V_A \approx V_B$$

$$V_B = V_{in} - I_R \cdot R_1 \quad \text{--- (1)}$$

From KCL, (part A)

$$I_R + I_f = I_A \quad \text{--- (2)}$$

Applying KVL:

$$\frac{V_A - V_B}{R_1} = I_A \Rightarrow \frac{V_o - V_A}{R_f} = I_A$$

$$[V_o - R_f \cdot I_A] = V_A - R_1 \cdot I_A$$

$$\frac{V_A}{R_1} = \frac{V_o - V_A}{R_f}$$

$$V_A \approx V_{in}$$


$$\frac{V_{in}}{R_1} \approx \frac{V_o - V_{in}}{R_f}$$

$$\frac{R_f}{R_1} = \frac{V_o - V_{in}}{V_{in}}$$

$$\frac{R_f}{R_1} = \frac{V_o}{V_{in}} - 1$$

$$A_v = \frac{V_o}{V_{in}} = \frac{R_f + 1}{R_1}$$

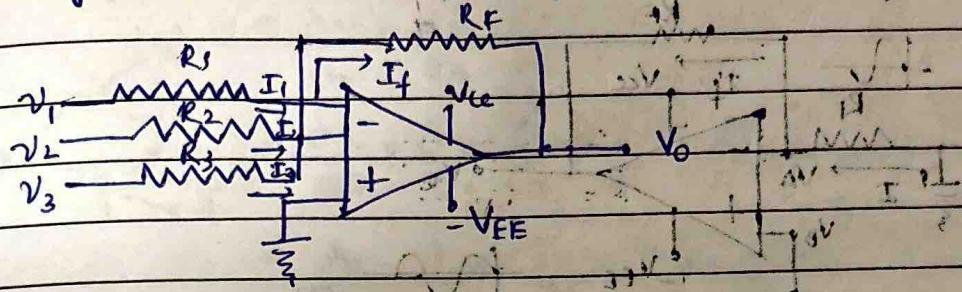Summing amplifier / summing junction inverter summing amplifier.



$$\frac{V_0}{A_{in}} = \frac{V_1 - V_A}{R_1} = \frac{V_A - V_0}{R_4}$$

$$I_f = I_1 + I_2 + I_3 \rightarrow KCL$$


$$\frac{V_0}{R_F} = \frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} \rightarrow KVL$$

$$V_0 = \frac{V_1 + V_2 + V_3}{R_F(A + R_F)} = \frac{V_1 + V_2 + V_3}{R_1 + R_2 + R_3}$$

$$V_0 = R_F \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

Assume, $R_1 = R_2 = R_3 = R_F = 1k\Omega$

$$V_0 = -R_F [V_1 + V_2 + V_3]$$

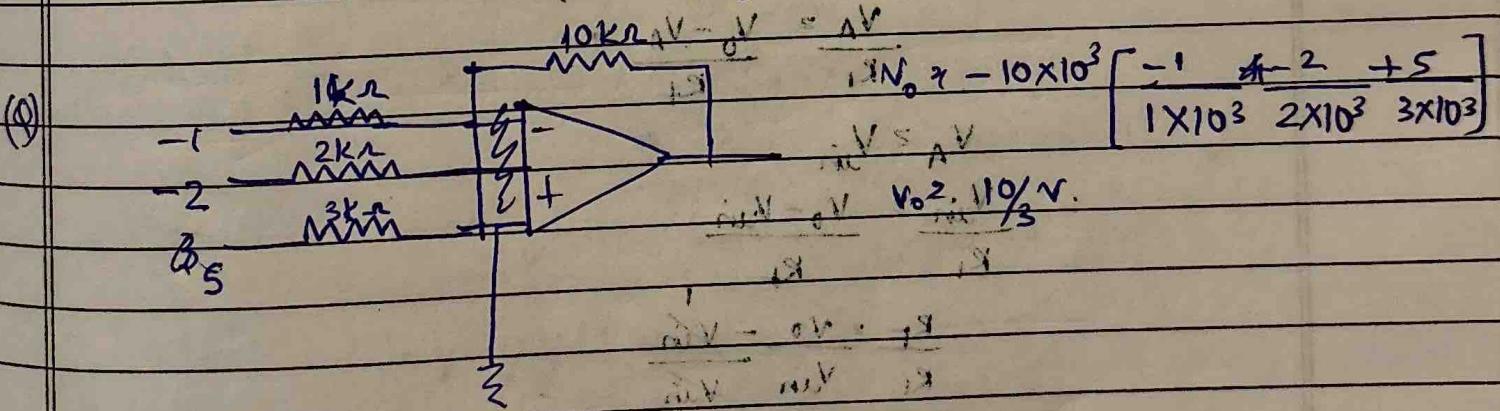

$$V_0 = -25 \times 10^3 \left[\frac{1}{1 \times 10^3} - \frac{2}{2 \times 10^3} + \frac{3}{3 \times 10^3} \right] = -25 \times 10^3 \left[\frac{6}{6 \times 10^3} \right] = 6 \times 10^3$$

$$V_0 = -15 \times 10^3 \left[\frac{-25}{20 \times 10^3} + \frac{30}{2 \times 10^3} \right]$$

$$= -15 \times 10^3 \left[\frac{-25 + 30}{20 \times 10^3} \right] = \frac{-15 \times 5}{200} =$$

(Q) A summer circuit using two ideal opAmps and calculate the different resistor values to obtain $V_o = 2V_1 - 4V_2 + 6V_3$, given V_1, V_2, V_3 are the input voltages.

$$(A) \quad V_o = \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$\frac{R_f}{R_1} = 2; \frac{R_f}{R_2} = 4; \frac{R_f}{R_3} = 6 \quad \text{resistance ratio cannot be negative}$$

$$(R_{in1}) = R_2 = V$$

$$R_3 = V$$

$$R_1 = V$$

$$R_f = V$$

$$V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6.$$

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 + \frac{R_f}{R_5} V_5 + \frac{R_f}{R_6} V_6 \right]$$

$$\frac{R_f}{R_1} = 1; \frac{R_f}{R_2} = 3; \frac{R_f}{R_3} = 5; \frac{R_f}{R_4} = 7; \frac{R_f}{R_5} = 9; \frac{R_f}{R_6} = 11.$$

$$V_o = -V_1 - 3V_2 - 5V_3.$$

$$V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6.$$


Assume, $R_f = 10\text{k}\Omega$

$$R_1 = \frac{R_f}{V_1} = \frac{10}{1} = 10\text{k}\Omega \quad R_3 = \frac{10}{5} = 2\text{k}\Omega$$

$$R_2 = \frac{10}{3} \approx 3.33\text{k}\Omega \quad R_4 = \frac{10}{7} \approx 1.4\text{k}\Omega$$

$$R_5 = \frac{10}{9} \approx 1.11\text{k}\Omega \quad R_6 = \frac{10}{11} \approx 0.909\text{k}\Omega$$

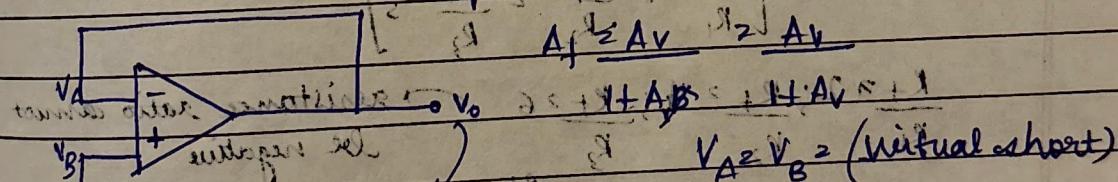Voltage follower: $V_o = V_A = V_B$ (100% negative feedback)



$$A_f \leq A_V$$

$$A_f = 1 + A_V$$

$$V_A = V_B = (\text{virtual short})$$

$$V_A = V_B = V_{in}$$

$$A_V = \frac{A}{1+A}$$

$$\text{Error} = \left| \frac{A}{1+A} \right| \times 100 \rightarrow \text{for percentage value}$$

$$V_o = V_B = V_{in}$$


determine the gain of the voltage follower if the $A_V = 1000$, also calculate the error in the gain from that of the voltage follower with that of an ideal opamp.

$$A_f = \frac{A}{1+A} = \frac{1000}{1+1000} = \frac{1000}{1001}$$

$$1 - \frac{1000}{1001} = \frac{0.001}{1000}$$

$$I = C \frac{dV}{dt}$$

Integrate (OpAmp as integrator):

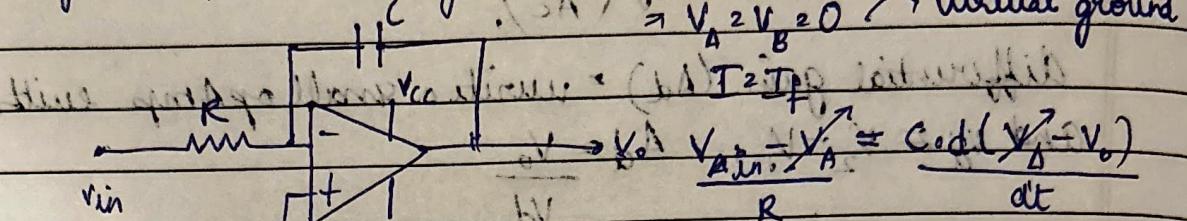

$V_{in} = V_{out}$ & $V_{out} = C \frac{d(V_o)}{dt}$

initial condition: $V_o = V_i$; $\frac{dV_o}{dt} = 0$

initial $t = 0 \rightarrow V_o = V_i$


now show smaller brief duration in after $t = 0$

neglect common mode voltage & apply J. on bs;

small brief voltage $V_o = i \cdot f/V_o \cdot dt$.

at $t = 0$ applying no position voltage $V_o = V_i$

Differentiator (OpAmp as differentiator)


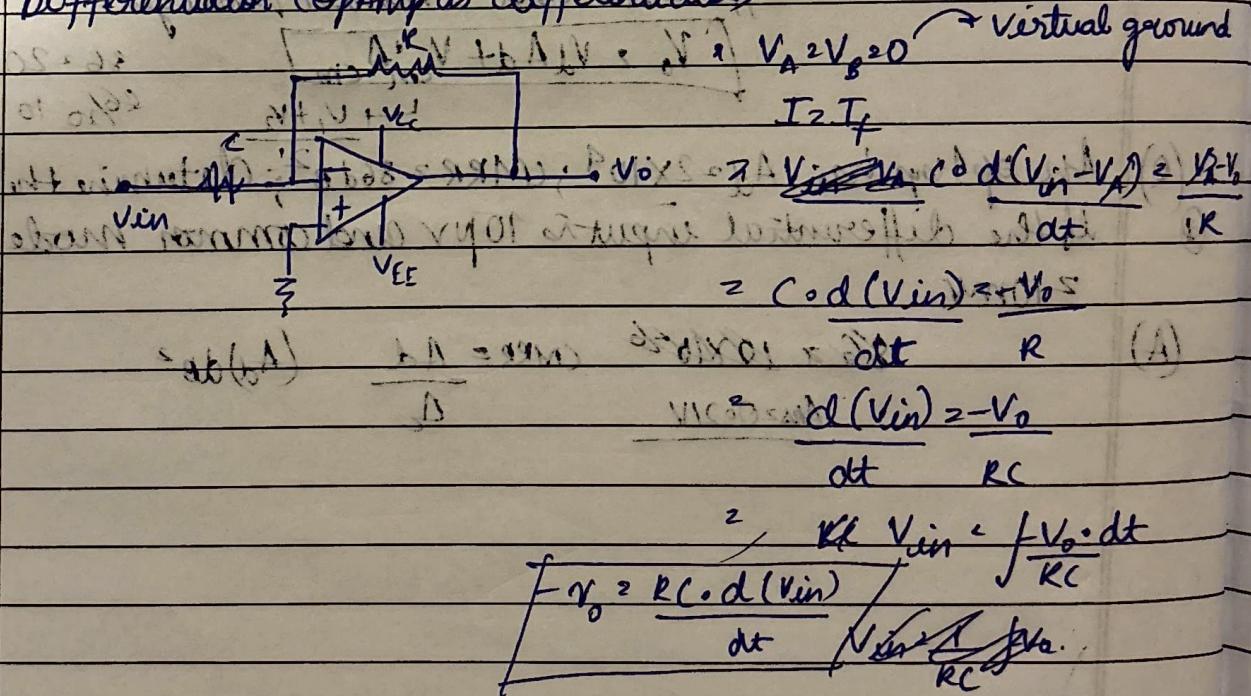


CMRR (common mode rejection ratio)

H is the ratio of common differential gain to the common mode gain.

$$CMRR = \frac{Ad}{A_{cm}}$$

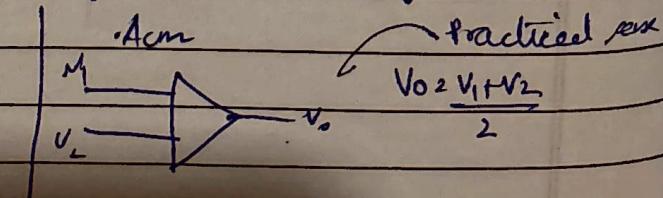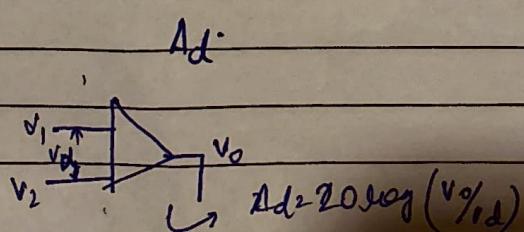differential gain of OpAmp
giving unequal voltages



$$\text{CMRR in dB} = 20 \log \left(\frac{A_d}{A_c} \right)$$

differential gain (A_d) = write a small opAmp with V_1 and V_2 and
and $V_o = V_2 - V_1$, so $A_d = \frac{V_o}{V_d}$

(A) \rightarrow write a small opAmp, with V_1 and V_2 and
 $V_1 = V_2, V_o = 0$ \rightarrow ideal condition

\therefore gain will be 0 \rightarrow CMRR \rightarrow infinity.

\therefore Practically, in order to find common mode gain, we
generally take output voltage as average of input
voltages and then find the CMRR

The net output voltage of an opAmp due to
differential and common mode gain:

$$V_o = V_d A_d + V_c \frac{A_c}{A_d + A_c}$$

$$26 = 20 \log_{10} (A_d)$$


(Q) An opAmp has $A_d = 2 \times 10^3$; $\text{CMRR} = 86 \text{ dB}$; determine the output
if the differential input is 10 mV and common mode input
 $= 10 \text{ mV}$.

$$(A) \quad 86 = 20 \log_{10} \frac{A_d}{A_c} \quad \text{CMRR} = \frac{A_d}{A_c} \quad (A_d)_{\text{dB}}^2$$

$$86 = 20 \log_{10} \frac{2 \times 10^3}{A_c} \quad A_c = 0.021V$$

Operational Amplifiers Communication Systems

Difference Amplifiers

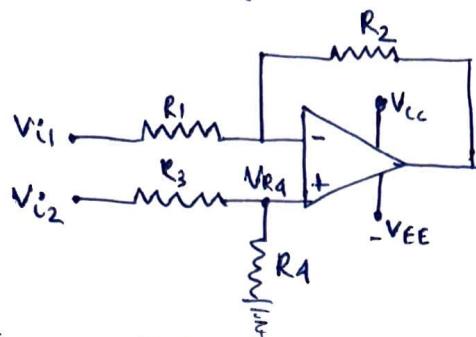

- It amplifies the difference between the two input voltages. The circuit shown is a combination of both inverting and non-inverting amplifiers.

Resistors R_1 , R_2 and spany constitute the inverting amplifier for the input voltage V_{ip} .

It is seen that, the drop across the resistance R_1 (V_{R1}) $\Rightarrow \frac{V_{i2} \times R_1}{R_2 + R_1}$ Using voltage divider rule

CASE 1:

dann $V_Q = 0$

$$V_{o1} = (\text{Gain})_{\text{inverting amplifier}} \times V_{i1}$$

$$\approx -R_2^{\uparrow} / R_1 \cdot V_{i1} \quad \rightarrow$$

CASE 2:

When $V_{ij} \geq 0$

$$V_{O2} \approx (\text{Gain})_{\text{non-inverting}} \times V_{R1}$$

$$g \left(1 + \frac{R_2}{R_1}\right) \times V_{RA} = \left(1 + \frac{R_2}{R_1}\right) \times \frac{V_{C2} \times R_4}{R_3 + R_4} \quad \text{--- (2)}$$

Assume $R_3 = R_1$ and $R_2 = R_4$

$$V_{O_2} \rightarrow R_2/R_1 \times V_{C_2} - \text{---} (3)$$

The net output voltage is $V_o = V_{O1} + V_{O2}$

$$V_o = -R_2 \frac{V_{C1}}{R_1} + R_2 \frac{V_{C2}}{R_1}$$

$$V_o = R_2 \frac{V_{i2} - V_{i1}}{R_1}$$

Condition considering common node voltages.

$$\left. \begin{array}{l} V_{i1} = V_{i2} = V \\ V_0 = 0 \end{array} \right\} \text{Ideal condition}$$

Substituting this condition in eq (2), we get

$$V_{O_2} = \left(\frac{1+k_2}{k_1} \right) \times \frac{V R_A}{R_2 + R_A}; V_{O_1} = -\frac{k_2}{k_1} \cdot V$$

$$V_o = -\frac{R_2}{R_1} \cdot V + \left[\left(1 + \frac{R_2}{R_1} \right) \frac{\frac{R_2}{R_1}}{R_3 + R_1} \right] \cdot V$$

inverting noninverting

$$0 = -\frac{R_2}{R_1}V + \left(\frac{R_1+R_2}{R_1}\right) \cdot \frac{R_3+R_4}{R_3+R_4} \cdot V_{out}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{\left(\frac{R_1+R_2}{R_1}\right) \cdot \frac{R_3+R_4}{R_3+R_4}}{1}$$

$$\Rightarrow R_2 = \frac{(R_1+R_2)(R_3+R_4)}{R_3+R_4}$$

$$\therefore \frac{R_2}{R_1} = \frac{R_3+R_4}{R_3+R_4}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{R_3+R_4}{R_3}$$

$$\therefore \boxed{R_2/R_1 = R_3/R_4}$$

(Q) Find the output voltage for the given difference amplifier

$$V_{i1} = 6V; V_{i2} = 6V; R_1 = 5K; R_2 = 5K; R_3 = 2K; R_4 = 4K;$$


$$(A) V_o = R_2/R_1 [V_{i2} - V_{i1}]$$

$$\Rightarrow 5K/5K [6 - 6] = 0.$$

$$V_{o1} = -\frac{3}{5} \times 6 = -9V$$

$$V_{o2} = (1+1) \times 8 = 16V$$


$$V_o = 16 - (-9) = 25V$$

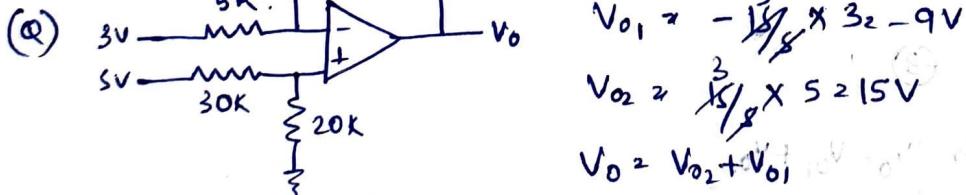

$$V_{o1} = -\frac{3}{5} \times 3 = -9V$$


$$V_{o2} = \frac{3}{5} \times 5 = 15V$$

$$V_o = V_{o2} + V_{o1} = 15 - 9 = 6V$$

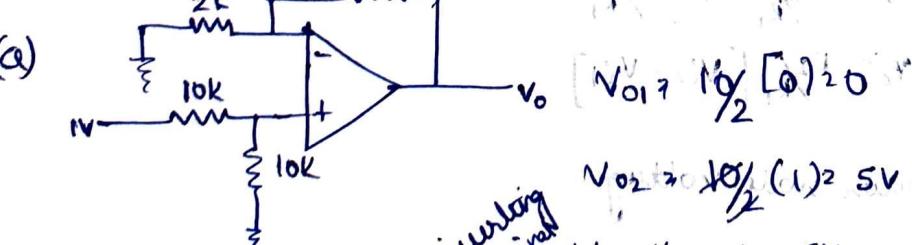

$$V_{o2} = \frac{10}{2} (1) = 5V$$

$$V_o = V_{o1} + V_{o2} = 5V$$

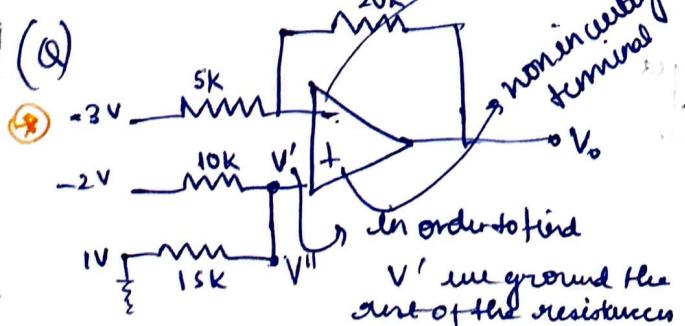

$$V_{o1} = -\frac{1}{5} [-3] = +12V$$

$$V_{o2} = \left(1 + \frac{1}{5}\right) \left(\frac{+2 \times 1.5K}{10K + 1.5K}\right) < 5V$$

$$\therefore (5) \left(\frac{+20K}{25K}\right) V' = 6V$$


$$V'' = \frac{1 \times 10k}{10k + 15k}$$

$$V_{03} = \left(1 + 20\%_s\right) \times V''$$


$$= \left(1 + 20\%_s\right) \cdot \left(\frac{10k}{10k + 15k}\right) = 5 \times \frac{10k}{25k} = 2k$$

$$V_o = V_{01} + V_{02} + V_{03}$$

$$= 12 - 6 + 2 = 8V.$$

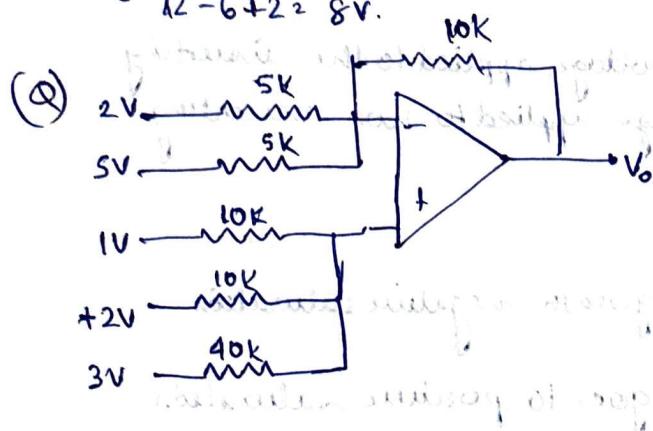

Instrumentation Amplifier.

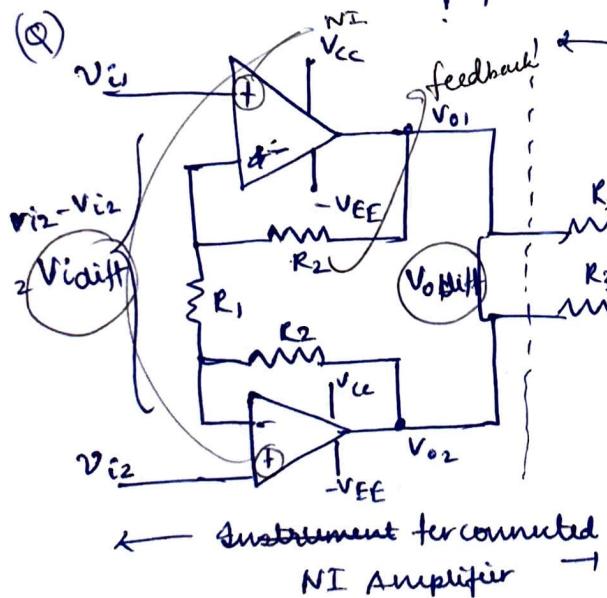

$$A_v = \underbrace{\frac{R_4}{R_3}}_{\text{gain}} \left[1 + \frac{R_2}{R_1} \right]$$

difference amplifier \rightarrow
low input impedance

$$V_{o1} = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{i1} \quad \text{--- (1)}$$

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{i2} \quad \text{--- (2)}$$


$$V_{odiff} = \left(1 + \frac{R_2}{R_1}\right) (V_{i2} - V_{i1})$$

$$V_o = \frac{R_4}{R_3} [V_{odiff}]$$

$$\boxed{\frac{2R_4}{R_3} \left[1 + \frac{R_2}{R_1} \right] (V_{i2} - V_{i1})} \rightarrow V_{o2} - V_{o1}$$

Comparator:

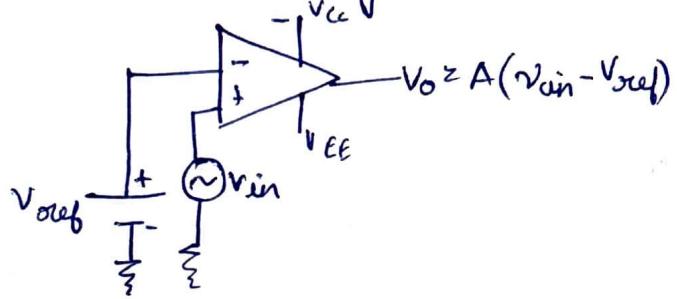
It compares the magnitude of two input voltages.




Here V_{ref} represents the constant reference voltage applied to the inverting terminal. (V_{in}) represents the variable voltage applied to non-inverting terminal. $V_d = V_{in} - V_{ref}$

Condition for comparator:

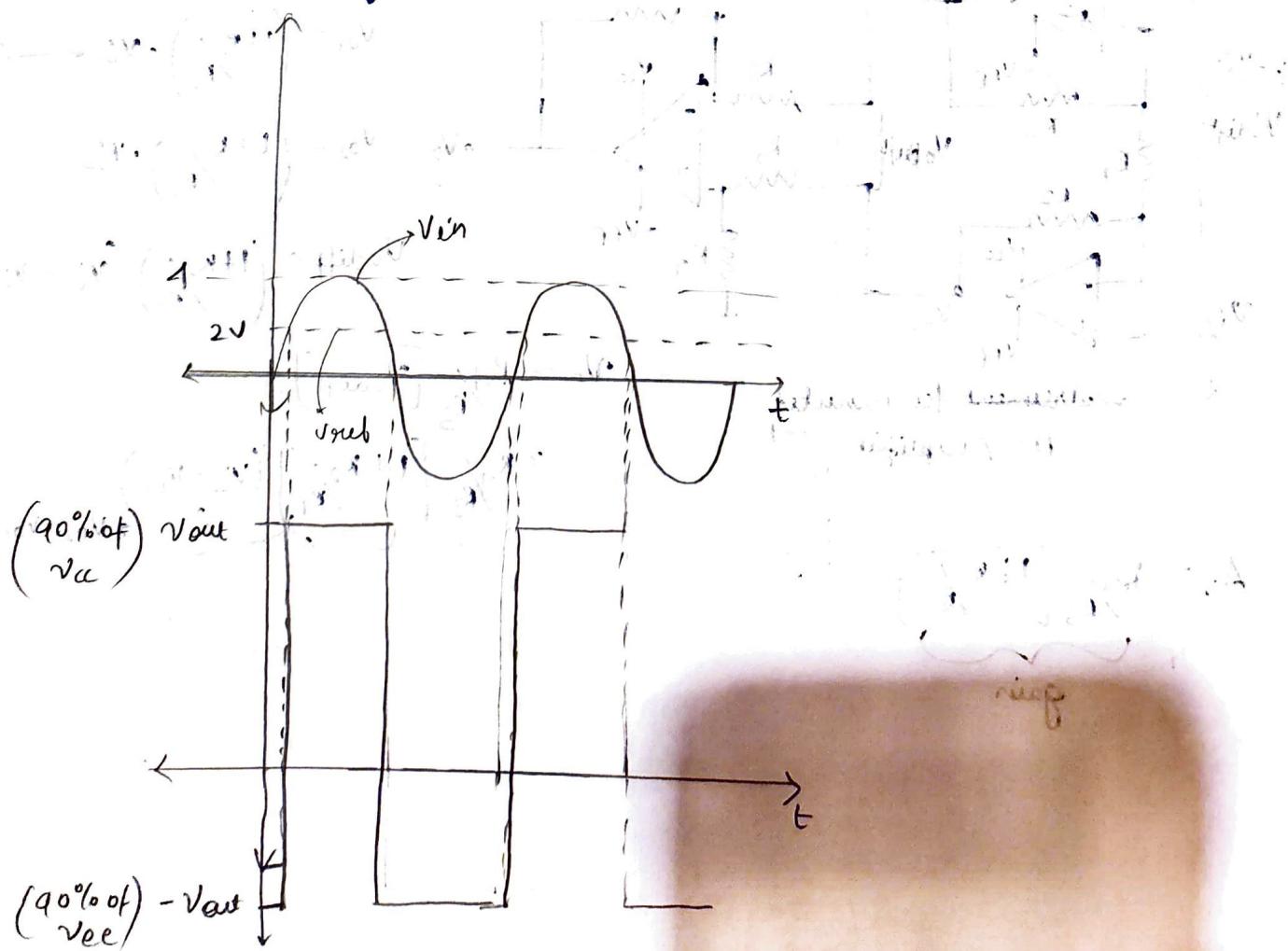- (1) $V_i < V_{ref} \rightarrow$ the V_d is negative; $V_o \rightarrow$ goes to negative saturation.
 - (2) $V_i > V_{ref} \rightarrow$ then V_d is positive; $V_o \rightarrow$ goes to positive saturation.
 - (3) $V_i = V_{ref} \rightarrow V_d = 0; V_o \rightarrow 0$.
- (4) $V_{in} = 4.5 \text{ sin } \omega t; V_{ref} = 2V$



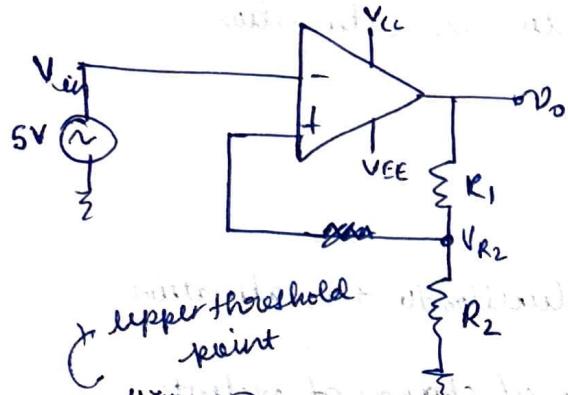Schmidt trigger. \checkmark no feedback \rightarrow feedback was always given to negative, now given to positive.



\curvearrowleft upper threshold point

UTP

LTP

+Vout

-Vout

It is a fast operating voltage level detector.

Extension of comparator

When the input voltage arrives at a level determined by the circuit, the output voltage switches rapidly between maximum positive level and maximum negative level.

$$V_{R2} = \frac{V_0 \cdot R_2}{R_1 + R_2}$$

The input voltage V_i is applied to inverting terminal of the opamp and the feedback goes to non-inverting input.

The waveform shows that output switches rapidly from positive saturation to negative saturation only when input exceeds a certain positive level (upper trigger point).

The output voltage switches from low to high when the input goes below a negative trigger point (LTP).


The expression for UTP and LTP are:

$$V_{R2} = UTP = \frac{V_0 \cdot R_2}{R_1 + R_2} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$LTP = -V_0 \cdot R_2 = \frac{-V_{EE} \cdot R_2}{R_1 + R_2}$$

Hysteresis (V_H) = UTP - LTP

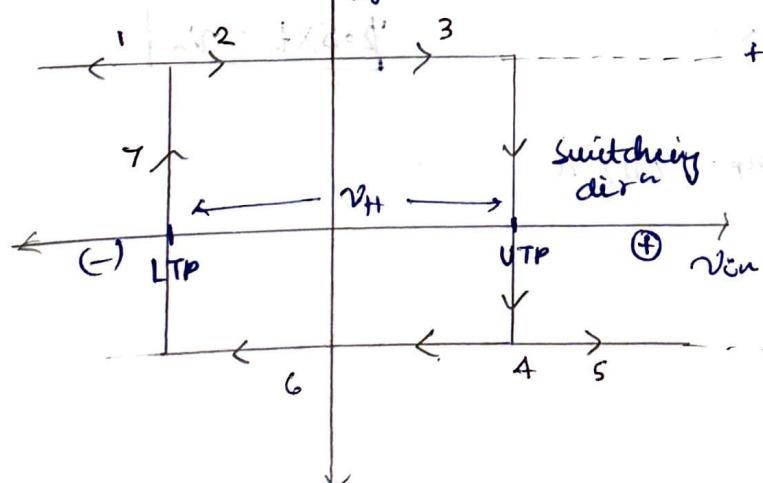Input output characteristic of Schmidt trigger / I/O characteristics / Transfer characteristics



Point 1 $\rightarrow V_i < LTP, V_0 \rightarrow -V_{0sat}$

Point 2 \rightarrow 1 through 2 and 3

$V_i > LTP, V_i = LTP,$

$V_0 \rightarrow +V_{0sat}$

③ $v_{in} \geq UTP$; $v_o \rightarrow +ve$ saturation switches from +ve saturation to -ve saturation
 (negative bias) \rightarrow Point ③

④ $v_{in} > UTP \rightarrow v_o \rightarrow +ve$ saturation

at the negative saturation output level


⑤ $v_{in} \leq UTP$; $v_{in} \geq UTP \rightarrow v_o \rightarrow -ve$ saturation

⑥ $v_{in} = UTP$; $v_o \rightarrow$ switches from -ve saturation to +ve saturation

slew rate (SR) \rightarrow defined as maximum rate of change of output voltage.

$$SR = \frac{\partial v_o}{\partial t}_{max} = V/MS$$

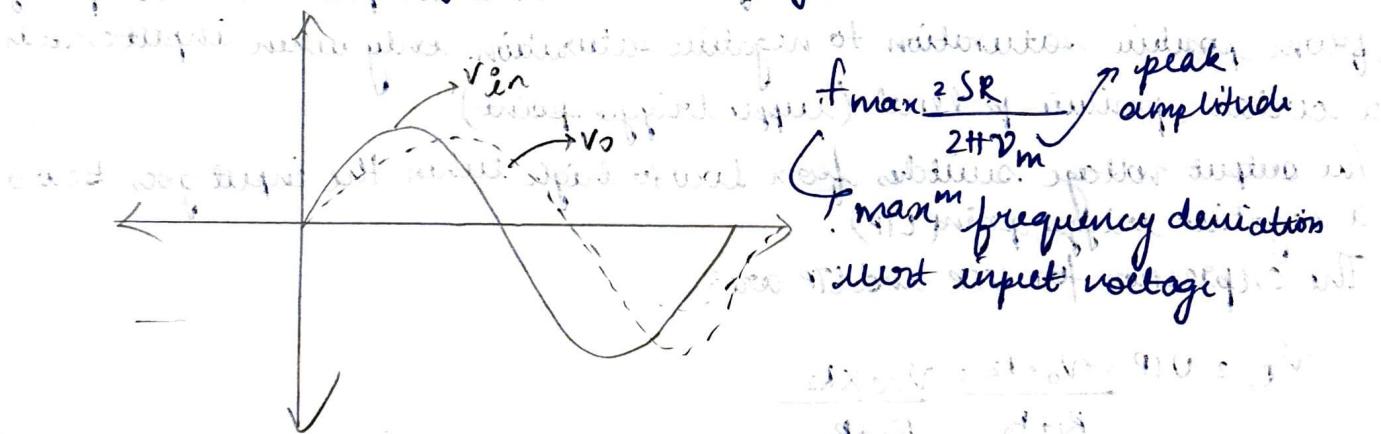slew rate is a measure of how fast the opamp output can change in response to changes in the input signal



(Q) The output signal of an opamp with a slew rate of $25V/MS$ has a peak to peak value of $18V$. Find the max^m frequency deviation due to the output voltage.

$$(A) \quad 2\pi f_{max}^m = \frac{25}{2 \times 10^6} \quad 2.5 \times 10^6$$

$$2 \times \pi \times 18 \times 10^6$$

$$2.5 \times t = v_o$$

Duck configuration of opamp. (741) IC