

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®
(An Autonomous Institution affiliated to VTU)
I Semester B. E. Examinations April -2021

Common to All Branches

ELEMENTS OF ELECTRONICS ENGINEERING

Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:


1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6


PART-A

1	1.1	The forward voltage drop of a diode at $27^{\circ}C$ is $550mV$, the forward voltage drop at $57^{\circ}C$ is _____.	01
	1.2	The diffusion capacitance of a forward biased diode _____ with decrease in the forward current.	01
	1.3	The full wave bridge rectifier has dc load current $I_{dc} = 100mA$, input ac voltage is $220V, 50Hz$ and $C = 1000\mu F$. The peak to peak ripple voltage is _____.	01
	1.4	A dc power supply has a no load voltage of $30V$ and a full load voltage of $25V$ at a full load current of $1A$. Calculate the load regulation and its output resistance.	02
	1.5	In a voltage divider circuit for a silicon transistor having $\beta = 49$ has $R_E = 4k\Omega$ and $R_{th} = 60k\Omega$, $S_{(I_{CO})} =$ _____.	01
	1.6	A ratio of I_C/I_E is usually less than one and is defined for _____ configuration.	01
	1.7	The output of a cascaded chain of three amplifiers is $8V$, when the input voltage is $2\mu V$. If the voltage gain of first and third stages are $20dB$ and $40dB$ respectively, the voltage gain in the second stage is _____.	02
	1.8	An amplifier without feedback has a gain of 100 and a distortion of 8% . If 3% negative feedback is provided to the amplifier, the distortion is _____ %.	01
	1.9	An n -channel $MOSFET$ operating in saturation has $I_D = 4mA$ and $V_{ov} = 2V$. Its trans-conductance (g_m) is _____.	01
	1.10	A $MOSFET$ uses the electric field of a _____ to control the channel current.	01
	1.11	A $1MHz$ sinusoidal carrier is amplitude modulated by a symmetrical wave of period $100\mu sec$. Calculate the upper side band frequency.	01
	1.12	Calculate the total modulation index if an AM signal has modulation indices of 0.3 & 0.4 .	01
	1.13	The minimized form of logic expression $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + ABC$ is _____.	01
	1.14	In a 3-to-8 decoder, with $X_2X_1X_0$ as the inputs and Y_0 to Y_7 as the outputs, what should be the input code so that Y_6 is high and all other outputs are low?	01
	1.15	The total number of gates required to implement $64:1$ multiplexer is _____.	01

1.16	The minimum number of <i>NAND</i> gates required to realize <i>XOR</i> gates is _____.	01
1.17	The output signal of an op-amp with a slew rate of $2.5V/\mu\text{sec}$ has a peak to peak value of $18V$. Find the maximum frequency of undistorted output signal.	01
1.18	An op-amp has a differential gain of 86dB and common mode gain of 20dB . The <i>CMRR</i> in <i>dB</i> is _____.	01

PART-B

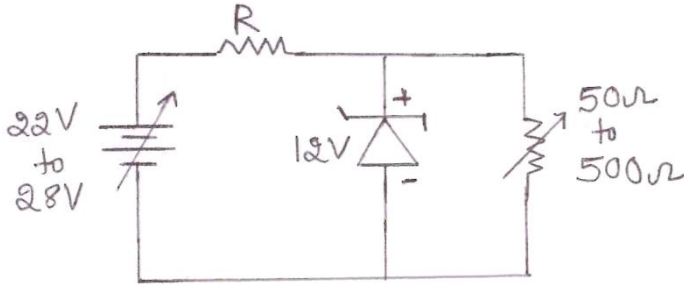2	<p>a List any four specifications of a PN junction diode and indicate their typical values.</p> <p>b A full wave bridge rectifier using ideal diodes is supplied from the secondary of a 10:1 transformer whose primary is connected to $220V, 50\text{Hz}$ main supply. The output of the rectifier is connected to a load resistance of 220Ω in parallel with a capacitor filter C. Calculate the value of C required so that the ripple factor is 3%. Also determine:</p> <p>i) The dc output voltage</p> <p>ii) The peak to peak voltage</p> <p>iii) The load regulation.</p> <p>c In a Zener regulation circuit of Fig 2c, design the value of R, so that circuit performs satisfactorily under all the given conditions. Given $P_{d(max)} = 6W, I_{Zmin} = 10\text{mA}, V_Z = 12V$.</p>	04
	 <p style="text-align: center;">Fig 2c</p>	06
3	<p>a Explain the different operating regions of a transistor along with the applications and draw the output characteristics for transistor in common emitter configuration.</p> <p>b In a <i>RC</i> coupled <i>CE</i> amplifier, $R_1 = 120k\Omega, R_2 = 40k\Omega, R_E = 1.5k\Omega, R_C = R_L = 2.7k\Omega, V_{CC} = 12V$ and $\beta = 99$. Determine the operating point of a silicon transistor and also calculate the voltage gain.</p> <p>c Mention any six advantages of negative feedback. Prove that the stability of the gain of an amplifier with negative feedback is $(1 + A\beta)$ times better compared to that of the amplifier without feedback.</p>	04
	OR	06
4	<p>a Explain the following:</p> <p>i) Thermal runaway</p> <p>ii) Early effect.</p> <p>b A voltage amplifier needs 2mV input to give a $10V$ output. When negative feedback is provided to this amplifier, it needs 200mV to deliver the same output. Determine the open loop gain, closed loop gain, feedback factor and amount of feedback in <i>dB</i> for this amplifier.</p> <p>c Explain the working of <i>RC</i> coupled amplifier with the circuit diagram. Draw its frequency response and briefly explain three regions.</p>	04
		06

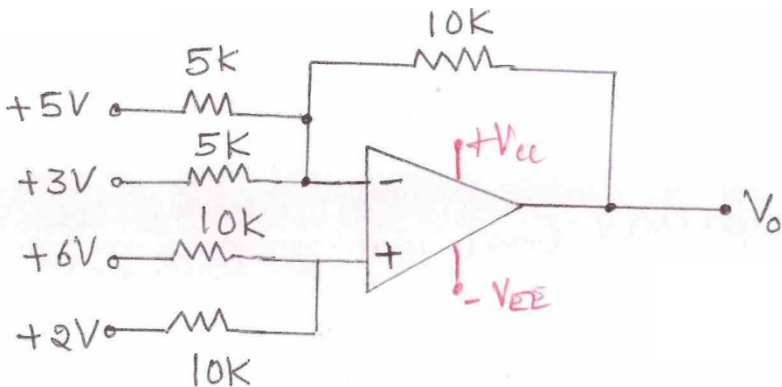5	a	Draw the circuit diagram and explain the operation of a two input <i>CMOS NOR</i> gate.	04
	b	An <i>n</i> –channel <i>MOSFET</i> has $V_t = 0.9V$. If $V_{gs} = V_{ds} = 2.5V$, the drain current I_D is $0.75mA$, i) Find I_D , if $V_{gs} = 4.1V$ and $V_{ds} = 4V$ ii) Find the trans-conductance g_m , if $V_{gs} = 3.4V$ iii) Find r_{ds} for small value of V_{ds} if $V_{gs} = 4.9V$.	06
	c	Draw the block diagram of a communication system and explain the function of each block. List the need for modulation (any four).	06
OR			
6	a	List eight differences between amplitude modulation and frequency modulation.	04
	b	Explain the operation of a <i>n</i> –channel enhancement <i>MOSFET</i> with a suitable diagram along with its output characteristics.	06
	c	An amplitude modulated wave with a modulation index of 50% produces sideband frequencies of $8.824MHz$ and $8.854MHz$. The amplitude of each sideband is $50V$. Determine the amplitude and frequency of both carrier and modulating signals.	06
7	a	Starting from the logic expression, realize <i>XNOR</i> gate using minimum number of <i>NAND</i> gates.	04
	b	Simplify the logic expression using <i>K</i> –map and implement the logic circuit using basic gates. $f(a,b,c,d) = \sum m(0,1,2,3,4,6,8,9,10,11,12,14)$	06
	c	Explain the operation of a 1 – to – 4 demultiplexer and write the logic expressions for its outputs. Also draw the logic circuit to realize the demultiplexer.	06
8	a	Draw the circuit of an integrator using an op-amp. Derive the expression for the output voltage.	04
	b	Draw the circuit and design the values of different resistors of a summer circuit using 2 ideal op-amps to get an output voltage $V_o = V_1 - 2V_2 - 4V_3 + 6V_4 + 8V_5$ where V_1, V_2, V_3, V_4 and V_5 are the available input voltages.	06
	c	Calculate the output voltage V_o for the circuit shown in Fig 8c.	
 <p style="text-align: center;">Fig 8c</p>			06