



RV College of  
Engineering®

# Verilog Fundamentals

Dr. Uma B.V

*Go, change the world®*



# HDL

*Go, change the world®*


Hardware Description Languages (HDLs) are absolutely foundational to modern digital design.

HDLs are specialized programming languages used to describe the structure, behavior, and timing of electronic circuits.

The two most widely used HDLs are

- 1.VHDL (VHSIC Hardware Description Language)**
- 2. Verilog**
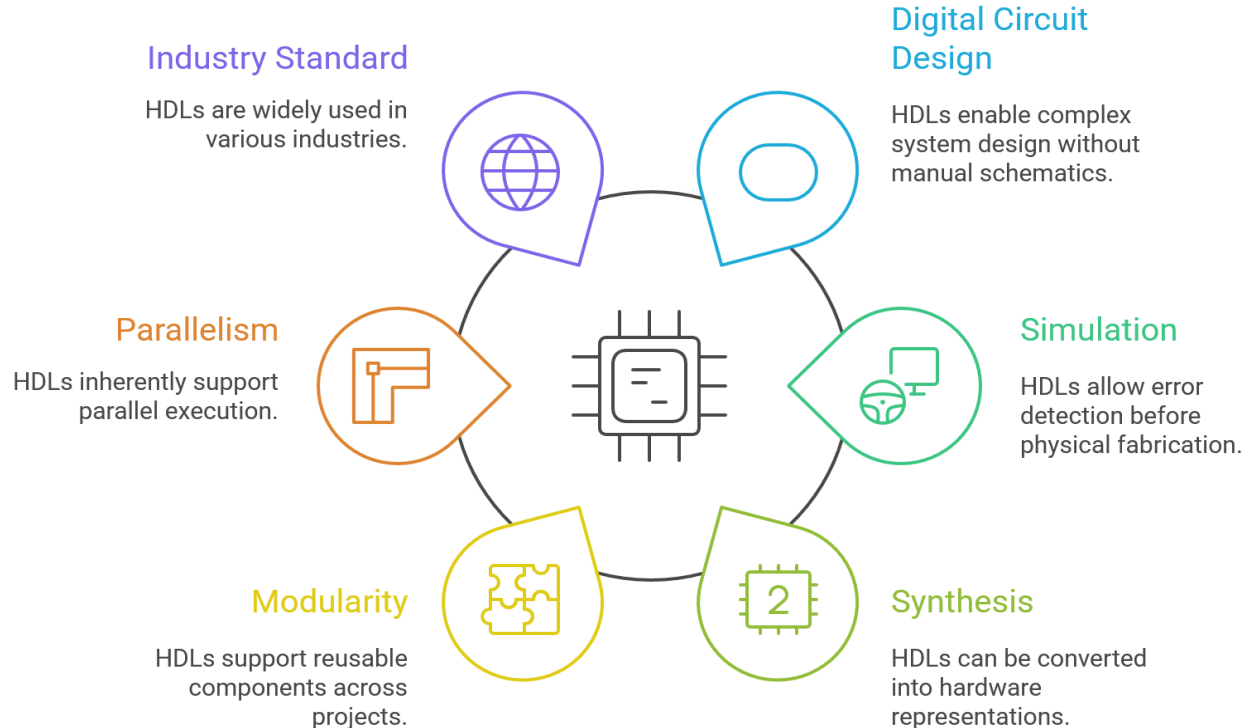
## Advantages of Hardware Description Languages





RV College of  
Engineering®

## Digital Circuit Design

# Significance of HDL

*Go, change the world®*

HDLs allow engineers to design complex digital systems without manually drawing schematics.

- **Simulation Before Fabrication**

Before a chip is physically built, HDLs let designers simulate its behavior to catch errors early. This saves time, money, and headaches.

- **Synthesis to Hardware**

HDL code can be synthesized into gate-level representations, which are then used to fabricate actual hardware (like FPGAs or ASICs).

- **Modularity and Reusability**

Just like software, HDL designs can be modular. You can reuse components like adders, multiplexers, or memory blocks across multiple projects.

- **Parallelism**

Unlike traditional programming languages, HDLs inherently support parallel execution, which mirrors how hardware operates in real time.

- **Industry Standard**

HDLs are the backbone of chip design in industries ranging from consumer electronics to aerospace and defense.



# Verilog HDL

*Go, change the world®*

- Verilog HDL has a syntax that describes precisely the legal constructs that can be used in the language.
- Syntax is pre-defined, lowercase, identifiers that define the language constructs.
- Example : *module, endmodule, input, output wire, and, or, not* , etc.,
- Any text between two slashes (//) and the end of line is interpreted as a comment.
- Blank spaces are ignored and names are case sensitive.

- Comments
- // The rest of the line is a comment
- /\* Multiple line comment \*/
- /\* Nesting /\* comments \*/ do **NOT** work \*/



# module: example1

□ Circuit

*ange the world®*


A *module* is the building block in Verilog.

- declared by the keyword **module**
- always terminated by the keyword **endmodule**

Each statement is terminated with a semicolon, but there is no semi-colon after *endmodule*.

&	→ bitwise AND
	→ bitwise OR
~	→ bitwise NOT
^	→ bitwise XOR
~^ or ^~	→ bitwise XNOR

Operation on bit by bit basis

 

// A simple example

**module** and2 (c, a ,b);

**input** a, b;

**output** c;

**assign** c = a & b;

**end module**

← comment line

← module name  
port list

← port declarations

← body



← end module



# module: example 2

*Go, change the world®*

Example: Half Adder

  

& → bitwise AND  
| → bitwise OR  
~ → bitwise NOT  
! → logical NOT  
^ → bitwise XOR  
~^ or ^~ → bitwise XNOR

Operation on bit by bit basis

*port  
types*

*module name*

```
module half_adder(S, C, A, B);  
  output S, C;  
  input A, B;  
  
  wire S, C, A, B;  
  
  assign S = A ^ B;  
  assign C = A & B;  
  
endmodule
```

*module  
contents*

## Identifiers

Formed from {[A-Z], [a-z], [0-9], \_, \$},  
but ..

.. can't begin with \$ or [0-9]

myidentifier

allowed

m\_y\_identifier

allowed

3my\_identifier

Not allowed

\$my\_identifier

Not allowed

\_myidentifier\$

allowed

## Case sensitivity

myid ≠ Myid



# module Port List

*Go, change the world®*

Multiple ways to declare the ports of a module

Scalar (single bit) - don't specify a size  
**input** cin;

```
module Add_half(c_out, sum, a, b);  
  output sum, c_out;  
  input a, b;  
  ...  
endmodule
```

```
module Add_half(output c_out, sum,  
  input a, b);  
  ...  
endmodule
```

type of port  
**input**  
**output**  
**inout** (bidirectional)

Vector (multiple bits) - specify size using range  
Range is MSB to LSB (left to right)

```
output [7:0] OUT;  
input [0:4] IN;
```

```
module xor_8bit(xout, a, b);  
  output [7:0] xout;  
  input [7:0] a, b;  
  ...  
endmodule
```

```
module xor_8bit(output [7:0] xout, input [7:0] a, b);  
  ...  
endmodule
```





# Basic gates in Verilog

*Go, change the world®*

```
module basic_gate(C, A, B);  
output [3:0]C;  
input [3:0]A,B;  
wire C, A, B;  
  
assign C[0] = A[0] & B[0];    // AND GATE  
assign C[1] = A[1] | B[1];    // OR GATE  
assign C[2] = A[2] ^ B[2];    // XOR GATE  
assign C[3] = !(A[3] & B[3]); // NAND GATE  
endmodule
```

//Multiple inputs and output using vector




RV College of  
Engineering®

# Module style

*Go, change the world®*

## Unified Module Design

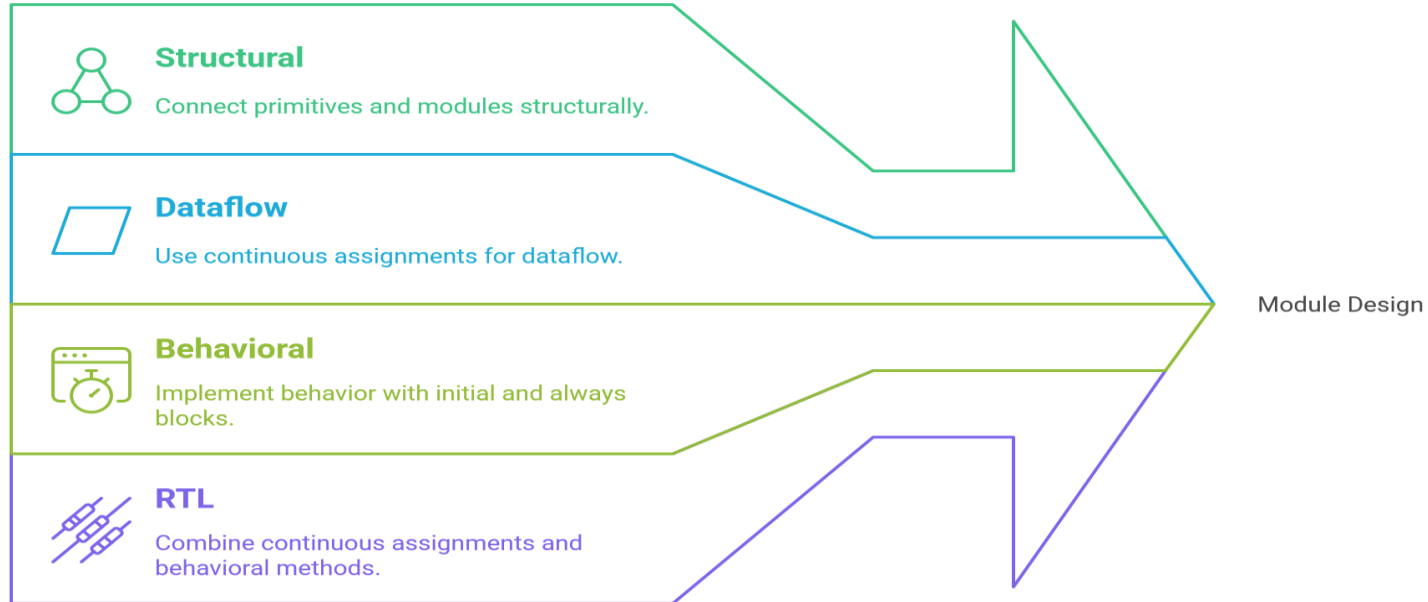



# Dataflow model

*Go, change the world®*

- Dataflow models describe **combinational circuits** by their *function* rather than by their gate structure.
- A common form of dataflow modeling of combinational logic uses **concurrent signal assignment statements** and built-in language operators to express how signals are assigned values.

## Example

```
module half_adder(S, C, A, B);  
  output S, C;  
  input A, B;  
  wire S, C, A, B;  
  
  assign S = A ^ B;  
  assign C = A & B;  
  
endmodule
```



# Half adder simulation


```
module HA1(  
    input a,b,  
    output s,c  
);  
    assign s = a^b;  
    assign c = a&b;  
endmodule
```





# Dataflow model-Full adder

*Go, change the world®*

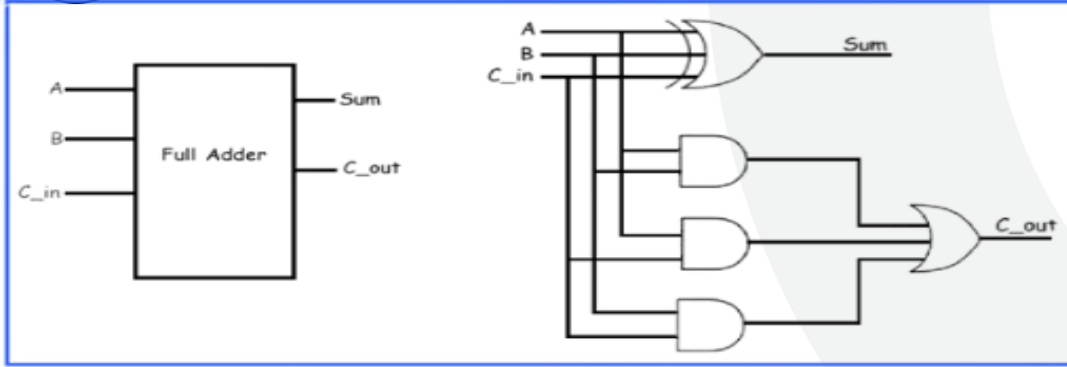

## Example 3

```
module full_adder(Sum, C_out, A, B,Cin);  
output Sum, C_out;  
input A, B, Cin;  
//wire Sum, C_out, A, B, Cin;  
assign Sum = A ^ B ^ Cin;  
assign C_out = (A & B) | (B & Cin) | (A &  
Cin);  
endmodule
```




# Full adder simulation

FA1.v

Untitled 1

```
module FA1(  
    input a,b,cin,  
    output s,co  
);  
    assign s = a^b^cin;  
    assign co= (a&b) | (b&cin) | (a&cin);  
endmodule
```

Name	Value
a	1
b	0
cin	0
s	1
co	0

 




# Dataflow model- Logic circuit

*Go, change the world®*

```
module or_and (  
    output E,  
    input  A, B, C  
);  
    wire D;  
    assign D = A || B;      // | is logical "OR" operator  
    assign E = C && D;      // & is the logical "AND" operator  
    // This is a single-line comment  
    /* The text here and below  
       form a multi-line comment  
    */  
endmodule
```

 




# Dataflow model-Boolean function

*Go, change the world®*

 1. Write a continuous assignment statement that describes  $Y$  in the logic diagram in [Fig. PE3.12](#), where  $A$ ,  $B$ ,  $C$ , and  $D$  are Boolean variables.



**Answer:** assign  $Y = (!((!A) || B)) \&\& C$

## Boolean Function



$$E = A + BC + B'D \quad F = B'C + BC'D'$$

## Verilog Code




```
module Circuit_Boolean_CA (E, F, A, B, C, D);  
    output E, F;  
    input  A, B, C, D;  
    assign E = A || (B && C) || ((!B) && D);  
    assign F = ((!B) && C) || (B && (!C) && (!D));  
endmodule
```





# Data flow model- MUX 4:1

*Go, change the world®*

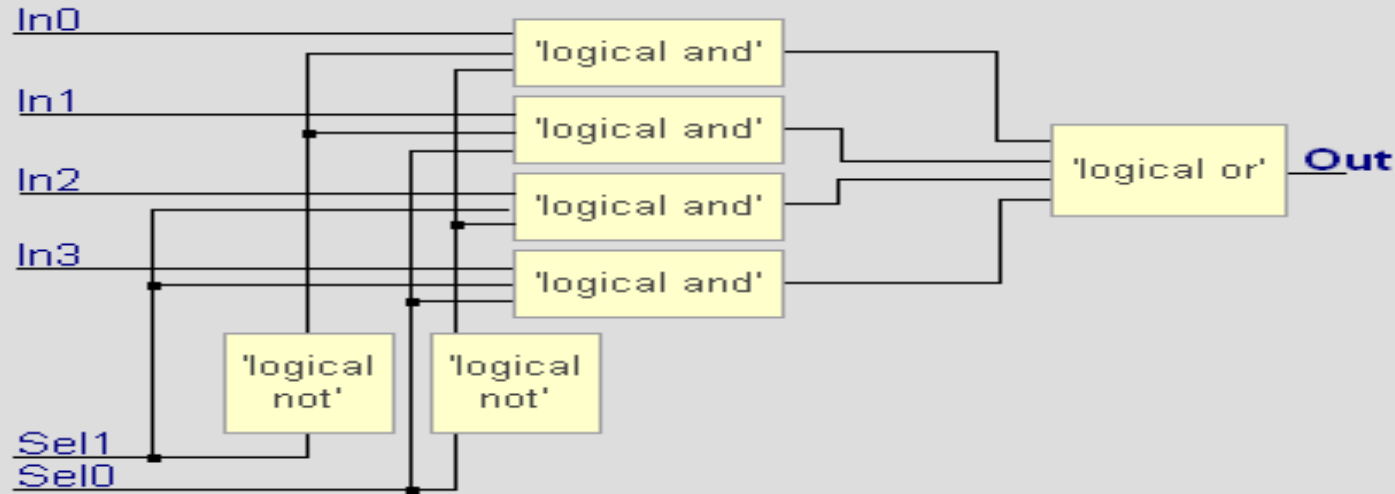

```
module mux_4_to_1 (Out, In0, In1, In2, In3, Sel1, Sel0);  
  
  output Out;  
  input In0, In1, In2, In3, Sel0, Sel1;  
  
  assign Out = (~Sel1 & ~Sel0 & In0) | (~Sel1 & Sel0 & In1)  
              | (Sel1 & ~Sel0 & In2) | (Sel1 & Sel0 & In3);  
  
endmodule
```



# Dataflow Model of 2:4 decoder

*Go, change the world®*

```
module decoder_2to4_df (output [0: 3] D, input  
A, B, enable );
```


```
assign D[0] = !((!A) && (!B) && (!enable)),
```

```
D[1] = !((!A) && B && (!enable)),
```

```
D[2] = ((A) && (! B) && (!enable)),
```

```
D[3] = !(A && B && (!enable));
```

```
endmodule
```

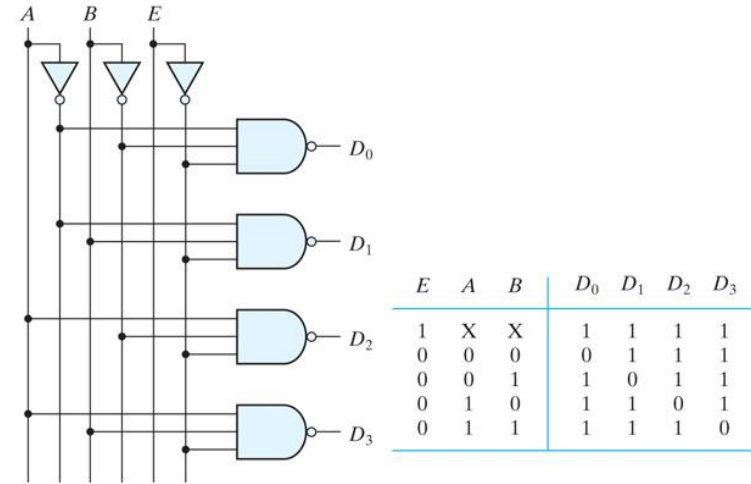



RV College of

*Go, change the world<sup>®</sup>*

**Symbol      Operation      Symbol      Operation**

+      binary addition

-      binary subtraction

&      bitwise AND

&&      logical AND

|      bitwise OR

||      logical OR

^      bitwise XOR

~      bitwise NOT

!      logical NOT

= =      equality

>      greater than

<      less than

{ }      concatenation







RV College of  
Engineering®


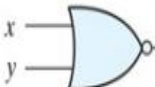

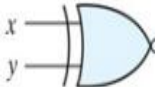
# Verilog - predefined primitives

*Go, change the world®*

- Verilog includes 12 basic logic gates as predefined primitives.
- Four of these primitive gates are of the three-state type.
- The other eight are the basic gates.
- They are declared with the lowercase keywords **and**, **nand**, **or**, **nor**, **xor**, **xnor**, **not**, and **buf**.
- Primitives such as **and** are n-input primitives, because they can have any number of scalar inputs (e.g., a three-input and primitive).
- The **buf** and **not** primitives are n-output primitives because a single input to a buf or not gate can drive multiple outputs.



Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	

*Go, change the world<sup>®</sup>*

NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

## Verilog: four types of predefined three-state gates


gate name (output, input, control);

  

- Verilog has four types of predefined three-state gates, as shown in Fig.
- The buif1 gate behaves like a normal buffer if `control = 1`. The output goes to a high-impedance state `z` when `control = 0`.
- The buif0 gate behaves in a similar fashion, except that the high-impedance state occurs when `control = 1`.
- The two notif gates operate in a similar manner, but the output is the complement of the input when the gate is not in a high-impedance state. The gates are instantiated with the statement
- `gate name (output, input, control);`



 
# Structural design: Half adder using Gates



```
module Add_half (input a, b, output c_out, sum),  
    xor G1(sum, a, b);           // Gate instance names are option  
    and G2(c_out, a, b);  
endmodule
```


 
## Structural design: Full Adder using two half adder




```
module Add_full (input a, b, c_in, output c_out, sum);    // see  
Fig.  
4.8
```

```
    wire w1, w2, w3;                                // w1 is c_out; w2 is sum  
    Add_half M1 (a, b, w1, w2);  
    Add_half M0 (w2, c_in, w3, sum);  
    or (c_out, w1, w3);  
endmodule
```




 
# Structural design: 4 bit Adder using 4 full adders



```
module Add_rca_4 (input [3:0] a, b, input c_in output c_out, ou
    wire c_in1, c_in3, c_in4;           // Intermediate carries
    Add_full M0 (a[0], b[0], c_in, c_in1, sum[0]);
    Add_full M1 (a[1], b[1], c_in1, c_in2, sum[1]);
    Add_full M2 (a[2], b[2], c_in2, c_in3, sum[2]);
    Add_full M3 (a[3], b[3], c_in3, c_out, sum[3]);
endmodule
```




# Data flow model of 4 bit binary Adder

```
module binary_adder ( output C_out, output [3: 0] Sum, input [3: 0] A, B, input C_in  
);  
assign {C_out, Sum} = A + B + C_in // Continuous assignment statement  
endmodule
```


 
# Structural design: Logic Circuit with propagation delay



Time Units (ns)

		A	B	C	w1	D
Initial	—	0	0	0	1	0
Change	—	1	1	1	0	1
10		1	1	1	0	0
20		1	1	1	0	0
30		1	1	1	0	1
40		1	1	1	0	1


```

module and_or_prop_delay (
    input A, B, C;
    output D, E);
);
wire w1;

    and G1 #30 (w1, A, B);
    not G2 #10 (E, C);
    or G3 #20 (D, w1, E);
endmodule
  
```


 
# Structural Model of 2:4 decoder *Go, change the world®*



E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

```
module decoder_2to4_gates (D, A, B, enable);
```

```
output [0: 3] D;
```

```
input A, B;
```

```
input enable;
```

```
wire A_not, B_not, enable_not;
```

```
not
```

```
G1 (A_not, A), // Comma-separated list of primitives
```

```
G2 (B_not, B),
```

```
G3 (enable_not, enable);
```

```
nand
```

```
G4 (D[0], A_not, B_not, enable_not),
```

```
G5 (D[1], A_not, B, enable_not),
```

```
G6 (D[2], A, B_not, enable_not),
```


```
G7 (D[3], A, B, enable_not);
```

```
endmodule
```



# Structural Model of 4:1 MUX

*Go, change the world®*

 


```
module m41(y, I0, I1, I2, I3, s0, s1);  
output y;  
input I0, I1, I2, I3, s0, s1;  
wire sobar, slbar, T1, T2, T3, T4;
```

```
not  
G1(s0bar, s0),  
G2(slbar, s1);  
and  
G3(T1,I0, s0bar, slbar),  
G4(T2,I1, s0bar, s1),  
G5(T3,I2, s0, slbar),  
G6 T4,I3, s0, s1);  
Or G7(y, T1, T2, T3, T4);  
endmodule
```


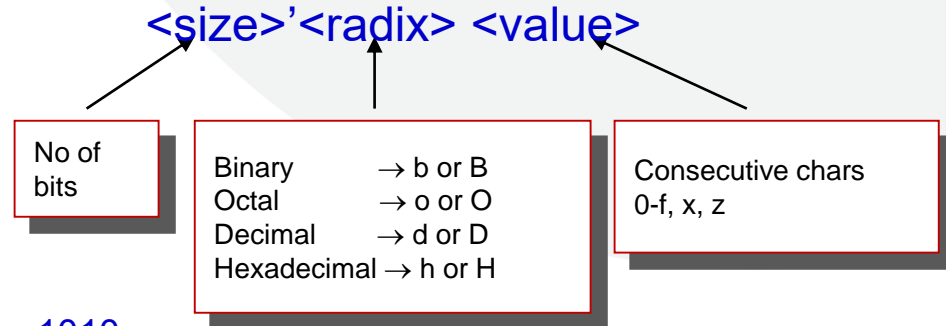
# Value and numbers in Verilog® *So, change the world®*

- 0 represents low logic level or false condition
- 1 represents high logic level or true condition
- x represents unknown logic level
- z represents high impedance logic level



- 8'h ax = 1010xxxx
- 12'o 3zx7 = 011zzzxxx111



# Number example

*Go, change the world®*

Number	Decimal Equivalent	Actual Binary
4'd3	3	0011
3'hA	10	010
8'o26	22	00010110
5'b111	7	00111
8'bx1101	-	xxxx1101
'o7	7	00000.....111(32 bits)
10	10	????

*Numbers with MSB of x or z extended with that value*



# Numbers in verilog

*Go, change the world®*

- can insert “\_” for readability

- 12'b 000\_111\_010\_100
- 12'b 000111010100
- 12'o 07\_24

} Represent the same number

- Bit extension

- MS bit = 0, x or z  $\Rightarrow$  extend this
  - 4'b x1 = 4'b xx\_x1
- MS bit = 1  $\Rightarrow$  zero extension
  - 4'b 1x = 4'b 1xxx

- If *size* is ommitted it is inferred from the *value* or takes the simulation specific number of bits or takes the machine specific number of bits

- If *radix* is ommitted then decimal is assumed

15 = <size>'d 15






# Logical Operators

*Go, change the world®*

- `& &` → logical AND
- `| |` → logical OR
- `!` → logical NOT
- Operands evaluated to ONE bit value: 0, 1 or x
- Result is ONE bit value: 0, 1 or x
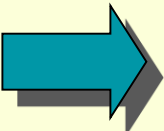
<code>A = 6;</code>		<code>A &amp;&amp; B → 1 &amp;&amp; 0 → 0</code>
<code>B = 0;</code>		<code>A    !B → 1    1 → 1</code>
<code>C = x;</code>		<code>C    B → x    0 → x</code>



## Bitwise Operators (i) & Reduction operator

$\&$  → bitwise AND  
 $|$  → bitwise OR  
 $\sim$  → bitwise NOT  
 $\wedge$  → bitwise XOR  
 $\sim \wedge$  or  $\wedge \sim$  → bitwise XNOR

Operation on bit by bit basis



- $\&$  → AND
  - $|$  → OR
  - $\wedge$  → XOR
  - $\sim \&$  → NAND
  - $\sim |$  → NOR
  - $\sim \wedge$  or  $\wedge \sim$  → XNOR
  - One multi-bit operand → One single-bit result
- ```
a = 4'b1001;  
c = |a; // c = 1|0|0|1 = 1  
Y= &a; // Y= 1&0&0&1 = 0
```




## Bitwise Operators (ii)

*Go, change the world®*

•  $a = 4'b1010;$   
 $b = 4'b1100;$

  

$a = 4'b1010;$   
 $b = 2'b11;$

 



# Concatenation Operator

- {op1, op2, ..} → concatenates op1, op2, .. to single number
- Operands must be sized !!

```
reg a;  
reg [2:0] b, c;  
a = 1'b 1;  
b = 3'b 010;  
c = 3'b 101;  
catx = {a, b, c};           // catx = 1_010_101  
caty = {b, 2'b11, a};       // caty = 010_11_1  
catz = {b, 1};              // WRONG !!
```

- Replication ..

```
catr = {4{a}, b, 2{c}};    // catr = 1111_010_101101
```



# Shift Operators

- `>>` → shift right
- `<<` → shift left
- Result is same size as first operand, **always zero filled**

```
a = 4'b1010;
```

```
...
```

```
d = a >> 2; // d = 0010
```

```
c = a << 1; // c = 0100
```




# Net /Wire

*Go, change the world®*
 
## Nets

- Purpose:** Represent physical connections between components.
- Behavior:** Do **not store** values; instead, they reflect the value driven by connected sources.
- Common Types:** wire, tri, wand, wor, trireg.
- Usage Scenarios:**
  - Connecting module ports.
  - Left-hand side of continuous assignments (assign).
  - Signals driven by gates or other modules.




```
wire a, b, c;  
assign c = a & b;
```

 
## Nets (ii)

*Go, change the world®*

Y is evaluated, **automatically**, every time A or B changes


 
```
wire Y; // declaration
assign Y = A & B;
```




```
wand Y; // declaration
assign Y = A;
assign Y = B;
```

| Y | A |   |
|---|---|---|
|   | 0 | 1 |
| B | 0 | 0 |
|   | 1 | 0 |

```
wor Y; // declaration
assign Y = A;
assign Y = B;
```

| Y | A |   |
|---|---|---|
|   | 0 | 1 |
| B | 0 | 1 |
|   | 1 | 1 |

 


```
tri Y; // declaration
assign Y = (dr) ? A : z;
```


 
# Registers (reg)

*Go, change the world®*

- **Purpose:** Represent **storage elements** inside procedural blocks.
- **Behavior:** Retain their value until explicitly changed.
- **Common Types:** reg, integer, real, time.
- **Usage Scenarios**
  - Inside always block
  - Used in the design of latches, flipflops etc
  - Example



```
module D_ff(q,d,clk,res);  
output q;  
input d,clk,res;  
reg q;
```

```
always @(posedge res or negedge clk);  
If (res)  
q=1'b0;  
else  
q=d;  
endmodule
```





# Register

- Variables that stores values
- Do not represent real hardware
- Assigned a value only in procedural statements, user defined sequential statements, tasks or function
- Reg: can not be output of primitive gates, input, inout, output port of module or target of continuous assignment statement
- Example: reg

```
reg A, C; // declaration
// assignments are always done inside a procedure
A = 1;
C = A; // C gets the logical value 1
A = 0; // C is still 1
C = 0; // C is now 0
```


- Register values are updated explicitly!!


 
# Conditional Operator

*Go, change the world®*

- `cond_expr ? true_expr : false_expr`
- 2-to-1 mux ..




`Y = (sel) ? A : B;`



## 4:1 MUX using conditional operator

*Go, change the world®*

 

(a) Logic diagram

| $s_1$ | $s_0$ | $Y$   |
|-------|-------|-------|
| 0     | 0     | $I_0$ |
| 0     | 1     | $I_1$ |
| 1     | 0     | $I_2$ |
| 1     | 1     | $I_3$ |

(b) Function table

```
module mux4to1(output y, input i0, i1, i2,
i3, s0, s1);
  assign y = s1 ? ( s0 ? i3:i2) : (s0 ? i1:i0);
  //nested conditional operator
endmodule
```



# Assignment statement

*Go, change the world®*

## ❑ Regular continuous assignment

```
assign y = in1 & in2;  
assign addr[15:0] = addr1[15:0] || addr2[15:0]  
assign {cout, sum[3:0]} = a[3:0] + b[3:0] + cin;
```

## Syntax:

```
assign #del <id> = <expr>;
```

## ❑ Implicit continuous assignment

```
wire y = in1 & in2;
```

## ❑ With delay

```
wire # 10 y = in1 & in2  
wire y;  
assign #10 y = in1 & in2
```

Propagation **delay**(inertial) can be associated with a continuous assignment  
Facilitates logic function and timing characteristic of the design to be same as  
**hardware circuit**




# Continuous Assignments

*Go, change the world®*

- Where to write them:
  - inside a module
  - outside procedures
- Properties:
  - they all execute in parallel
  - are order independent
  - are continuously active

Example: Logic circuit with delay

 


```
module aoi (xin1,xin2,xin3,xin4,xin5,e,yout);  
input xin1,xin2,xin3,xin4,xin5,e;  
output yout;  
wire #1 y1= (xin1 & xin2);  
wire #1 y2= (xin3 & xin4 & xin5);  
wire #1 y3= !(y1 | y2);  
assign yout = e ? y3: 1b'z;  
endmodule
```


 
## With Conditional operator ?

*Go, change the world®*

- Same as if then else
- If condition true:  
expression after ? is  
evaluated and assigned  
to target
- If condition is false:  
expression after : is  
evaluated and assigned  
to target




```
module aoi (xin1,xin2,xin3,xin4,xin5,e,yout);  
input xin1,xin2,xin3,xin4,xin5,e;  
output yout;  
assign yout = e ? ! ((xin1 && xin2)|(xin3 && xin4 &&  
xin5)): 1b'z;  
endmodule
```



# Structural design- 2:4 Decoder

*Go, change the world®*

 

| $E$ | $A$ | $B$ | $D_0$ | $D_1$ | $D_2$ | $D_3$ |
|-----|-----|-----|-------|-------|-------|-------|
| 1   | X   | X   | 1     | 1     | 1     | 1     |
| 0   | 0   | 0   | 0     | 1     | 1     | 1     |
| 0   | 0   | 1   | 1     | 0     | 1     | 1     |
| 0   | 1   | 0   | 1     | 1     | 0     | 1     |
| 0   | 1   | 1   | 1     | 1     | 1     | 0     |



RV College of  
Engineering®

*Go, change the world®*


- Write a continuous assignment statement that is equivalent to the logic of *G4* in *decoder\_2x4\_gates*.
- **Answer: assign D[0]=! ((!A) && (!B) && (!enable));**




 
# Testing methodology

A logic circuit must be tested systematically to ensure that all of its logic has been exercised and functionally correct



**Test bench:** applies stimulus patterns to the circuit and displays output waveforms

Separate verilog module which resides at the top of the design

Testing environment consists of stimulus generator, response monitor and an instantiation of the unit under test



# Testing methodology - cntd

Stimulus generator: verilog statement to define patterns

Response monitor: selectively gathers data on signals within the design and displays in text or graphical format

Simulator task:

- (1) checks source code,
- (2) reports any violations of the language's syntax
- (3) determines whether the number of ports specified by a model are actually connected to it in an instantiation
- (4) simulates the behavior of the circuit under the application of input signals that are defined in testbench


Syntax errors must be eliminated before a simulation can run



# Testing methodology - cntd

*Go, change the world®*

## Simulation Process Sequence

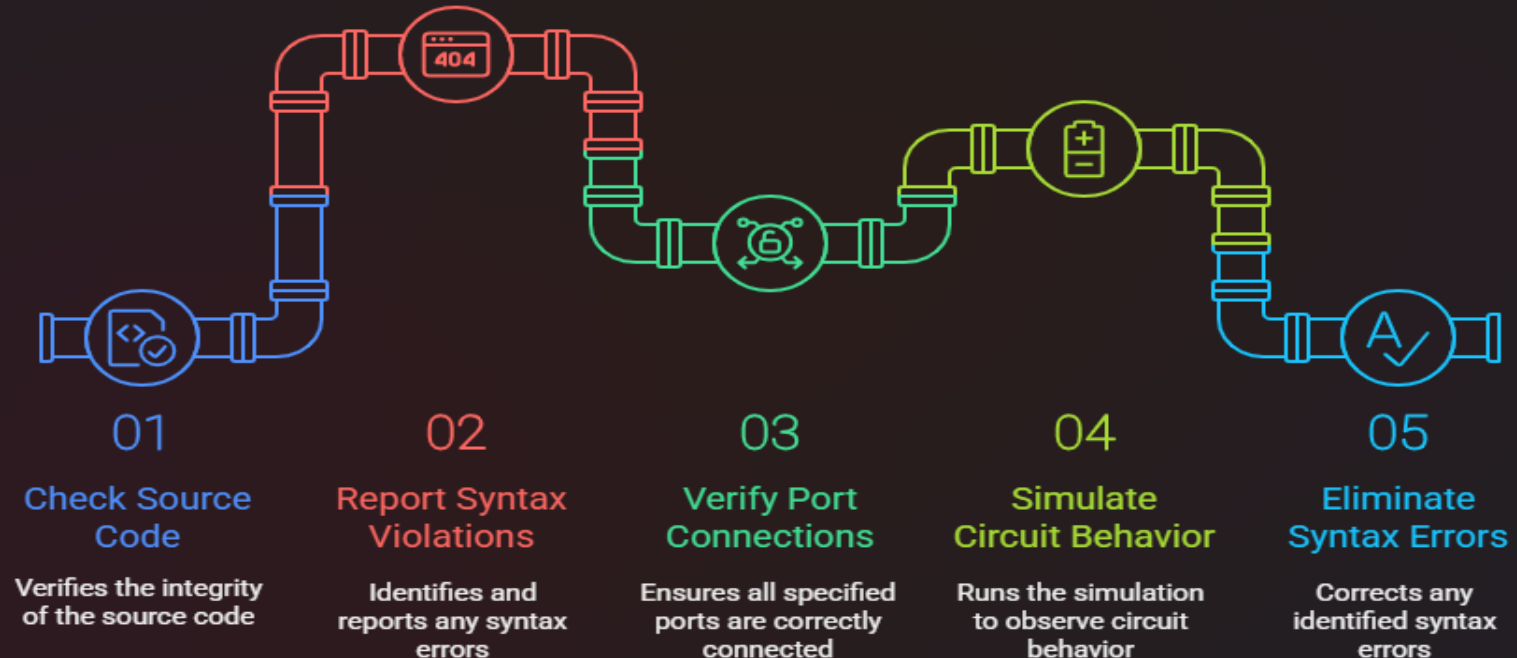



# Signal generators for testbench

*Go, change the world®*

- Initial declares a single pass behavior that begins executing when the simulator is activated at tsim=0
- Statements within begin and end are called procedural statements
- = operator is procedural assignment
- Statements executes sequentially from top to bottom
- # is a delay control operator: suspends the execution of that statement and hence subsequent statement until specified time

```
module halfadd;  
  reg a,b;  
  wire carry, sum;  
  halfadd    u1(carry, sum, a ,b);
```


```
Initial  
begin  
  #10 a=0'b0;b=0'b0;  
  #10 a=0'b0;b=1'b0  
  #10 a=1'b0;b=0'b0 ;  
  #10 a=1'b0;b=1'b0;  
  #100 $finish;  
end  
endmodule
```


 
# Testbench

*Go, change the world®*

- Reg variable takes the value x in the beginning of simulation until it is loaded with different values by explicit statement
- Each statement is delayed by 10 unit
- Delay accumulates (40 u)
- Simulation terminates after 100 u





# Writing Testbenches

*Go, change the world®*

```
module test;  
reg a, b, sel;
```

Inputs to device under test

```
mux m(y, a, b, sel);
```

Device under test

```
initial begin
```

\$monitor is a built-in event driven "printf"

```
$monitor($time, "a = %b b=%b sel=%b y=%b", a, b, sel, y);
```

```
  a = 0; b = 0; sel = 0;
```

```
  #10 a = 1;
```

```
  #10 sel = 1;
```

```
  #10 b = 1;
```

```
  #10 b = 0;
```

Stimulus generated by sequence of  
assignments and delays

```
end
```



RV College of  
Engineering®

# Testbench-AND gate

*Go, change the world®*

```
module test1;  
  reg a,b;  
  wire y;  
  ANDGATE u1(a,b,y);  
  initial  
  begin  
    a=1'b0;b=1'b0;  
    #10 a=1'b0;b=1'b1;  
    #10 a=1'b1;b=1'b0;  
    #10 a=1'b1;b=1'b1;  
    #100 $finish;  
  end  
endmodule
```



# Full adder test bench

```
timescale 1ns / 1ps
module full_adder_tb;
    // Inputs
    reg a;
    reg b;
    reg cin;
    // Outputs
    wire sum;
    wire cout;

    // Instantiate the Unit Under Test
    (UUT)
        full_adder uut (.a(a), .b(b),
        .cin(cin), .sum(sum), .cout(cout) ); endmodule
```

```
initial begin
    // Apply all input combinations
    a = 0; b = 0; cin = 0; #10;
    a = 0; b = 0; cin = 1; #10;
    a = 0; b = 1; cin = 0; #10;
    a = 0; b = 1; cin = 1; #10;
    a = 1; b = 0; cin = 0; #10;
    a = 1; b = 0; cin = 1; #10;
    a = 1; b = 1; cin = 0; #10;
    a = 1; b = 1; cin = 1; #10;
    $finish;
```

end