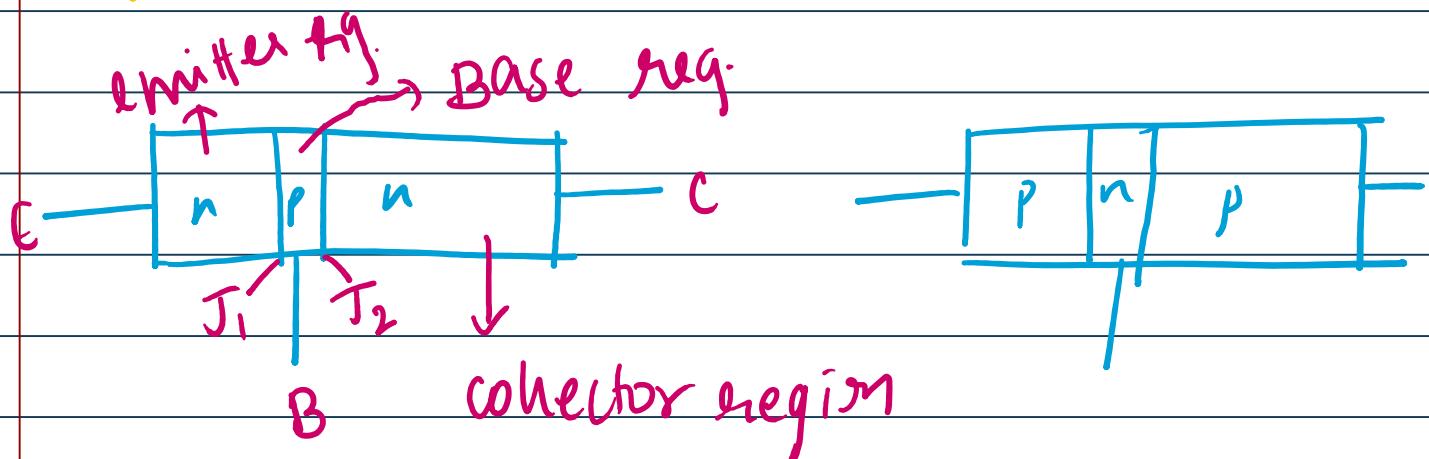


BJT (Bipolar Junction Transistor)

- 3-terminal device.
- amplification of weak signals.
- switching operations

Physical Structure:



$J_1 \rightarrow$ Emitter - Base Junction

$J_2 \rightarrow$ Collector - Base Junction

width : $C > E > B$


↓

more width, better heat dissipation.



more width, better heat dissipation.

doping: $E > C > B$


Cross-sectional view:

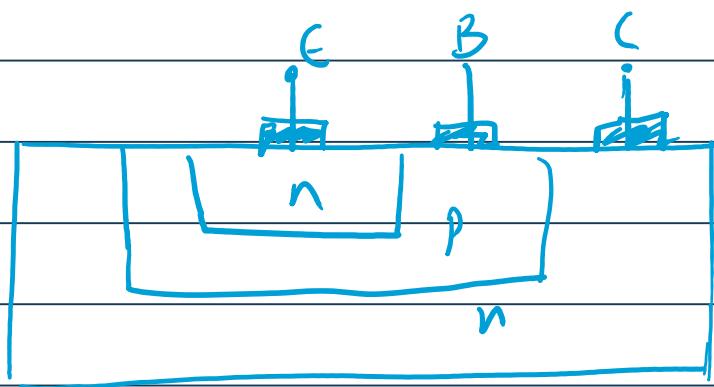



Symbol

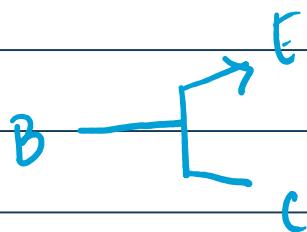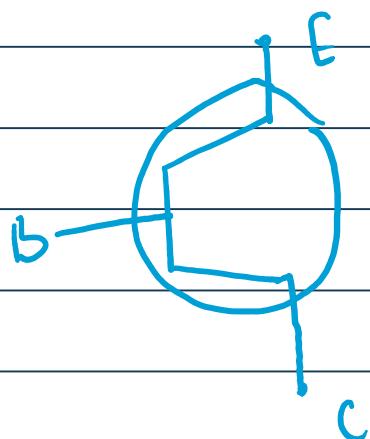


npn

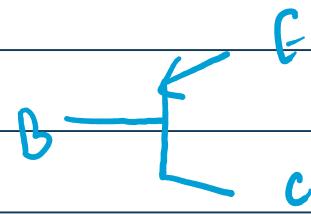

pnp

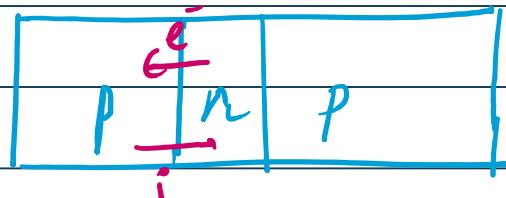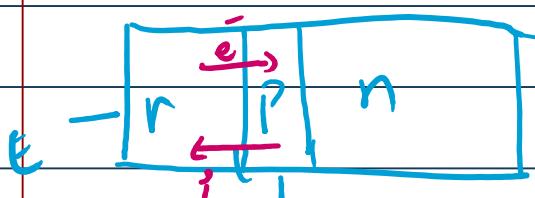

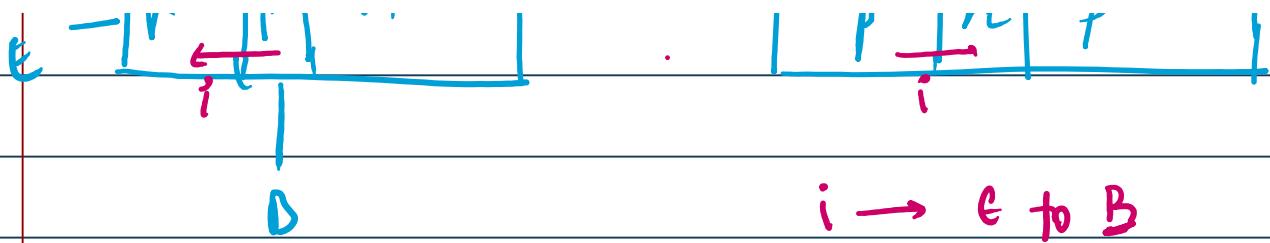

* Generally n-p-n is used as mobility of $e^- >$ mobility of holes.

Bipolar Jum. Transistor

base + Resistor

$J_1 \rightarrow f.b$ (low R)

$J_2 \rightarrow r.b$ (high R)

Regions of op.:

FB

RB

active

Amplifies

FB

FB

Saturation

"ON"

Rb

RB

cutoff

"OFF"

Rb

FB

inverted


Working of Transistor

27 October 2024 11:26 AM

Working of Transistor:


Active mode :
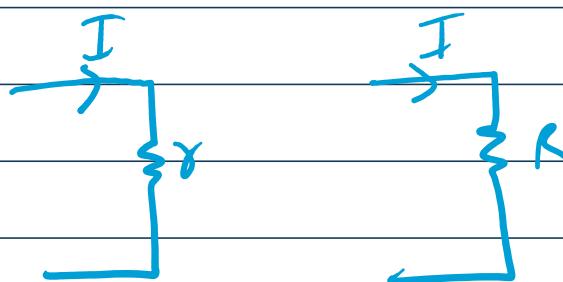
$$\begin{array}{ll} J_1 \rightarrow f.b & R \leq 0 \\ J_2 \rightarrow \gamma \cdot b & R = \infty \end{array}$$



$$V_i = I g_n < \underbrace{V_o = I R}_{\text{amplified signal at output}}$$

amplified signal at output

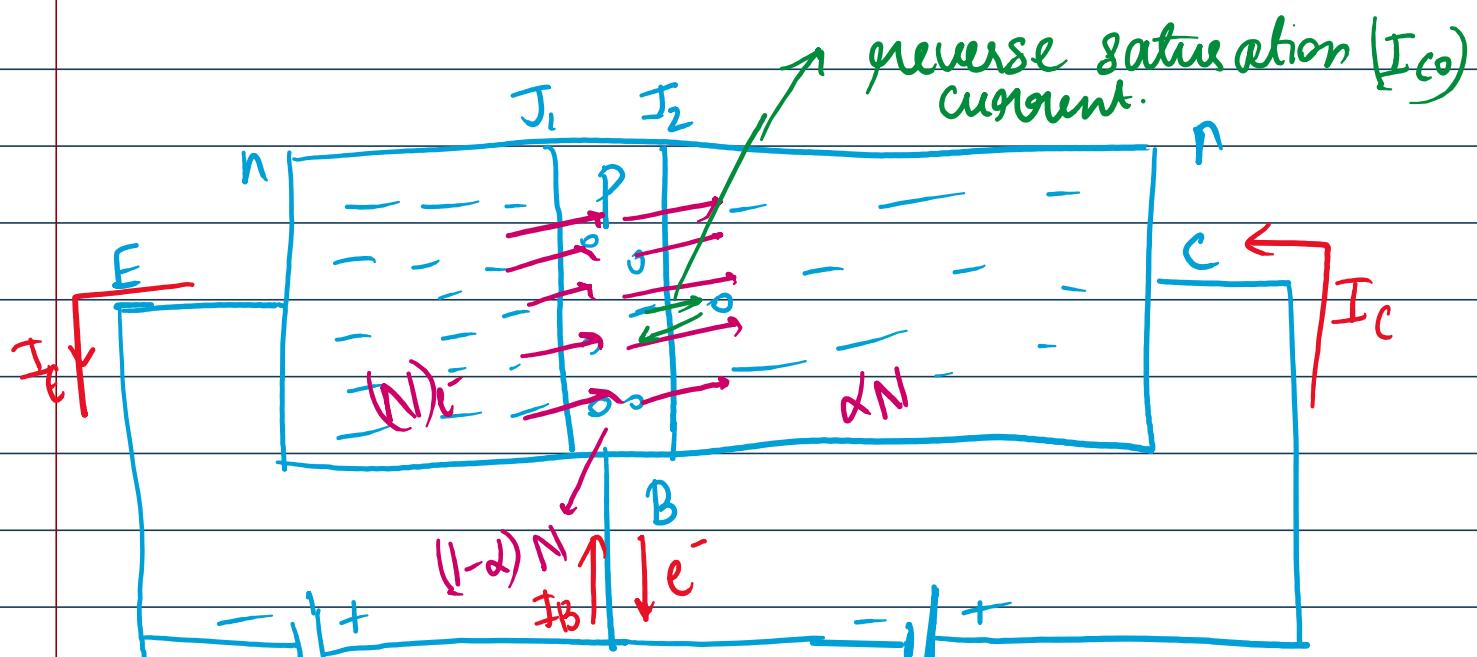



base \rightarrow very small + lightly doped } most e^- from E go to collector.

e^- : 97% - 99% at base

95% - 98% at collector.

$$I_C = \alpha I_E + I_{CO}$$


KCL: $I_E = I_B + I_C$

CB config

27 October 2024 11:42 AM

B, F and C

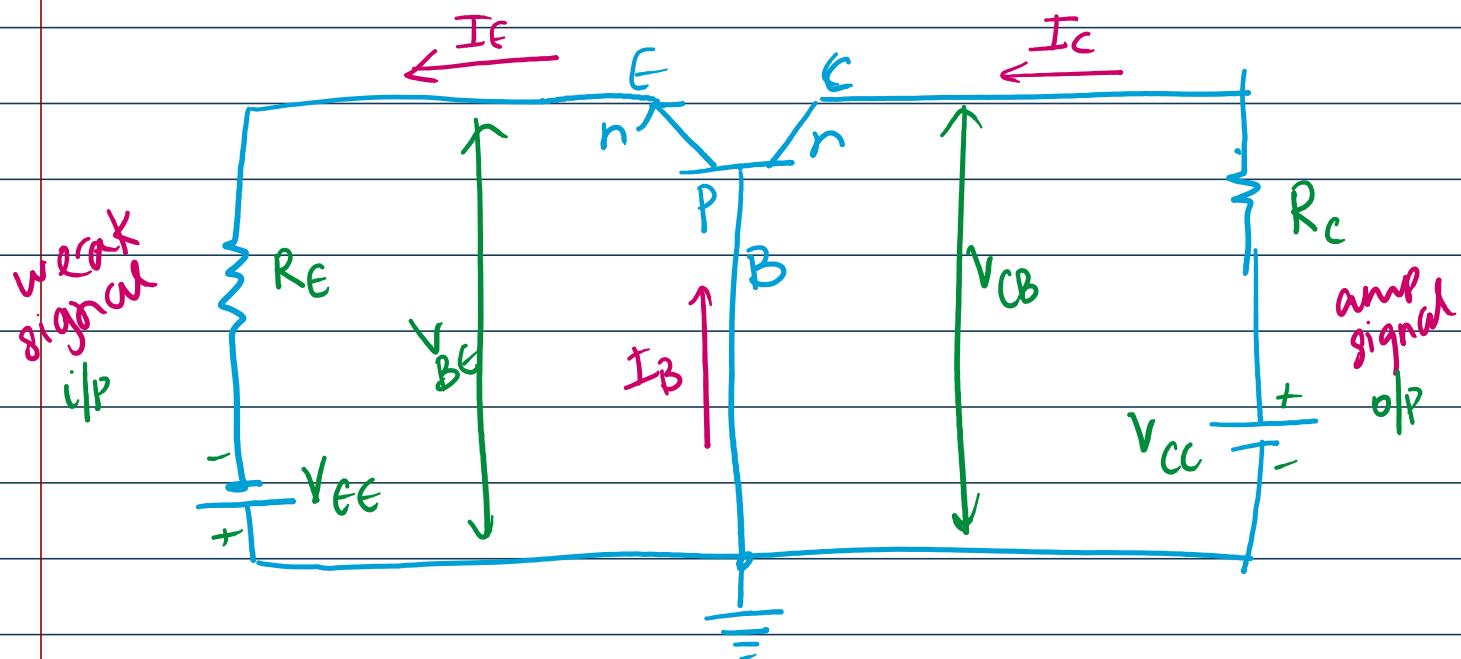- i) Common Base
- ii) Common Emitter
- iii) Common Collector



$$V_{BE} = V_{EE}$$

low pot

~~V_{FB}~~ high pot

$$V_{CB} = V_{CC}$$

→ i/p char. → I_Q vs V_{BC}

o/p char. $\rightarrow I_C$ vs V_{CB}

\rightarrow KCL: $I_C = I_B + I_C$

leaving current = entering current

$$I_C = \alpha I_E + I_{C0} \quad (\text{Q.S.C.})$$

or $I_C = \alpha I_E + I_{CBO}$ \leftarrow open circuit

$$I_C = \alpha I_E$$

$$\cancel{I_E} \gg \cancel{I_{CBO}}$$

can be neg.

$$\alpha = \frac{I_C}{I_E}$$

common base current gain

$$\text{gain} = \frac{\text{o/p}}{\text{i/p}}$$


$$\alpha \rightarrow 0.95 - 0.98$$

$$I_B = (1-\alpha) I_E$$

CB (i/p char)


27 October 2024 12:15 PM

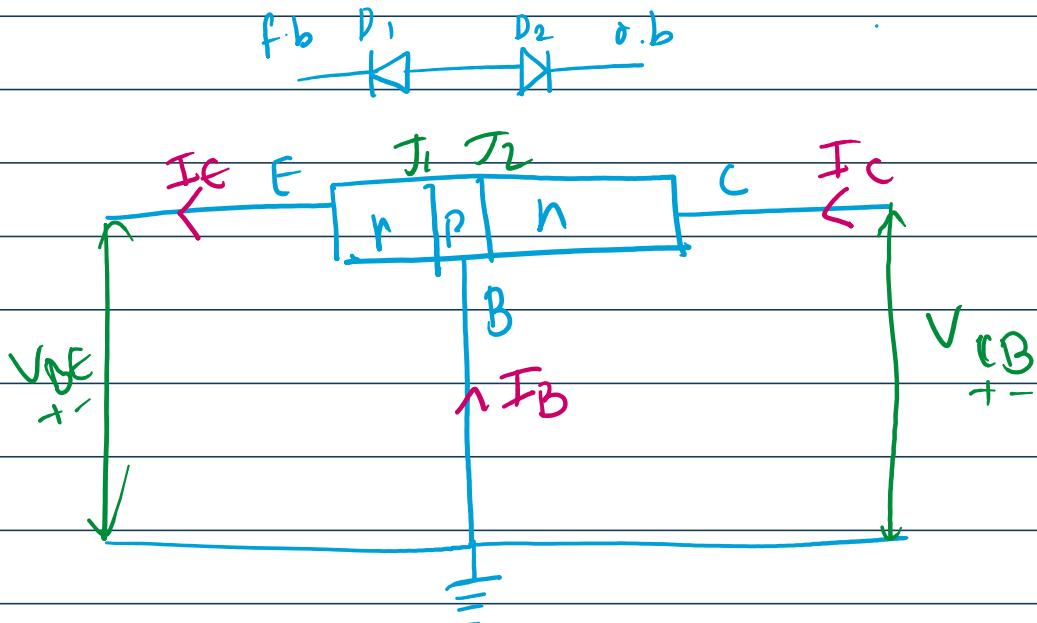(B Trans. (I_p char.) [Early effect]
↓
f.b. diode



$$\text{ifp} \quad I = I_E \\ \text{ifp} \quad V = V_{BE}$$
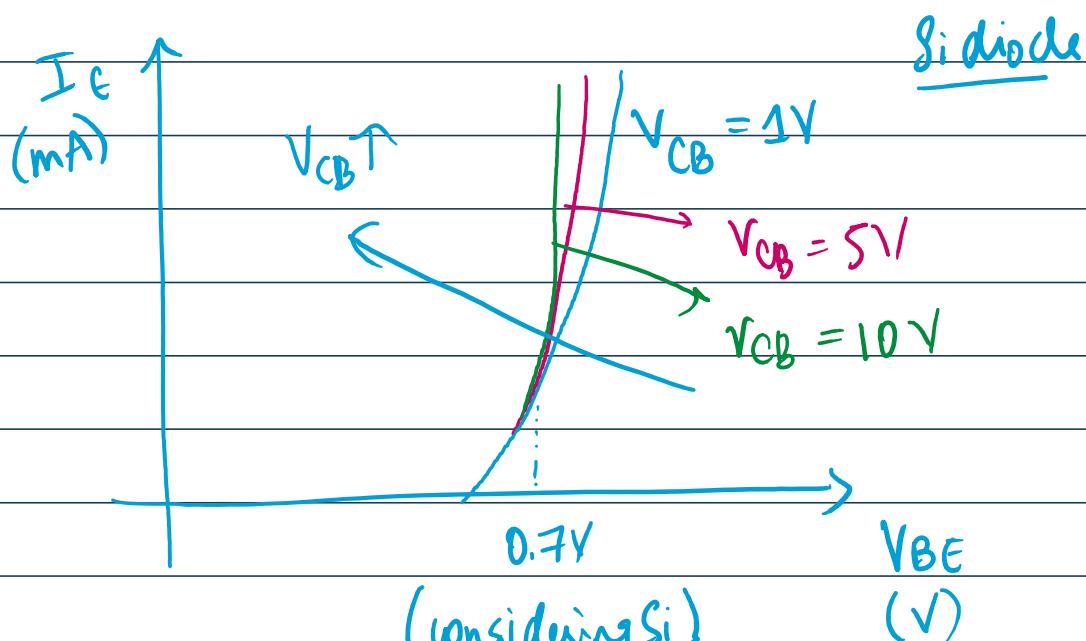
$$\text{o/p} \quad I = I_C \\ \text{o/p} \quad V = V_{CB}$$




(considering Si)

V_{DC}

(✓)

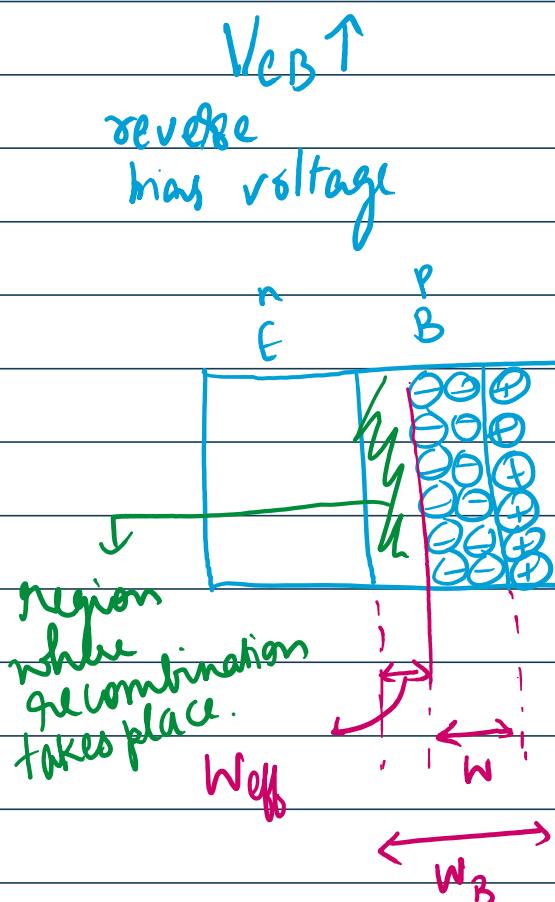Early Effect. (aka base-width modulation)



$$w_B = w_{eff} + w$$

$$w_{eff} = w_B - w$$

if $V_{CB} \uparrow \Rightarrow w \uparrow \Rightarrow w_{eff} \downarrow$


(change of recombination)

$\Rightarrow I_C \uparrow$


(conc. gradient \uparrow)

more e^- flow towards base.

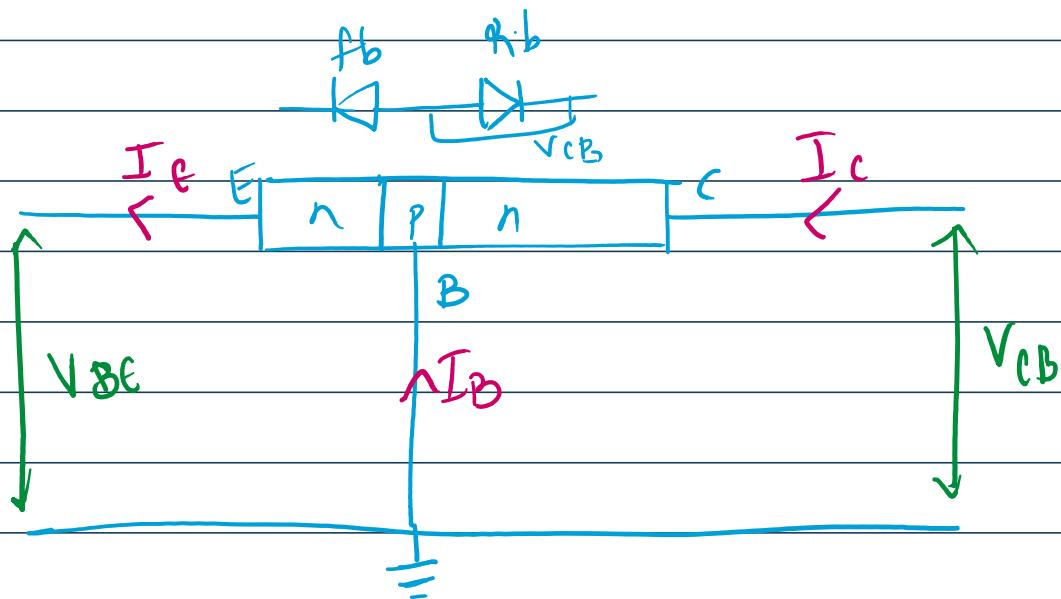CB Trans (o/p char) \rightarrow r.b. diode.



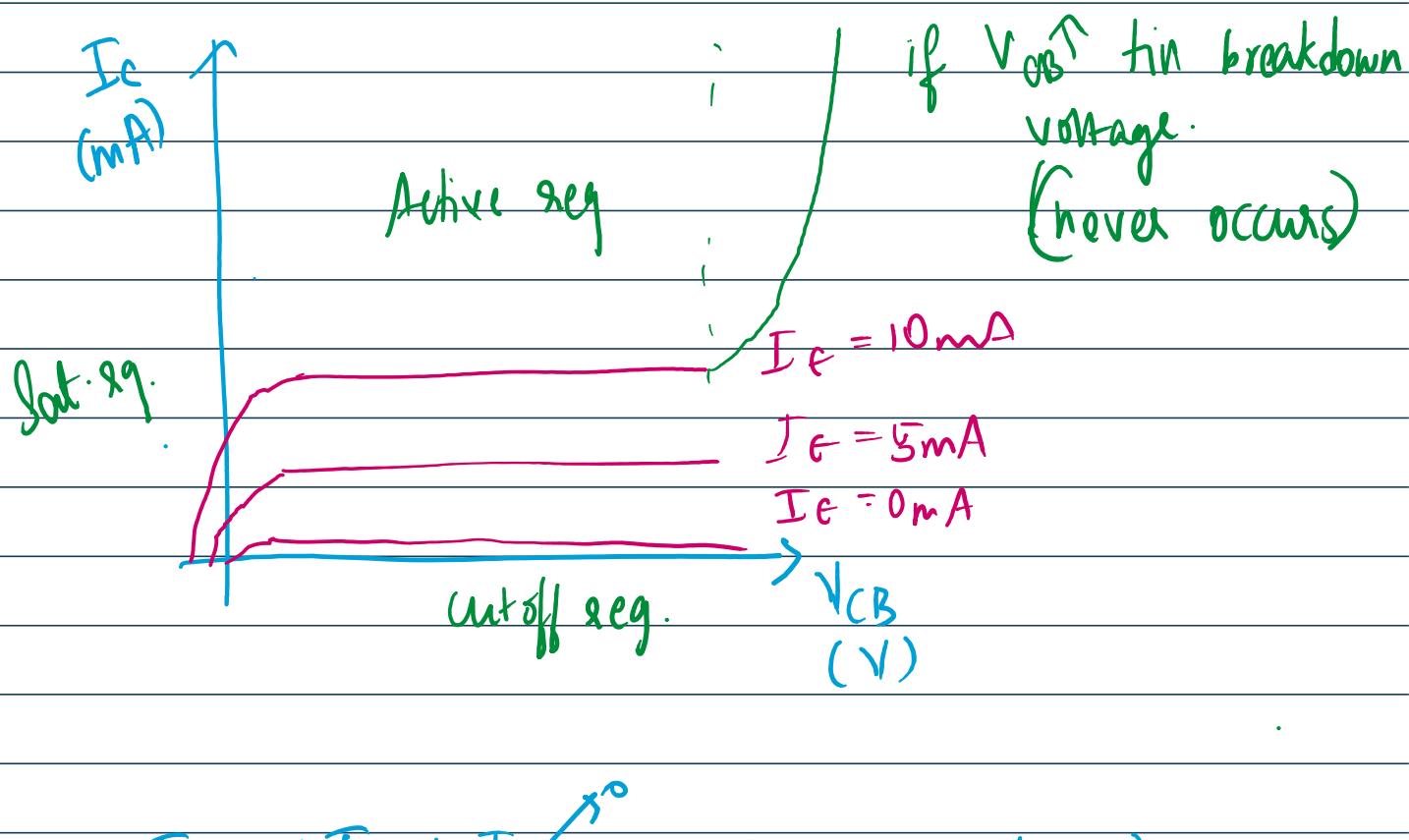o/p I (I_C) vs o/p v (V_{CB}) for various levels of i/p I (I_E)



$$I_C = \alpha I_E + I_{CBO} \quad (\text{independent of } V_{CB})$$

$$I_C = \alpha I_E$$




$$I_C \approx I_E \quad (\alpha = 0.95 - 0.98)$$

o/p ↑ i/p ↑

Tras amp action

27 October 2024 01:04 PM

Transistor Amplifying Action:

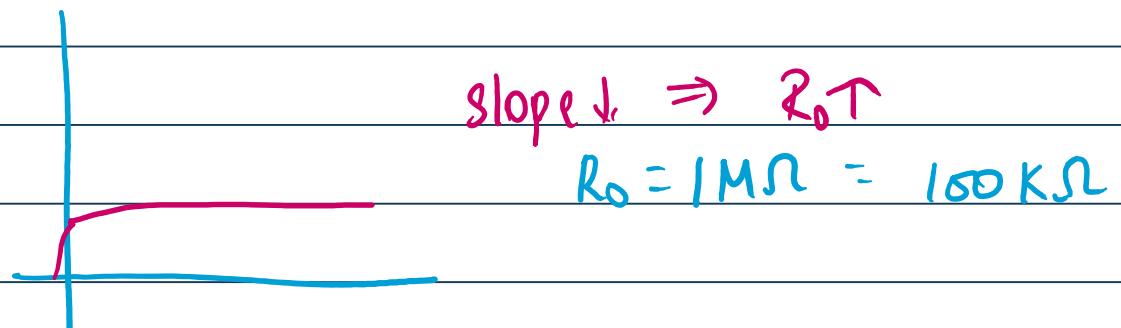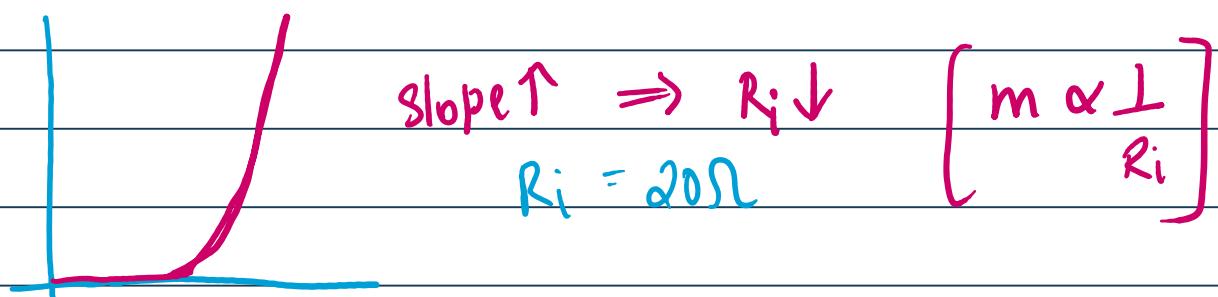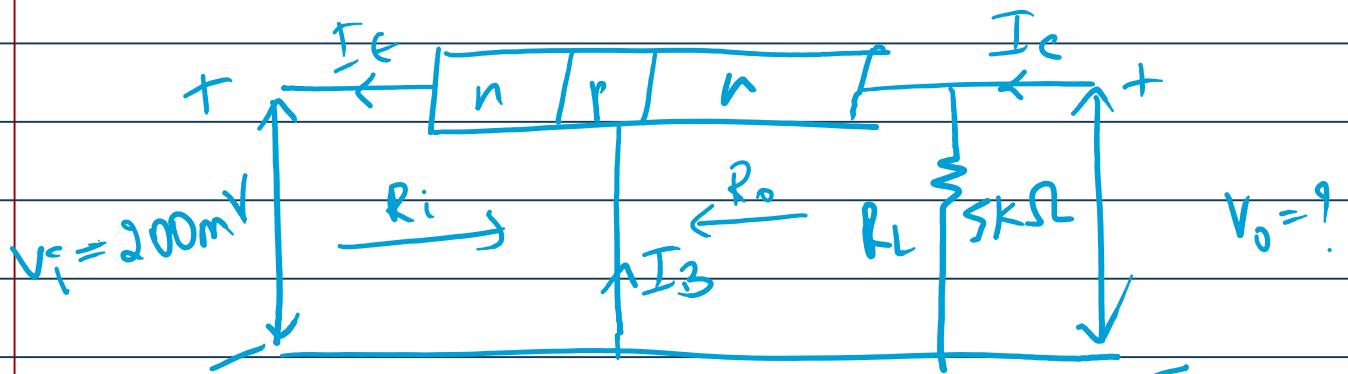

$$\boxed{61}: \quad V_i = I_i R_i$$

$$V_i = I_C R_i \Rightarrow I_C = \frac{V_i}{R_i} = \frac{200\text{mV}}{20\Omega} = 10\text{mA}$$

$$I_C = 10\text{mA}$$

$$I_C = 10 \text{ mA}$$

$$I_C = I_E = 10 \text{ mA}$$

$$\begin{aligned} V_o &= I_C R_L \\ &= (10 \text{ mA}) \times (5 \text{ k}\Omega) \end{aligned}$$

$$V_o = 50 \text{ V}$$

Voltage Amps.

$$A_v = \frac{V_o}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 50$$



V_o is amplified 50 times.

Amplification of current is always less than 1

CE config

27 October 2024 05:23 PM

Common Emitter Config.

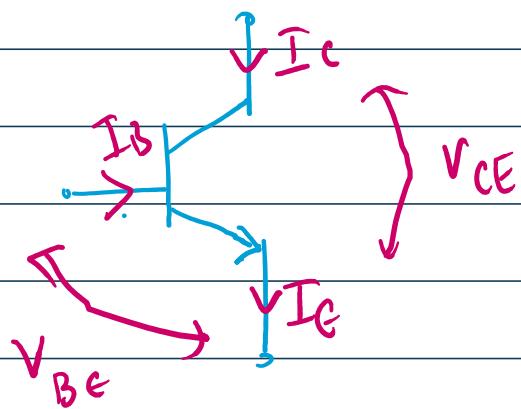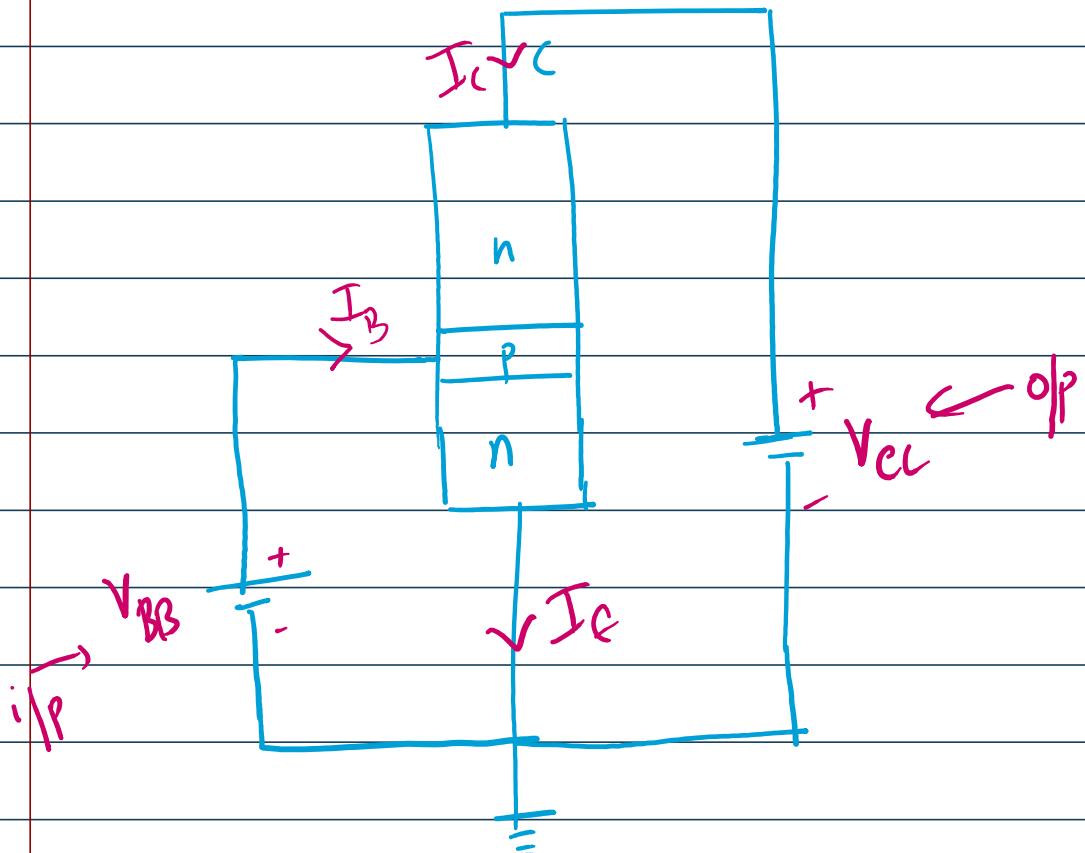

$$i/p \quad I \rightarrow I_B$$

$$i/p \quad V \rightarrow V_{BE}$$

$$o/p \quad I \rightarrow I_C$$

$$o/p \quad V \rightarrow V_{CE}$$

$$I_e = I_c + I_b$$

$$I_c = \alpha I_e + I_{CBO}$$

$$I_e = \alpha (I_c + I_b) + I_{CBO}$$

$$I_c = \alpha I_e + \alpha I_b + I_{CBO}$$

$$(1 - \alpha) I_c = \alpha I_b + I_{CBO}$$

$$I_c = \frac{\alpha}{1-\alpha} I_b + \frac{1}{1-\alpha} I_{CBO}$$

$$I_c = \beta I_b + (\beta + 1) I_{CBO}$$

$$\left\{ \beta = \frac{\alpha}{1-\alpha} ; \quad \beta + 1 = \frac{\alpha}{1-\alpha} + 1 = \frac{1}{1-\alpha} \right\}$$

$$(I : \alpha = 0.98 \quad \beta = \frac{0.98}{1-0.98} = 49)$$

$$(II : \alpha = 0.95 \quad \beta = \frac{0.95}{1-0.95} = 19)$$

slight change in α changes β significantly.

$$[\alpha < 1 \quad 50 \leq \beta \leq 400]$$

$$I_C = \underbrace{\beta I_B + (\beta+1) I_{CBO}}_{I_{CEO}}$$

reverse saturation current in
CE - config.

$$I_C = \beta I_B + I_{CEO}$$

$$I_{CEO} \ll \beta I_B$$

$$I_C = \beta I_B$$

$$\boxed{\beta = \frac{I_C}{I_B}}$$

current amplification factor.

NOTE : $I_C = \alpha I_C + I_{CBO}$ CB config

$$I_C = \beta I_B + (\beta+1)I_{CBO} \text{ CE config.}$$

contribution of leakage current in the b/p current is more in case of CE config. than CB config


$$\left. \begin{aligned} \beta &= 99, \quad I_C \text{ in CB config} \rightarrow 99 I_{CBO} \\ &\text{in CE config} \rightarrow 100 I_{CBO} \end{aligned} \right\}$$

CE (i/p char)


27 October 2024 05:39 PM

CE trans. (I/p char).


V_{BB} & V_{CC} \rightarrow Biasing pot.

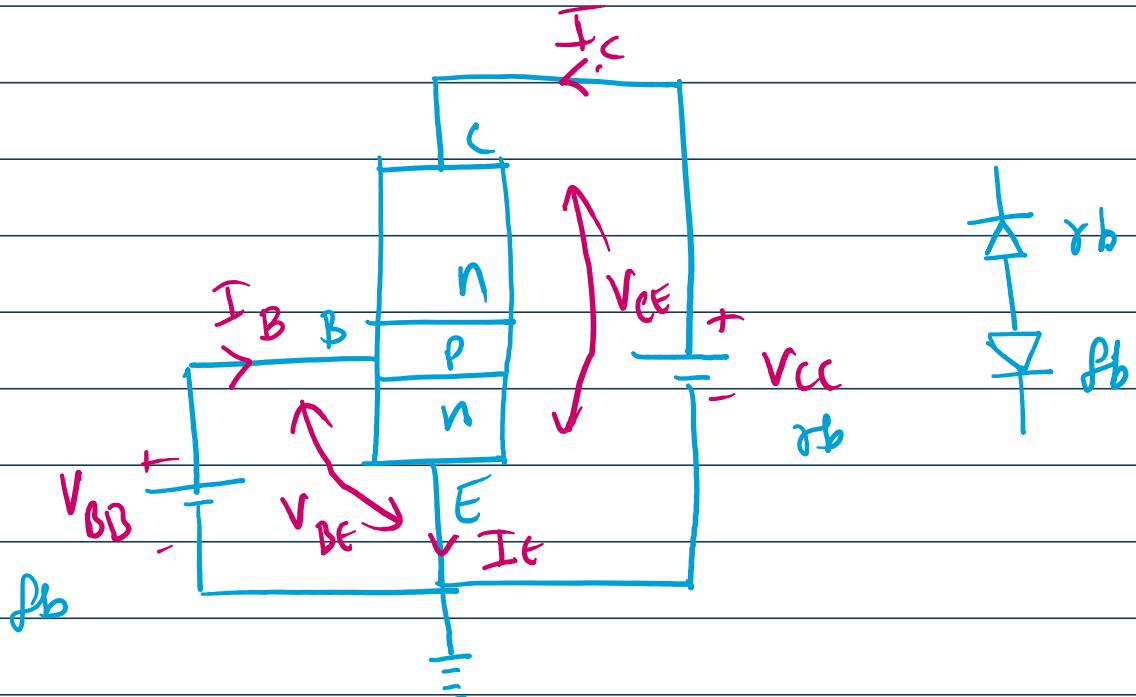

I_B vs V_{BE} for diff values of V_{CE}

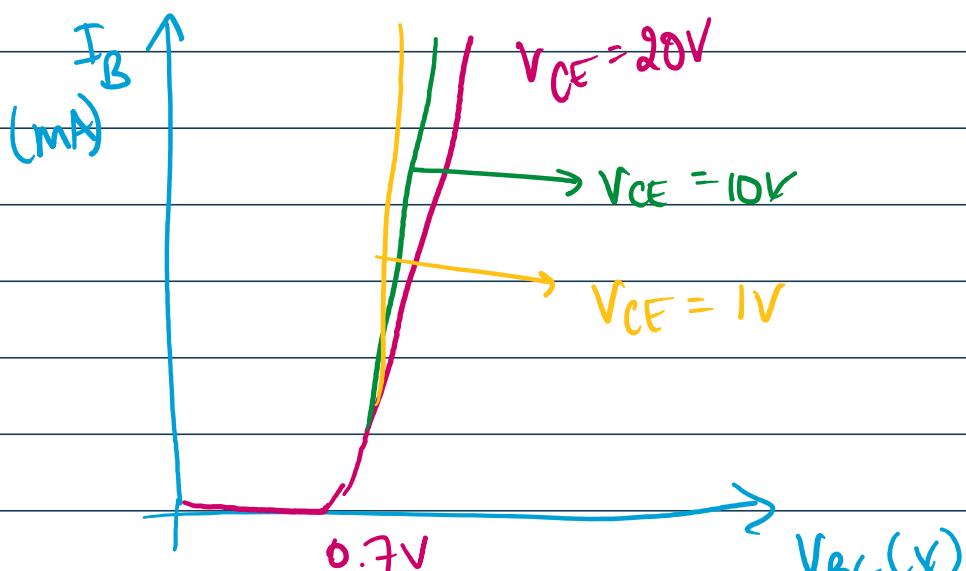

When $V_{BE} > V_b$
 barrier pot.

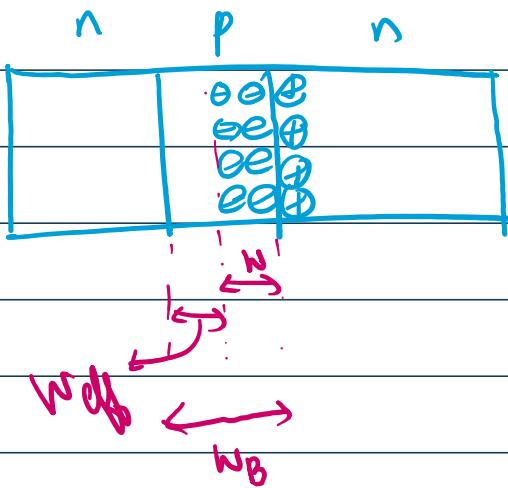

$$V_{CE} = V_{CB} + V_{BE}$$

$$W_{eff} = W_B - W$$

$$V_{CB} \uparrow \Leftrightarrow V_{CE} \uparrow \Rightarrow W \uparrow \Rightarrow W_{eff} \downarrow$$


$$\Rightarrow I_B \downarrow (I_E \uparrow)$$

CB (o/p char)

27 October 2024 05:49 PM

CE config (opp - char).

I_C vs V_{CE} for diff levels of I_B .

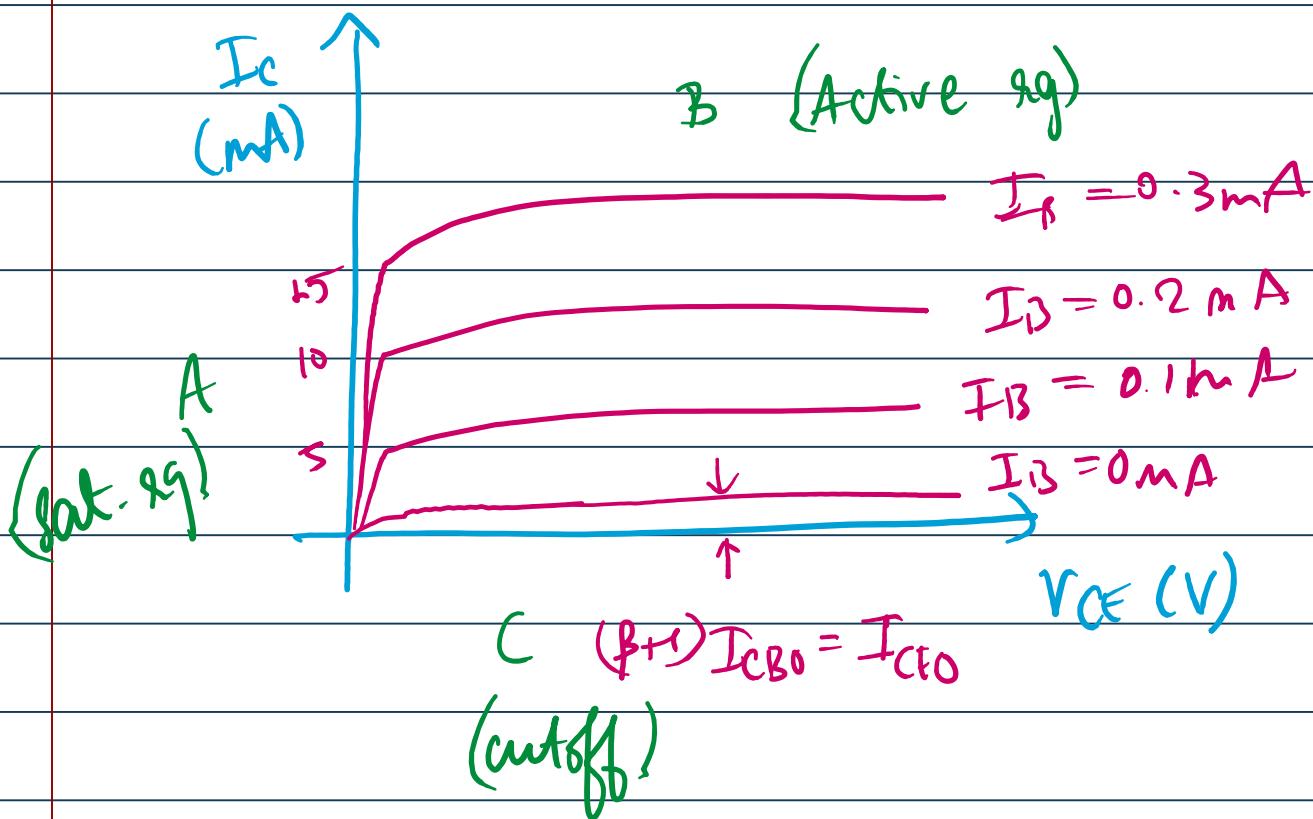

$$I_C = \beta I_B + (\beta + 1) I_{CB0}$$

$$I_B = 0, \quad I_C = (\beta + 1) I_{CB0}$$

$$I_B = 0.1 \text{ mA} \rightarrow I_C = 5 \text{ mA}$$

$$I_B = 0.2 \text{ mA} \rightarrow I_C = 10 \text{ mA}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{10 - 5}{0.2 - 0.1} = 50.$$



$$\uparrow V_{CE} = V_{CB} + V_{BE}$$

$\hookrightarrow W_{off} \downarrow \Rightarrow I_B \downarrow \Rightarrow I_C \uparrow$

CC config

27 October 2024 05:56 PM

Common Collector Config

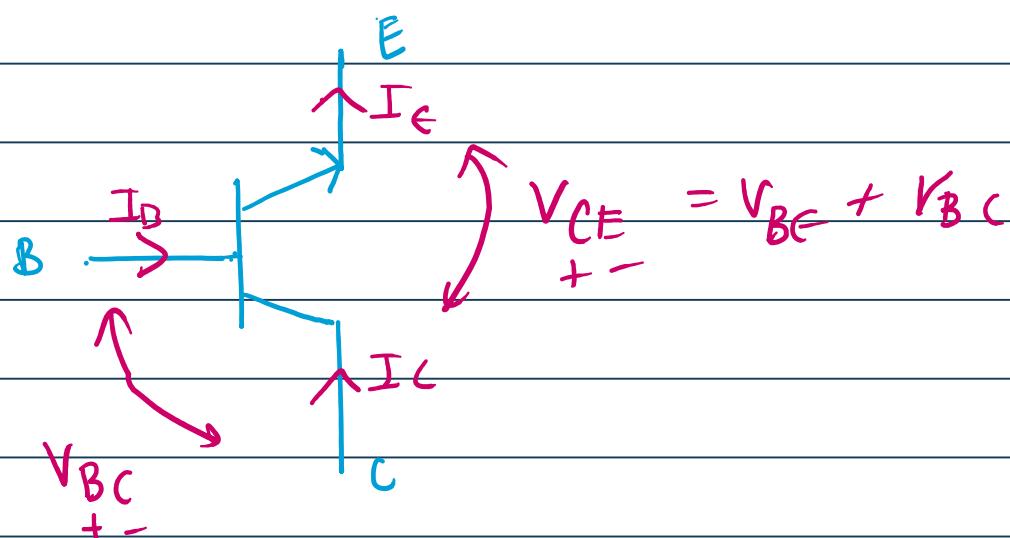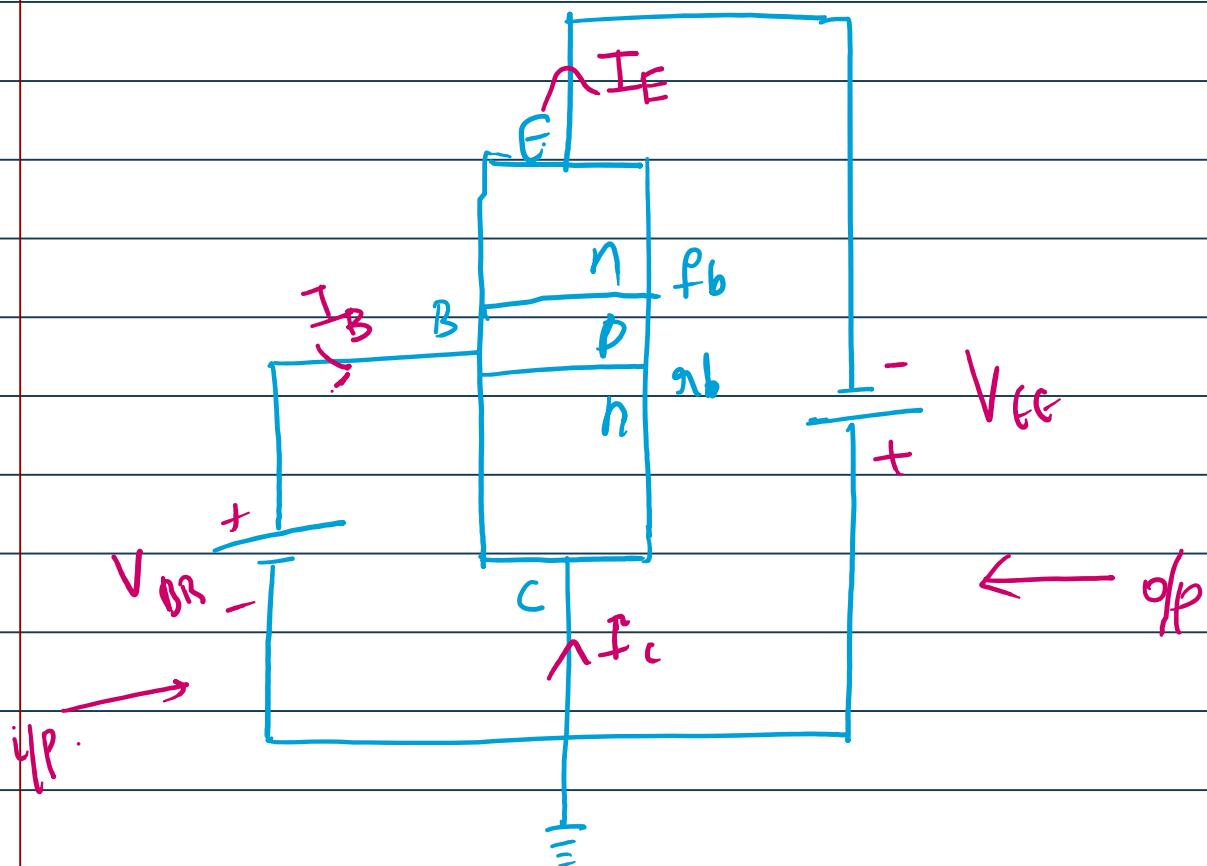

~~i_f~~ vs V_{CE} for various levels of I_B

$$I_C \left\{ \begin{array}{l} I_C = \alpha I_E \quad \alpha \Rightarrow 0.95 - 0.98 = 1 \\ I_C \approx I_E \end{array} \right.$$

o/p char of CE \Leftrightarrow o/p char of CC.

$$\boxed{\beta = \frac{\Delta I_C}{\Delta I_B}}$$

current amplification factor.

$$I_E = I_C + I_B \rightarrow ①$$

$$I_C = \alpha I_E + I_{CBO} \rightarrow ②$$

$$I_E = \alpha I_E + I_{CBO} + I_B$$

$$(1-\alpha) I_E = I_B + I_{CBO}$$

$$I_E = \frac{1}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$I_E = \gamma I_B + \gamma I_{CBO}$$

$$\left\{ \gamma = \frac{1}{1-\alpha} \right\}$$

Relation b/w 3 amp factors

27 October 2024 06:08 PM

Relation b/w α, β, γ . Amplification factors

$$(CB) \alpha \rightarrow \alpha_{dc} = \frac{I_c}{I_t}$$

$$\alpha_{ac} = \frac{\Delta I_t}{\Delta I_c} \quad | V_{CB} = \text{const}$$

$$(CE) \beta \rightarrow \beta_{dc} = \frac{I_c}{I_B}$$

$$\beta_{ac} = \frac{\Delta I_c}{\Delta I_B} \quad | V_{CE} = \text{const}$$

$$(CC) \gamma \rightarrow r_{dc} = \frac{I_t}{I_B}$$

$$r_{ac} = A I_t \quad |$$

$$Y_{AC} = \frac{AI_C}{I_B} \quad | V_{CE} = 10mV$$

$$I_E = I_C + I_B$$

$$\frac{I_E}{I_B} = \frac{I_C}{I_B} + \frac{I_B}{I_B}$$

$$\gamma = \underline{\underline{\beta + 1}}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\gamma = \frac{\alpha}{1-\alpha} + 1$$

$$\gamma = \frac{1}{1-\alpha}$$

$$\boxed{\gamma = \beta + 1 = \frac{1}{1-\alpha}}$$

.


DC Biasing

27 October 2024 06:12 PM

DC Biasing of Transistors

→ Biasing: the process in which we apply external dc voltages to select the appropriate or proper OP. (Operating point).

→ mpn CE trans. used.

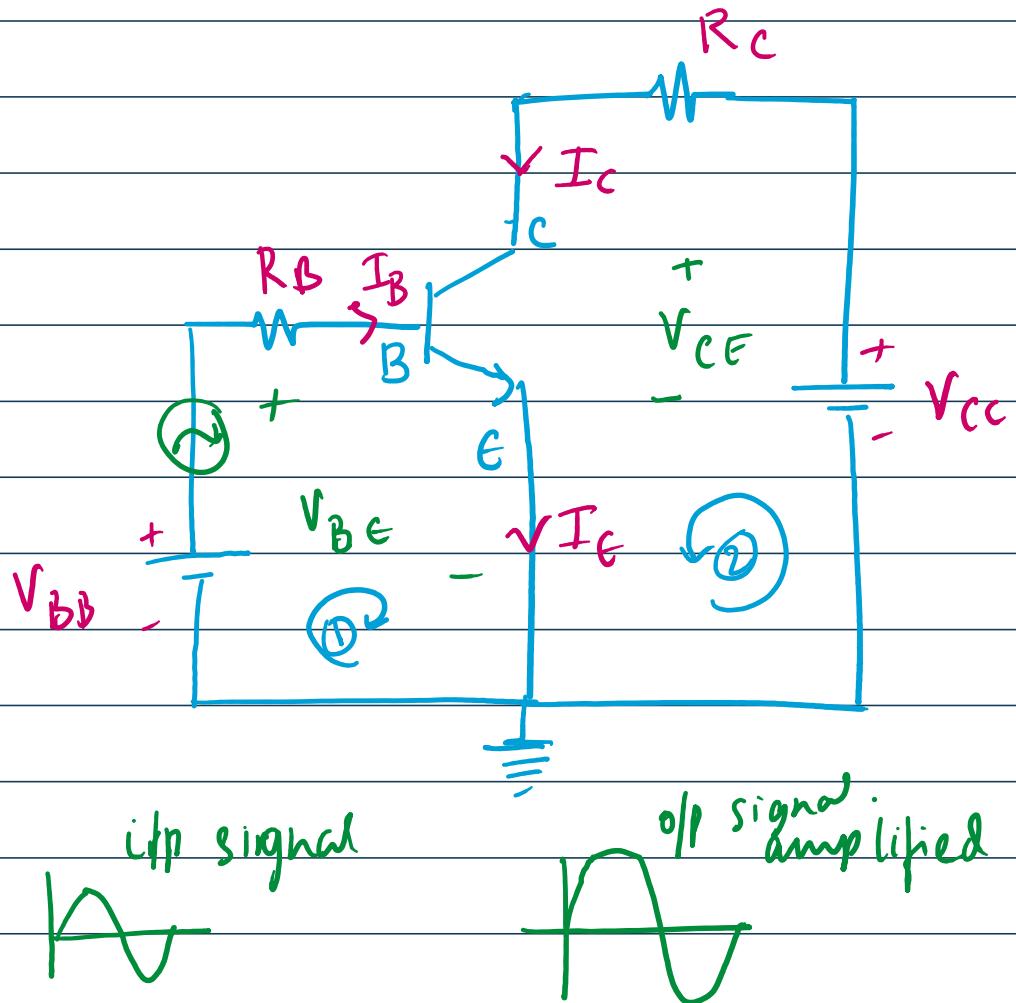

i/p OP —

→ KVL in loop ①:


$$+V_{BB} - (I_B R_B) - V_{BE} = 0$$

$$P_1 = (0, I_c)$$

$$P_2 = (V_{BE}, 0)$$

$$\rightarrow V_{BE} = 0 \quad . \quad \rightarrow I_B = 0$$
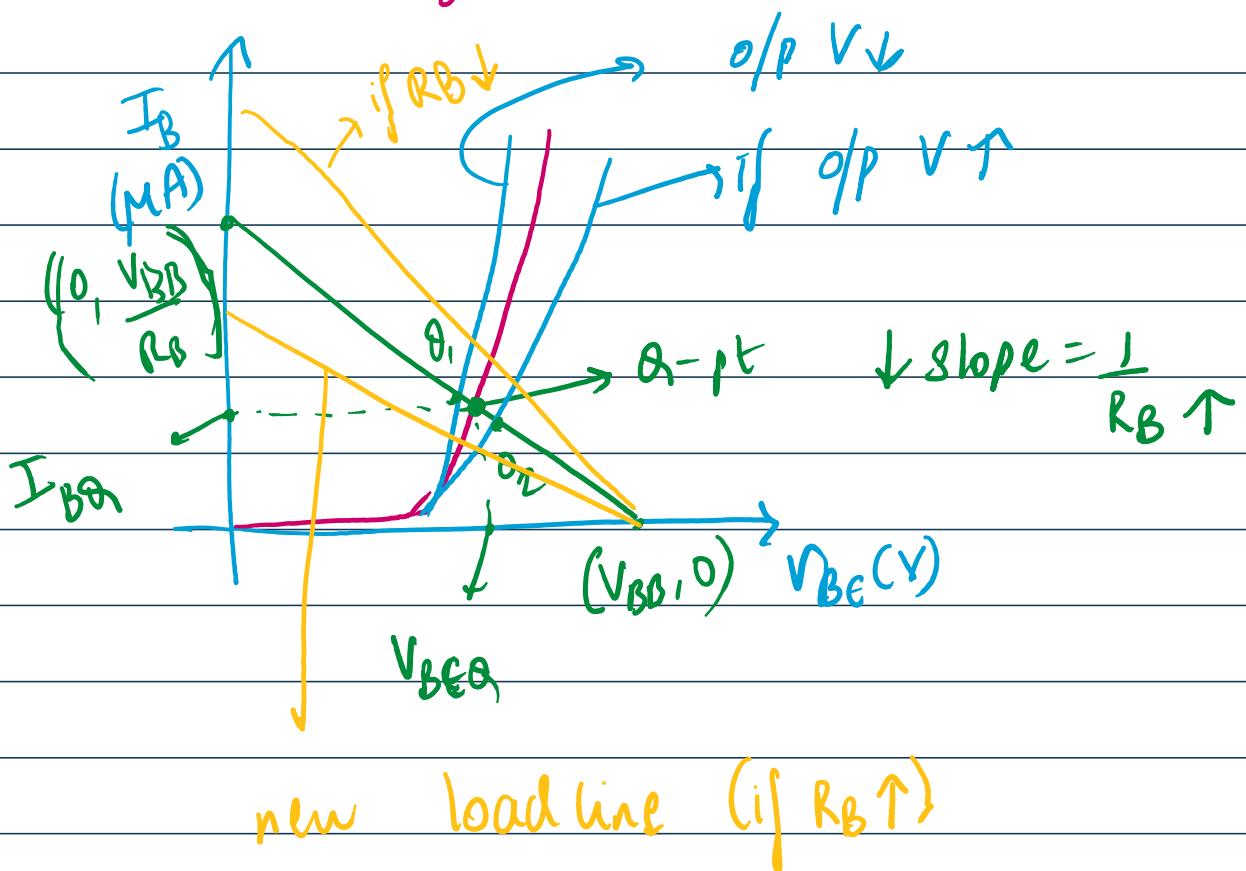
$$I_B = \frac{V_{BB}}{R_B} \quad V_{BE} = V_{BB}$$



→ KVL in loop ②:

- $\Delta V_L \propto I_C$

$$V_{CC} - (I_C R_C) - V_{CE} = 0$$


$$P_1 \equiv (0, I_C) \quad P_2 \equiv (V_{CE}, 0)$$

$$V_{CE} = 0$$

$$I_C = \frac{V_{CC}}{R_C}$$

$$I_C = 0$$



$$V_{CE} = V_{CC}$$

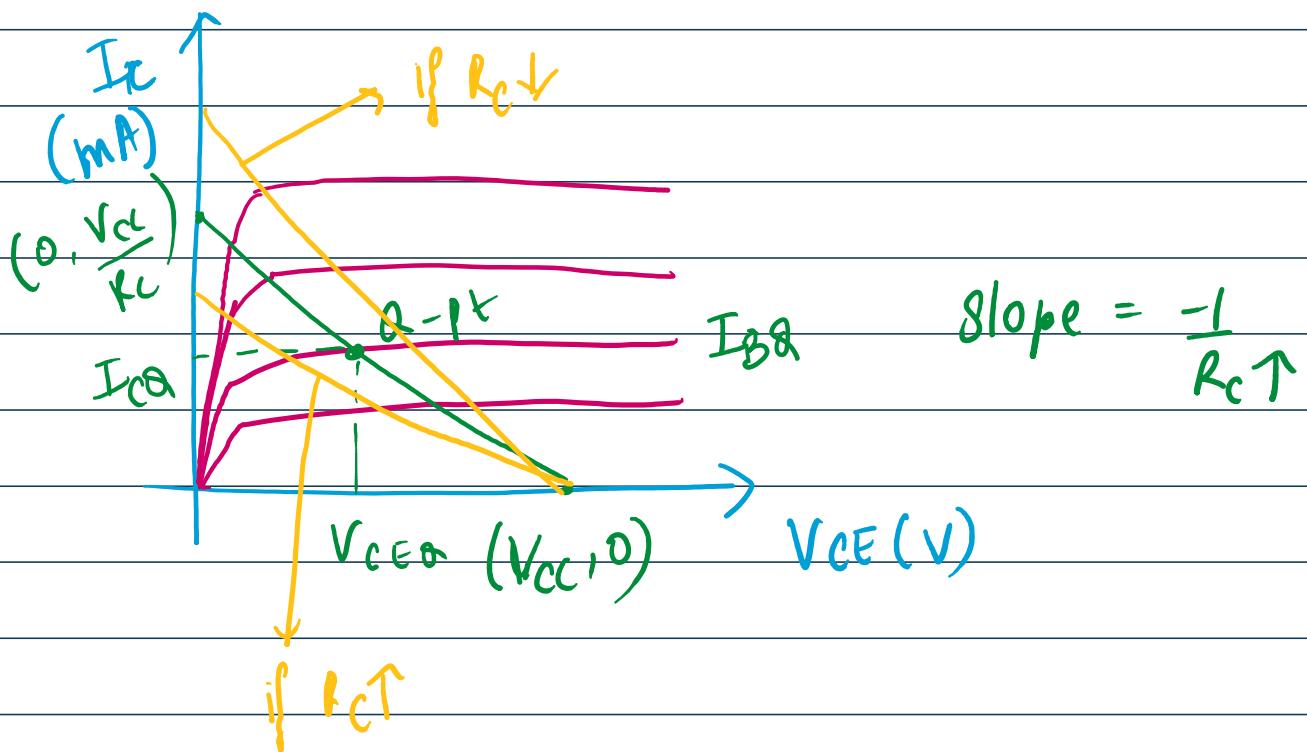

Fixed Bias Config

27 October 2024 11:37 PM

Fixed Bias Configuration

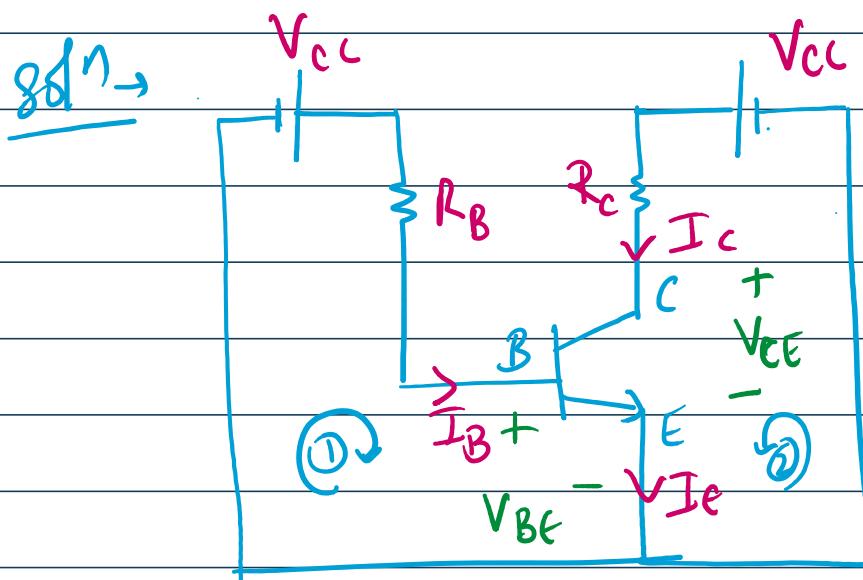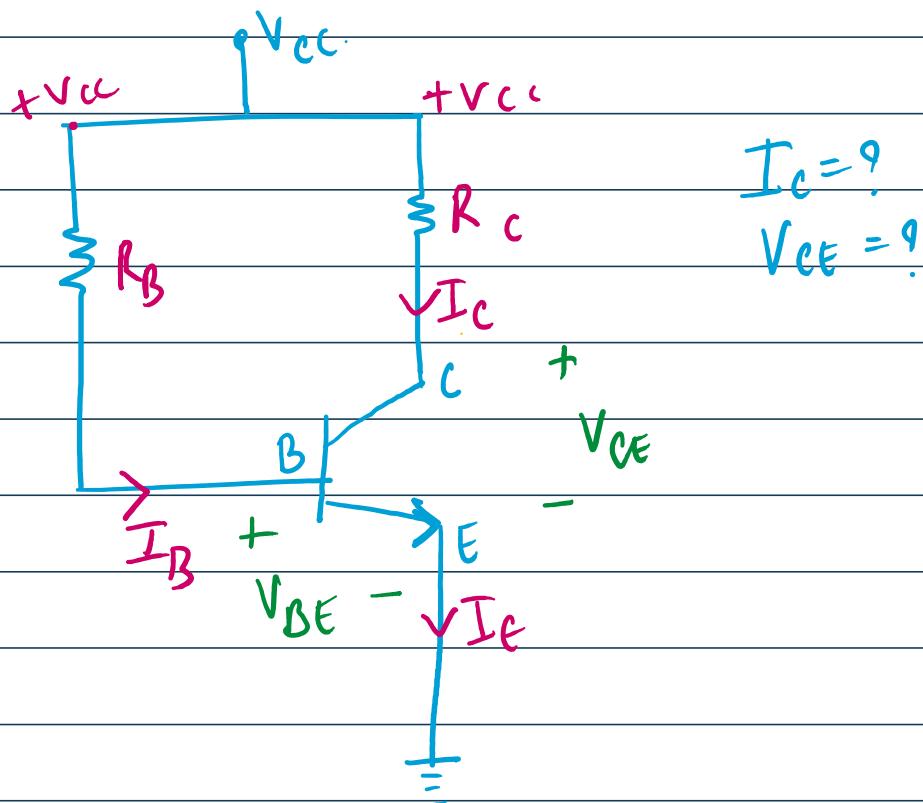

\rightarrow KVL for loop (1):

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B}$$

0.7V (V_i)
0.3V (V_e)


→ KVL for loop ②:

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

ex:

① For the fixed bias config., determine,

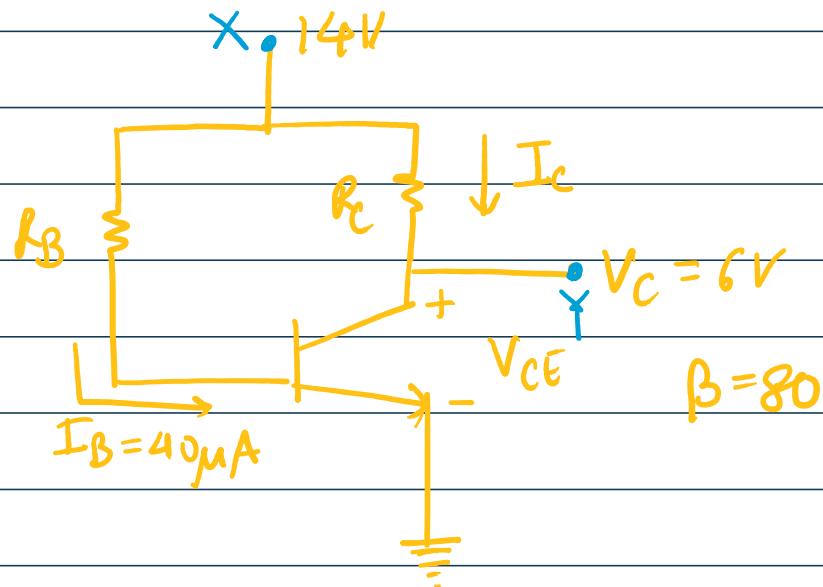

find \rightarrow

- (a) I_C
- (b) R_C
- (c) R_B
- (d) V_{CE}

Soln.

$$V_{CC} = 14V$$

$$I_B = 40\mu A$$

$$\beta = 80$$

$$V_C = 6V$$

$$\rightarrow \text{Wkt, } I_C = \beta I_B \\ = 80 \times 40\mu A$$

$$= 3200\mu A$$

$$I_C = 3.2mA \quad (\text{a}).$$

=====

$$\rightarrow \text{KVL, (from } X \rightarrow Y)$$

$$14 - I_C R_C = 6$$

$$I_C R_C = 8$$

$$R_C = \underline{8}$$

$$3.2mA$$

$$R_C = 2.5k\Omega \quad (\text{b})$$

=====

→ KVL, (in i/p loop)

$$14 - I_B R_B - V_{BE} = 0$$

$$R_B = \frac{14 - V_{BE}}{I_B}$$


$$= \frac{(14 - 0.7)}{40 \mu A}$$


$$= \frac{13.3}{40 \mu A}$$

$$R_B = 332.5 \text{ k}\Omega \quad (\text{c})$$

→ $V_{CE} = V_C - V_E$
= 6 - 0

$$V_{CE} = 6V \quad (\text{d})$$

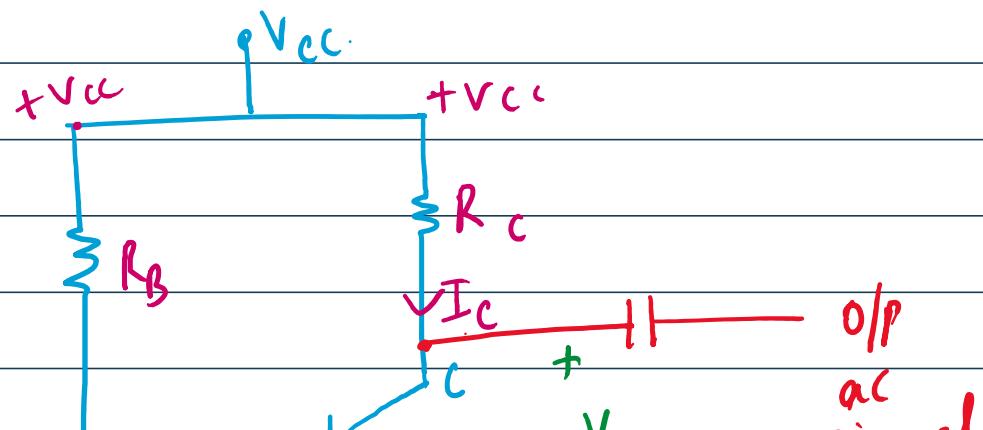

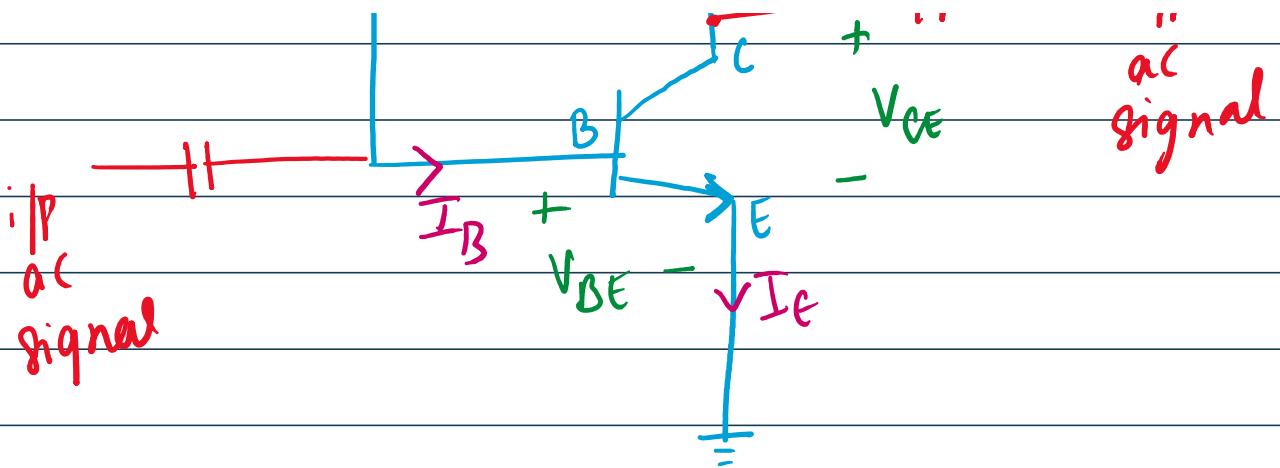

$$\alpha_C = \frac{1}{2\pi f C}$$

$\beta = 0$ (in case of dc)


$$\alpha_C = \frac{1}{0} = \infty$$

\Rightarrow thus, --- part becomes
an open circuit -- --
and is ignored in dc.

② For the fixed bias config,
determine

find :

- (a) I_C
- (b) V_{CC}
- (c) β
- (d) R_B

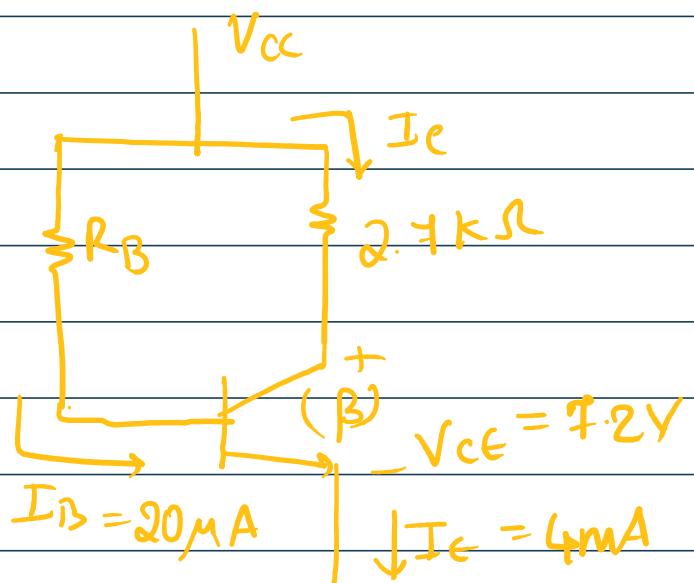

$$I_B = 20 \mu A \quad | \quad I_C = 4 \mu A$$

Soln: we have, $R_C = 2.7k\Omega$
 $V_{CE} = 7.2 V$
 $I_E = 4 \mu A$
 $I_B = 20 \mu A$

$$\rightarrow I_E = I_B + I_C$$

$$\begin{aligned}
 I_C &= I_E - I_B \\
 &= 4 \mu A - 20 \mu A \\
 &= 4 \times 10^{-3} - 20 \times 10^{-6} \\
 &= 4 \times 10^{-3} (1 - 5 \times 10^{-3}) \\
 &= 4 \times 10^{-3} \times 0.995 \\
 I_C &= 3.98 \mu A \quad (a) \\
 \hline
 \end{aligned}$$

$$\rightarrow KVL, \text{ (in o/p loop)}$$

$$\begin{aligned}
 V_{CC} - I_C R_C - V_{CE} &= 0 \\
 V_{CC} - (3.98 \mu A) (2.7k) - 7.2 &= 0
 \end{aligned}$$

$$V_{CC} - 10.7460 - 7.2 = 0$$

$$V_{CC} = 17.946 V \quad (b)$$

$$V_{CC} = 17.946 \text{ V } (b)$$

$$\rightarrow I_C = \beta I_B$$

$$\beta = \frac{I_C}{I_B} = \frac{3.98 \text{ mA}}{20 \mu\text{A}}$$

$$= \frac{3980}{20}$$

$$\beta = \underline{\underline{199}} \text{ (c)}$$

$\rightarrow KVL$, (in i/p loop)

$$V_{CC} - I_B R_B - V_{BE} = 0$$


$$R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$= \frac{17.946 - 0.7}{20 \mu\text{A}}$$

$$= \frac{17.246}{20} \times 10^6$$

$$\cdot R_B = \underline{\underline{862.3 \text{ k}\Omega}}$$

Emitter Bias Config

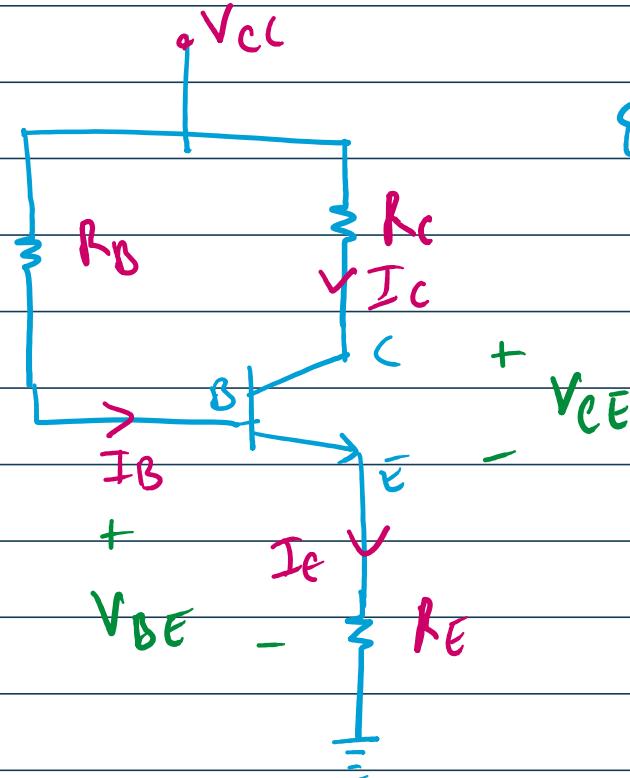

$$\Delta-\text{pt} \equiv (I_{CQ}, V_{CEQ})$$

\rightarrow KVL, (in ip loop):

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\boxed{\begin{aligned} I_E &= I_C + I_B \\ &= \beta I_B + I_B \\ I_E &= (\beta + 1) I_B \end{aligned}}$$

$$V_{CC} - \underline{I_B R_B} - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$V_{CC} - I_B (R_B + (\beta + 1) R_E) - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$I_C = \beta I_B$$

$$I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \right)$$

→ KVL, (in o/p loop)

$$V_{CC} - I_C R_C - \underline{V_{CE}} - I_E R_E = 0$$

$$[I_E \approx I_C]$$

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0$$

$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0$$

$$V_{CE} = V_{CC} - (R_C + R_E) I_C$$

Advantage of using R_E :

1) Temp $\uparrow \Rightarrow I_C \uparrow \quad \{ I_C = \beta I_B + (\beta + 1) I_{CBO} \}$

$$\Rightarrow I_C R_E \uparrow$$

\uparrow as $I_C \uparrow$

$$\Rightarrow I_B \downarrow \Rightarrow I_C \downarrow$$

ii) β changes, I_C changes.

$$I_C = \frac{\beta(V_{CC} - V_{BE})}{R_B + (\beta + 1)R_E} \quad [\beta + 1 \approx \beta]$$

$$= \frac{\beta(V_{CC} - V_{BE})}{R_B + \beta R_E} \quad [\beta R_E \gg R_B]$$

$$= \frac{\beta(V_{CC} - V_{BE})}{\beta R_E}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_E}$$


independent of β .

Ex:


① For emitter-bias config., determine:

(a) R_C

(b) R_E

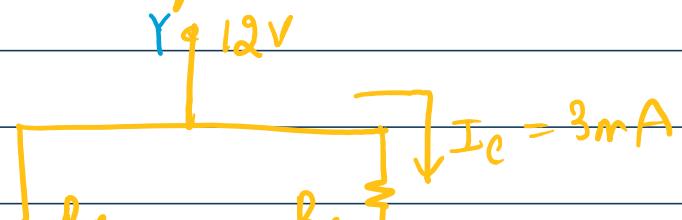

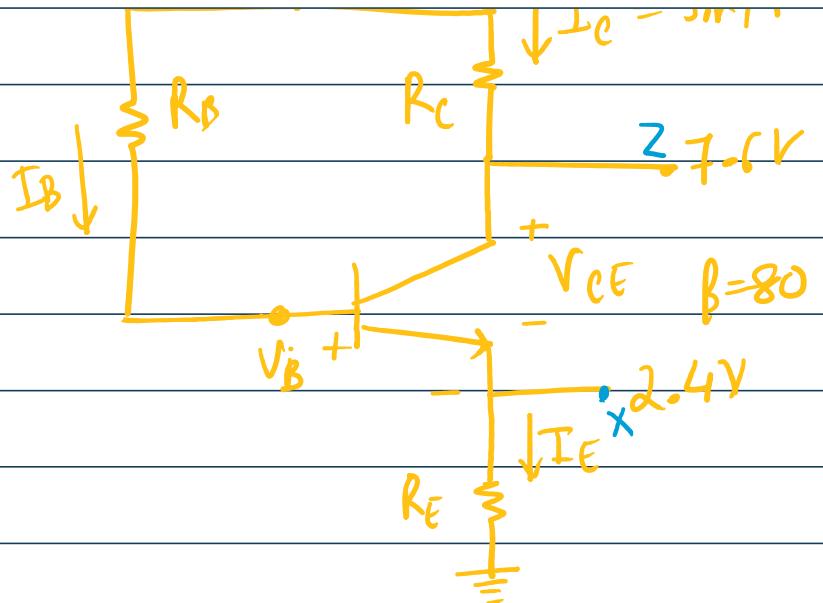- (b) R_E
- (c) R_B
- (d) V_{CE}
- (e) V_B



Sol: we have, $V_{CC} = 12V$ $V_{BE} = 0.7V$
 $I_C = 3mA$
 $\beta = 80$
 $V_C = 7.6V$
 $V_E = 2.4V$

$$\rightarrow V_{CE} = V_C - V_E = 7.6 - 2.4$$

$$V_{CE} = 5.2V \quad (d)$$



$$\rightarrow V_{BE} = V_B - V_E$$

$$0.7 = V_B - 2.4$$

$$V_B = 3.1V \quad (e)$$



$$\rightarrow KVL, \text{ (in i/p loop)}$$

$$V_{CL} - I_B R_B = V_B$$

$$I_C = \beta I_B$$

$$R_B = \frac{V_{CC} - V_B}{I_B}$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{3m}{80}$$

$$= \frac{12 - 3.1}{37.5M}$$

$$I_B = 37.5 \mu A$$

$$= \frac{8.9}{37.5} \times 10^6$$

$$R_B = 237.33 k\Omega (c)$$

→ KVL, (from X → ground)

$$24 - I_E R_E = 0$$

$$I_E = I_C$$

$$R_E = \frac{2.4}{I_C}$$

$$= \frac{2.4}{3m}$$

$$R_E = 0.8 k\Omega (b)$$

→ KVL, (from Y to Z)

$$12 - I_O R_C = 7.6$$



$$R_C = \frac{12 - 7.6}{I_C}$$
$$= \frac{4.4}{3m}$$

$$R_C = 1.4667 k\Omega$$

Voltage Divider Bias

28 October 2024 01:24 AM

Voltage Divider Bias

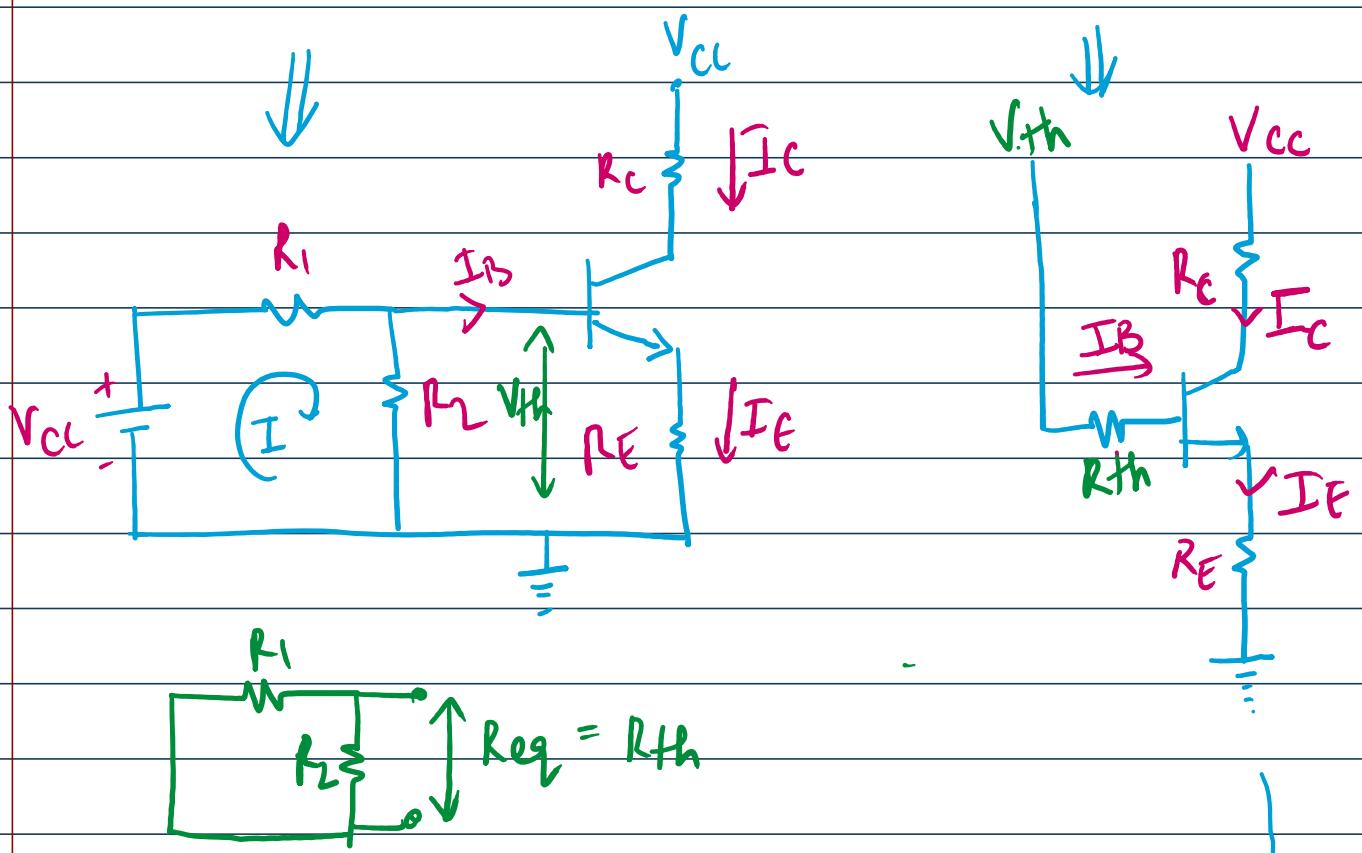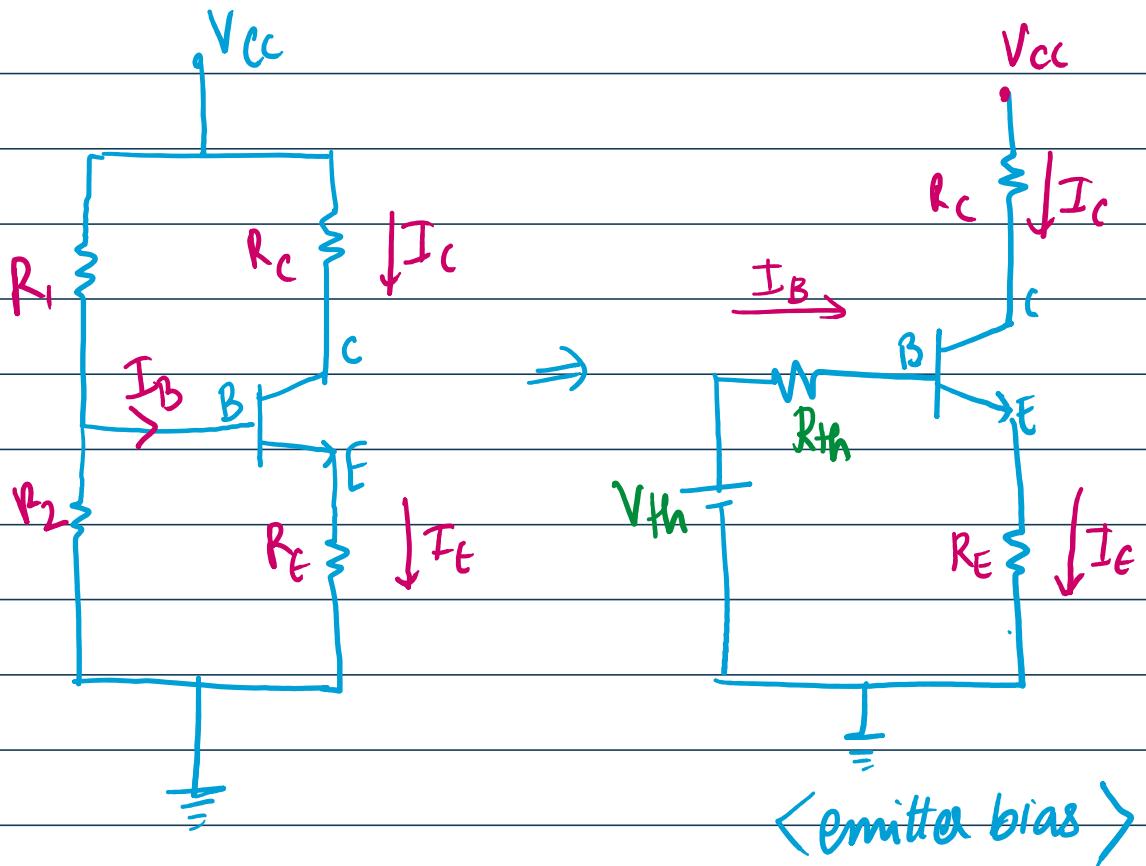

$$I_{BQ} \downarrow \quad \dots$$

$$R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V_{cc}}{R_1 + R_2}$$

$$V_{th} = IR_2 = \frac{R_2 V_{cc}}{R_1 + R_2}$$

$$\rightarrow V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \frac{\beta (V_{th} - V_{BE})}{R_{th} + (\beta + 1) R_E}$$

If $R_{th} \ll (\beta + 1) R_E$
then I_C is independent of β .

• Then I_C is independent of β .


$$\rightarrow V_{CC} - I_C R_C - \underline{V_{CE}} - \overbrace{I_C R_E}^{I_C} = 0$$

$$\boxed{V_{CE} = V_{CC} - I_C (R_C + R_E)}$$

ex:

① For the voltage divider bias, determine -

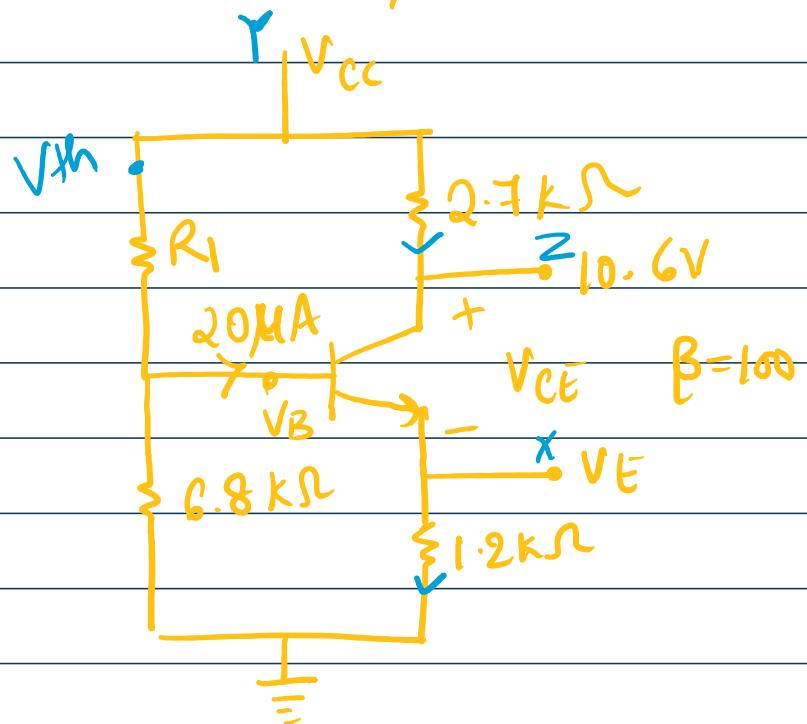- (a) I_C
- (b) V_E
- (c) V_{CE}
- (d) V_{CE}
- (e) V_B
- (f) R_1



Ans: We have, $R_C = 2.7 \Omega$

$$V_C = 10.6 V$$

$$\beta = 100$$

$$R_E = 1.2 k\Omega$$

$$R_2 = 6.8 k\Omega$$

$$R_2 = 6.8k\Omega$$

$$I_B = 20\mu A$$

$$\rightarrow I_C = \beta I_B \\ = 100 \times 20\mu \\ I_C = 2mA \quad (\text{a})$$

\rightarrow KVL, (from X to ground)

$$V_E - I_E R_E = 0$$

$$I_F = I_C + I_B$$

$$= 2m + 20\mu$$

$$V_E = I_E R_E \\ = (2.02m) (1.2k)$$

$$= 2 \times 10^{-3} (1 + 10 \times 10^{-3}) \\ = 2 \times 10^{-3} \times (1.01)$$

$$V_E = 2.424 \quad (\text{b})$$

$$I_F = 2.02mA$$

$$\rightarrow V_{CE} = V_C - V_E \\ = 10.6 - 2.424$$

$$V_{CE} = 8.176V \quad (\text{d})$$

\rightarrow KVL, (from Y to Z)

$$V_{CC} - I_C R_C = V_C$$

$$V_{CC} - (2m)(2.7k) = 10.6$$

$$V_{CC} = 10.6 + 5.4$$

$$V_{CC} = 10.6 + 5.4$$
$$\underline{V_{CC} = 16V \text{ (c)}}$$

$$\rightarrow V_{BE} = V_B - V_E$$
$$0.7 = V_B - 2.424$$
$$\underline{V_B = 3.1240V \text{ (e)}}$$

$$\rightarrow V_{th} \approx V_B$$

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$3.124 = \frac{16 \times 6.8k}{R_1 + 6.8k}$$

$$R_1 + 6.8k = \frac{108.8k}{3.124}$$

$$R_1 + 6.8k = 34.8271k$$
$$\underline{R_1 \approx 28.0271k \Omega \text{ (f)}}$$

Thermal runaway

30 October 2024 05:43 PM

Thermal runaway in Transistors

$$\rightarrow I_c = \beta I_B + (\beta + 1) I_{CBO}$$

I_{CBO} cause → flow of minority charge carriers (MCC)


$T \uparrow \Rightarrow$ conc of MCC $\uparrow \Rightarrow I_{CBO} \uparrow \Rightarrow I_c \uparrow$

$$I_c \propto \text{Temp.}$$

\rightarrow With every 20° rise in temp,
 I_{CBO} doubles

\rightarrow flow of $I_c \rightarrow$ produces heat
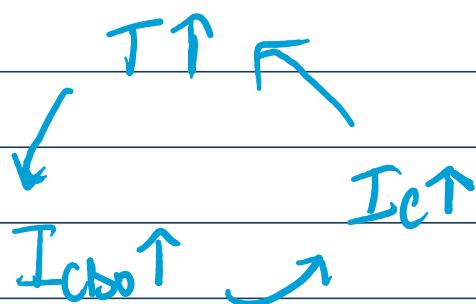
$$\downarrow \\ T \uparrow \Rightarrow I_c \uparrow$$



I_{CBO} ↑

→ Because of the cumulative process, in few seconds collector current will become large enough to burn the transistor.

→ Definition of thermal runaway:

The self destruction of unstabilized transistor.

→ mitigation of thermal runaway.

→ introduction of Negative feedback.

$$I_C \uparrow \Rightarrow I_B \downarrow \Rightarrow I_C \downarrow \\ (\text{presence of } I_E)$$

→ Heat sinks → dissipation of heat

Bias stabilization

30 October 2024 06:15 PM

Bias Stabilization and Stability factors.

→ Stabilization:

$$\alpha - \beta t (V_{CB}, I_c)$$

The process of making OP ($\alpha - \beta t$) independent of temperature changes and variations in transistor parameters.

→ Causes of unstabilization:

$\alpha - \beta t$ will shift $\rightarrow I_T \downarrow$

w/ change in $\frac{\beta}{I}$


when transistor change, β changes

ii) change in $T \rightarrow T \uparrow \Rightarrow I_{CBO} \uparrow \Rightarrow I_c \uparrow$

[$10^\circ C \uparrow$, I_{CBO} doubles.]

[$1^\circ C \uparrow$, $V_{BE} \downarrow$ by 2.5 mV]

$$\frac{i_p I}{I_B} \rightarrow V_{BE}$$

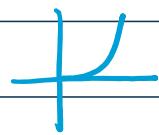

→ Stability factor:

The ratio of change of collector current w.r.t the leakage current (I_{CBO}) at constant i/p v and amp. factor

(V_{BE})

(β)

$$S = \left| \frac{\partial I_C}{\partial I_{CBO}} \right| \text{ at const } V_{BE} \text{ & } \beta .$$


$$S' = \left| \frac{\partial I_C}{\partial V_{BE}} \right| \text{ at const } I_{CBO} \text{ & } \beta$$

$$S'' = \left| \frac{\partial I_C}{\partial \beta} \right| \text{ at const } I_{CBO} \text{ & } V_{BE}$$

Stability factor (FBC)

30 October 2024 06:26 PM

Stability Factor for fixed Bias config.

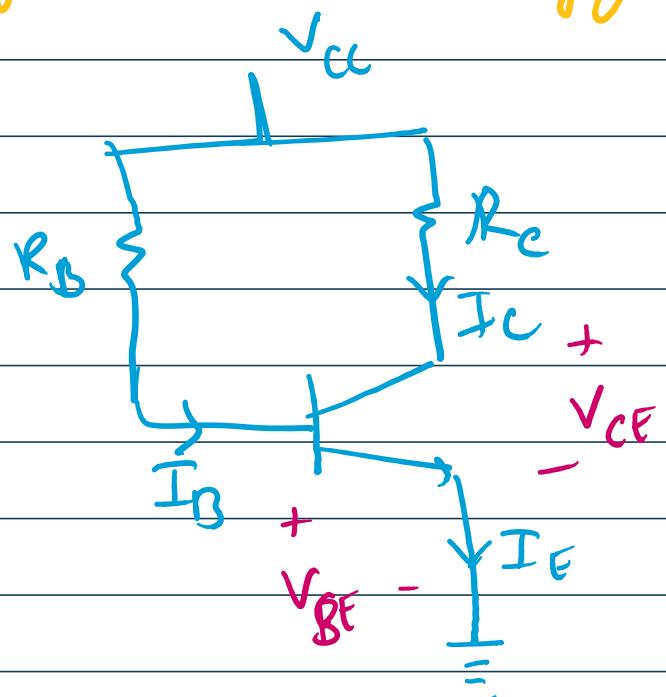

Step 1: KVL in i/p loop.

$$V_{ce} - I_B R_B - V_{BE} = 0$$

$$\bar{I}_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Step 2: $I_C = \beta \bar{I}_B + (\beta + 1) I_{CB0} \rightarrow ①$

$$I_C = \beta \frac{(V_{CC} - V_{BE})}{R_B} + (\beta + 1) I_{CB0} \rightarrow ②$$

diff ② w.r.t I_C .

$$S = \frac{\partial I_C}{\partial I_{CBO}} \quad \text{at const } V_{BE} \& \beta$$

Step 3 :

$$\frac{\partial I_C}{\partial I_C} = \frac{\beta}{R_B} \frac{d}{dI_C} (V_{CC} - V_{BE}) + (\beta+1) \frac{dI_{CBO}}{dI_C}$$

$$1 = (\beta+1) \left(\frac{1}{S} \right)$$

$S = \beta+1$

→ General exp of S-F-

diff ① w.r.t I_B

$$\frac{\partial I_C}{\partial I_C} = \beta \frac{\partial I_B}{\partial I_C} + (\beta+1) \frac{\partial I_{CBO}}{\partial I_C}$$

$$1 = \beta \frac{dI_B}{dI_C} + \frac{\beta+1}{S}$$

$$S = \frac{(\beta+1)}{\left(1 - \beta \frac{dI_B}{dI_C}\right)}$$

$$S = \frac{\beta+1}{1-0} = \beta+1$$

$$\star S = \frac{dI_C}{dI_{CBO}} \quad | \quad V_{BE} \& \beta$$


$$\delta^l = \frac{dI_C}{dV_{BE}} \quad | \quad I_{CBO} \& \beta$$

$$\delta^{ll} = \frac{dI_C}{d\beta} \quad | \quad I_{CBO} \& V_{BE}$$

Stability factor (EBC)

30 October 2024 06:43 PM

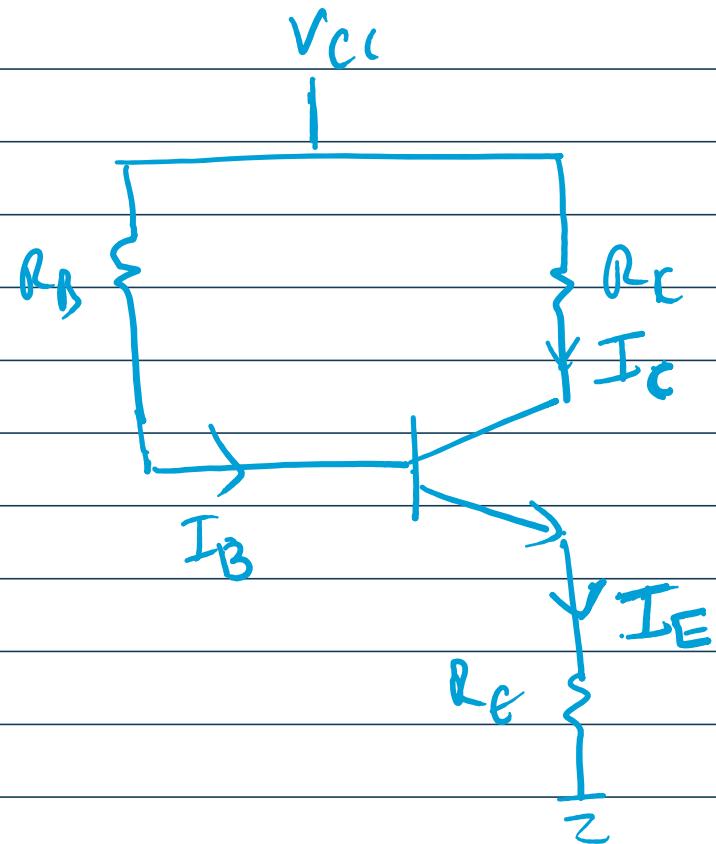Stability factor for Emitter Bias config.



S1.

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = I_C + I_B$$

$$V_{CC} - I_B R_B - V_{BE} - I_C R_E - I_B R_E = 0$$

$$V_{CC} - I_B (R_B + R_E) - V_{BE} - I_C R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE} - I_C R_E}{R_B + R_E} \rightarrow ①$$

$$R_B + R_E$$

$$S-2: I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$I_C = \beta \frac{(V_{CC} - V_{BE} - I_{CBO})}{R_B + R_E} + (\beta + 1) I_{CBO}$$

→ ②

diff ② w.r.t. I_C

$$\frac{dI_C}{dI_C} = \frac{\beta}{R_B + R_E} \cdot \frac{d(V_{CC} - V_{BE} - I_{CBO})}{dI_C}$$

$$+ (\beta + 1) \frac{dI_{CBO}}{dI_C}$$

$$1 = \frac{\beta}{R_B + R_E} [0 - 0 - I_C(1)] + \frac{\beta + 1}{S}$$

$$1 = -\frac{\beta R_E}{R_B + R_E} + \frac{\beta + 1}{S}$$

$$S = \frac{\beta + 1}{1 + \frac{\beta R_E}{R_B + R_E}}$$


$$S = \frac{(\beta + 1)(R_B + R_E)}{\dots}$$

$$Y = \frac{(\beta + 1)(k_B T_N)}{R_B + (\beta + 1)R_E}$$

$$S = \frac{\beta + 1}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

(Gen. expression)

S-F for Voltage divider Bias.

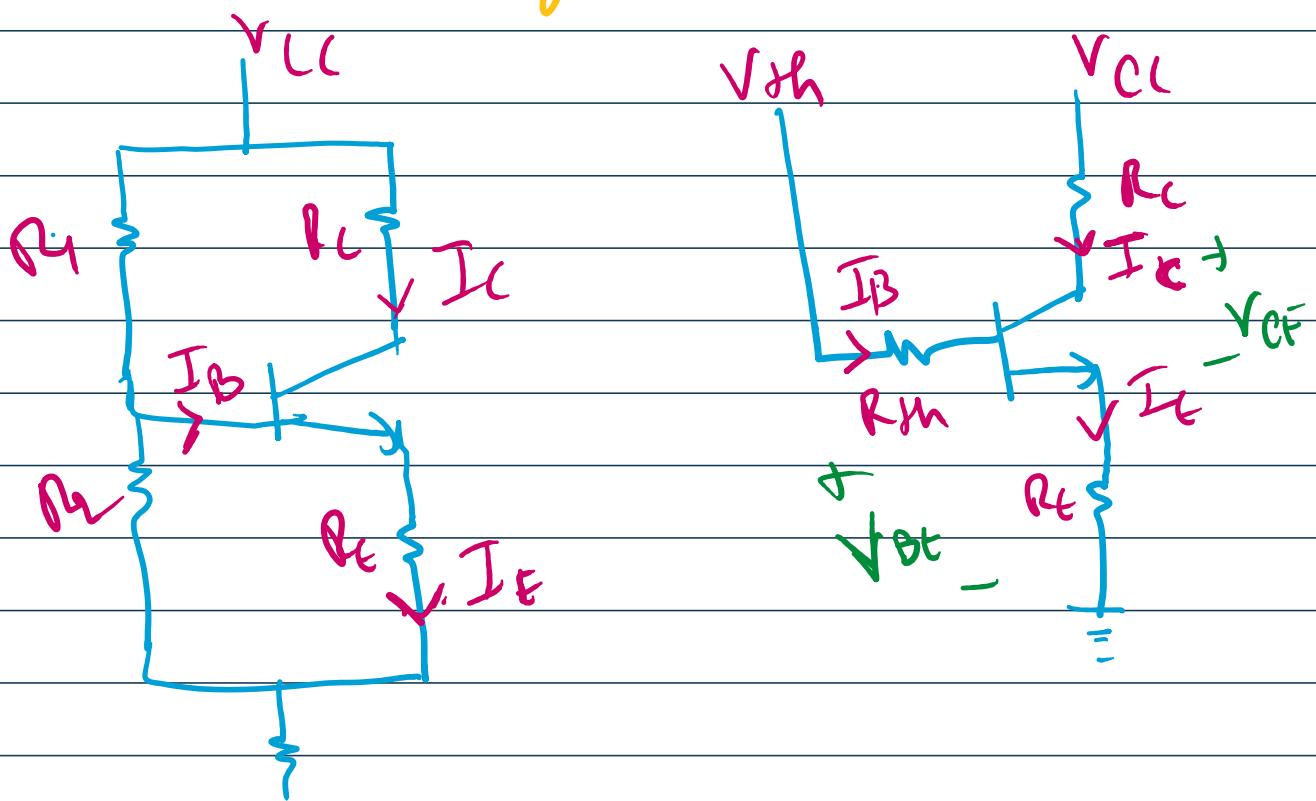

$$V_{th} = \frac{R_2 V_{cc}}{R_1 + R_2}$$

$$R_{th} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

S1: KVL in 4P $\rightarrow I_B = 1$

S2: $I_C = \beta I_B + (\beta + 1) I_{CBO}$

S3: diff w.r.t I_C keeping β & V_{BE} const

$$S = \frac{(\beta+1)(R_{th} + R_E)}{R_{th} + (\beta+1)R_E}$$

$s(I_{C35})$

$$S = \frac{(\beta+1)(R_B + R_E)}{R_B + (\beta+1)R_E}$$

↓
↑
changed term from CE.

$$\delta' = \frac{-\beta}{R_{th} + (\beta+1)R_E}$$


$$\delta' = \frac{-\beta}{R_B + (\beta+1)R_E}$$

$s(v_{BE})$

Small signal analysis of bjt

30 October 2024 07:07 PM

Small signal analysis of BJT :

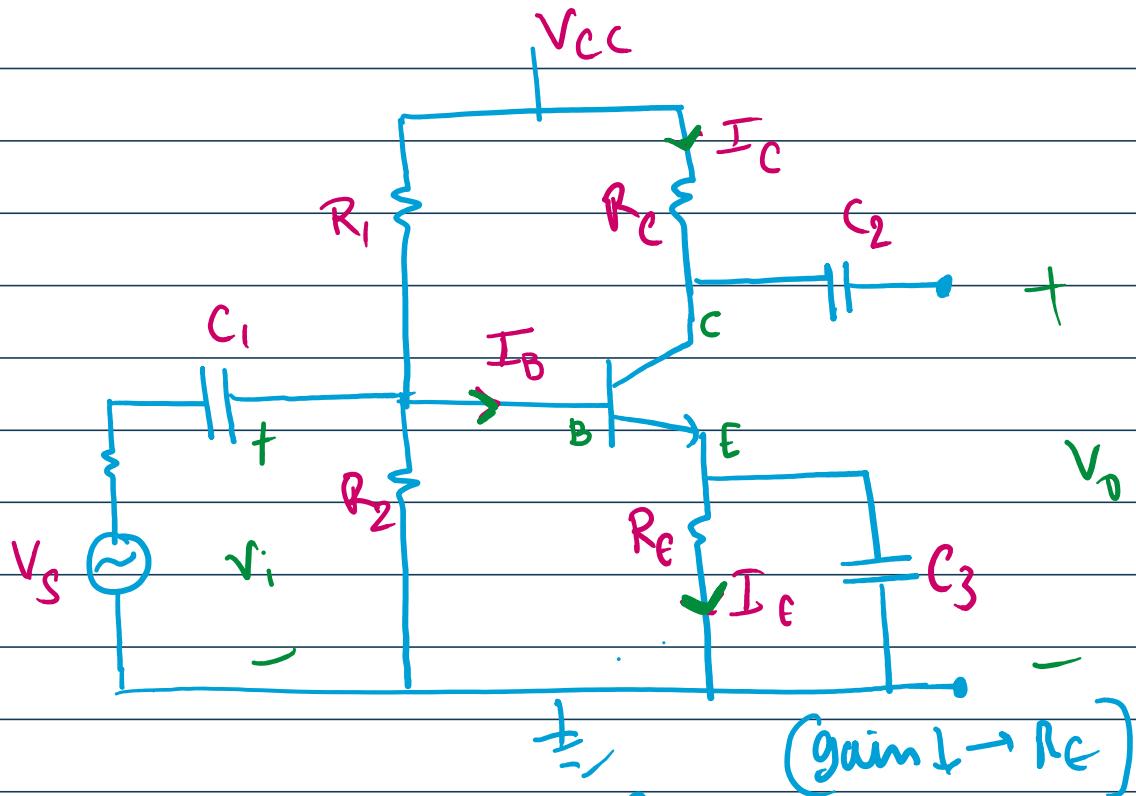

$C_1 \& C_2 \rightarrow$ coupling capacitors

$C_3 \rightarrow$ bypass capacitors

$$X_C = \frac{1}{2\pi f C}$$


dc signal $\Rightarrow f=0 \Rightarrow X_C=\infty$.
open circuit

ac signal $\Rightarrow f \neq 0, C \uparrow \uparrow \Rightarrow X_C \approx 0$


AC response:

AC Equivalent circuit of BJT Amplifier


S1: Short circuit all the dc sources.



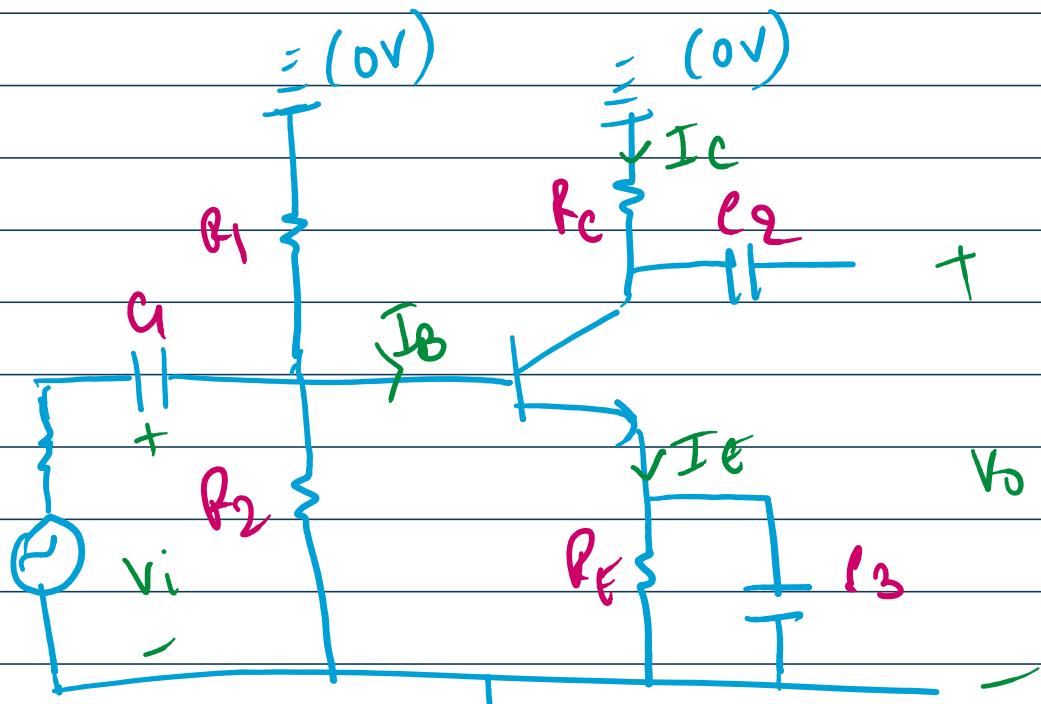


Sq.: Short all capacitors.

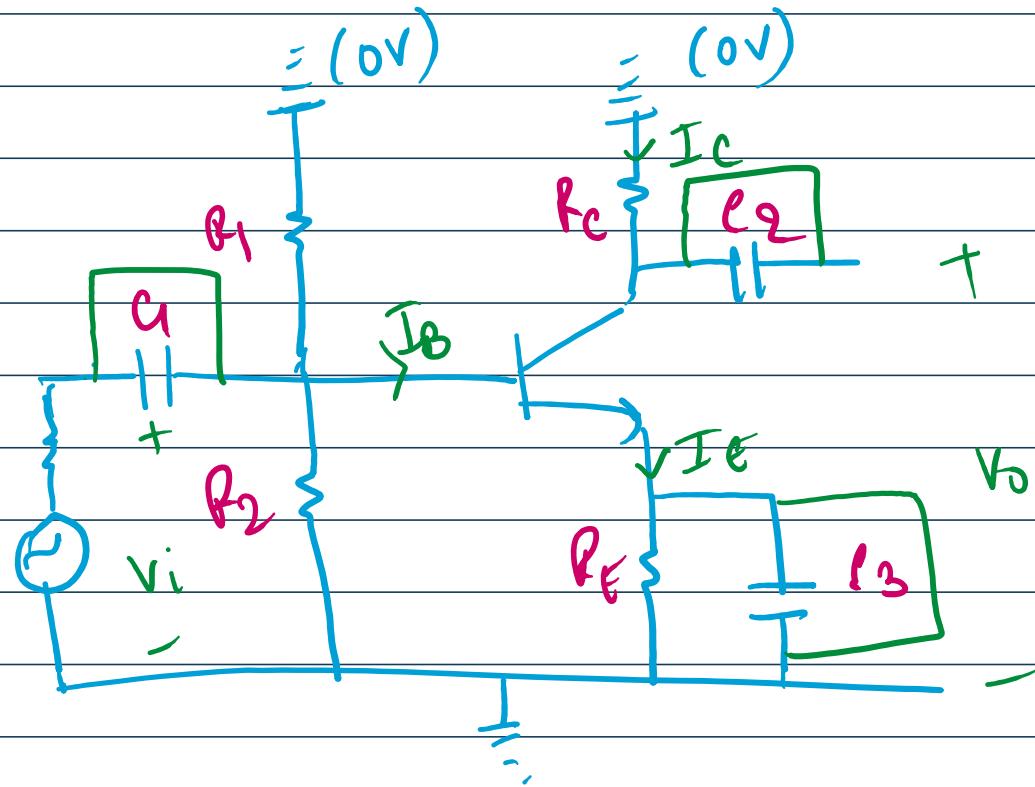

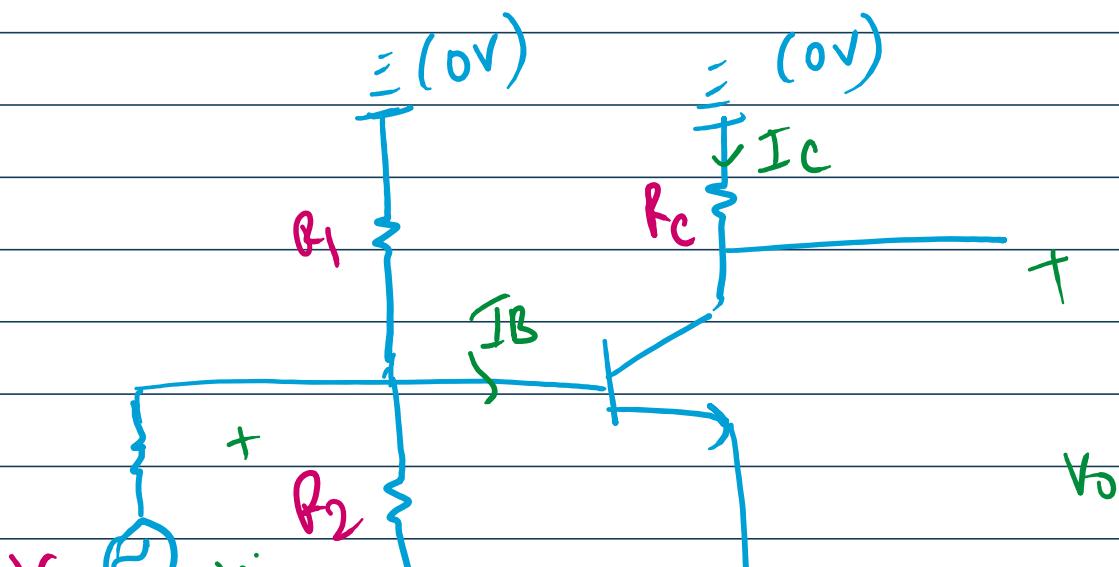S3: Redraw the network removing all the elements which are short circuited in S1 & S2



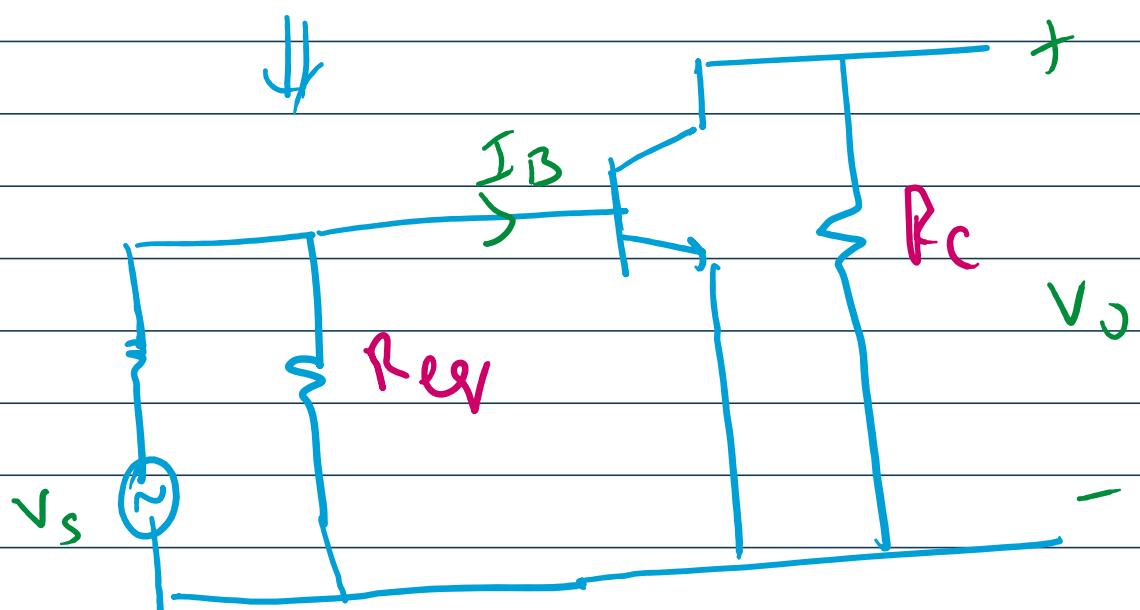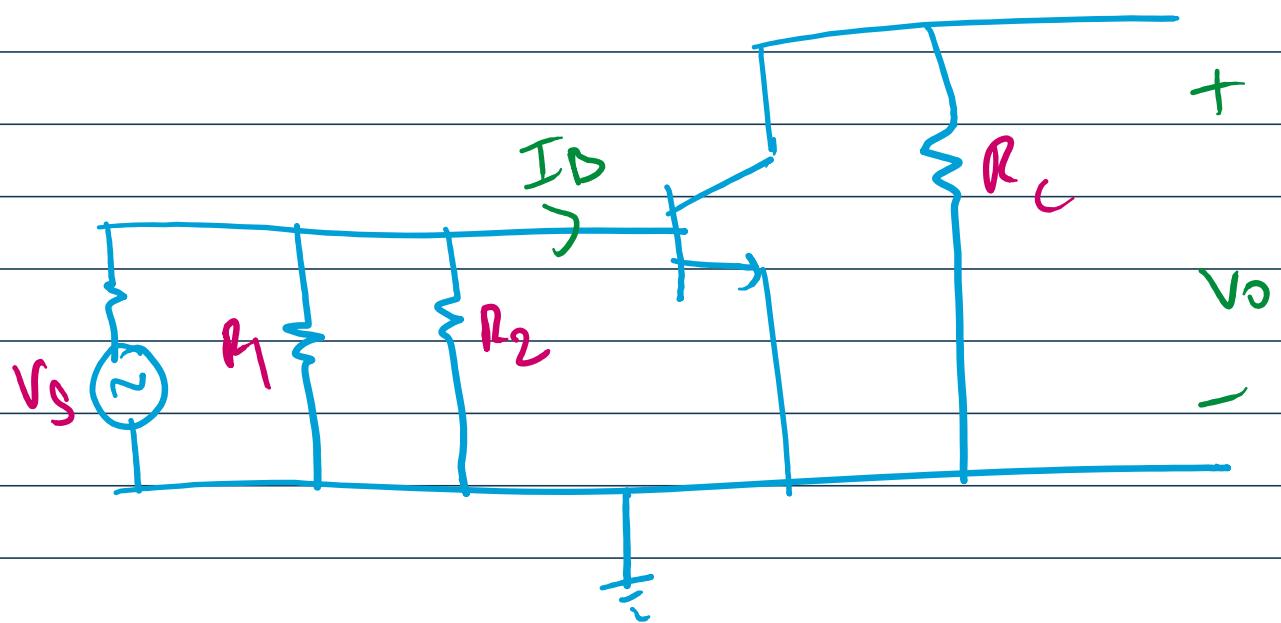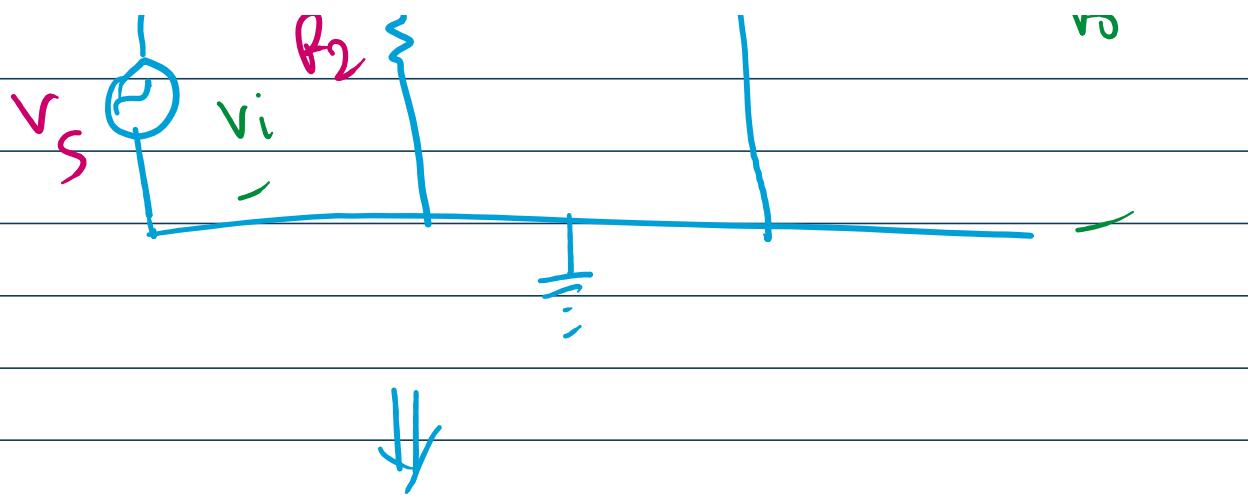


$$R_{\text{in}} = R_1 \parallel R_2$$

→ What is an eq model?




An equivalent model is combination of circuit elements properly chosen to best represent the actual behaviour of device under specific operating point


Re Transistor model.

(T-model)

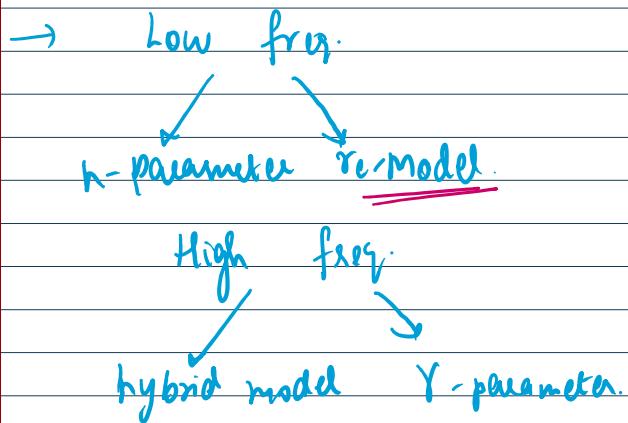


→ CE-trans.

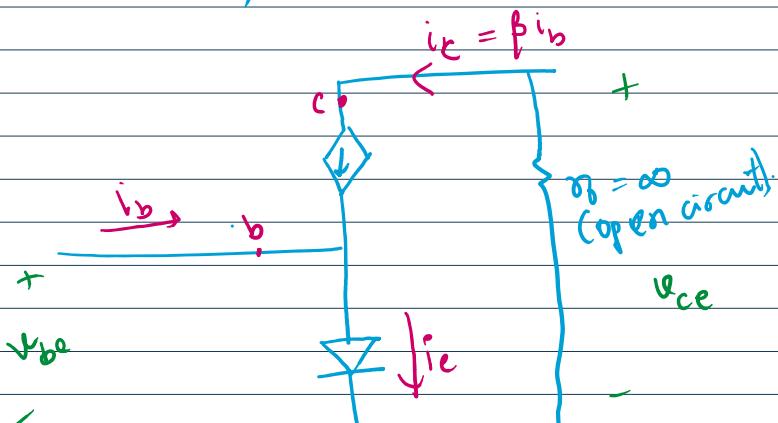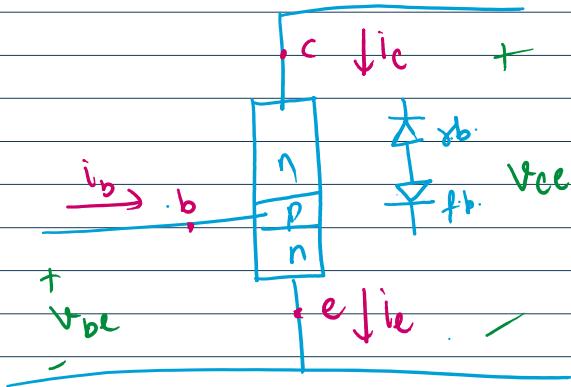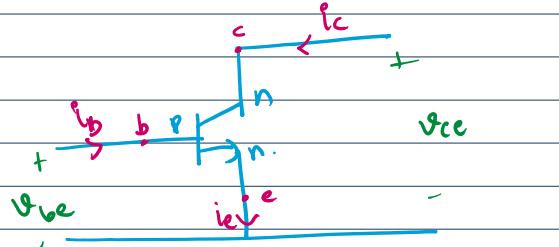


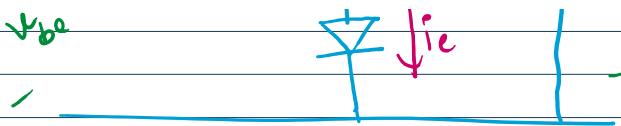
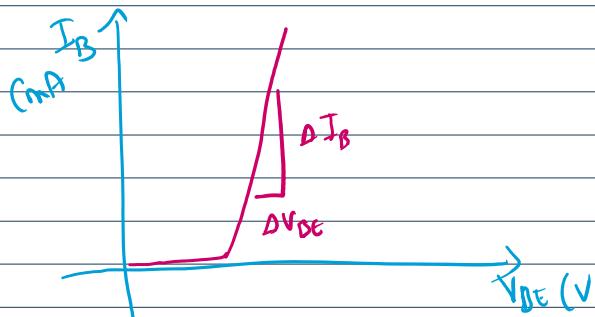
$$r_o = \frac{1}{\text{slope}} \approx 0 \Rightarrow r_o \approx \infty$$


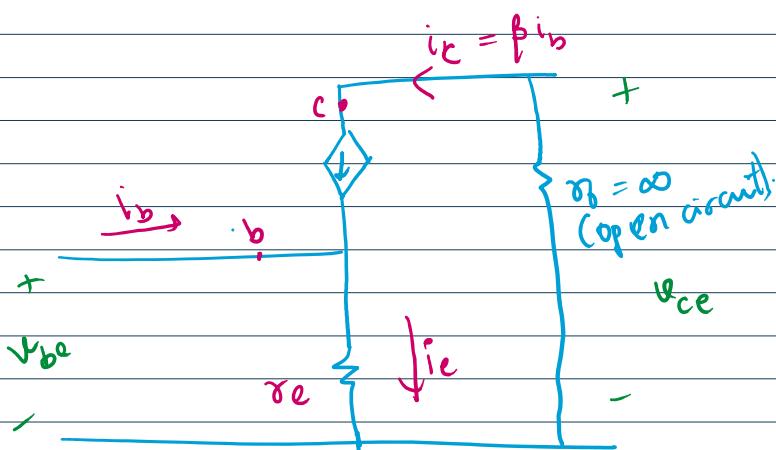
$$r_d = \frac{\Delta V_{BE}}{\Delta I_B} \quad r_d \rightarrow r_o$$



$$\tau_s \cdot C = I_S$$

$$I_D = I_S (e^{\frac{V_D}{nV_T}} - 1)$$

$$\frac{dI_D}{dV_D} = I_S \frac{d}{dV_D} (e^{\frac{V_D}{nV_T}} - 1)$$

$\eta = 1$
when $I_D \uparrow$.

$$T = 300 \text{ K}$$

$$\frac{1}{r_d} = \frac{I_S e^{\frac{V_D}{nV_T}}}{V_D}$$

$$\frac{1}{r_d} = \frac{I_S e \sqrt{V_T}}{V_T}$$



$$\frac{1}{r_d} = \frac{I_D - I_S}{V_T}$$

$$\frac{1}{r_d} = \frac{I_D}{V_T}$$

$$r_d = \frac{V_T}{V_0}$$

$$r_d = \frac{26 \text{ mV}}{I_D}$$

$$r_e = \frac{26 \text{ mV}}{I_E}$$

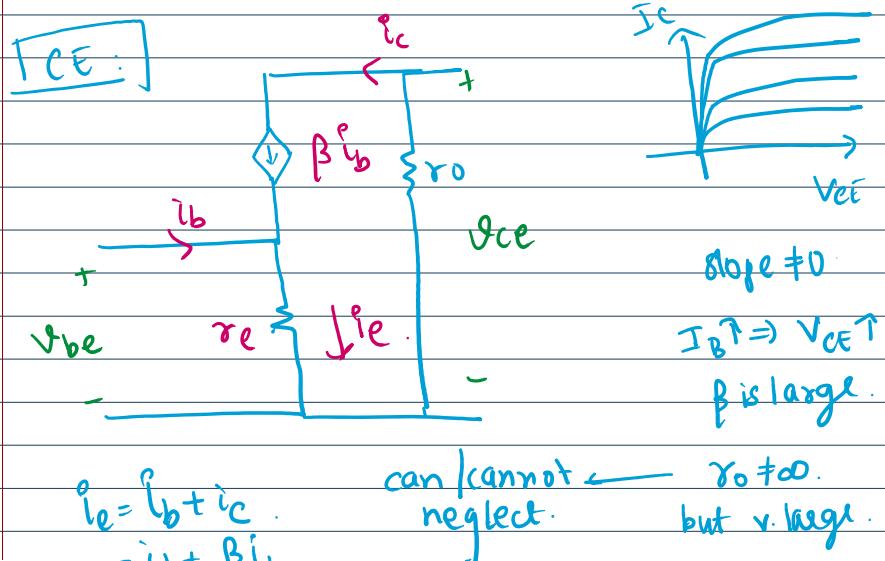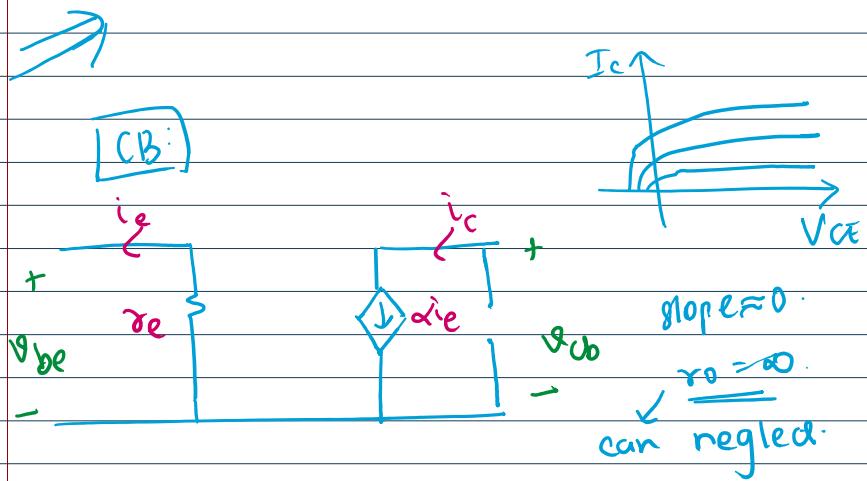

$$i_e = i_b + i_c$$


$$= i_b + \beta i_b$$

$$i_e = (1 + \beta) i_b$$

can/cannot ← $r_o \neq \infty$.
neglect. but v. large.

→ drop across $r_e = r_e \cdot i_e$

$$= r_e (\beta + 1) i_b$$


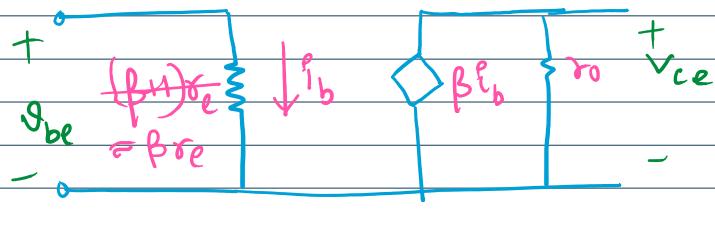




$$\beta + 1 \approx \beta$$

Re model (FBC)

31 October 2024 10:45 AM

Re Model (Fixed Bias config)

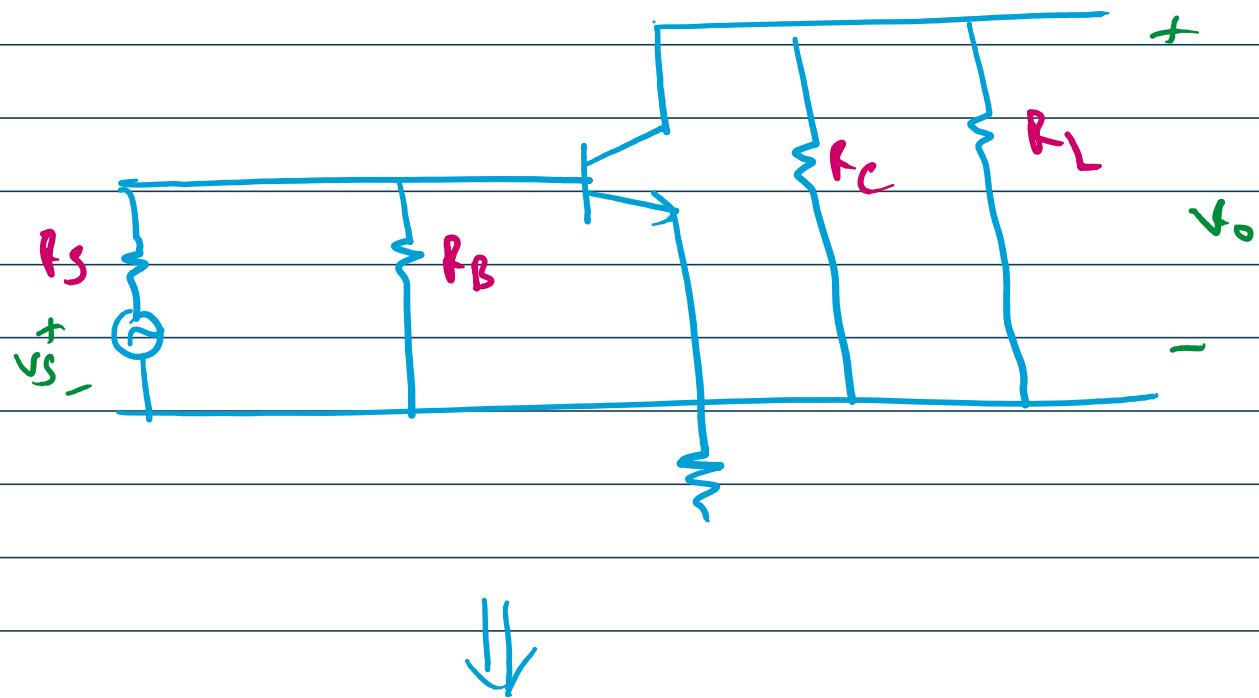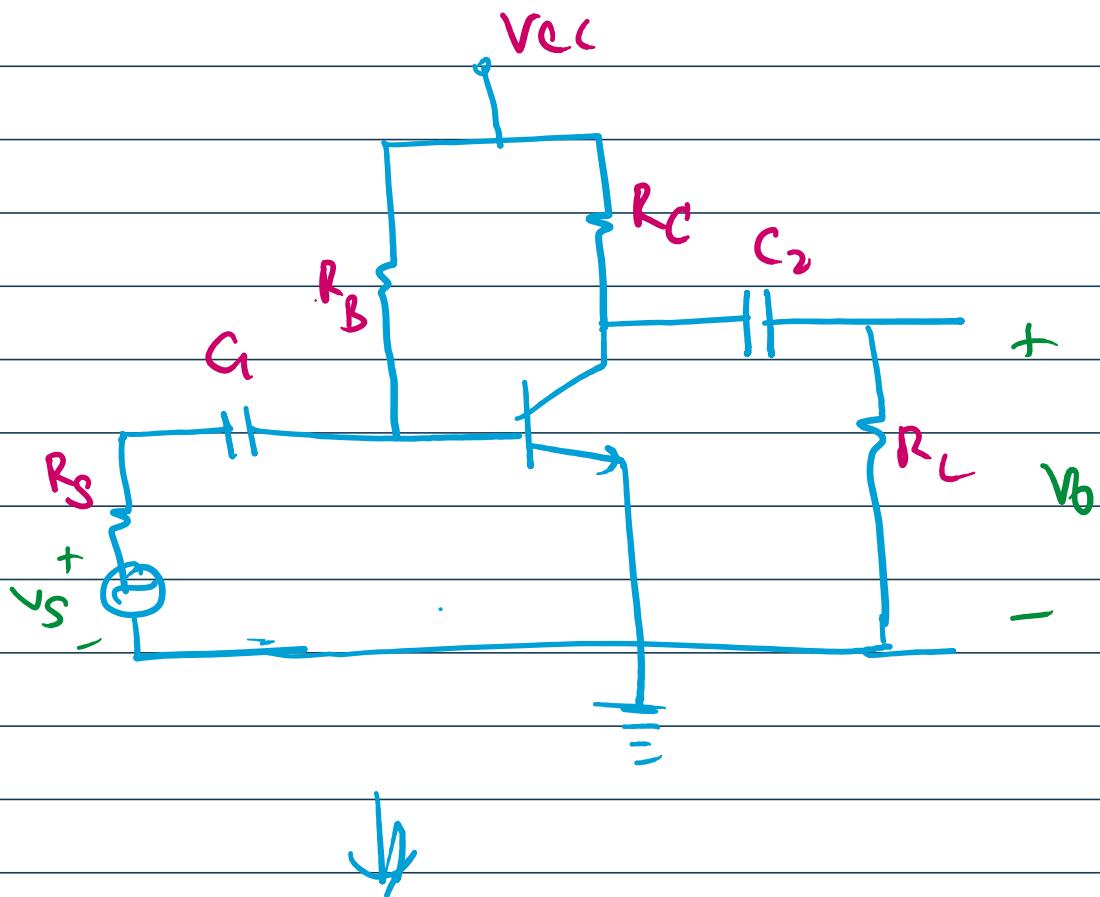

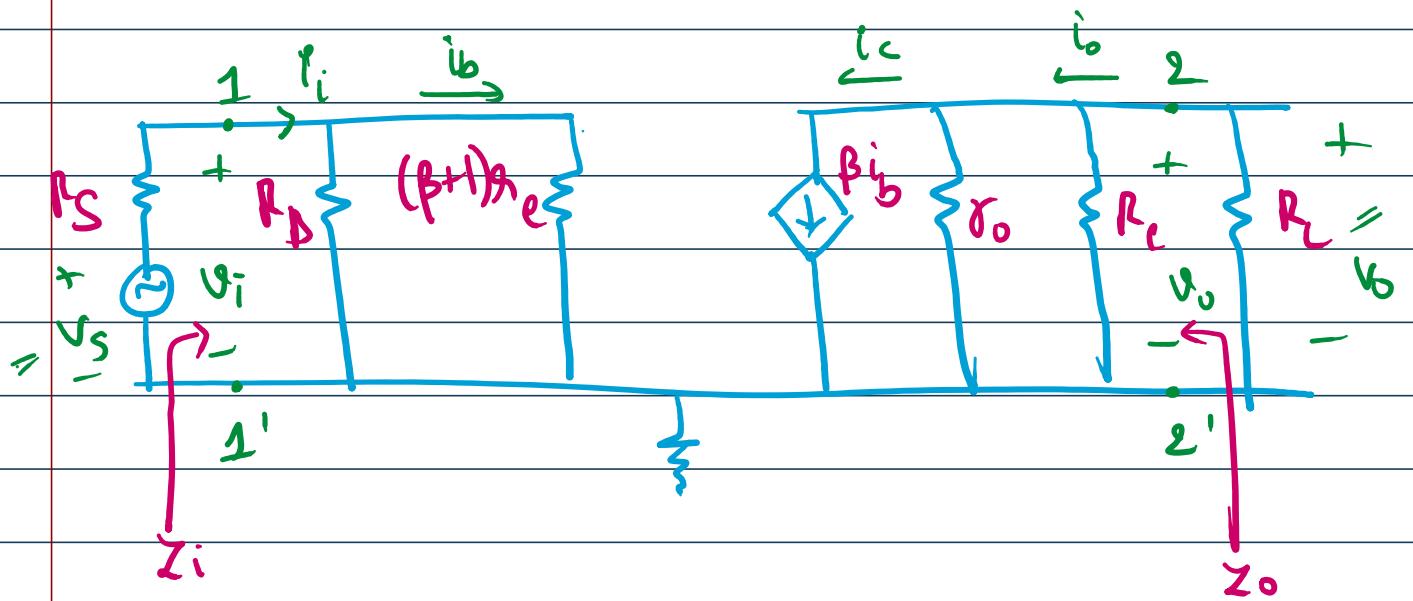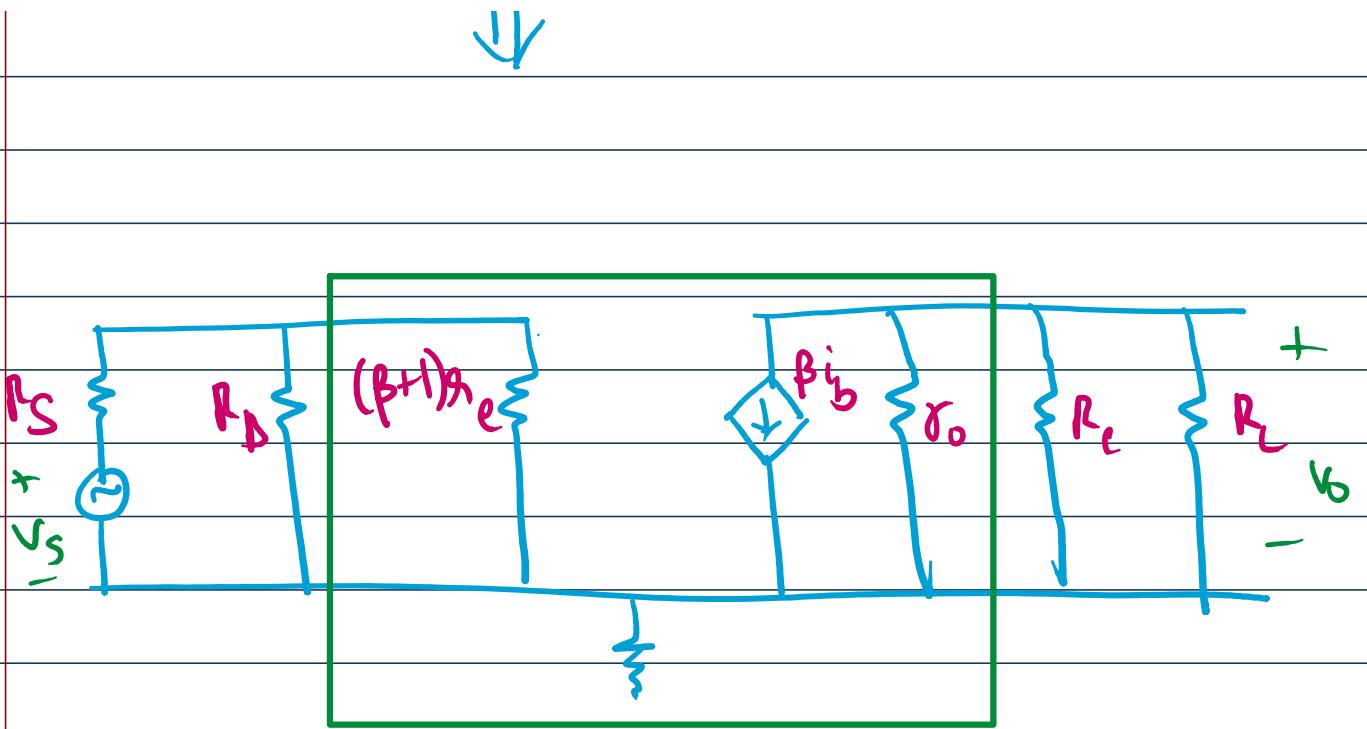

→ input impedance.

$$Z_i = \frac{v_i}{i_b}$$

$$Z_i = R_B \parallel (\beta + 1)R_F$$

$$Z_i = \frac{R_B (\beta+1) r_e}{R_B + (\beta+1) r_e}$$

Alley: $Z_i = \frac{(\beta+1) r_e \cdot i_b}{i_i} \leftarrow v_i$

current divider rule \rightarrow

$$Z_i = \frac{(\beta+1) r_e \frac{i_b R_B}{i_i}}{R_B + (\beta+1) r_e}$$


$$Z_i = \frac{(\beta+1) r_e R_B}{R_B + (\beta+1) r_e}$$


\rightarrow output impedance .

$$Z_o = \frac{v_o}{i_o}$$

$$V_g = 0V \Rightarrow V_i = 0V \Rightarrow i_b = 0A \Rightarrow i_c = 0A$$

$$R_L = \infty \Omega$$

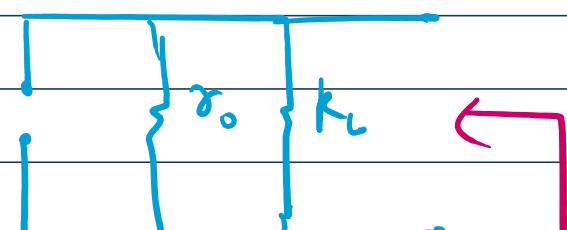

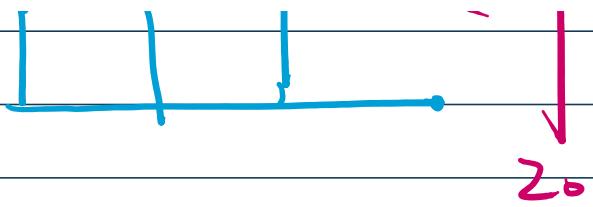

$$Z_0 = \gamma_0 \parallel R_C$$

$$Z_0 = \frac{\gamma_0 \cdot R_C}{\gamma_0 + R_C}$$

$$\rightarrow \beta + 1 \approx \beta$$

$$(\beta + 1) r_e \approx \beta r_e$$

$$R_B \geq 10 \underbrace{(\beta + 1) r_e}_{\text{neg.}}$$

$$Z_i = \frac{R_B (\beta + 1) r_e}{R_B}$$

$$Z_i = (\beta + 1) r_e$$


when $R_B \geq 10(\beta + 1)r_e$.

$$\rightarrow \gamma_0 \geq 10 R_C$$

$$Z_0 = \frac{\gamma_0 \cdot R_C}{\gamma_0 + R_C}$$

δ_0

$Z_0 = R_C$
when $\delta_0 \geq 10R_C$

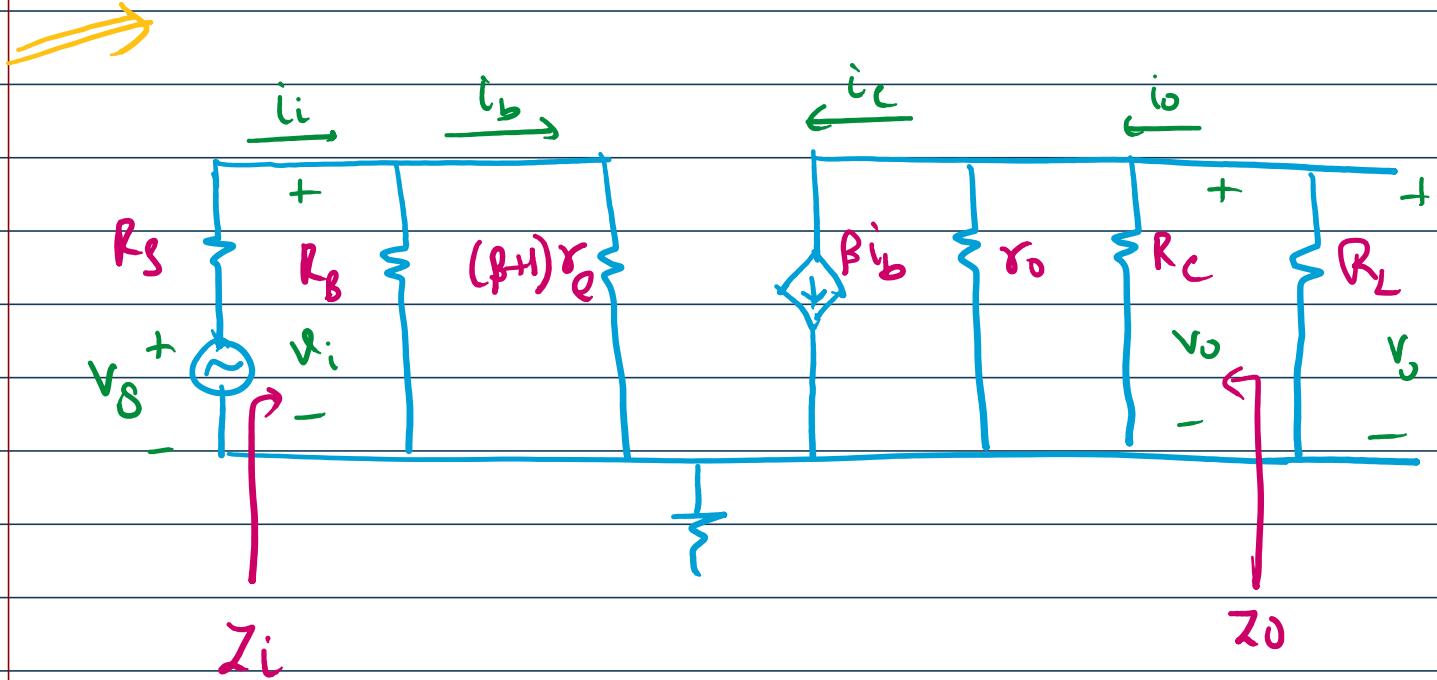

$$Z_i = R_B \parallel (\beta + 1) r_e$$

$$Z_0 = r_o \parallel R_C$$

$$\text{if } R_B \geq 10(\beta + 1)r_e$$

$$Z_i = (\beta + 1)r_e$$


$$\text{if } r_o \geq 10R_C$$

$$Z_0 = R_L$$

\Rightarrow Current Gain:


$$A_i = \frac{i_o}{i_i}$$

→ Current divider rule: (CDR)

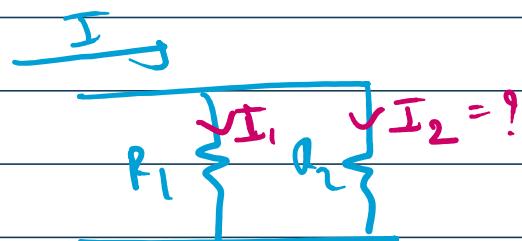

$$I_2 = \frac{IR_1}{R_1 + R_L}$$

$$I_1 = \frac{IR_L}{R_1 + R_L}$$

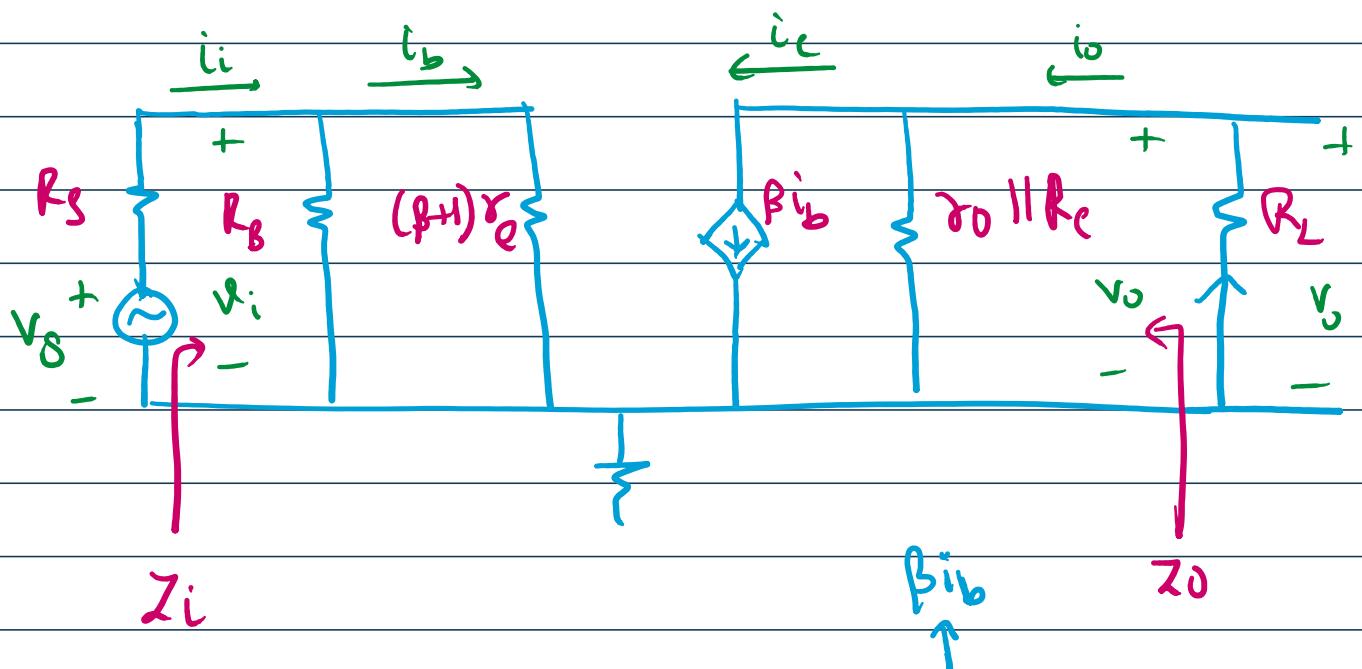

using CDR,

$$i_b = \frac{i_c (\gamma_o || R_C)}{\gamma_o || R_C + R_L}$$

$$A_i = \frac{\gamma_o}{i_i} = \frac{\beta i_b (\gamma_o || R_C)}{\gamma_o || R_C + R_L}$$

$$i_b^o = \frac{r_i R_B}{R_B + (\beta+1)r_e}$$

r_i

$$A_i = \frac{\beta \left(\frac{r_i R_B}{R_B + (\beta+1)r_e} \right) \left(\frac{r_o || R_C}{r_o || R_C + R_L} \right)}{x}$$

$$A_i = \beta \left(\frac{R_B}{R_B + (\beta+1)r_e} \right) \left(\frac{r_o || R_C}{r_o || R_C + R_L} \right)$$

Case 1: $r_o \geq 10 R_C$

$$r_o || R_C = R_C$$

$$A_i = \beta \left(\frac{R_C}{R_B + (\beta+1)r_e} \right) \left(\frac{R_C}{R_C + R_L} \right)$$

Case 2: $R_B \& R_C = \infty$

$$r_o < R_C \Rightarrow r_o || R_C = r_o$$

$$A_i = \beta \left(\frac{R_B}{r_B} \right) \left(\frac{r_o}{r_o + R_L} \right)$$

$$A_i = \beta \left(\frac{r_o}{r_o + R_L} \right)$$

→ Overall current gain: (A_{is})

$$A_{is} = \frac{i_o}{i_s} = A_i \left(\frac{r_o}{r_o + Z_C} \right)$$

→ Voltage Gain: (A_V)

$$A_V = \frac{V_o}{V_i}$$

$$V_o = -i_o R_L \quad [-i_o R_L - V_s = 0]$$

$$V_o = -\beta i_b \left(\frac{r_o || R_C}{r_o || R_C + R_L} \right) R_L$$

$$V_i = i_b (\beta + 1) r_e .$$

$$\rightarrow A_v = -\frac{\beta (\gamma_0 || R_C || R_L)}{(\beta + 1) g_e}$$

(i) $\beta + 1 \approx \beta$

$$\rightarrow A_v = -\frac{(\gamma_0 || R_C || R_L)}{g_e}$$

ii) $\gamma_0 \gg 10R_C$

\downarrow negligible

$$\rightarrow A_v = -\frac{R_C || R_L}{g_e}$$

iii) $R_L = \infty \gg R_C$

$$\rightarrow A_v = -\frac{R_C}{g_e}$$

Overall Voltage Gain (A_{vS})


$$A_{vS} = \frac{V_o}{V_S}$$

$$A_{vS} = \frac{V_o}{V_S}$$

$$A_{vS} = A_v \left(\frac{Z_i}{Z_i + R_S} \right)$$

Note: -ve sign in the above formula

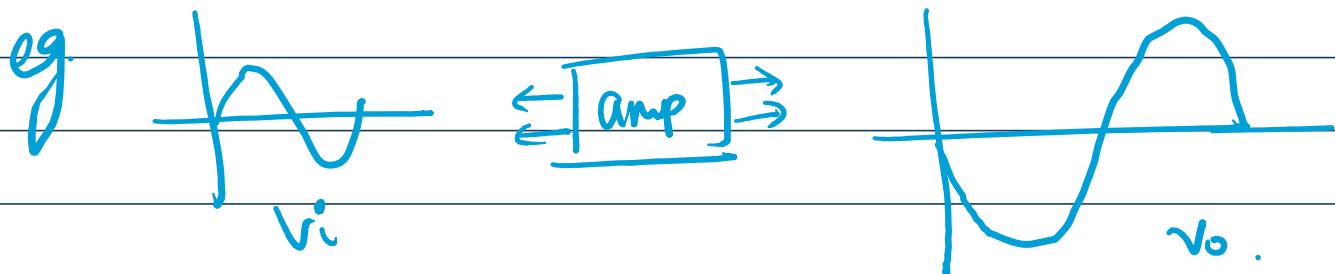
represents 180° phase shift b/w the o/p V & i/p V




$$r_e = \frac{26mV}{I_F}$$

ex:

①

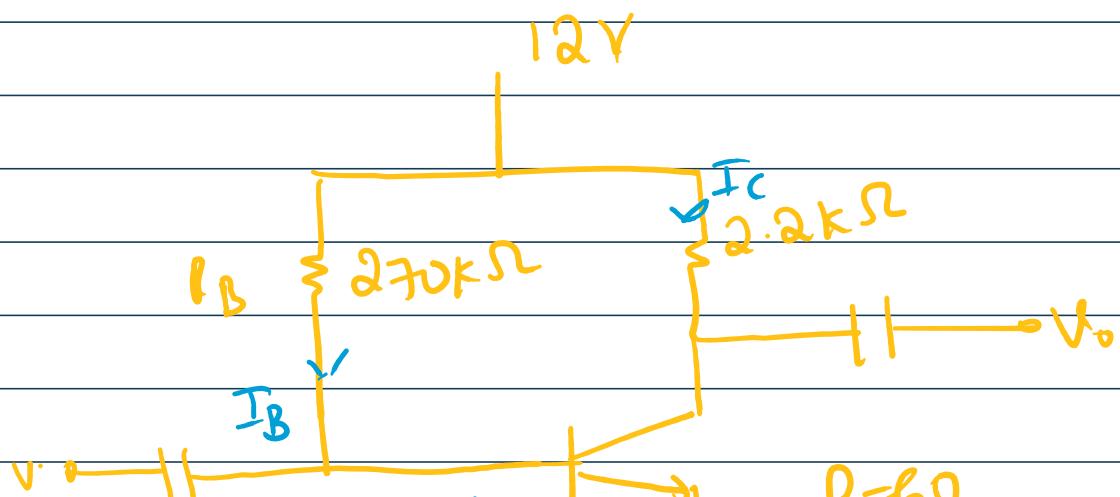

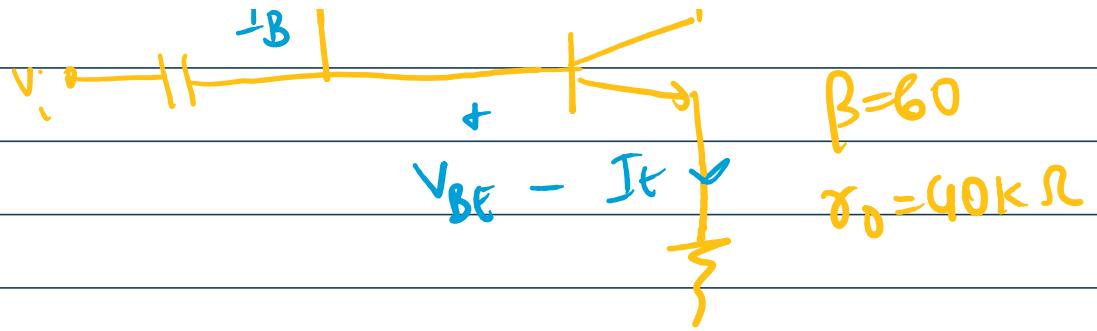

For the network shown:

- (i) Determine i/p & o/p impedances
- (ii) Determine voltage gain.
- (iii) Determine current gain

givn:

$$R_B = 270\text{k}\Omega$$

$$R_C = 2.2\text{k}\Omega$$

$$\beta = 60$$

$$r_o = 40\text{k}\Omega$$

→ $r_L = \frac{26\text{mV}}{I_C}$

→ KVL in i/p loop.

$$12 - I_B R_B - V_{BE} = 0$$

$$12 - I_B(270\text{k}) - 0.7 = 0$$

$$12 - I_B(270\text{K}) - 0.7 = 0$$

$$I_B = 0.0419 \text{ mA}$$

$$I_B = 41.9 \mu\text{A}$$

$$I_C = I_B + I_E$$

$$I_C = (1+\beta) I_B$$


$$= 61 \times 41.9 \mu\text{A}$$

$$I_E = 2.55 \text{ mA}$$

$$\rightarrow r_e = \frac{26 \text{ mV}}{2.55 \text{ mA}}$$

$$r_e = 10.18 \Omega$$

\rightarrow find ac eqn circuit

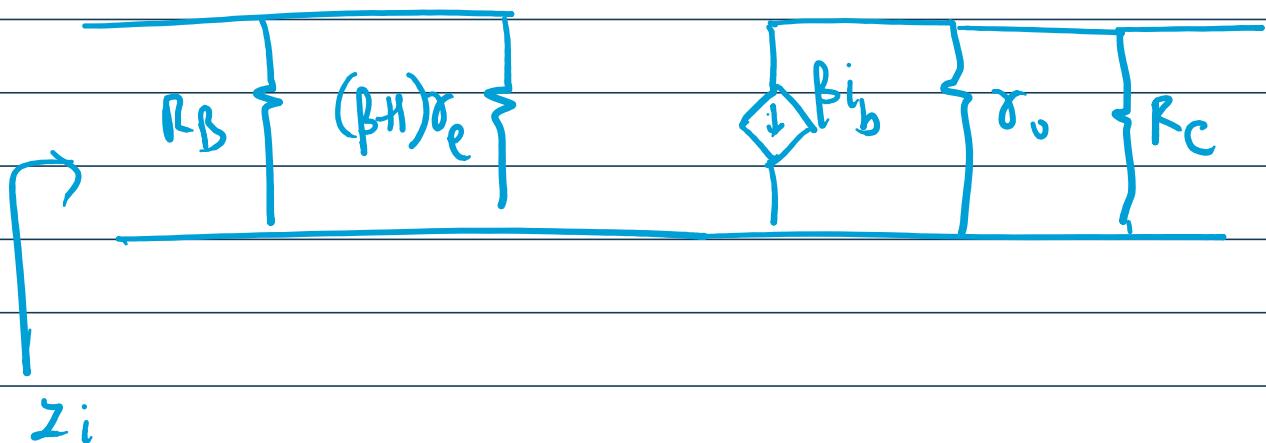

$$Z_i = R_B \parallel (\beta + 1) r_e$$

$$= \frac{R_B (\beta + 1) \alpha_e}{R_B + (\beta + 1) \alpha_e}$$

$$= \frac{(270k) (61) (10 \cdot 18)}{270k + (61)(10 \cdot 18)}$$

$$= 0.6195 k\Omega$$

$$Z_i = 619.5 \Omega$$

(DR) $\left[\begin{array}{l} \text{if } R_B \gg 10(\beta + 1) \alpha_e \\ \hookrightarrow \text{can be neg} \end{array} \right]$

$$Z_i = (\beta + 1) \alpha_e$$

$$= 61 \times 10 \cdot 18$$

$$= 0.621 k\Omega$$

$$\underline{\underline{Z_i = 621 \Omega}}$$

$$Z_o = r_o \parallel R_C$$

$$= \frac{r_o \parallel R_C}{r_o + R_C}$$

$$= \frac{(40k) (2.2k)}{(40k) (2.2k)}$$

$$= \frac{(40k)(22k)}{40k + 2.2k}$$

$$Z_0 = 2.085 \text{ k}\Omega$$

[b)] $10R_C = 22 \text{ k}\Omega < g_o$

$$\Rightarrow Z_0 = R_C = 2.2 \text{ k}\Omega$$

$$A_V = \frac{V_o}{V_i} = \frac{-R_C}{g_e}$$

$$A_V = -\underline{216.1}$$


$$A_i = \frac{i_o}{i_i}$$

Cascaded systems

31 October 2024 12:28 PM

Cascaded Systems

Arranging obj in series/seq

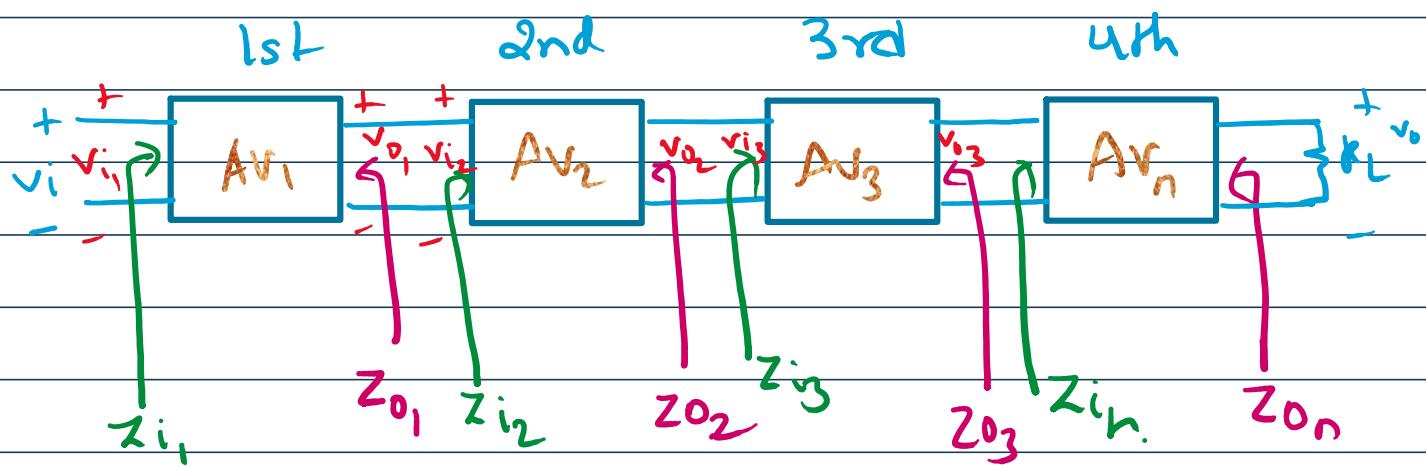

$$v_{i_1} = v_i \quad v_{o_1} = v_{i_2} \quad v_{o_2} = v_{i_3} \dots$$