
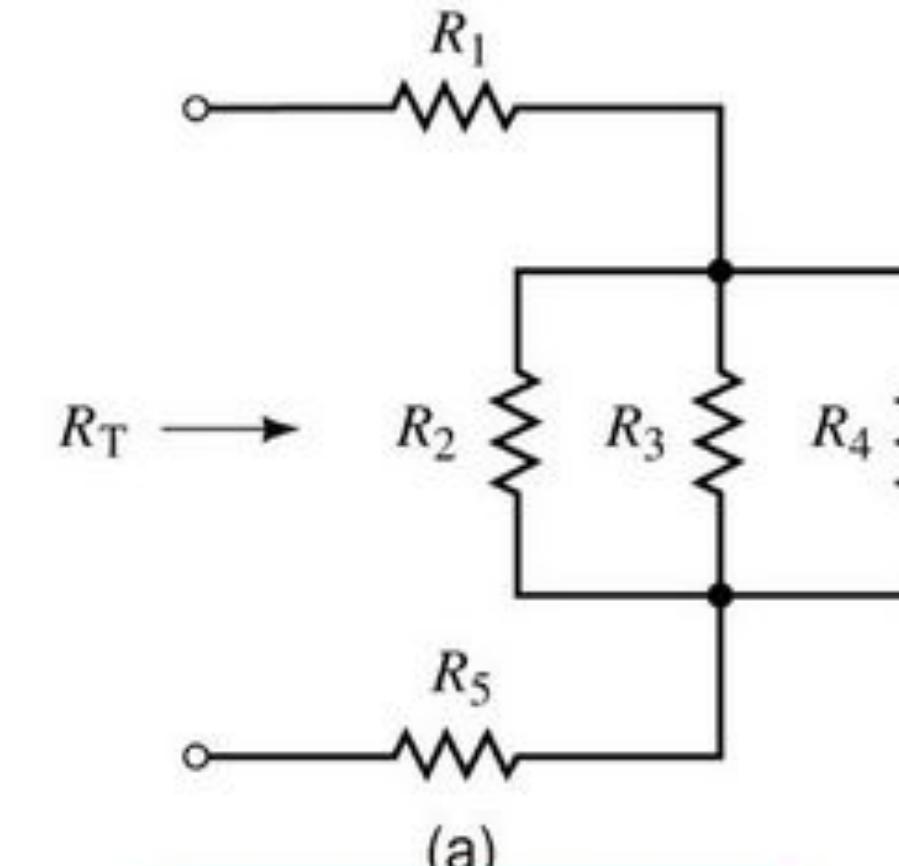


# RV College of Engineering®


## Department of Electrical and Electronics Engineering

### *Basics of Electrical Engineering - (22ES14D)*

#### *UNIT 1 – DC Circuits*

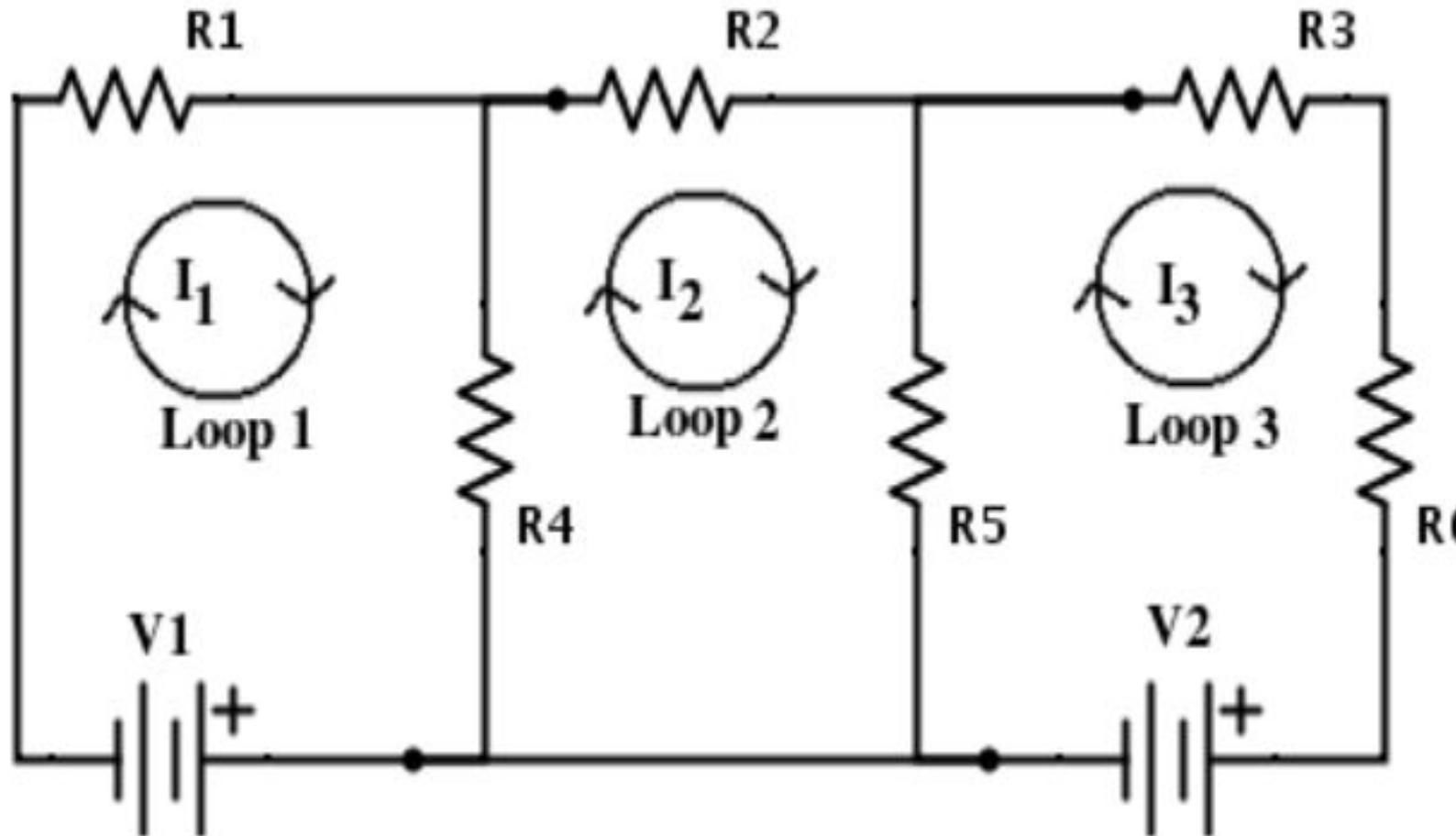
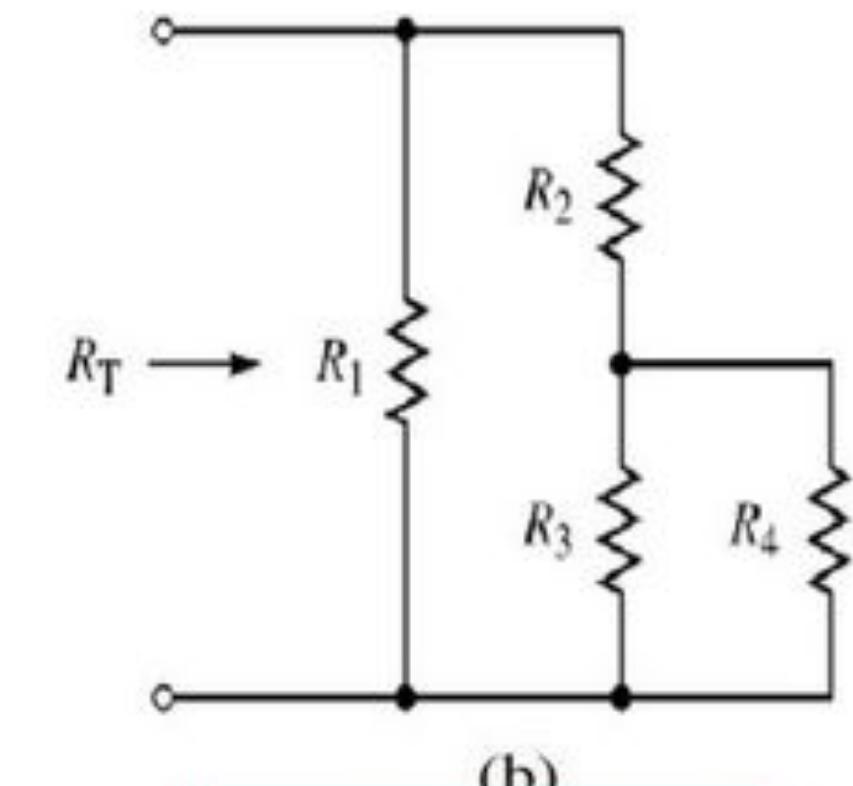
$$R_T = R_1 + (R_2 \parallel R_3 \parallel R_4) + R_5$$



$$R_T = R_1 \parallel (R_2 + (R_3 \parallel R_4))$$



## CHARGE AND CURRENT

- **Charge**

- most basic quantity in an electric circuit
- is an electrical property of the atomic particles of which matter consists, measured in coulombs (C).
- charge *e* on an electron is negative and equal in magnitude to  $1.602 \times 10^{-19} C$ , while a proton carries a positive charge of the same magnitude as the electron. The presence of equal numbers of protons and electrons leaves an atom neutrally charged.




## CHARGE AND CURRENT

- Points should be noted about electric charge:
  - The coulomb is a large unit for charges. In 1 C of charge, there are  $1/(1.602 \times 10^{-19}) = 6.24 \times 10^{18}$  electrons. Thus realistic or laboratory values of charges are on the order of pC, nC, or  $\mu$ C.
  - According to experimental observations, the only charges that occur in nature are integral multiples of the electronic charge  $e = -1.602 \times 10^{-19} C$ .
  - The **law of conservation of charge** states that charge can neither be created nor destroyed, only transferred. Thus the algebraic sum of the electric charges in a system does not change.
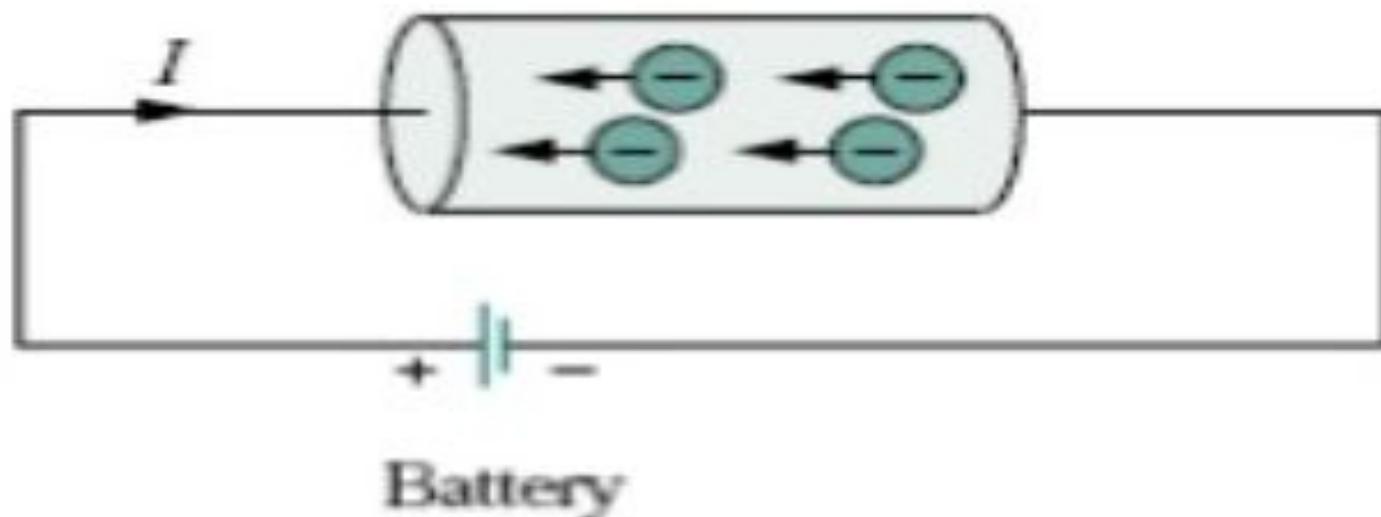
# CHARGE AND CURRENT

- Electric charge or electricity is mobile
  - Positive charges move in one direction while negative charges move in the opposite direction
  - Motion of charges creates electric current
  - **Conventionally** take the current flow as the movement of positive charges, that is, opposite to the flow of negative charges.




# CHARGE AND CURRENT

- **Electric current** is the time rate of change of charge, measured in amperes (A). **1 ampere = 1 coulomb/second**

$$\boxed{i = \frac{dq}{dt}} \quad \boxed{q = \int_{t_0}^t i dt}$$

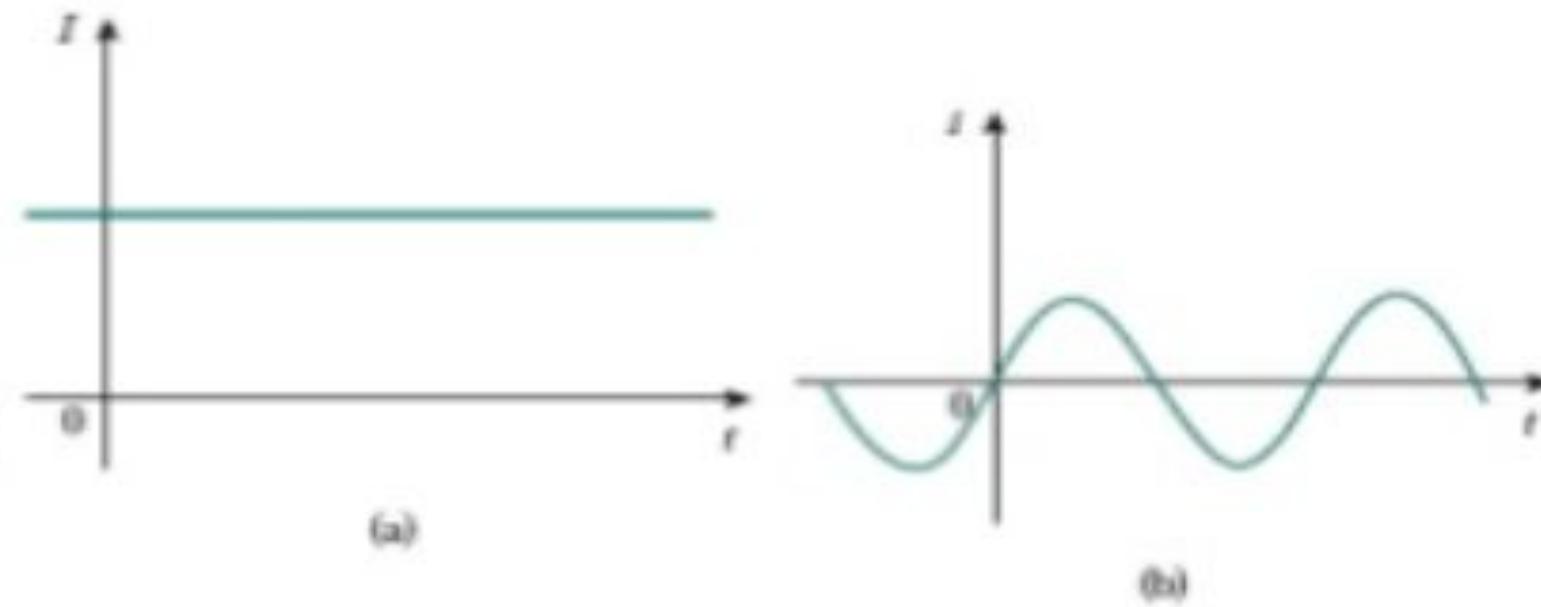- **Direct Current (DC)** is a current that does not vary with time.
- **Alternating Current (AC)** is a current that varies sinusoidally with time.





# VOLTAGE

- **Voltage** (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).
- Voltage  $v_{ab}$  between two points  $a$  and  $b$  in an electric circuit is the energy (or work) needed to move a unit charge from  $a$  to  $b$ ; *mathematically,*
  - where  $w$  is energy in joules (J) and  $q$  is charge in coulombs
  - Voltage  $v_{ab}$  or simply  $v$  is measured in volts (V)

$$v_{ab} = \frac{dw}{dq}$$



**1 volt = 1 joule/coulomb = 1 newton meter/coulomb**

# VOLTAGE


- The plus (+) and minus (-) signs are used to define reference direction or voltage polarity.

- (1) point **a** is at a potential of  $v_{ab}$  volts higher than point **b**  
(2) the potential at point **a** with respect to point **b** is  $v_{ab}$

$$v_{ab} = -v_{ba}$$

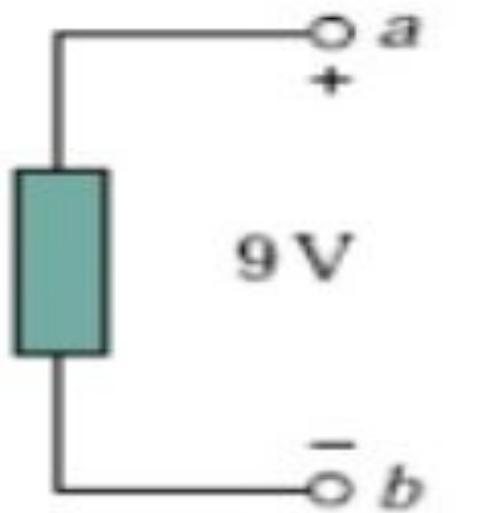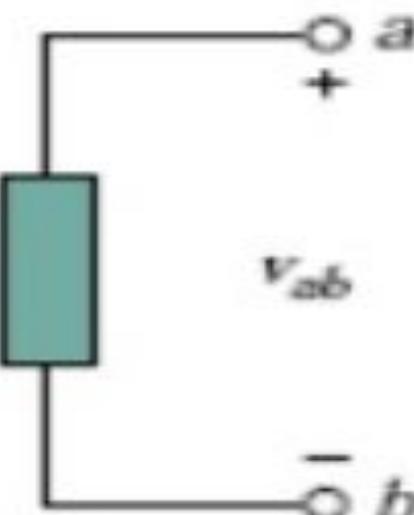

(a)

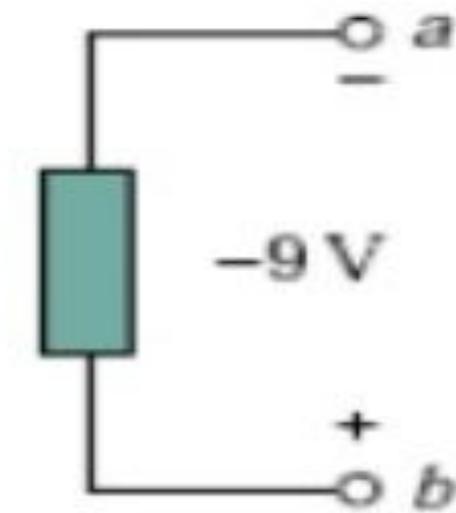

(b)

(a), there is a 9-V voltage drop from **a** to **b** or equivalently a 9-V voltage rise from **b** to **a**.

(b), point **b** is -9 V above point **a**.

A voltage drop from **a** to **b** is equivalent to a voltage rise from **b** to **a**.

constant voltage is called a dc voltage and is represented by V, whereas a sinusoidally time-varying voltage is called an ac voltage and is represented by

# POWER AND ENERGY

- **Power** is the time rate of expending or absorbing energy, measured in watts (W).

$$P = \frac{dw}{dt}$$


$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$

$$P = vi$$


- where  $P$  is power in vatts (W),  $w$  is energy in joules (J), and  $t$  is time in seconds (s).
- power  $P$  is a time-varying quantity and is called the instantaneous power.
- If the power has a + sign, power is being **delivered to or absorbed** by the element. If, on the other hand, the power has a - sign, power is being **supplied** by the element.

# POWER AND ENERGY


- **Passive sign convention** is satisfied when the current enters through the positive terminal of an element and  $p = +vi$ . If the current enters through the negative terminal,  $p = -vi$ .

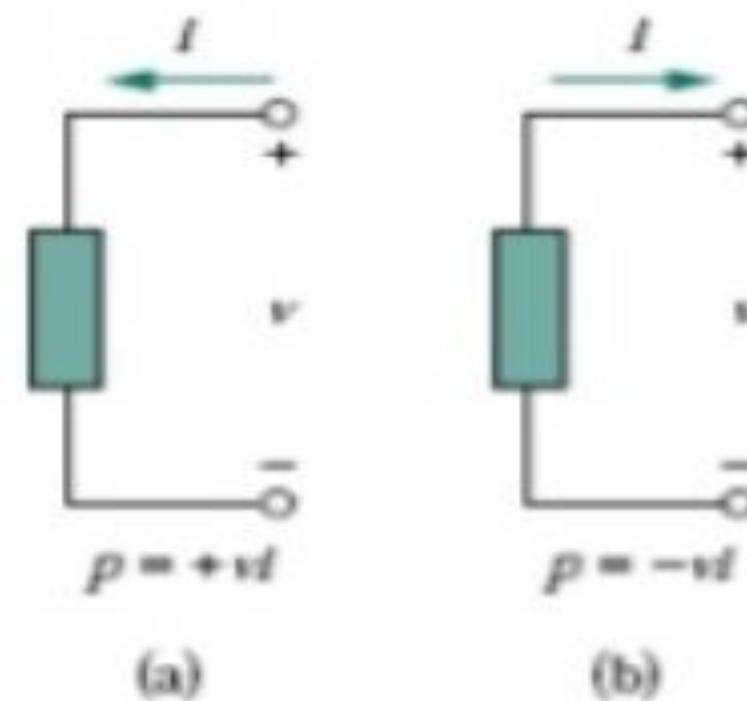

**Figure 1.8** Reference polarities for power using the passive sign convention: (a) absorbing power, (b) supplying power.

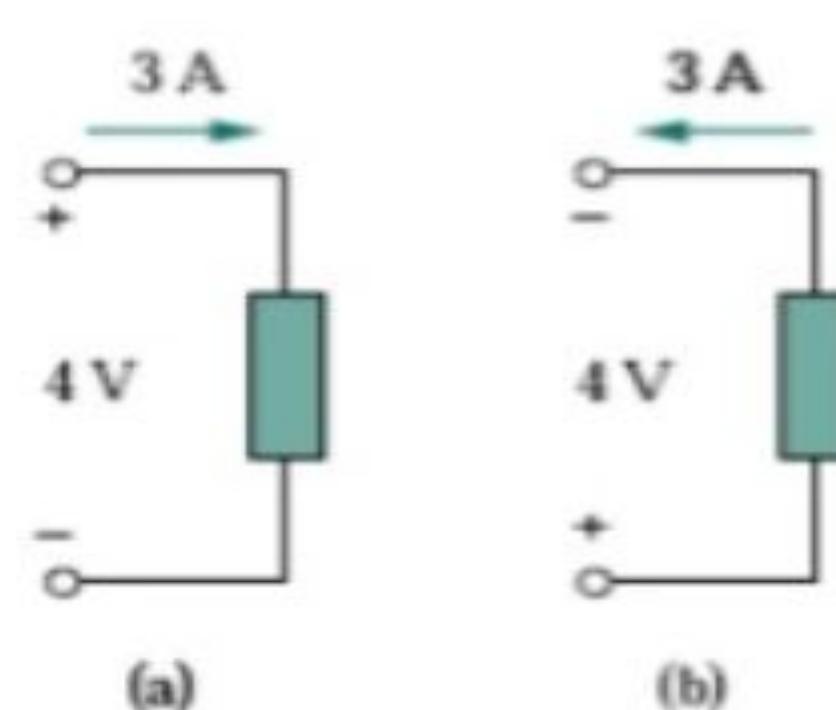

**Figure 1.9** Two cases of an element with an absorbing power of 12 W:  
 (a)  $p = 4 \times 3 = 12 \text{ W}$ ,  
 (b)  $p = 4 \times 3 = 12 \text{ W}$ .

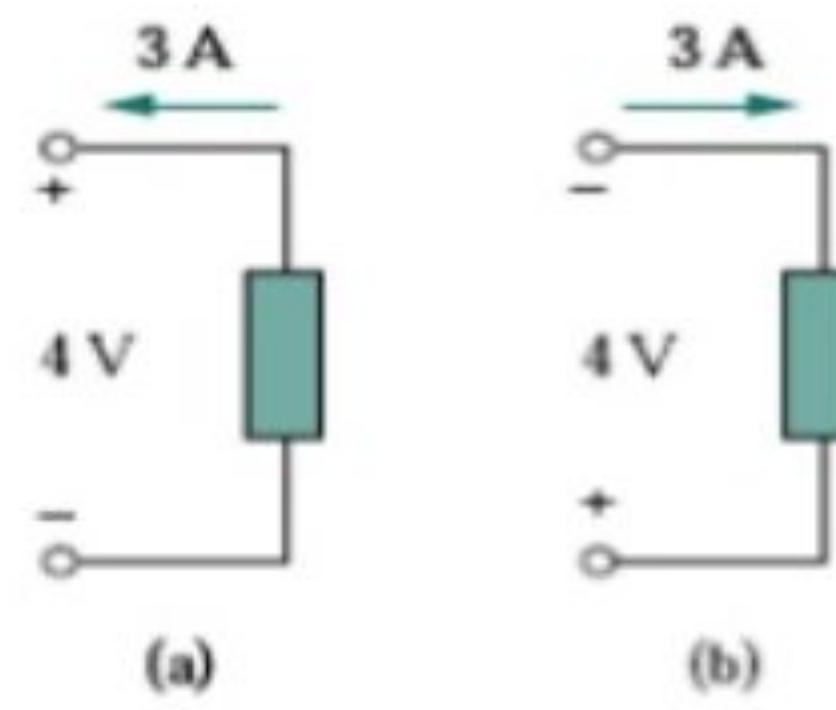

**Figure 1.10** Two cases of an element with a supplying power of 12 W:  
 (a)  $p = 4 \times (-3) = -12 \text{ W}$ ,  
 (b)  $p = 4 \times (-3) = -12 \text{ W}$ .

# POWER AND ENERGY

- ***law of conservation of energy must be obeyed:***

• algebraic sum of power in any instant of time, must be zero.

- Energy absorbed or supplied by an element from time  $t_0$  to time  $t$  is

- **Energy** is the capacity to do work, measured in joules ( J).

• electric power utility companies

$$w = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt \text{ hours (Wh)}$$


$$1 \text{ Wh} = 3,600 \text{ J}$$

# Electric Circuit

- An interconnection of simple electrical devices with at least one closed path in which current may flow

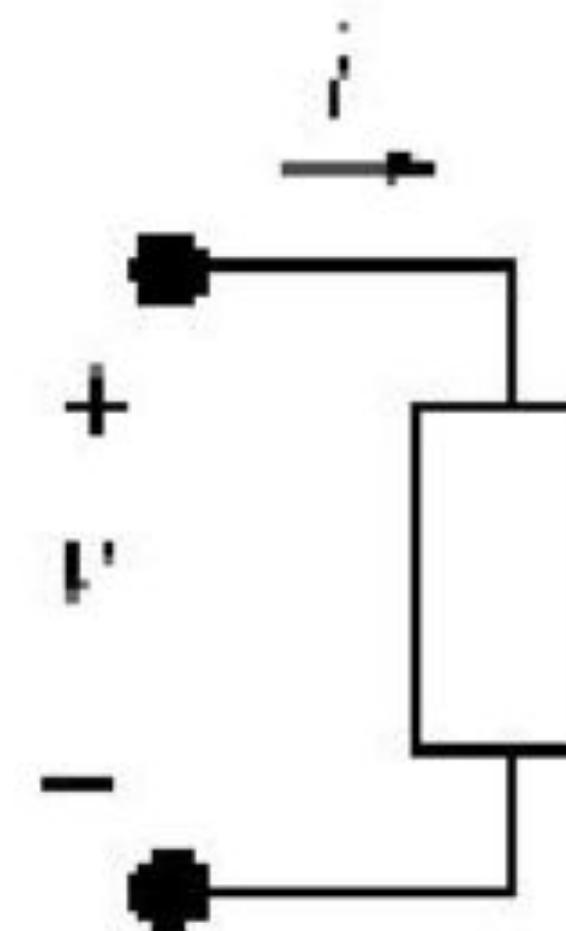
## Circuit Elements

- Active Elements
  - Voltage and Current sources
- Passive Elements
  - Resistors, Inductors and Capacitors



# Circuit Elements

Go, change the world

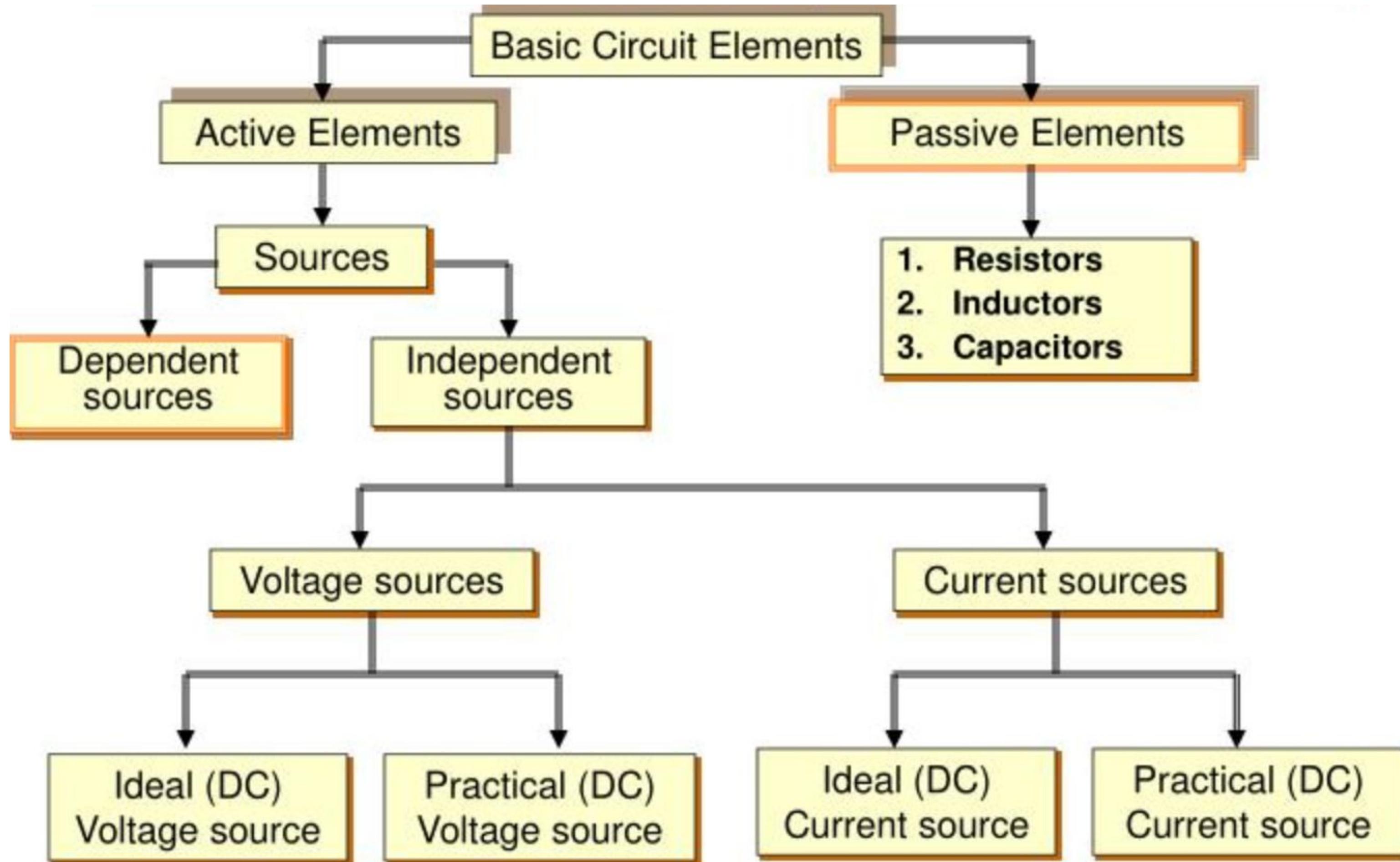



## ■ Resistance (**R**):

Property of opposition to flow of **current**

- The voltage across the resistor is proportional to the **current** flowing through it
- $V_R = IR$
- '**R**' =  $V_R/I$
- **Unit - Ohm**



## ■ Inductance (L):

Property of opposition to the rate of change of current

- The voltage induced in the inductor is proportional to the rate of change of current flowing through it
- $e_L = L (di/dt) = N (d\Phi/dt)$
- $L = N (d\Phi/di)$
- Unit – Henry (H)



## ■ Capacitance (C):

Property which opposes the **rate of change of voltage**

- The capacitive current is proportional to the rate of change of voltage across it
- $i_c = C (dv/dt)$
- Unit – **Farad (F)**.


# CIRCUIT ELEMENTS

- Two types of elements found in electric circuits:
  - **Passive element** – not capable of generating energy (resistors, capacitors, and inductors)
  - **Active element** - capable of generating energy (generators, batteries, and operational amplifiers)
- Two kinds of sources:
  - **Independent Sources** - an active element that provides a specified voltage or current that is completely independent of other circuit variables
  - **Dependent Sources** - an active element in which the source quantity is controlled by another voltage or current. (transistors, operational amplifiers and integrated circuits)

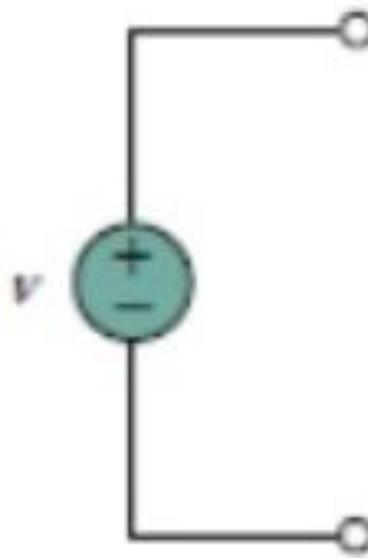
# CIRCUIT ELEMENTS

- **Ideal Independent Voltage Source** delivers to the circuit whatever current is necessary to maintain its terminal voltage (batteries and generators).

- Symbols for independent voltage, (a) used



(a)

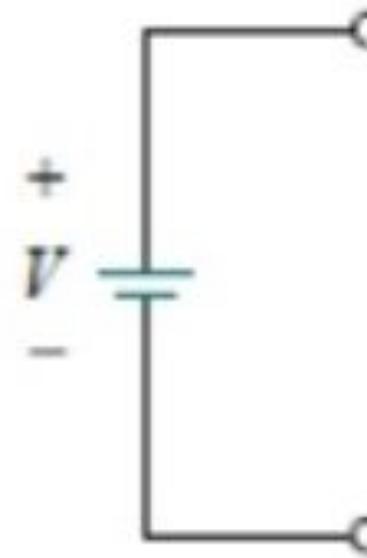


(b)

ed for constant or time-varying

# CIRCUIT ELEMENTS

- **Ideal Independent Current Source** is an active element that provides a specified current completely independent of the voltage across the source.


- Symbol for independent cu  $i$

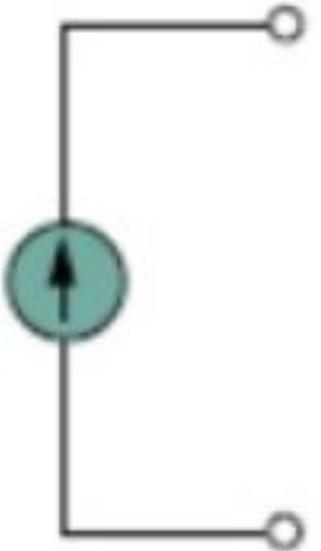


# CIRCUIT ELEMENTS

- Four possible types of dependent sources:
  - Voltage-Controlled Voltage Source (VCVS).
  - Current-Controlled Voltage Source (CCVS).
  - Voltage-Controlled Current Source (VCCS).
  - Current-Controlled Current Source (CCCS).

- Symbols for: (a) dep

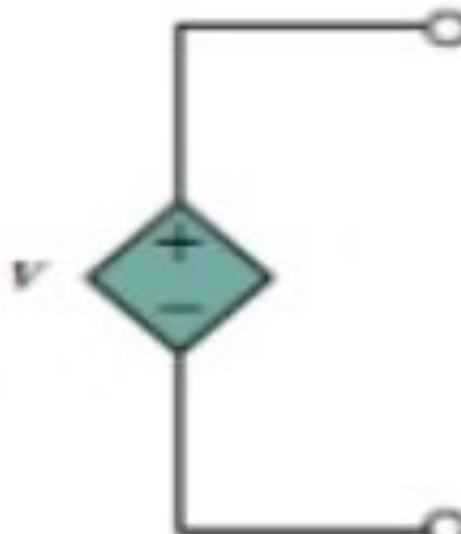

(a)

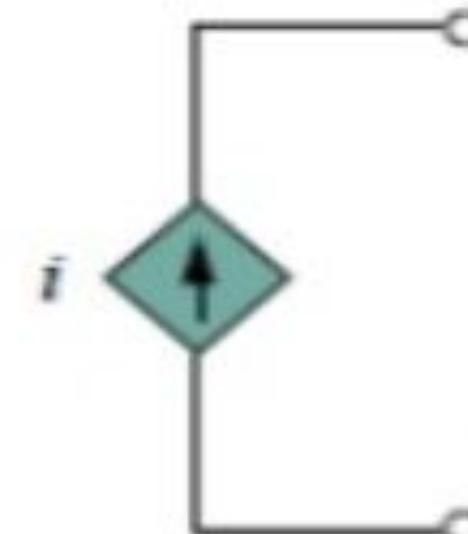

(b)

pendent current source.

# OHM'S LAW

- **Resistance ( $R$ )** –of an element denotes its ability to resist the flow of electric current; it is measured in ohms ( $\Omega$ ).
- The resistance of any material with a uniform cross-sectional area ( $A$ ) *depends on A and its length (l)*

$$R = \rho \frac{\ell}{A}$$


Where, rho is the resistivity of the material.

Good conductors like Copper and Aluminium have low resistivity while insulators such as Mica, Paper have high resistivities.

# OHM'S LAW

**TABLE 2.1** Resistivities of common materials.

Material	Resistivity ( $\Omega \cdot \text{m}$ )	Usage
Silver	$1.64 \times 10^{-8}$	Conductor
Copper	$1.72 \times 10^{-8}$	Conductor
Aluminum	$2.8 \times 10^{-8}$	Conductor
Gold	$2.45 \times 10^{-8}$	Conductor
Carbon	$4 \times 10^{-5}$	Semiconductor
Germanium	$47 \times 10^{-2}$	Semiconductor
Silicon	$6.4 \times 10^2$	Semiconductor
Paper	$10^{10}$	Insulator
Mica	$5 \times 10^{11}$	Insulator
Glass	$10^{12}$	Insulator
Teflon	$3 \times 10^{12}$	Insulator

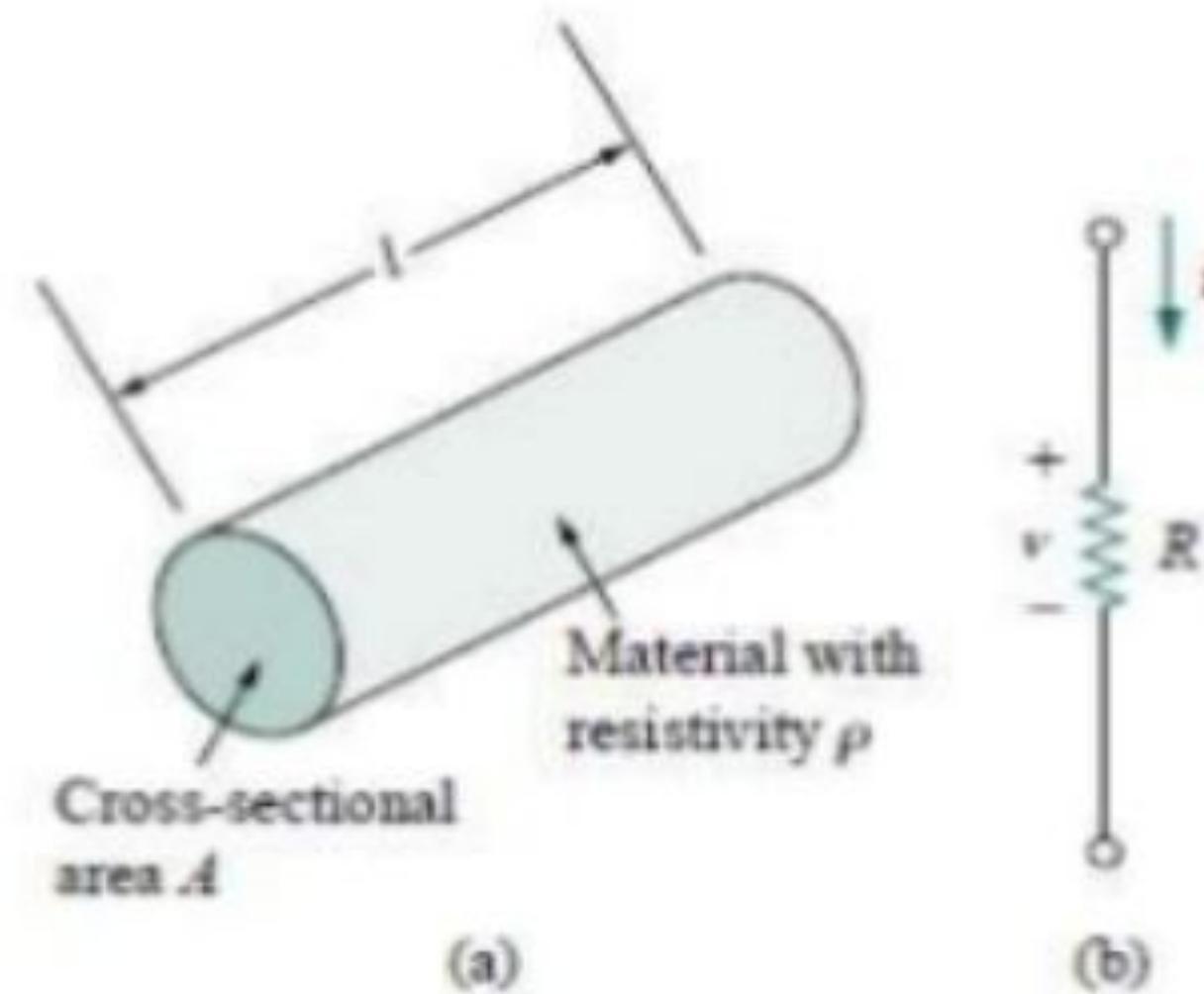

**(a) Resistor, (b) Circuit symbol for resistance.**



# OHM'S LAW

- **Ohm's law** states that the voltage “ $v$ ” across a resistor is directly proportional to the current “ $i$ ” flowing through the resistor.

$$v = iR$$

Short Circuit : is a circuit element where, resistance approaches to zero.


Open Circuit : is a circuit element where, resistance approaches to infinity.

# Ohm's law Magic Triangle


$$E = I R$$

$$I = \frac{E}{R}$$





$$R = \frac{E}{I}$$

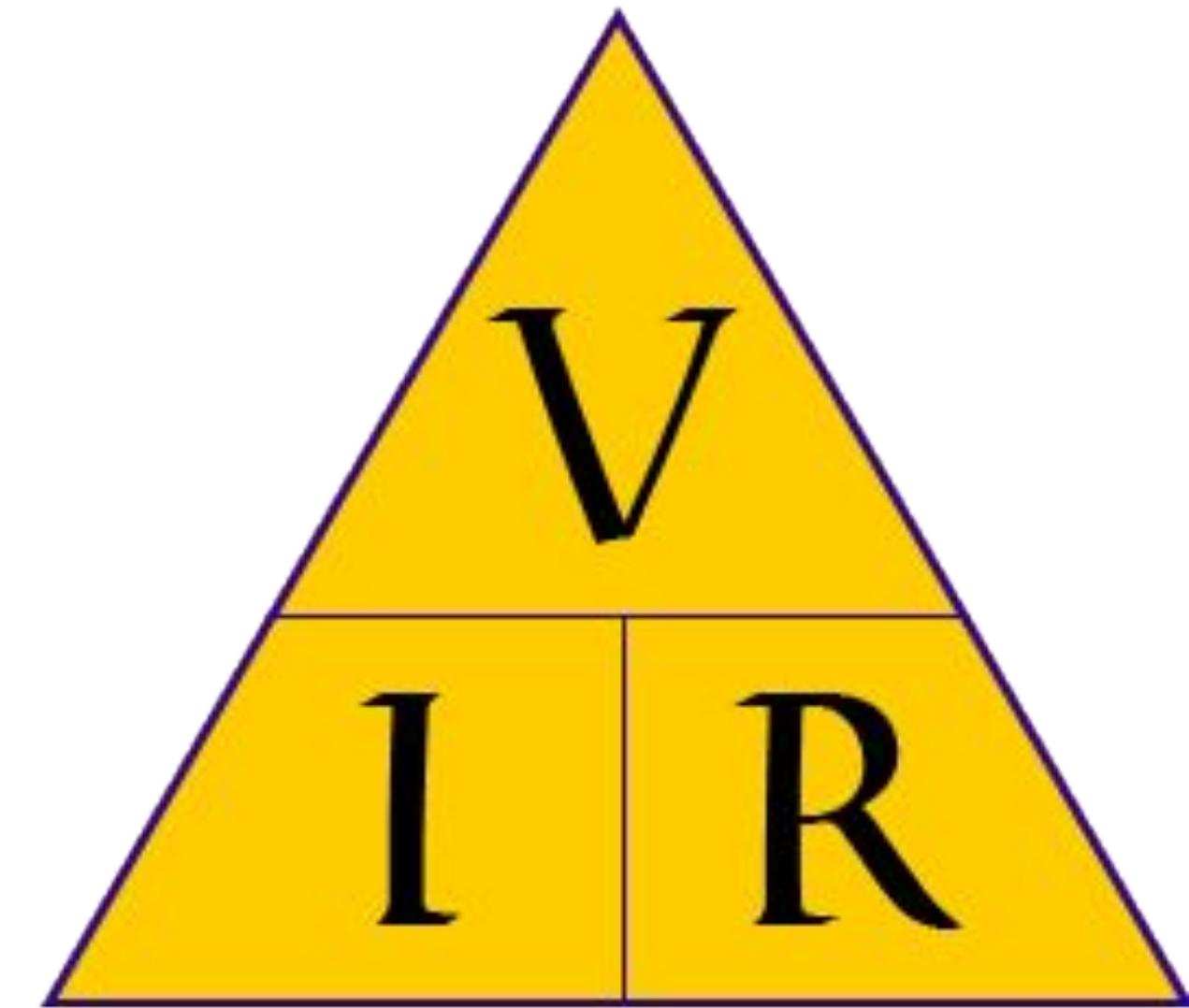

Quantity	Symbol	Unit of Measurement	Unit Abbreviation
Current	I	Ampere ("Amp")	A
Voltage	E or V	Volt	V
Resistance	R	Ohm	$\Omega$

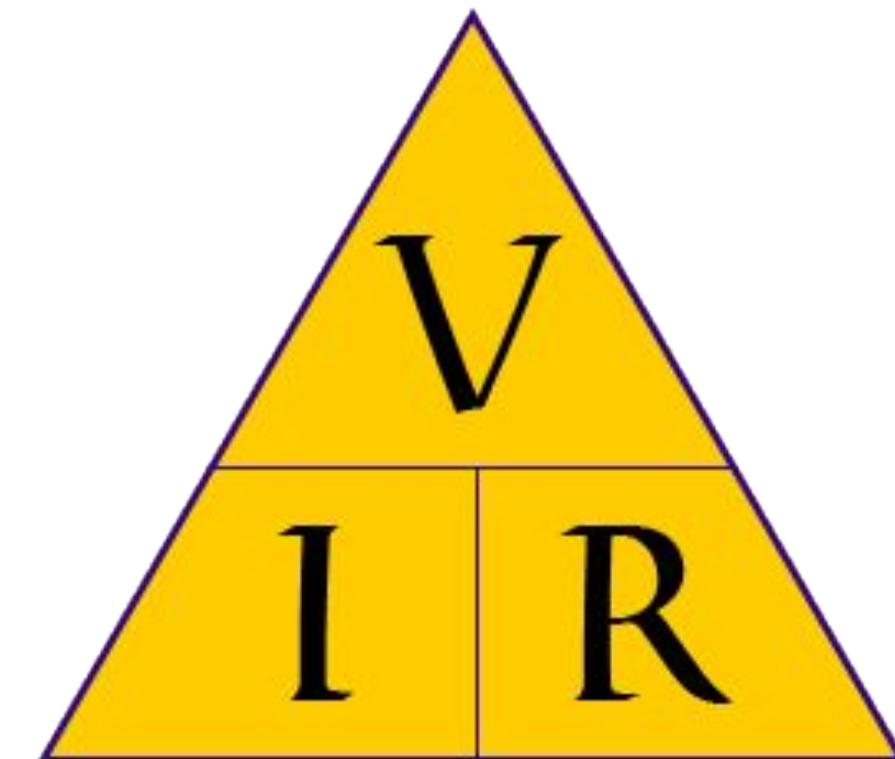

# Factors Affecting Resistance

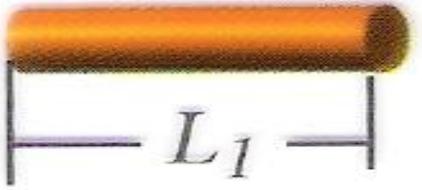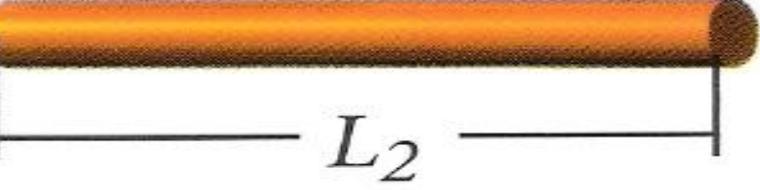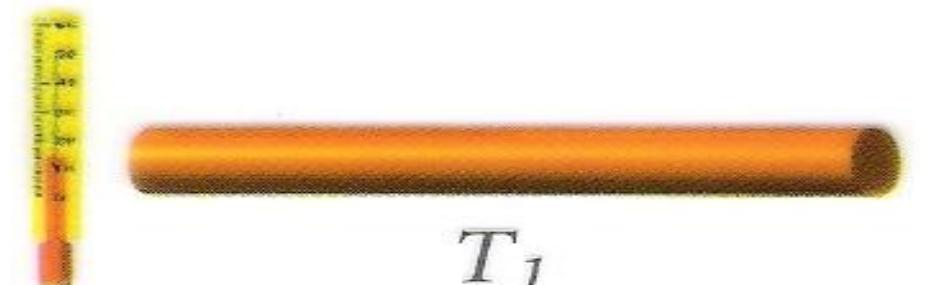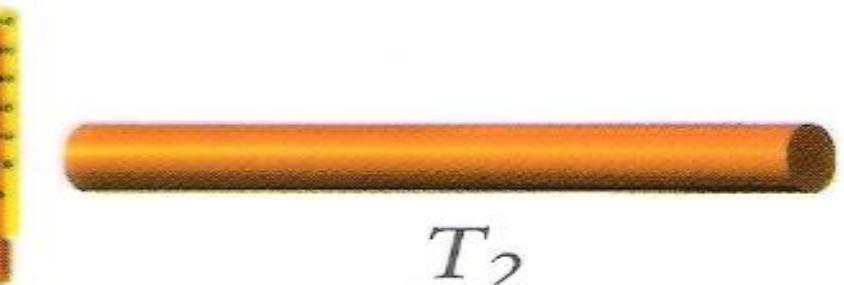Factor	Less resistance	Greater resistance
Length	 $L_1$	 $L_2$
Cross-sectional area	 $A_1$	 $A_2$
Material	 Copper	 Aluminum
Temperature	 $T_1$	 $T_2$

# OHM'S LAW

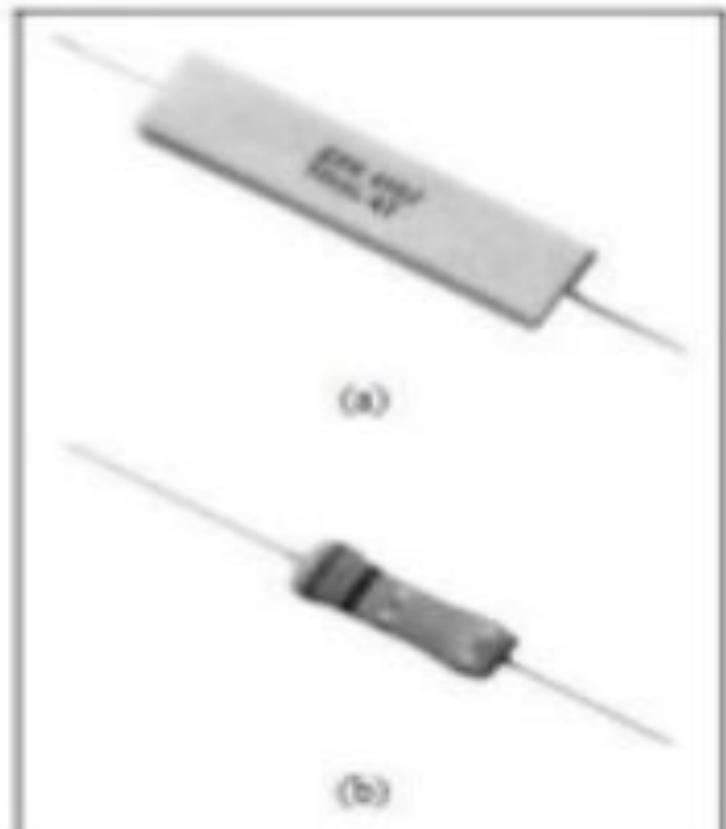
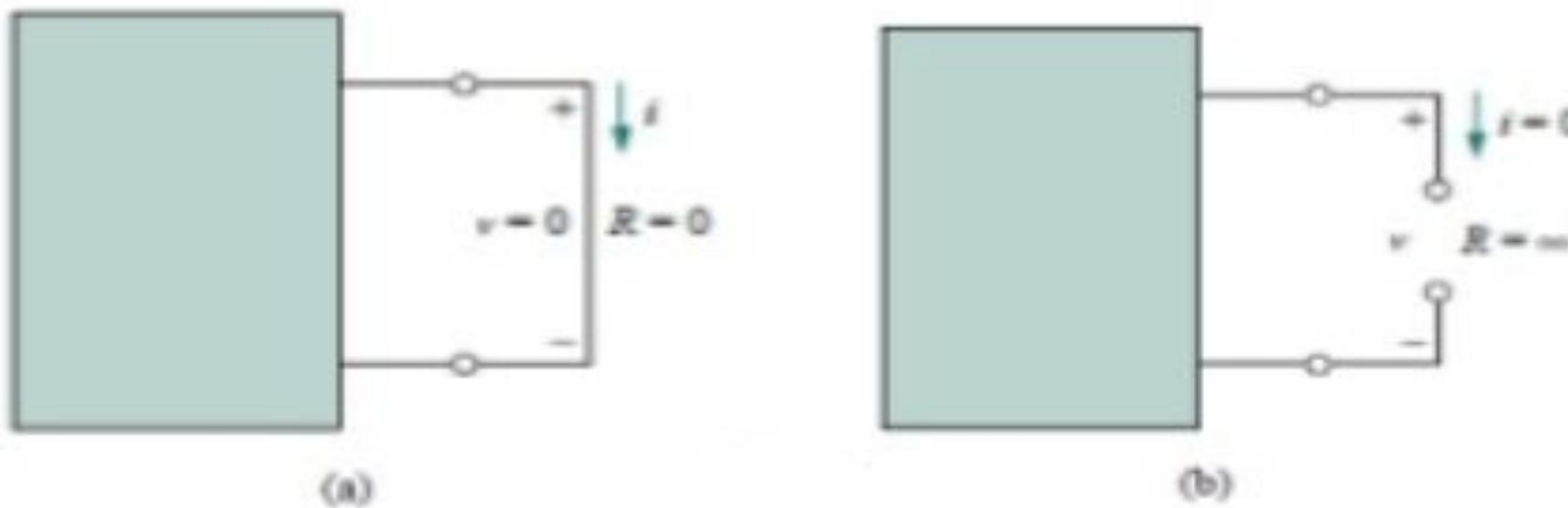


Figure 2.3 Fixed resistors: (a) wire-wound type, (b) carbon film type.

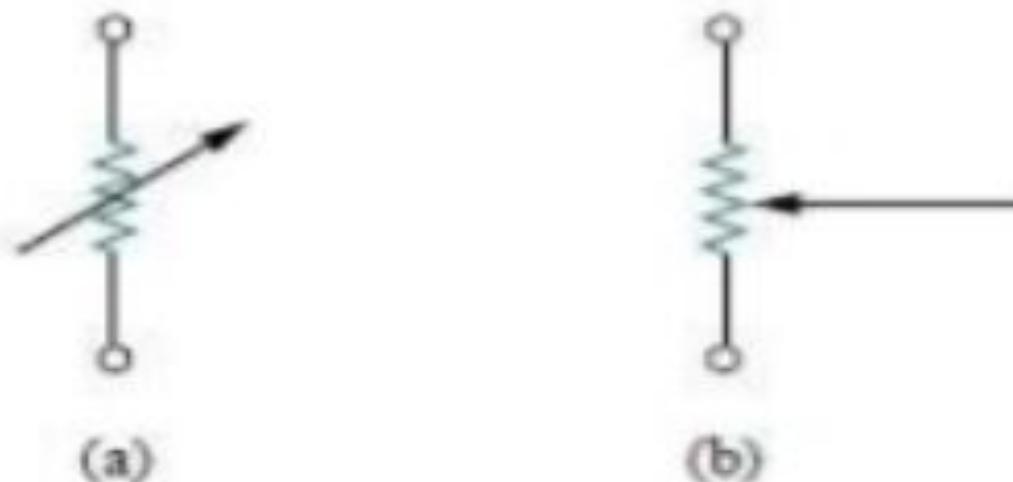


Figure 2.4 Circuit symbol for: (a) a variable resistor in general, (b) a potentiometer.




Figure 2.5 Variable resistors: (a) composition type, (b) slider pot.



# Series circuits and Parallel circuits

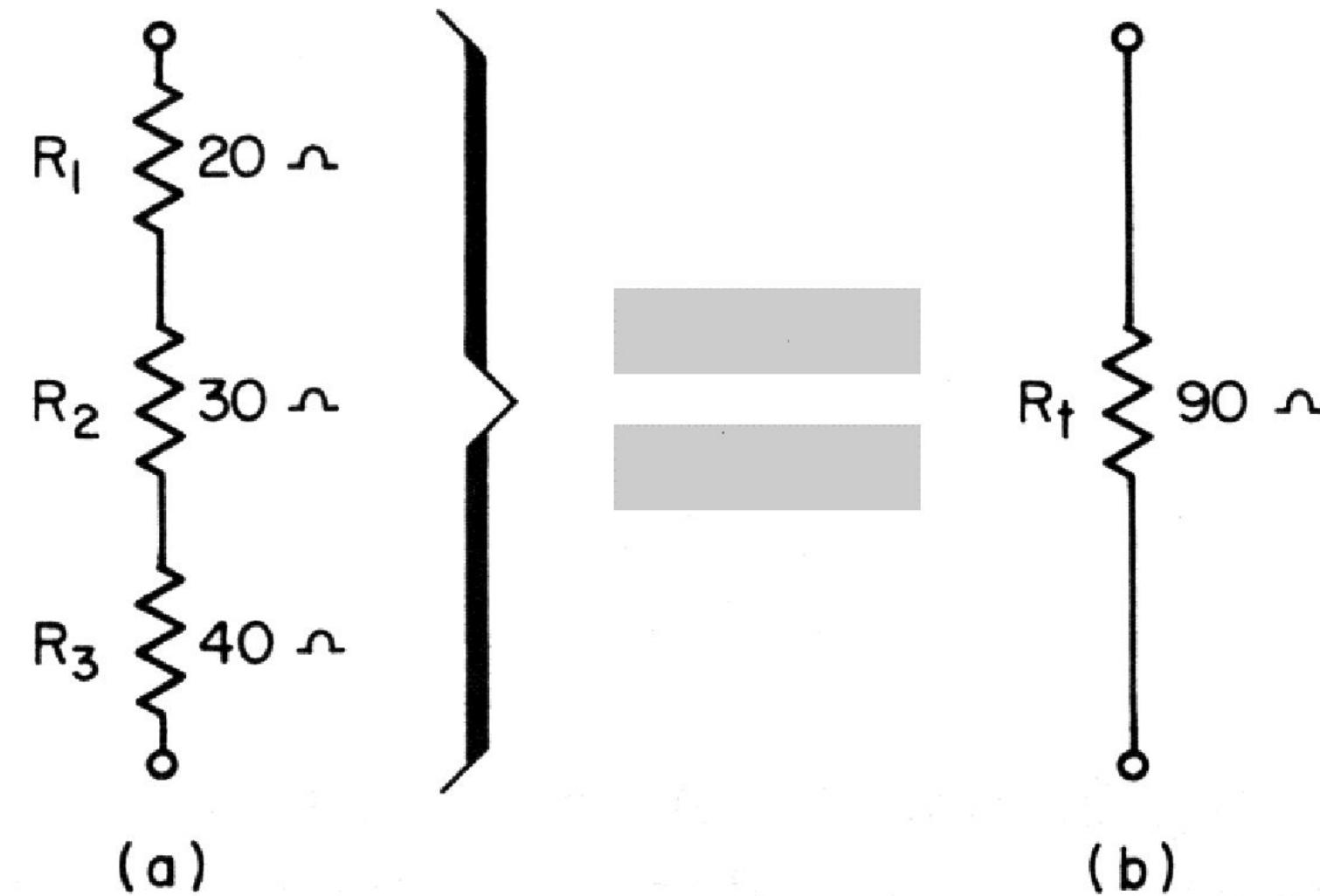
# Series Circuits

- Series Circuits are the simplest to work with.
- Here we have three resistors of different resistances.
- They share a single connection point.
- When added together the total resistance is 90-Ohms.


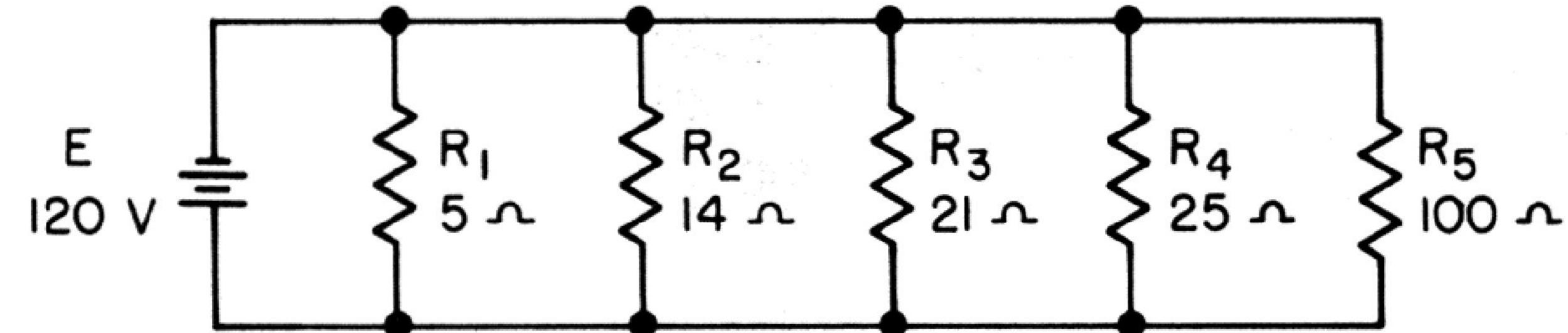
# Parallel Circuits

- A parallel circuit is shown here and it has TWO common connection points with another component.
- We cannot add the values of each resistor together like we can in the previous series circuit. So what do we need to do?



# Calculating Total Resistance of a Parallel Circuit


Two methods can be used to calculate the total resistance of the parallel circuit. They are the Product Over Sum equation or the Reciprocal Formula.

Product Over Sum is  $R_T = \frac{(R_1 \times R_2)}{(R_1 + R_2)}$


Reciprocal Formula is  $R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}}$
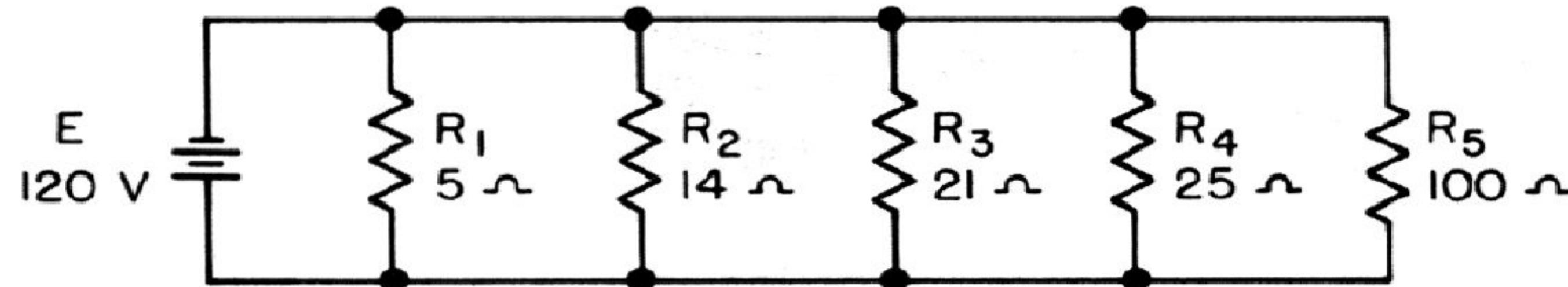
# Calculating Total Resistance of a Parallel Circuit

- So let use calculate  $R_T$  in this circuit.
- $$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}}$$


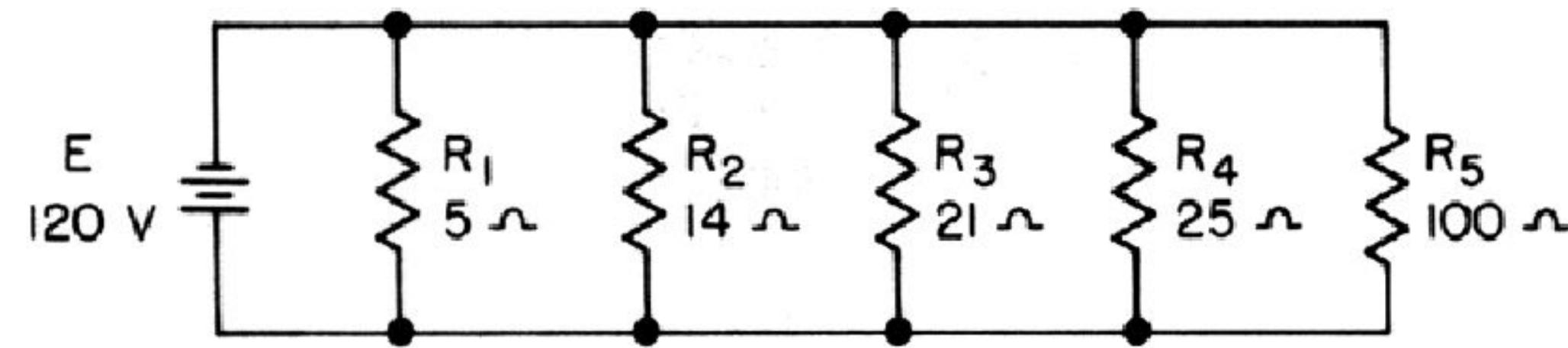
# Calculating Total Resistance of a Parallel Circuit



$$\begin{aligned}\bullet \quad R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}} = \frac{1}{\frac{1}{5} + \frac{1}{14} + \frac{1}{21} + \frac{1}{25} + \frac{1}{100}} \\ &= \frac{1}{0.2 + 0.0714 + 0.0476 + 0.04 + 0.01} = \frac{1}{0.369} = 2.7\Omega\end{aligned}$$


# Series-Parallel Circuits

If we combined a series circuit with a parallel circuit we produce a Series-Parallel circuit.

- R<sub>1</sub> and R<sub>2</sub> are in parallel and R<sub>3</sub> is in series with R<sub>1</sub> || R<sub>2</sub>.

The double lines between R<sub>1</sub> and R<sub>2</sub> is a symbol for parallel.

We need to calculate R<sub>1</sub> || R<sub>2</sub> first before adding R<sub>3</sub>.

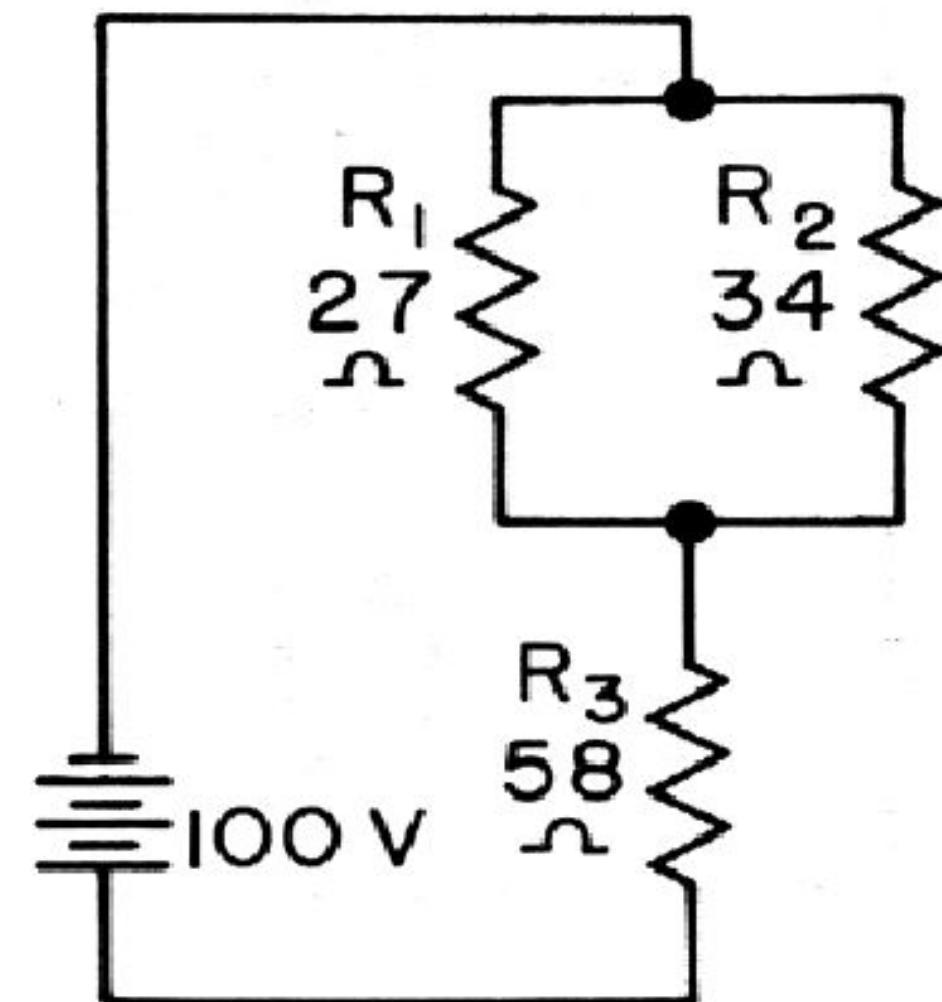

# Series-Parallel Circuits


- Here we can use the shorter Product Over Sum equation as we only have two parallel resistors.

$$R_{1 \parallel 2} = \frac{(R_1 \times R_2)}{(R_1 + R_2)} = \frac{27 \times 34}{27+34} = \frac{918}{61}$$

$$R_{1 \parallel 2} = 15.049\Omega + R_3 = R_T$$

$$R_T = 15.049 + 58 = 73.049\Omega$$

- $R_T = 73\Omega$

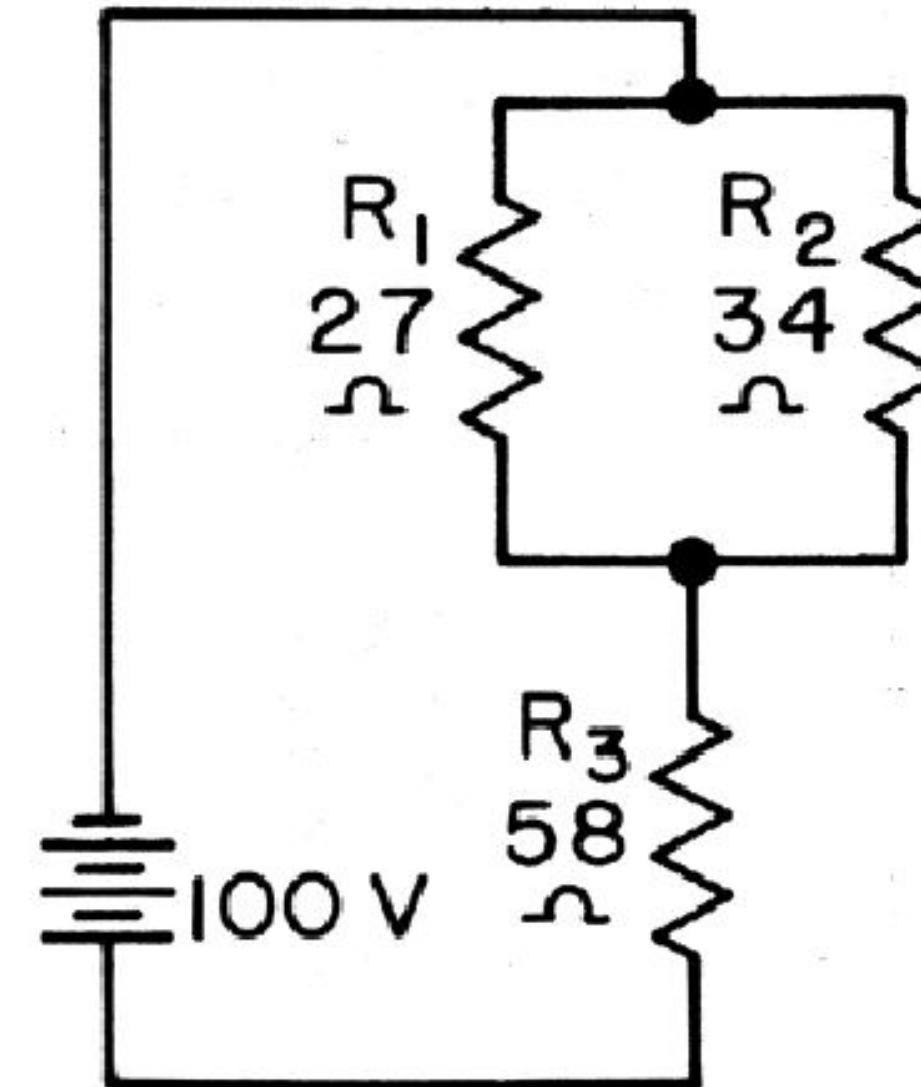


# Series-Parallel Circuits

- Now that we have our circuit resistance of  $R_T$  we can calculate circuit current by using Ohm's Law.

If  $R_T = 73\Omega$  and  $E = 100V$



$$I = \frac{100}{73} = 1.369 \text{ Amps or } 1.37 \text{ A}$$

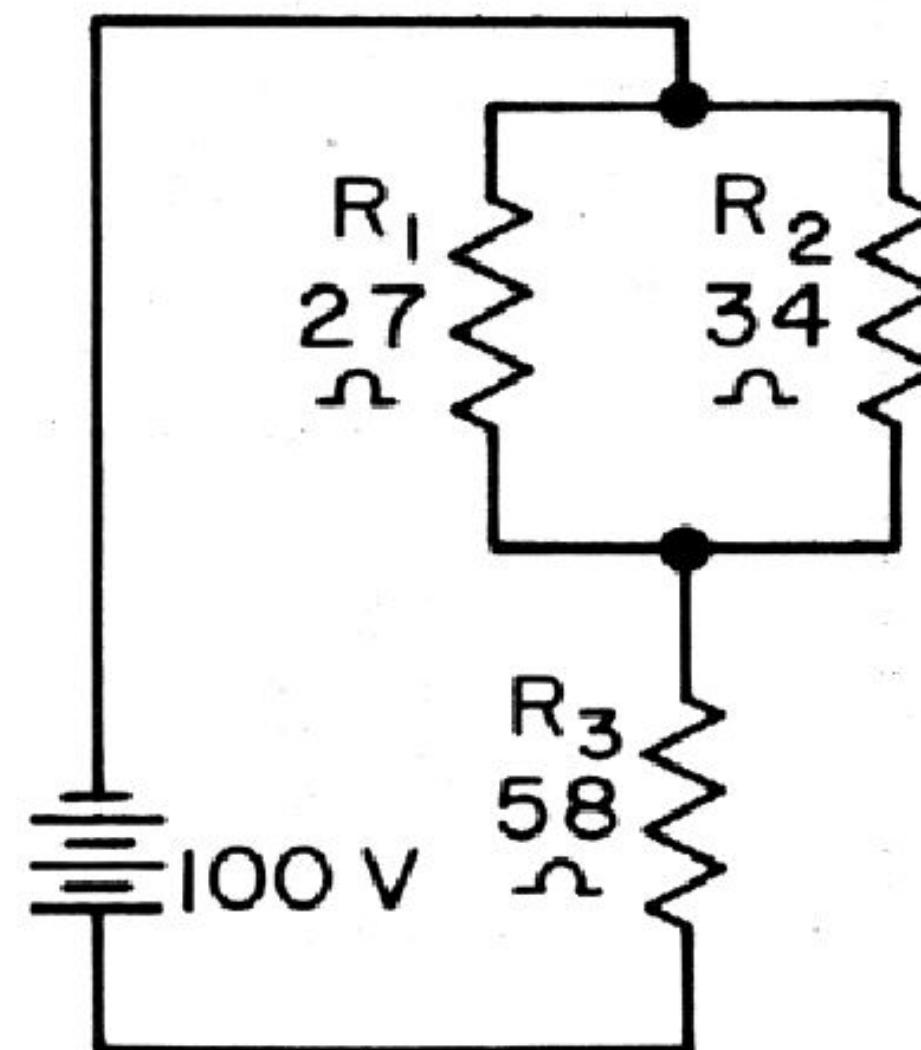The parallel resistors must be reduced to a single series value before being added to the series resistor.


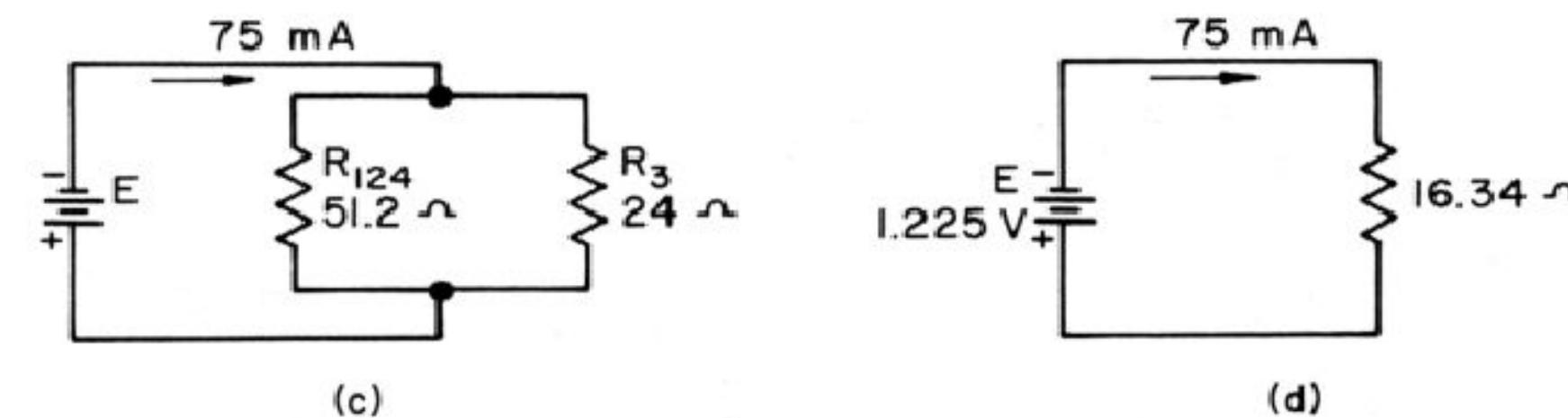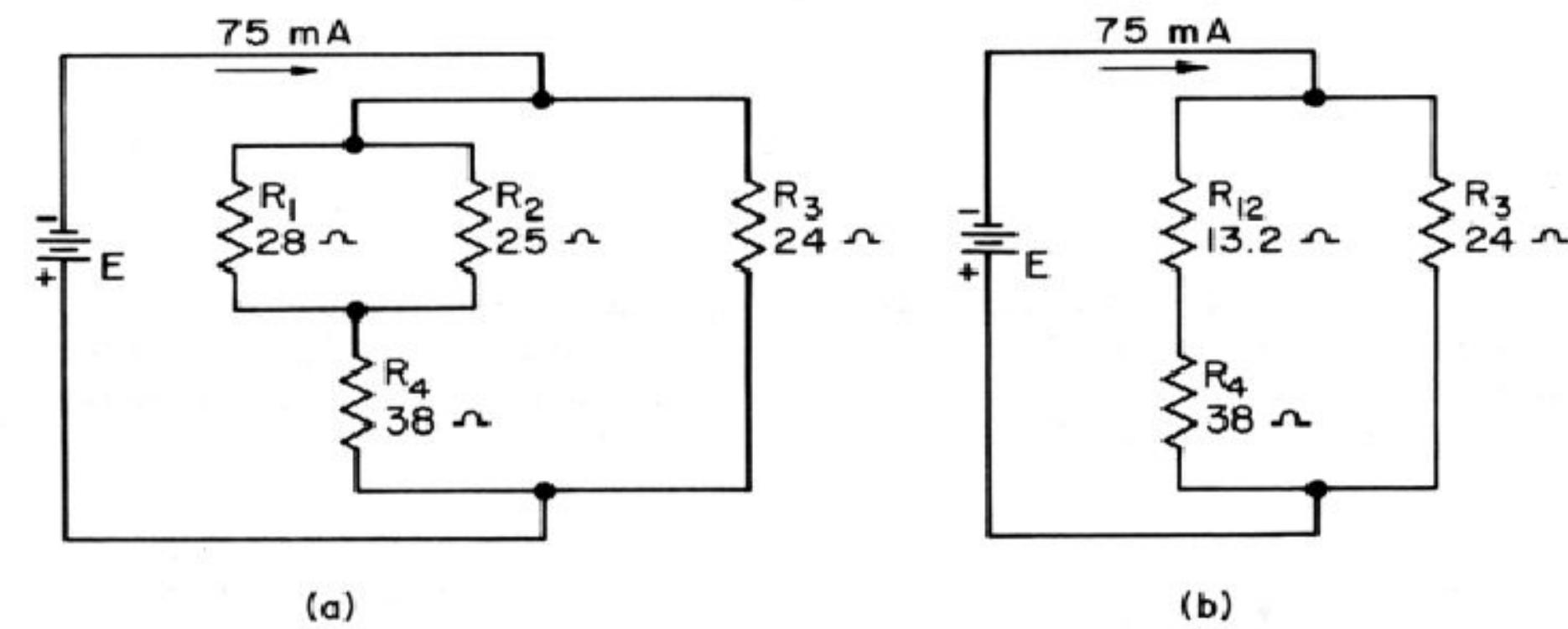
# Series-Parallel Circuits

- Series-Parallel circuits can be more complex as in this case:  
 In circuit (a) we have our original complex circuit. In circuit (b)  
 we have resistors  $R_1$   
 and  $R_2$  combined  
 to get  $13.2\Omega$ .  $R_4$  is  
 in series with the  
 newly combined  $R_{12}$   
 and their added  
 value is  $51.2\Omega$ .  
 And now (c) we are  
 left with  $R_{124}$  in  
 parallel with  $R_3$ .  
 (d) is our final circuit.



# Series-Parallel Circuits

- Series, Parallel and Series-Parallel circuits are our three main types of circuits and they are common in DC and AC supplied circuits.
- A series circuit has one shared connection point between components.
- A parallel circuit has two shared connection points between components.

# Series-Parallel Circuits


A series-parallel circuit can have two components sharing one connection point with a single component while they have two common connection points between them.

**Series**




(a)

**Series-Parallel**

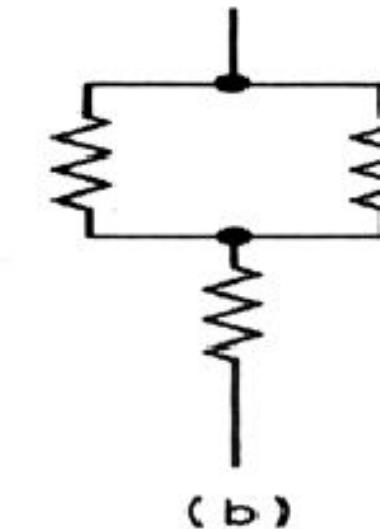


(b)

**Parallel**

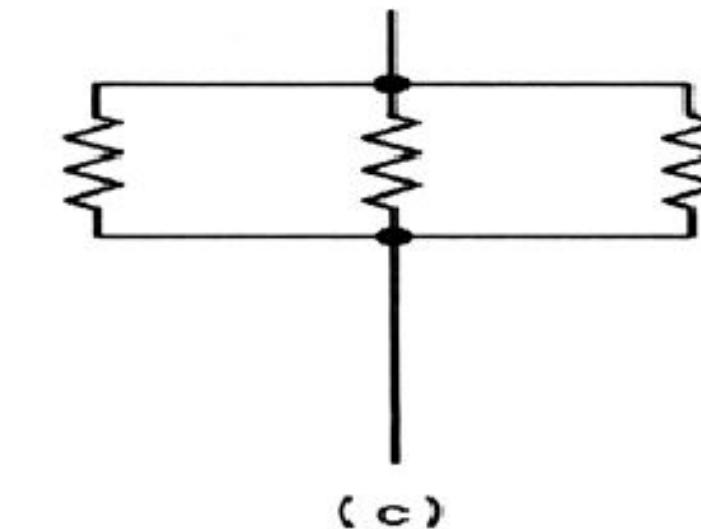


(c)


**Series-Parallel**

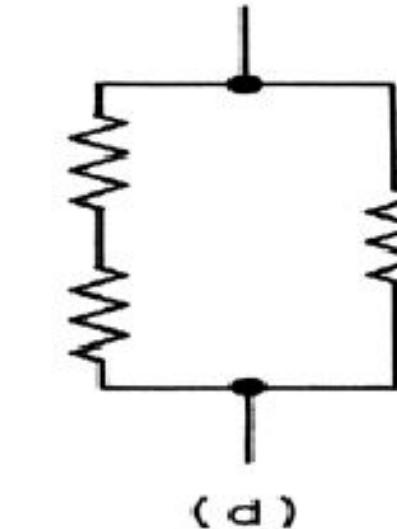

(d)

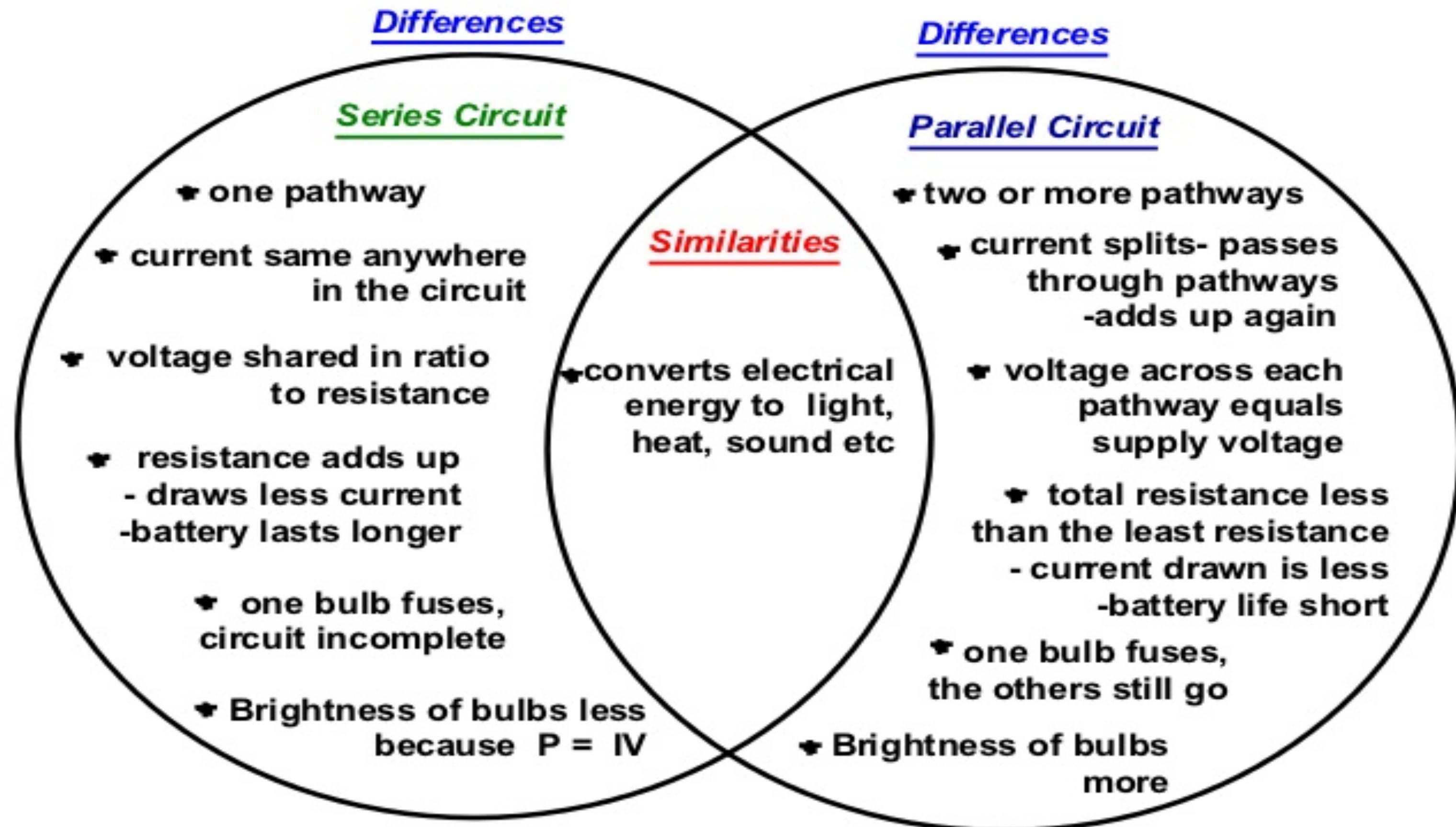

## Voltage Division Rule

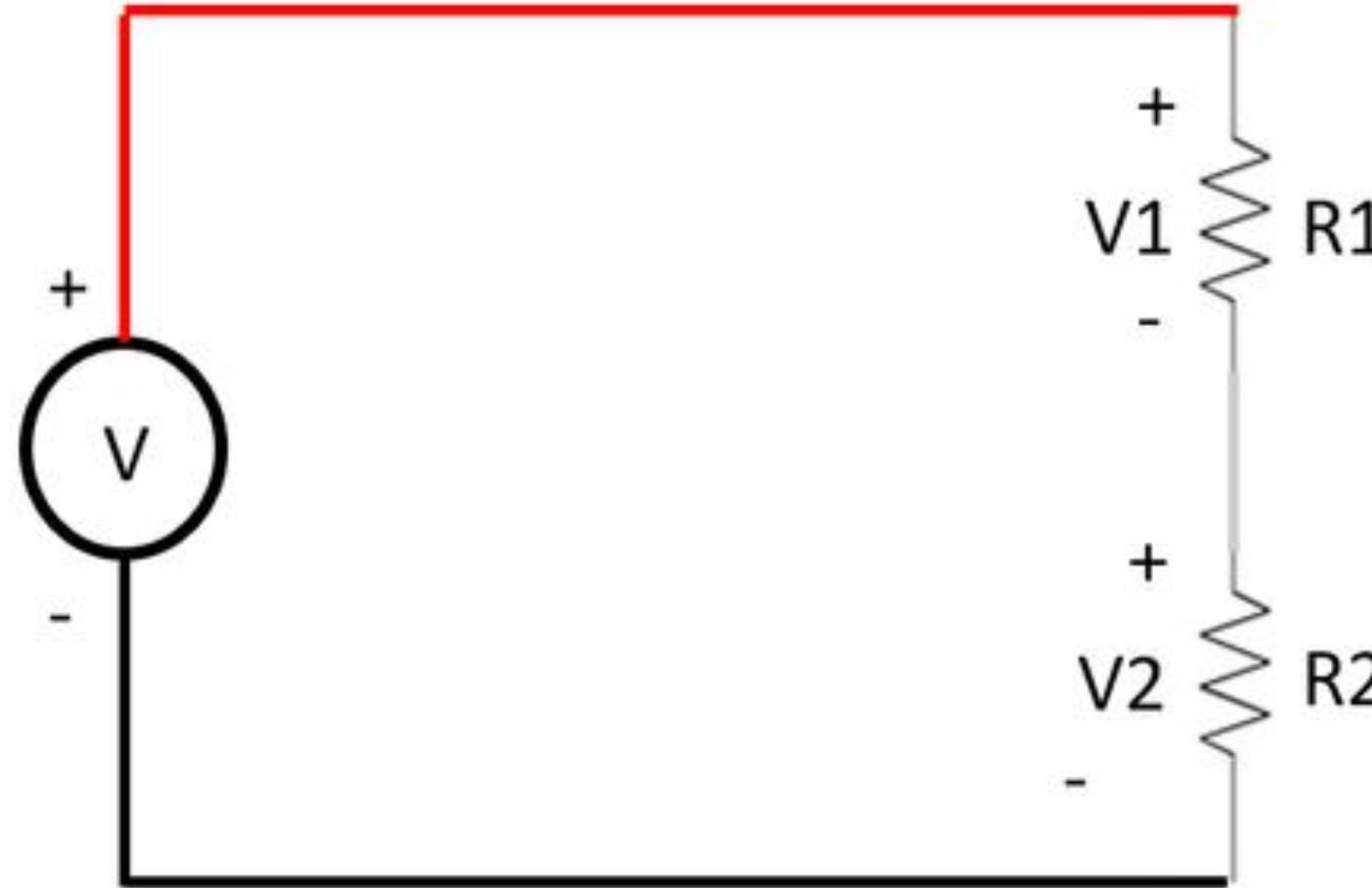

$V_1$  is the voltage across  $R_1$ :


$$V_1 = \frac{R_1}{R_1 + R_2} * V$$

$V_2$  is the voltage across  $R_2$ :

$$V_2 = \frac{R_2}{R_1 + R_2} * V$$

## Voltage division rule

## Current Division Rule

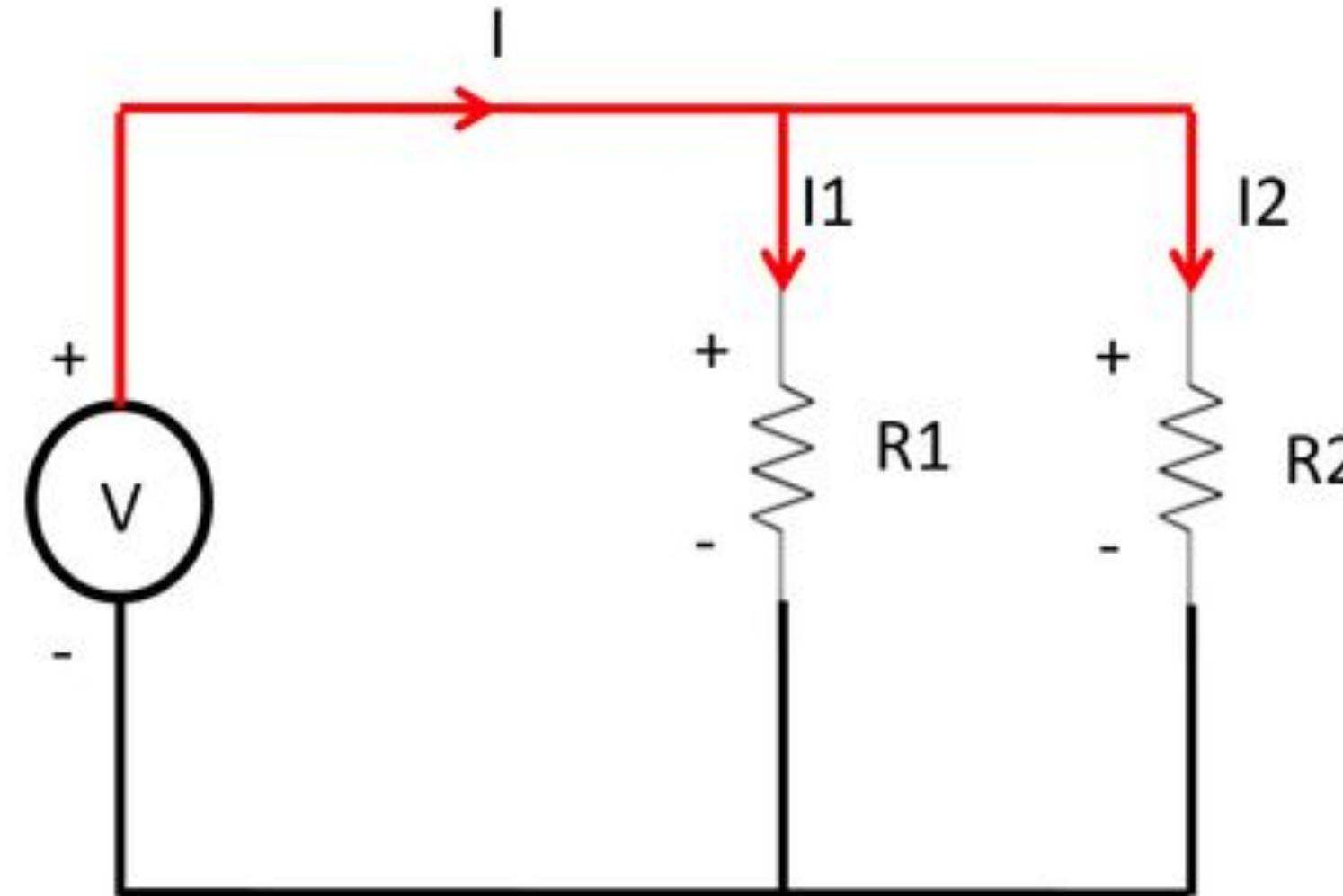

$I_1$  is the current following through  $R_1$ :


$$I_1 = \frac{R_2}{R_1 + R_2} * I$$

$I_2$  is the current following through  $R_2$ :



$$I_2 = \frac{R_1}{R_1 + R_2} * I$$

## Current division rule


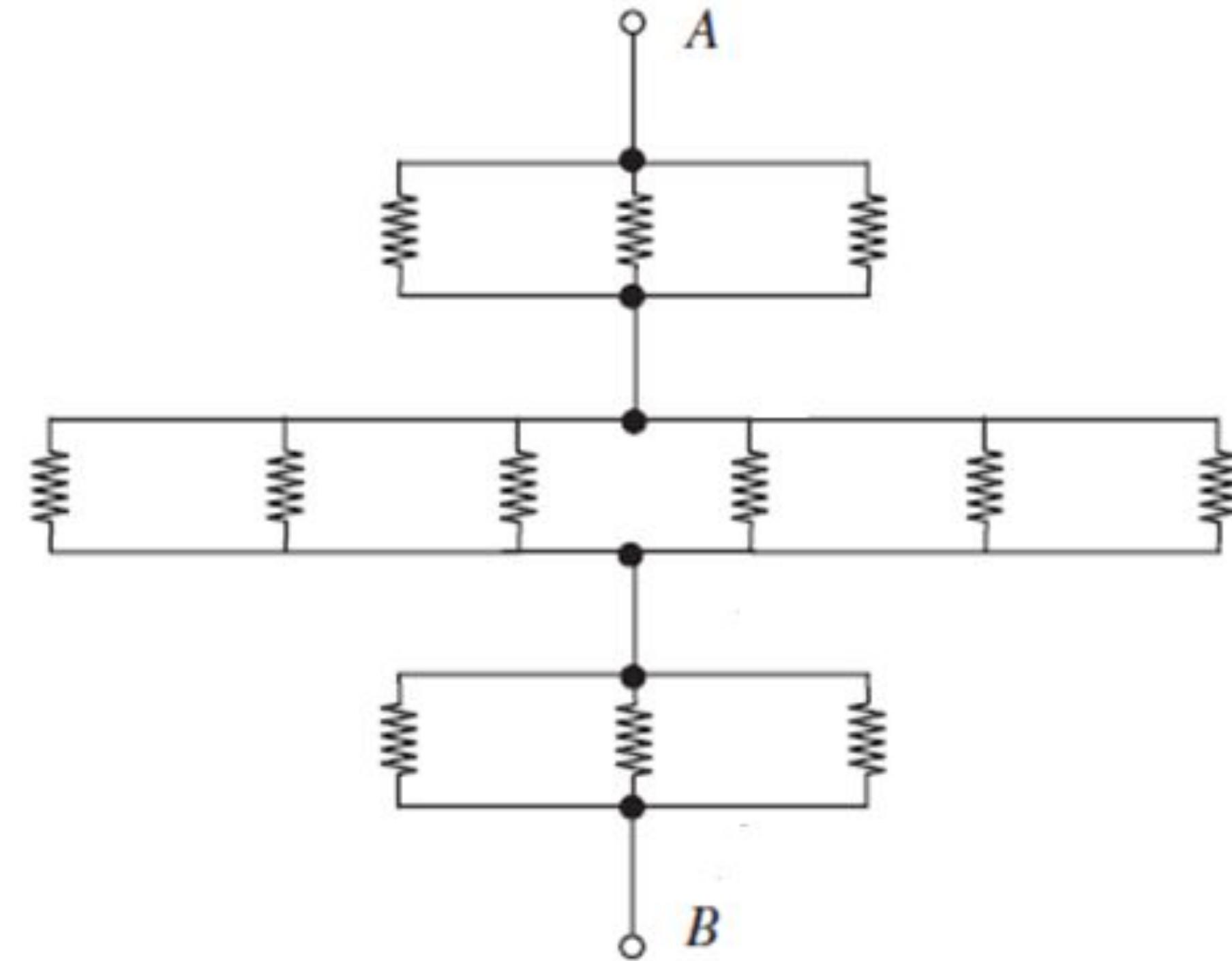
1. Each resistor is of 1Kohm. Calculate equivalent resistance.



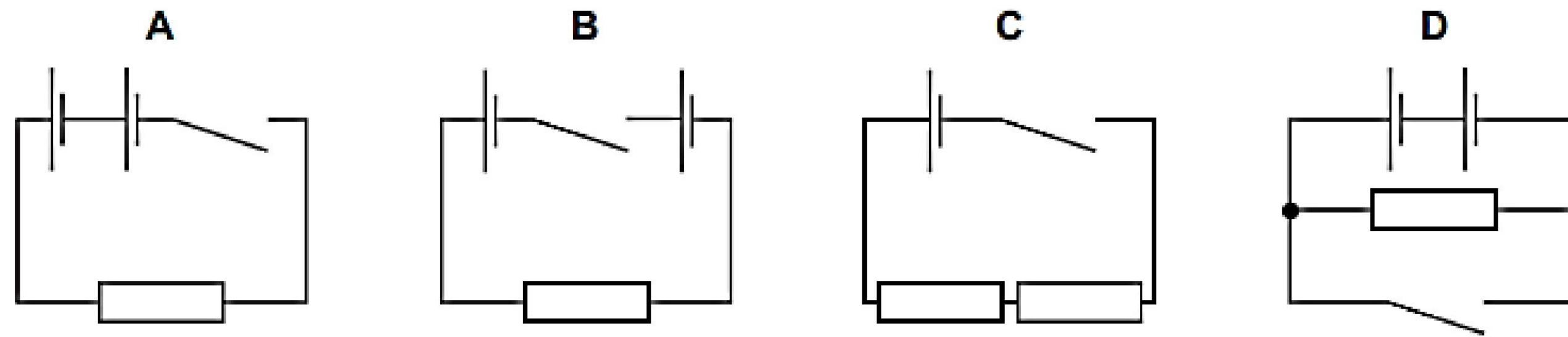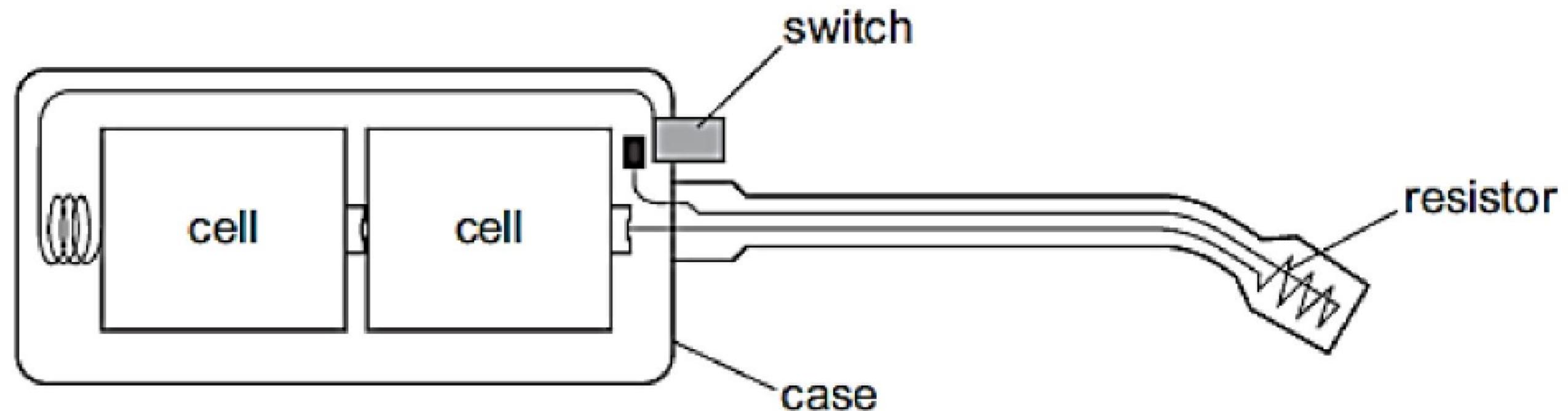
2. The diagram shows the components of a lighter for a gas cool lighter?



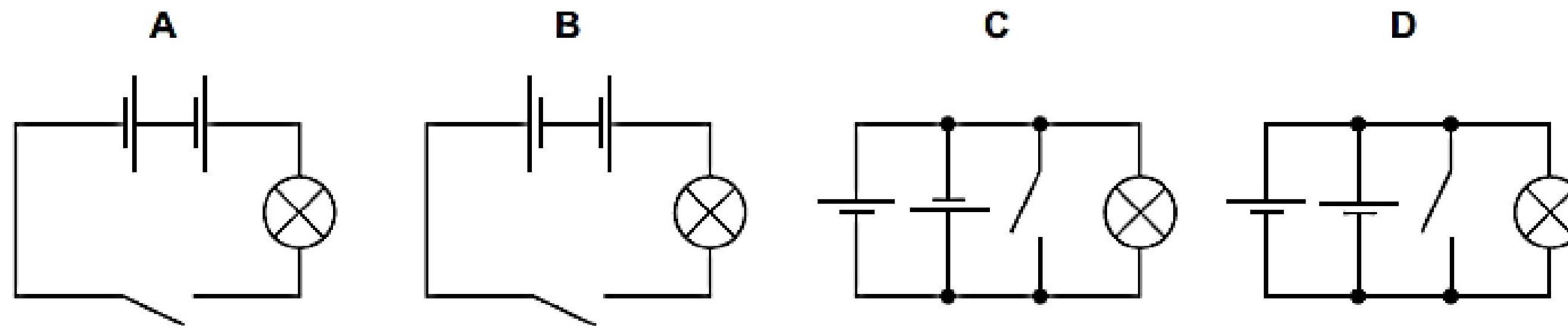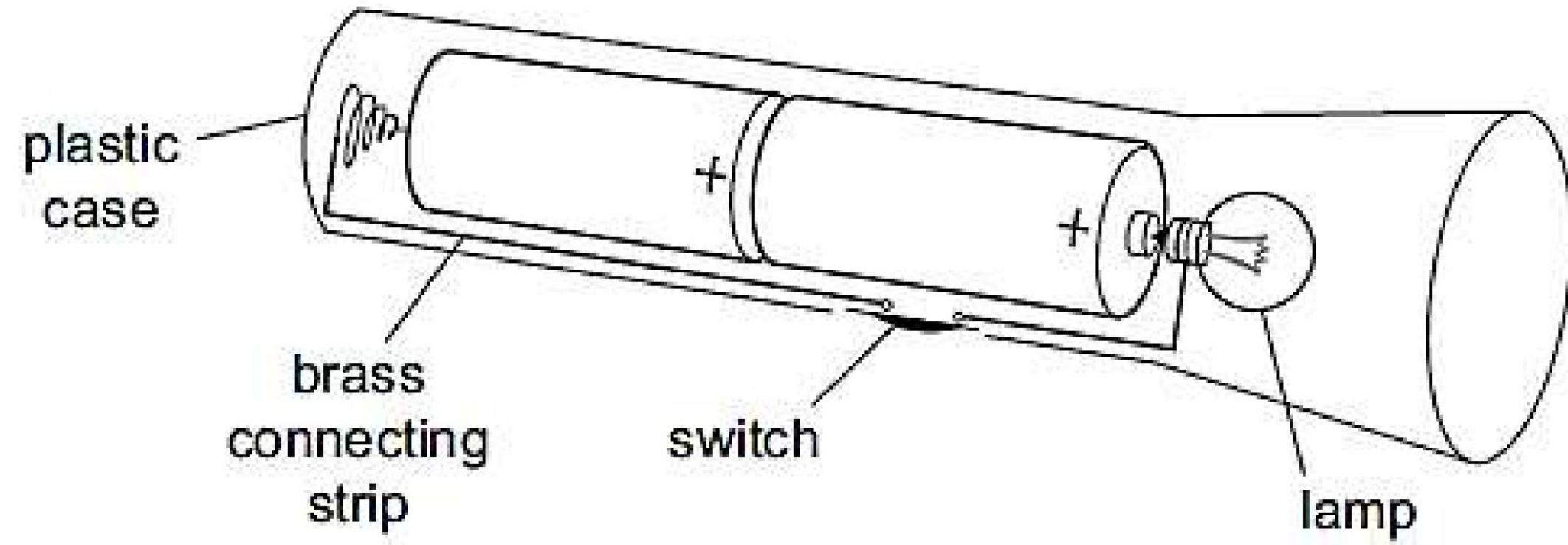3. The diagram shows a torch containing two cells, a switch and a lamp. What is the circuit diagram for the torch?




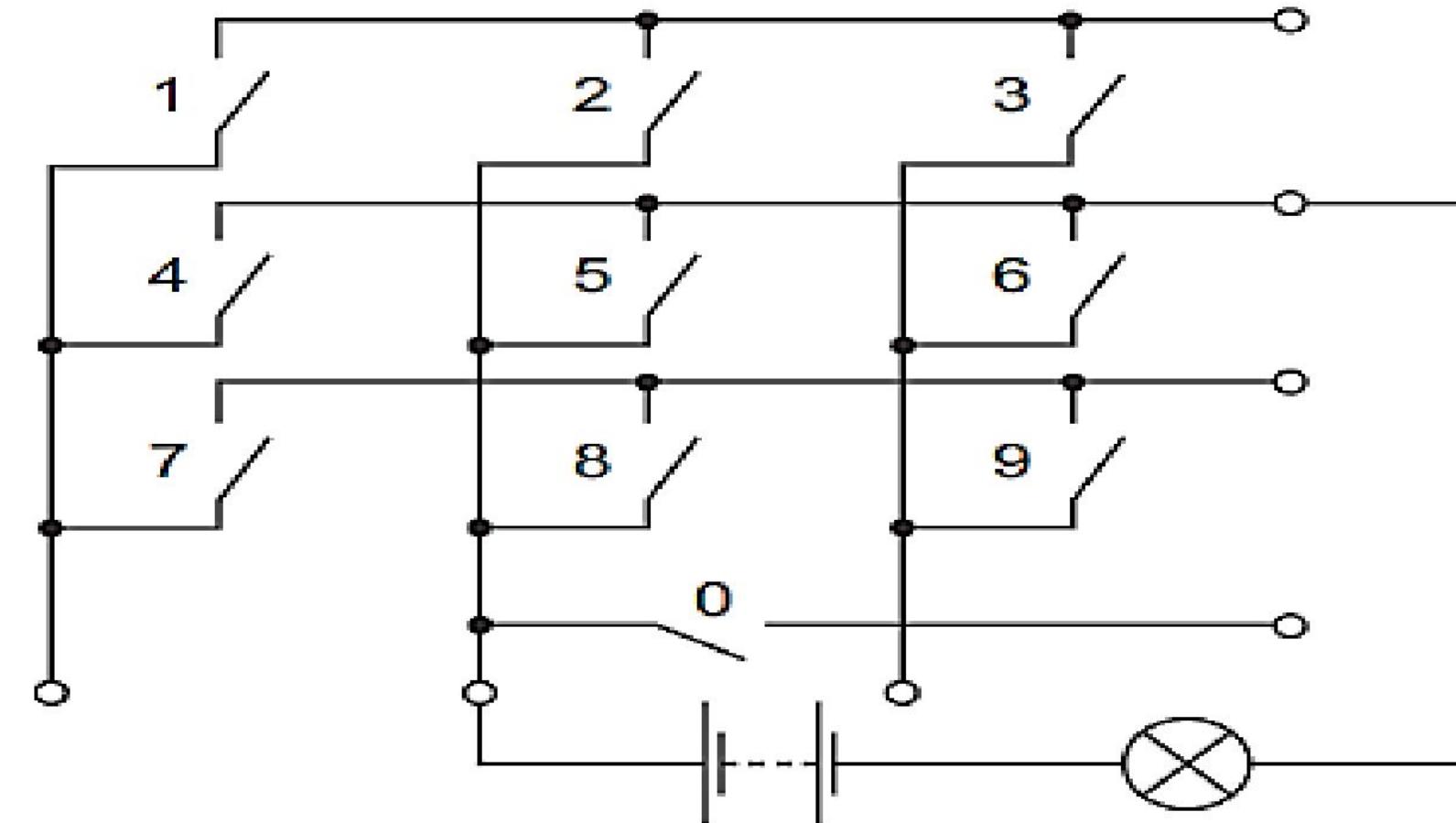4. A student tests the circuit of a press-button telephone with a lamp and a battery. Which single switch can be pressed to make the lamp light?



- A. 0
- B. 1
- C. 5
- D. 6

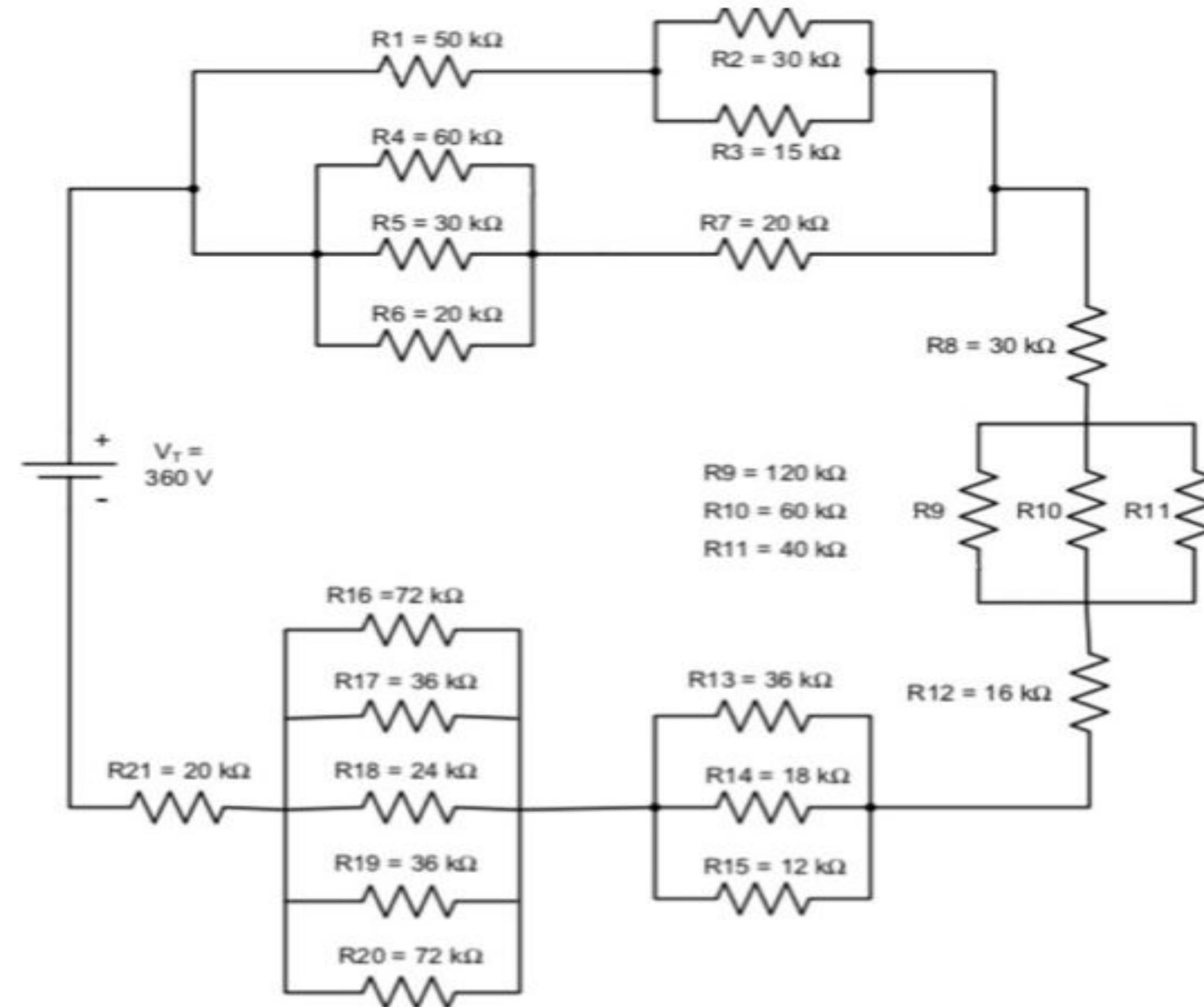5. Calculate the total resistance of the given network and calculate the total current in the circuit.



# NODES, BRANCHES, AND LOOPS

- A **branch** represents a single element such as a voltage source or a resistor
- A **node** is the point of connection between two or more branches
- A **loop** is any closed path in a circuit.
- A network with  $b$  branches,  $n$  nodes, and  $l$  independent loops will satisfy the fundamental theorem of network topology:


$$b = l + n - 1$$

# NODES, BRANCHES, AND LOOPS


- Two or more elements are in **series** if they are cascaded or connected sequentially and consequently carry the same current
- Two or more elements are in **parallel** if they are connected to the same two nodes and consequently have the same voltage across them.



# Example: Find the Nodes

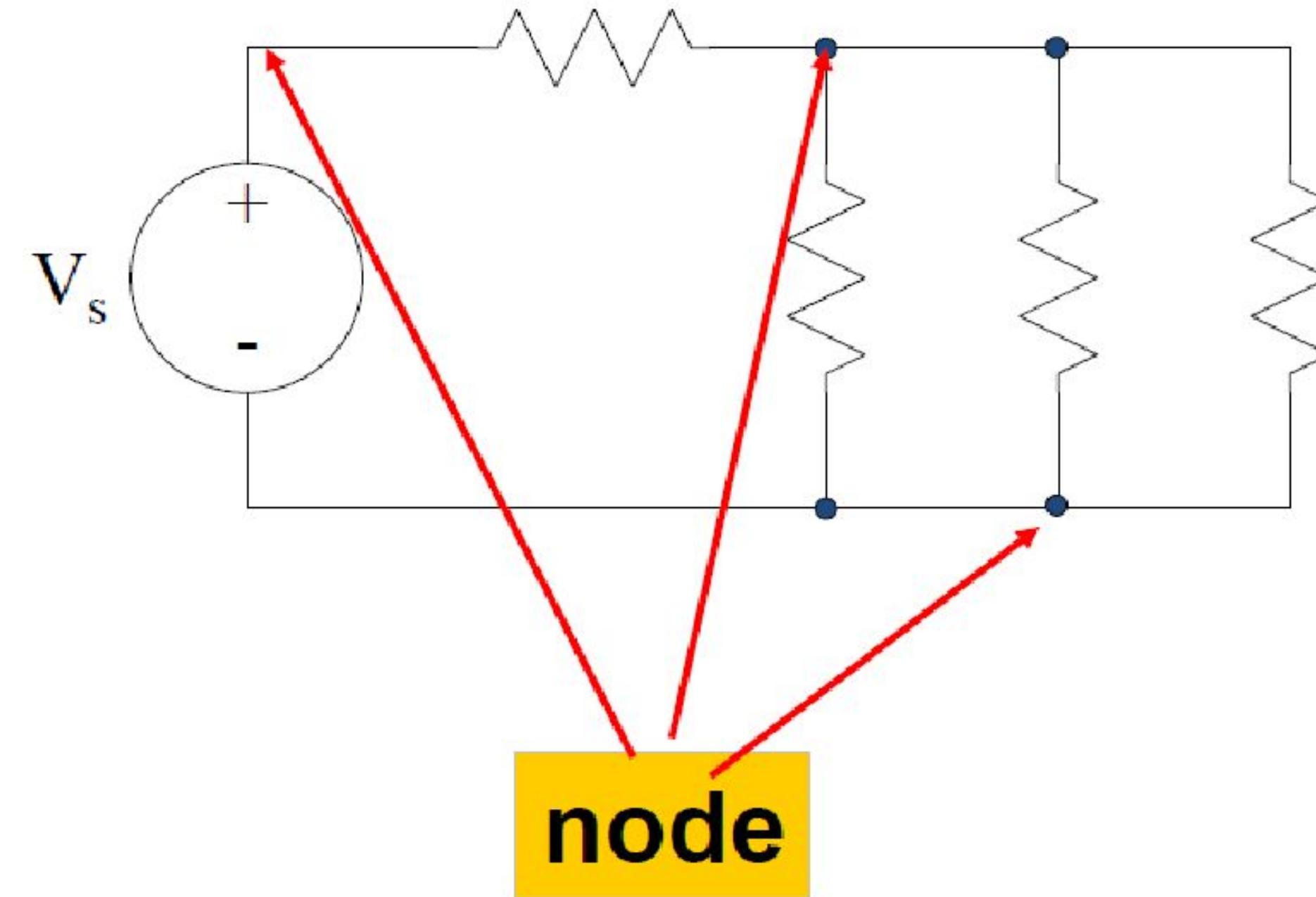

# Example: Find the loops

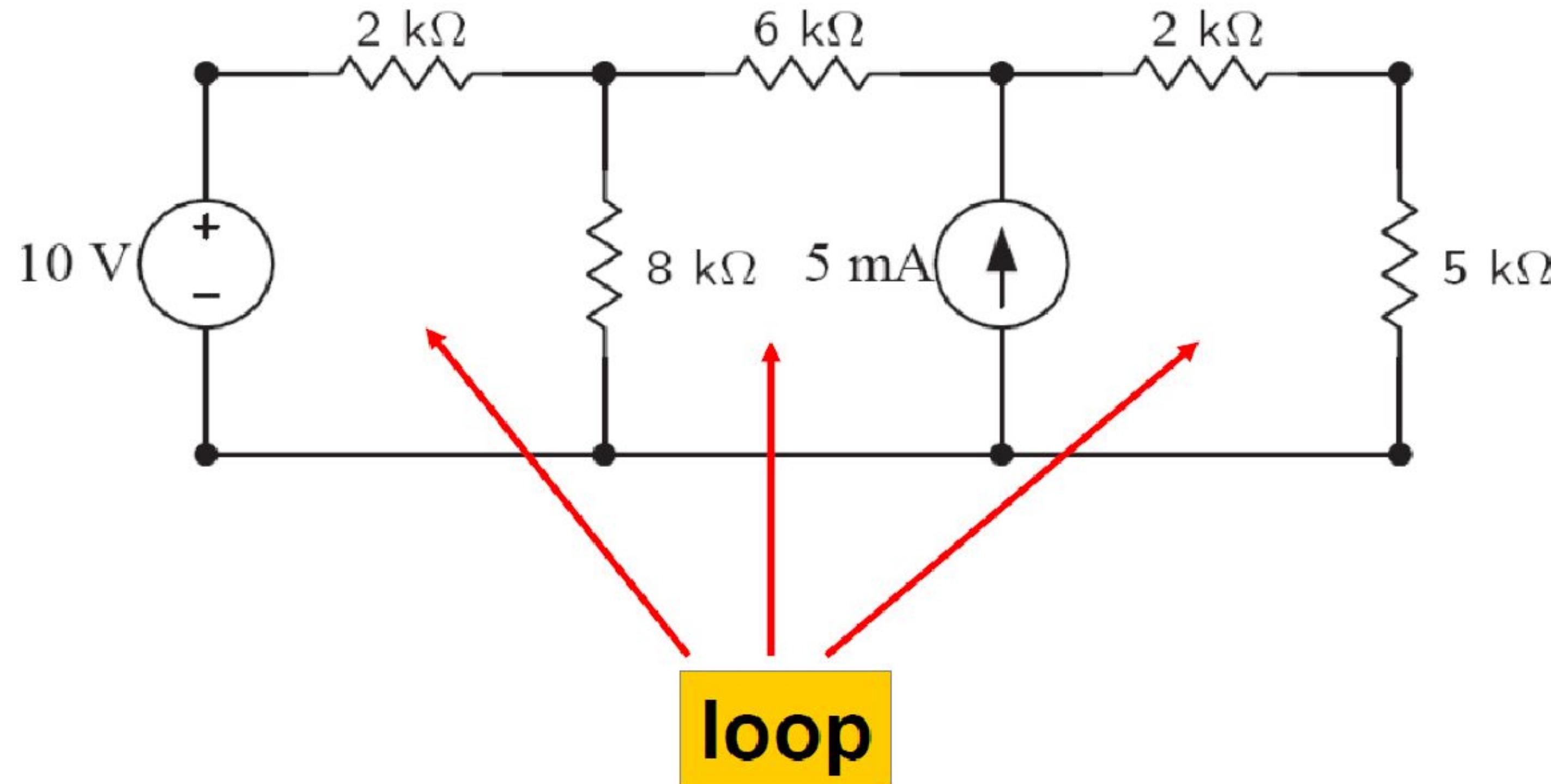


# Kirchhoff's laws

- Kirchoff's current law:-
- This law is also called **Kirchhoff's first law, Kirchhoff's point rule, or Kirchhoff's junction rule** (or nodal rule).
- The principle of conservation of electric charge implies that:
- At any node (junction) in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node, or: The algebraic sum of currents in a network of conductors meeting at a point is zero. Recalling that current is a signed (positive or negative) quantity reflecting direction towards or away from a node, this principle can be stated as:

$$\sum_{k=1}^n I_k = 0$$

- *n* is the total number of branches with currents flowing towards or away from the node.
- The law is based on the conservation of charge whereby the charge (measured in coulombs) is the product of the current (in amperes) and the time (in seconds).

# Cont..

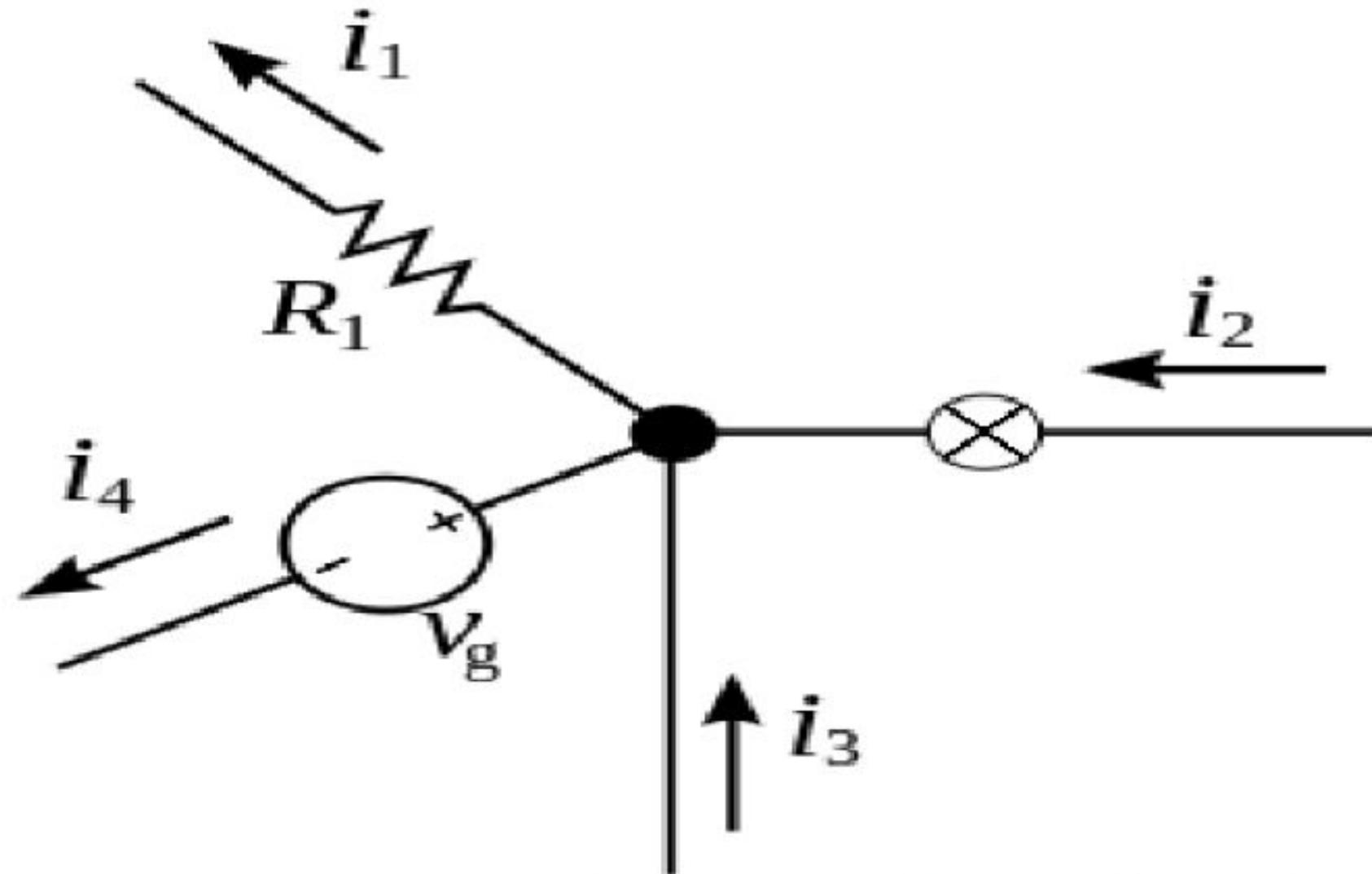

The current entering any junction is equal to the current leaving that junction.  $i_2 + i_3 = i_1 + i_4$




## Kirchoff's voltage law:

This law is also called **Kirchhoff's second law**, **Kirchhoff's loop (or mesh) rule**, and **Kirchhoff's second rule**.

- ✓ The principle of conservation of energy implies that, The directed sum of the electrical potential differences (voltage) around any closed network is zero, or
  - ✓ More simply, the sum of the emfs in any closed loop is equivalent to the sum of the potential drops in that loop, or
  - ✓ The algebraic sum of the products of the resistances of the conductors and the currents in them in a closed loop is equal to the total emf available in that loop.
- Similarly to KCL, it can be stated as:

Cont..

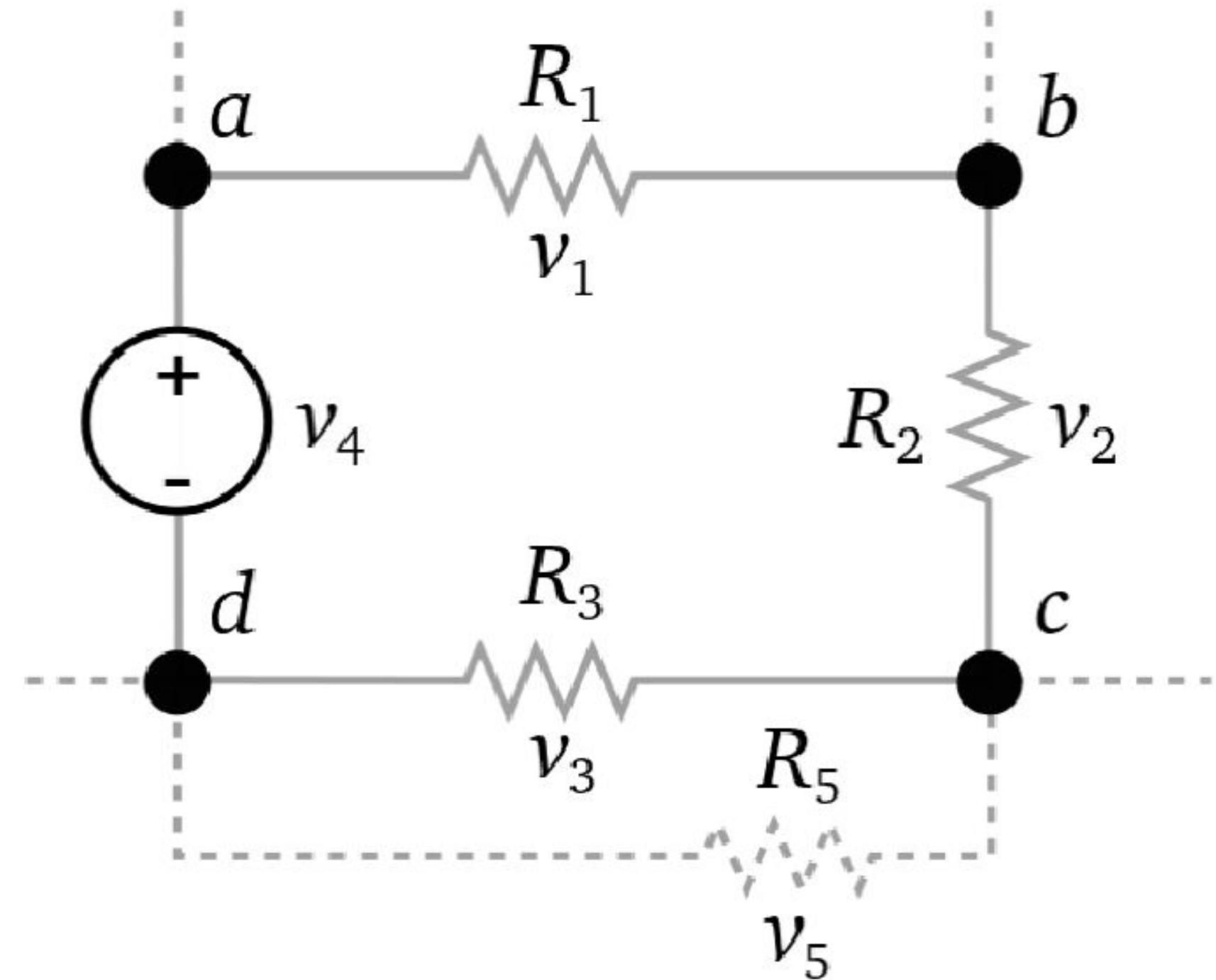

The sum of all the voltages around the loop is equal to zero.

$$v_1 + v_2 + v_3 - v_4 = 0$$

## Cont..

- Here,  $n$  is the total number of voltages measured. The voltages may also be complex:
- This law is based on the conservation of energy whereby voltage is defined as the energy per unit charge. The total amount of energy gained per unit charge must equal the amount of energy lost per unit charge, as energy and charge are both conserved.


# Methods of Analysis

- Introduction
- Nodal analysis
- Nodal analysis with voltage source
- Mesh analysis
- Mesh analysis with current source
- Nodal and mesh analyses by inspection
- Nodal versus mesh analysis


# Mesh Analysis

- Mesh analysis: another procedure for analyzing circuits, applicable to **planar** circuit.
- A **Mesh** is a loop which does not contain any other loops within it

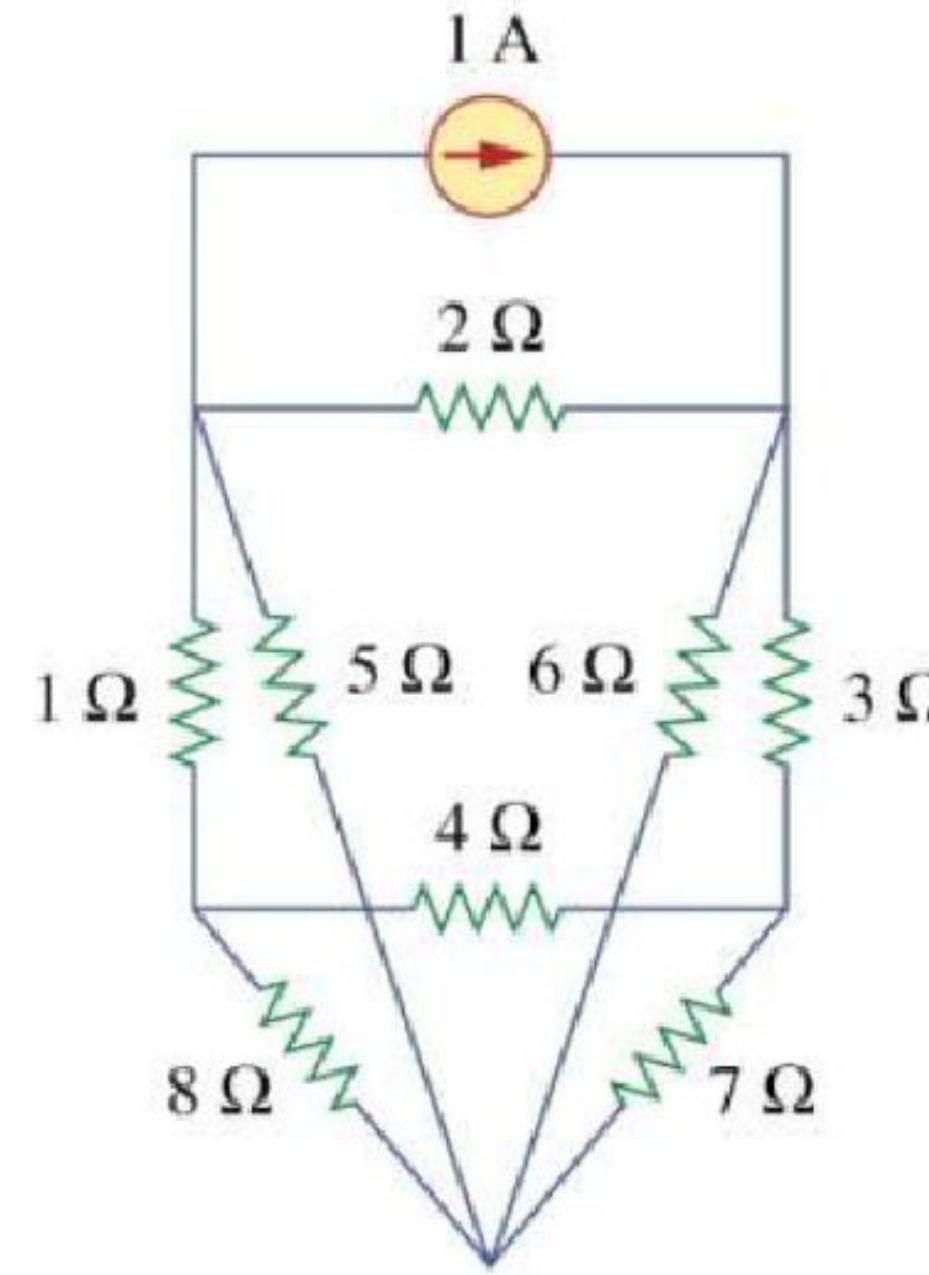- (a) A Planar circuit with crossing branches,  
(b) The same circuit redrawn with no crossing branches.



(a)

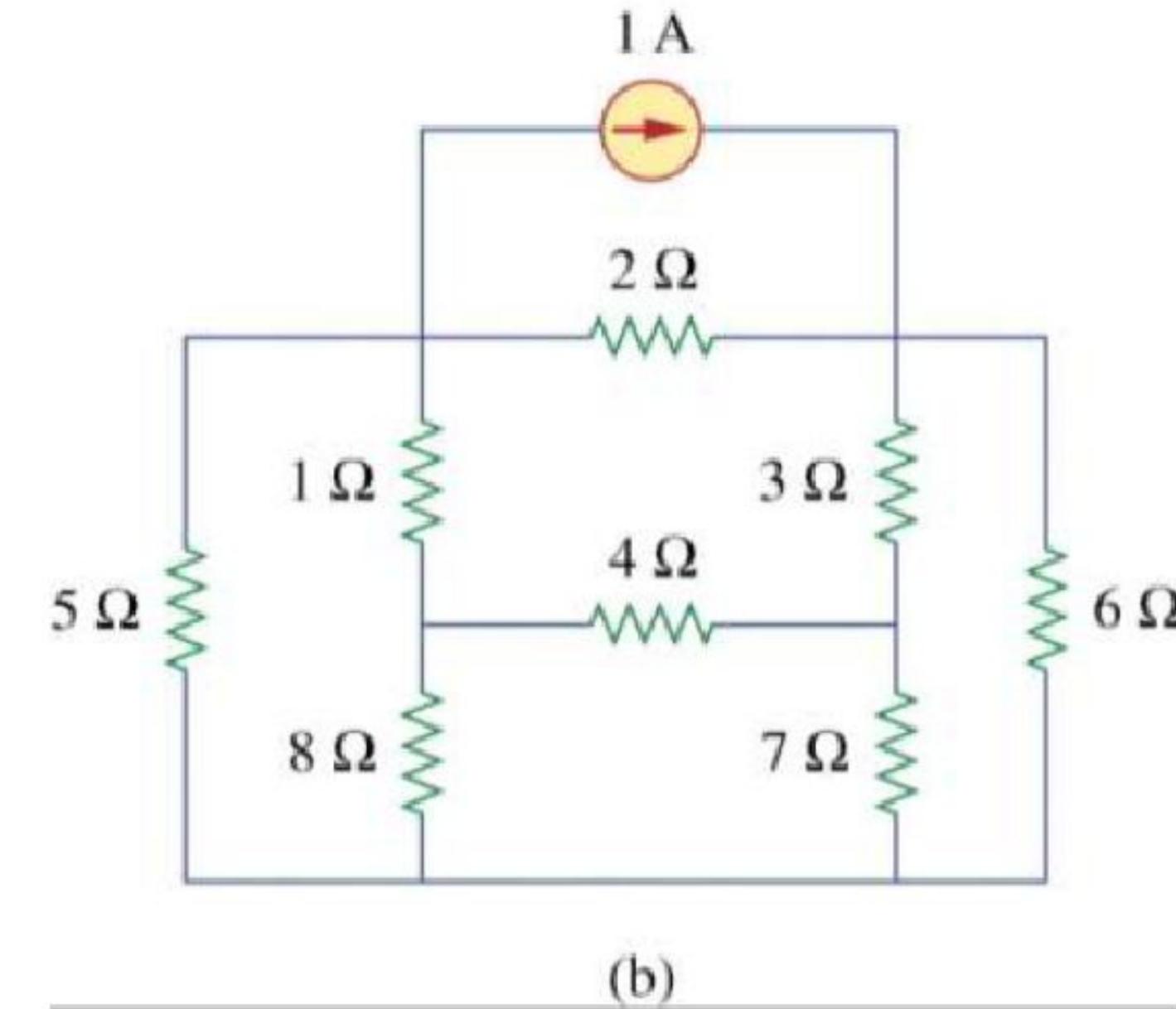


(b)

- **Steps to Determine Mesh Currents:**
  1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the n meshes.
  2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
  3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.

# Figure:

A circuit with two meshes.

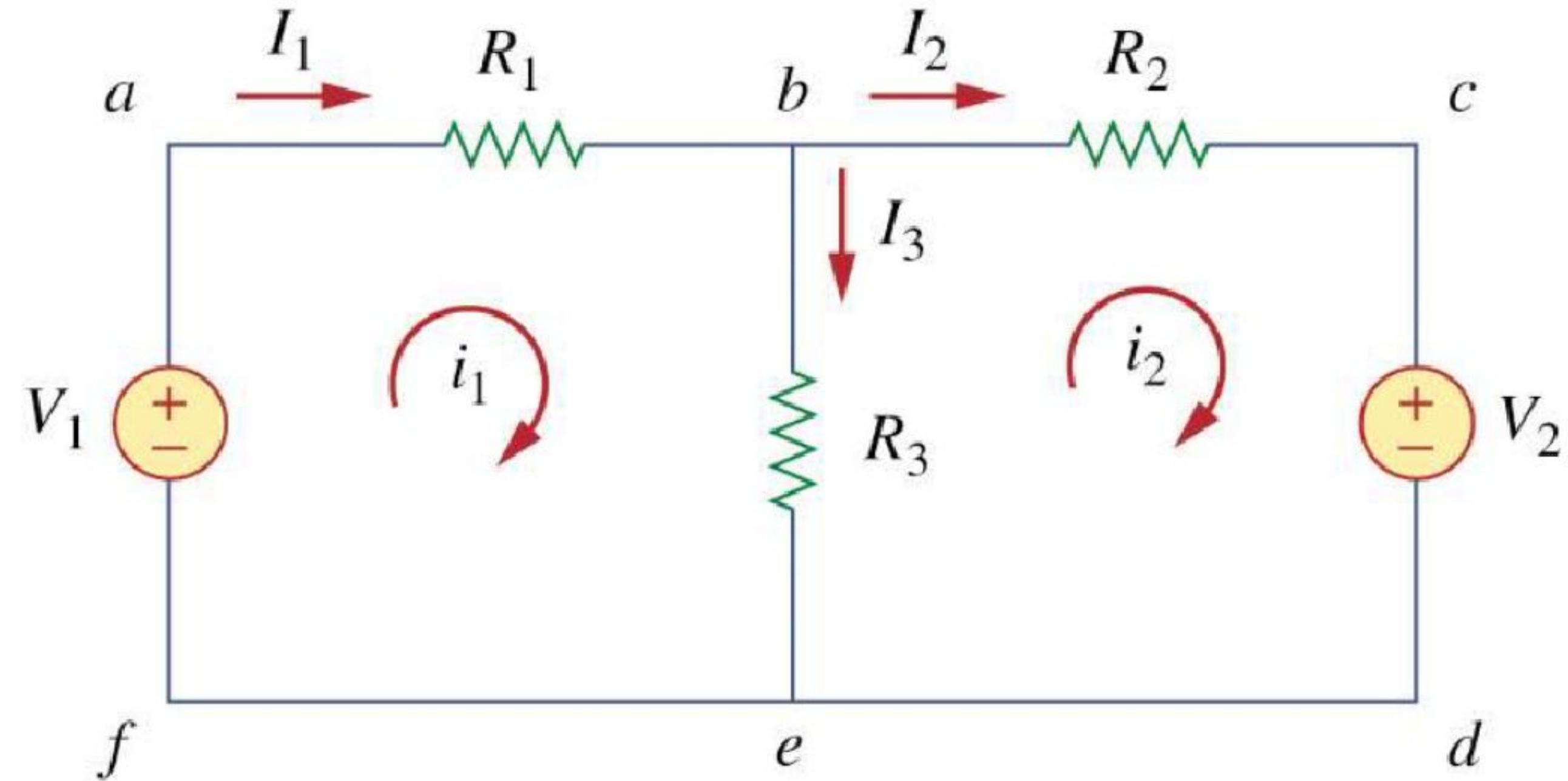

- Apply KVL to each mesh. For mesh 1,

$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$(R_1 + R_3)i_1 - R_3 i_2 = V_1$$

- For mesh 2,

$$R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0$$

$$-R_3 i_1 + (R_2 + R_3)i_2 = -V_2$$


- Solve for the mesh currents.

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

- Use  $i$  for a mesh current and  $I$  for a branch current. It's evident from Fig. 3.17 that

$$I_1 = i_1, \quad I_2 = i_2, \quad I_3 = i_1 - i_2$$

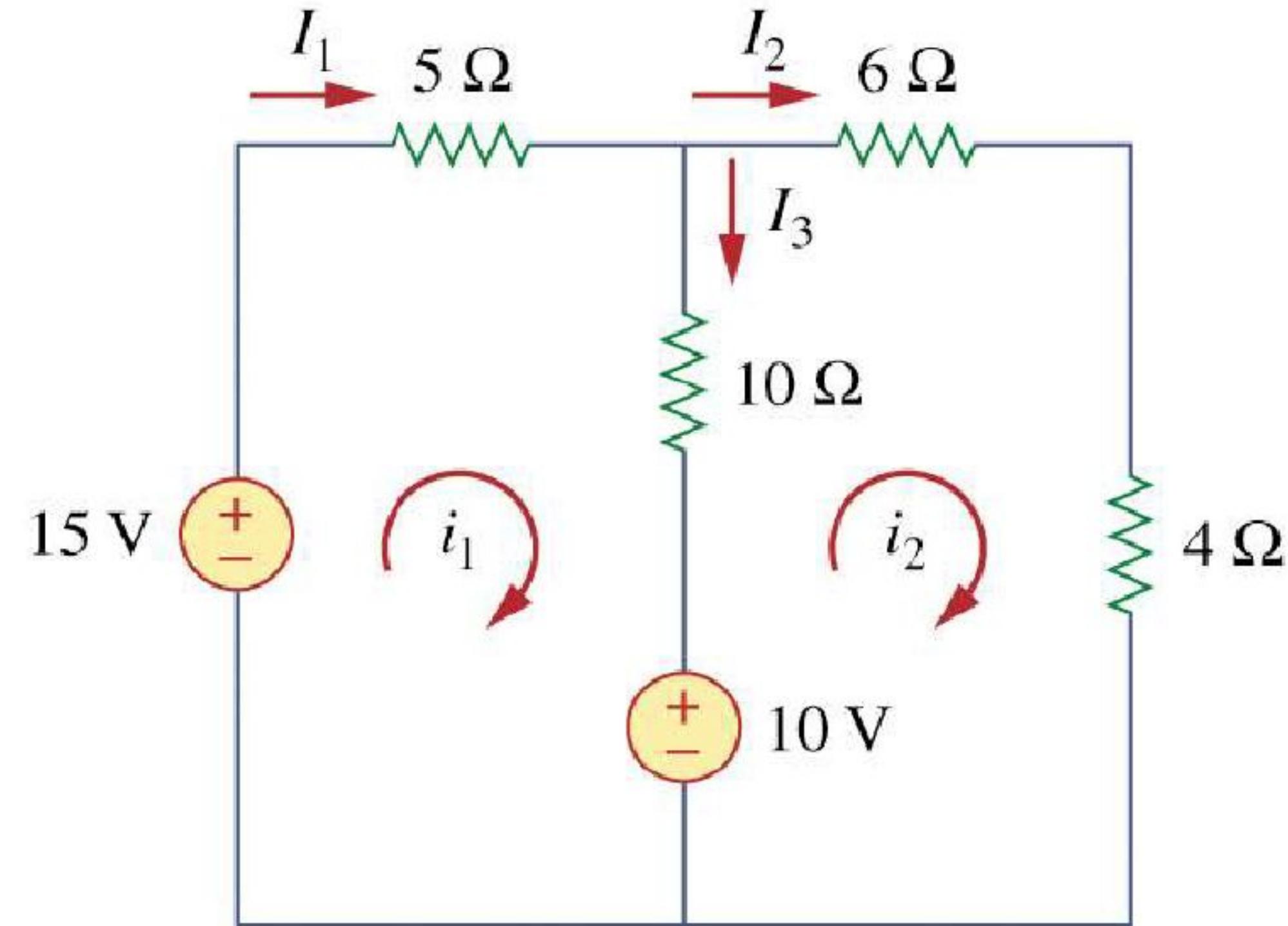- Find the branch current  $I_1$ ,  $I_2$ , and  $I_3$  using mesh analysis.



- For mesh 1,

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

$$3i_1 - 2i_2 = 1$$


- For mesh 2,

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

$$i_1 = 2i_2 - 1$$

- We can find  $i_1$  and  $i_2$  by substitution method or Cramer's rule. Then  $I_1 = i_1$ ,  $I_2 = i_2$ ,  $I_3 = i_1 - i_2$

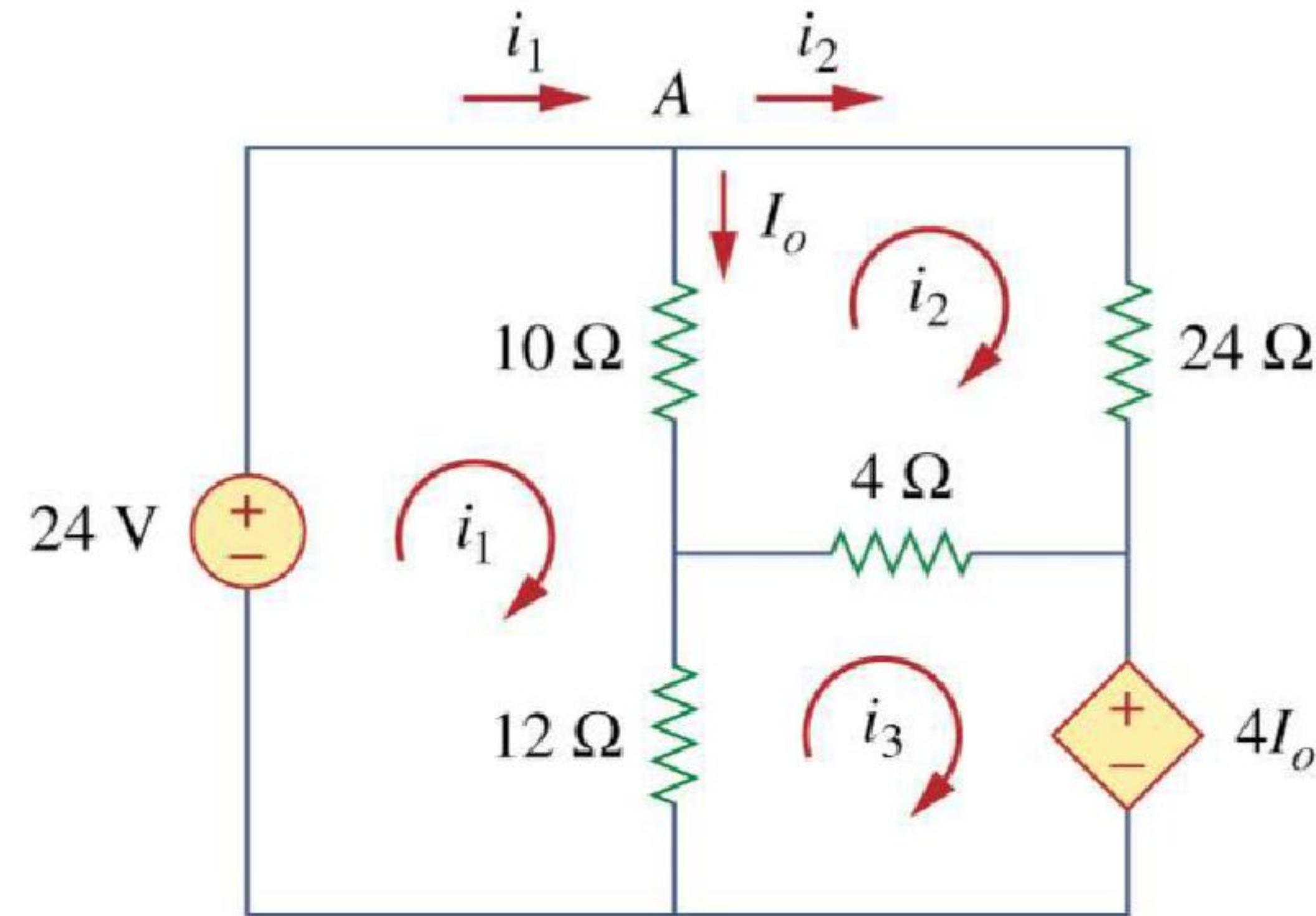- Use mesh analysis to find the current  $I_o$  in the circuit.



- Apply KVL to each mesh. For mesh 1,

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$\boxed{11i_1 - 5i_2 - 6i_3 = 12}$$

- For mesh 2,

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$\boxed{-5i_1 + 19i_2 - 2i_3 = 0}$$

- For mesh 3,

$$4I_0 + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

At node A,  $I_0 = I_1 - i_2$ ,

$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$-i_1 - i_2 + 2i_3 = 0$$


- In matrix form become

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

we can calculate  $i_1$ ,  $i_2$  and  $i_3$  by Cramer's rule, and find  $I_0$ .

# Mesh Analysis with Current Sources


A circuit with a current source.

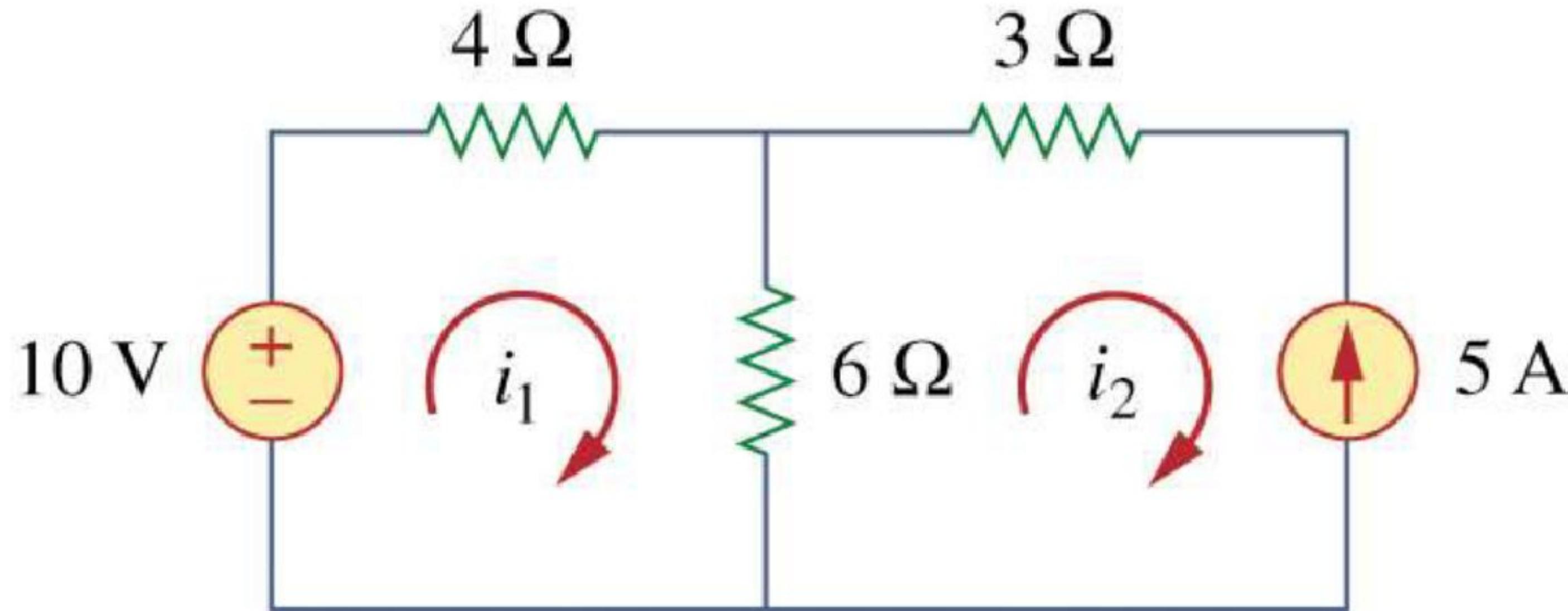

- Case 1
  - Current source exist only in one mesh  
 $i_1 = -2A$
  - One mesh variable is reduced
- Case 2
  - Current source exists between two meshes, a super-mesh is obtained.

## Equivalent Circuits:-

### Source Transformation

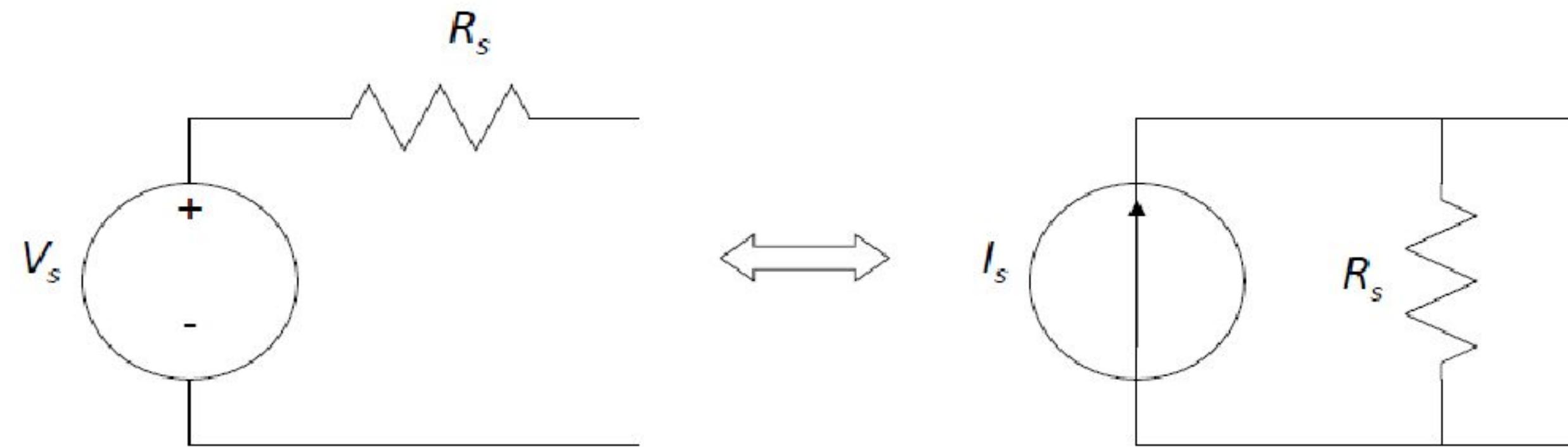

$$V_s = R_s I_s$$

$$I_s = \frac{V_s}{R_s}$$



**RV College of  
Engineering**

*Go, change the world*

---



**RV College of  
Engineering**

*Go, change the world*

---



**RV College of  
Engineering**

*Go, change the world*

---