



**DEPARTMENT OF**  
**ELECTRICAL AND ELECTRONICS ENGINEERING**

Date	7 <sup>th</sup> Sep 2023	Maximum Marks	50
Course Code	22ES24D	Duration	90 Mins
Sem	II Semester	IMPROVEMENT CIE	

**Basics of Electrical Engineering**

Q.No	IMPROVEMENT CIE	Marks	COs	BT
1. a)	Explain the advantages of 3 phase circuits over single phase circuits.	4	2	2
b)	Arrive at the Voltage and Current expressions for 2 types of connections of a 3-phase circuit.	6	2	3
2. a)	Three identical coils are connected in star to a 400V, 3-phase, 50Hz supply and each coil takes 300W of power. If the power factor is 0.8. Calculate i) line current ii) impedance and iii) resistance and inductance of each coil.	4	3	3
b)	Prove that, the readings of the wattmeter's are in terms of $\cos(30+\phi)$ and $\cos(30 - \phi)$ while measuring the power of a three-phase circuit.	6	2	3
3. a)	A three-phase delta connected motor operating on a 400 V supply is delivering 25 HP at an efficiency of 0.87 and power factor of 0.42. Calculate the line current, phase current and the readings of two-watt meters connected to measure the input. Assume, 1hp=746 w.	6	3	4
b)	Input power to a three phase circuit was measured by two wattmeter method. The readings were 3kW and 1.5kW. Determine the total power consumed and the power factor of the balanced three phase circuit.	4	3	3
4. a)	Explain the concept of power transmission and distribution through block diagrams.	4	4	2
b)	Estimate the monthly electricity bill for the subsequent load fitted in an electrical installation.  (a) 15 lamps 50 watts each working 4 hours/ day. (b) 4 ceiling fans 100 watts each working 8 hours/day. (c) 2 kw heater working 2 hours/day. (d) Water pump of 0.5 HP runs for 2 hours per day  Rate of charges for light and fans is 3.5 Rs / unit and heater and motor 4 Rs/unit.	6	4	3
5. a)	Describe the Working principle of Fuse and Miniature circuit breaker (MCB), Mention its merits and demerits.	5	4	3
b)	What is Electric Shock? What is the effect of Electric Shock on Human body? Mention the Precautions against Electric Shock.	5	4	2

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--

**RV COLLEGE OF ENGINEERING®**  
 (An Autonomous Institution affiliated to VTU)  
 I / II Semester B. E. Examinations Oct/Nov 2023  
 Common to all programs


### BASICS OF ELECTRICAL ENGINEERING

*Time: 03 Hours**Maximum Marks: 100*

*Instructions to candidates:*

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. Question number 2 is compulsory. Choose any one full question from 3 or 4, 5 or 6, 7 or 8 and 9 or 10.

#### PART-A

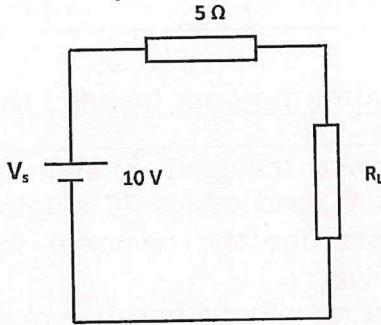1	1.1	The maximum power drawn by the load $R_L$ in Fig. 1.1 will be?	
			
		Fig. 1.1	02
	1.2	The resistance of the two coils is 250 ohms when connected in series, and 6 ohms when connected in parallel. Determine the individual resistances of the two coils.	02
	1.3	Define <ol style="list-style-type: none"> <li>Form factor</li> <li>Peak factor.</li> </ol>	02
	1.4	A 50 – Hz sinusoidal current has peak factor 1.4 and form factor 1.1. Its average value is 20A. The instantaneous value of current is 15A at $t = 0$ . Write the equation of current.	02
	1.5	In a balanced 3-phase system, power is measured by two wattmeters and the ratio of two wattmeter readings is 2:1. Determine the power factor of the system.	02
	1.6	State the differences between a core-type and a shell-type transformer.	02
	1.7	Why the rotor slots in a three-phase induction motor are purposely given a slight skew?	02
	1.8	List the types of single-phase induction motor.	02
	1.9	Mention the characteristics of fuse.	02
	1.10	What is an electric shock? Write safety precautions to avoid electric shock.	02

## PART-B

2 a	<p>Use Thevenin's theorem to determine the current through and the voltage across the <math>25\Omega</math> resistor given in Fig. 2a.</p>	06
b	<p>A network is arranged as shown in Fig. 2b. Determine the current in each resistance.</p>	06
c	<p>State and prove maximum power transfer theorem for dc networks.</p>	06 04
3 a	<p>What is an impedance triangle? Explain and draw the impedance triangle for a series <math>RL</math> and series <math>RC</math> single-phase a.c. circuits. Also, deduce an expression for the resonant frequency of a series <math>RLC</math> single-phase a.c. circuit.</p>	08
b	<p>A sinusoidal alternating voltage has an r.m.s value of <math>100V</math>. Find the</p> <ul style="list-style-type: none"> <li>i) Instantaneous value of <math>0.0125s</math> after passing through maximum positive value and</li> <li>ii) The time measured from a positive maximum value when the instantaneous voltage is <math>70.7V</math>.</li> </ul>	08
<b>OR</b>		
4 a	<p>Derive the expression for Average value and rms value of a sinusoidal waveform.</p>	08
b	<p>A coil and a non-inductive resistor are connected in series across a <math>200V, 50\text{ Hz}</math> supply. The voltage across the coil and resistor are <math>120V</math> and <math>140V</math> respectively. If the supply current is <math>0.5A</math>, calculate:</p> <ul style="list-style-type: none"> <li>i) The resistance and inductance of the coil</li> <li>ii) The power dissipated in the coil</li> <li>iii) The power factor of the coil</li> <li>iv) The power factor of the circuit.</li> </ul>	08
5 a	<p>The three arms of a three-phase load each comprise an inductor of resistance <math>25\Omega</math> and of inductance <math>0.15\text{ H}</math> in series with a <math>120\mu F</math> capacitor. The supply is <math>415V, 50\text{ Hz}</math>. Calculate the line current and the total power in watts, when the three arms are connected in:</p> <ul style="list-style-type: none"> <li>i) star</li> <li>ii) delta.</li> </ul>	08

b	<p>Give reasons:</p> <ul style="list-style-type: none"> <li>i) Copper loss is called as variable loss and iron loss is called as Constant loss.</li> <li>ii) The rating of transformer is in <math>kVA</math>.</li> <li>iii) Transformer cannot be excited by <math>DC</math> supply.</li> </ul>	08
	<b>OR</b>	
6 a	A single-phase transformer working at unity power factor has an efficiency of 90% at both half load and the full-load of 500W. Determine the efficiency at 75% full load and the maximum efficiency.	08
b	Derive the relationship between the line and phase values of voltage in a three-phase star connected system with the aid of a phasor diagram.	08
7 a	Explain the concept of rotating magnetic field of an Induction motor. Draw the torque-slip characteristics of a three-phase induction motor.	08
b	Describe the construction of a single-phase induction motor with the aid of a diagram.	08
	<b>OR</b>	
8 a	Explain the working principle of a single-phase induction motor. Discuss why single-phase induction motors do not have a starting torque.	08
b	Compare between Squirrel cage and slip ring induction motor. A 12-pole, 3-phase alternator is coupled to an engine running at 500 r.p.m. It supplies an induction motor which has a full-load speed of 1440 r.p.m Find the slip and the number of poles of the motor.	08
9 a	<p>In a residential house, the following load are connected:</p> <ul style="list-style-type: none"> <li>i) Six lamps of 40W each, switched on for 5 hours a day.</li> <li>ii) Two fans of 60W each, switched no for 12 hours a day.</li> <li>iii) One 100 W heater working for 2 hours per day.</li> <li>iv) One refrigerator of 250W working for 10 hours per day.</li> </ul> <p>If each unit of energy costs Rs. 1.90, what will be the total cost in the month of September?</p>	08
b	Illustrate the concept of power generation, transmission, and distribution system with block diagrams.	08
	<b>OR</b>	
10 a	What are the types of earthing? Explain with diagram any one type of earthing.	08
b	Explain the working of Miniature Circuit Breaker with neat diagram. Mention its merits and demerits.	08



Question No	PART - A	Marks
1.1	$P_{L(\max)} = \frac{V_{th}^2}{4R_{th}} = \frac{10 \times 10}{4 \times 5} = 5W$	<u>2M</u>
1.2	$R_1 + R_2 = 25 \Rightarrow R_2 = 25 - R_1$ $\frac{R_1 R_2}{R_1 + R_2} = 6 \Rightarrow \frac{R_1 R_2}{25} = 6 \Rightarrow R_1 R_2 = 150$ $\Rightarrow R_1(25 - R_1) = 150 \Rightarrow 25R_1 - R_1^2 = 150$ $\Rightarrow R_1^2 - 25R_1 + 150 = 0 \Rightarrow R_1^2 - 30R_1 + 5R_1 + 150 = 0$ $\Rightarrow R_1(R_1 - 30) + 5(R_1 - 30) = 0 \Rightarrow (R_1 - 30)(R_1 + 5) = 0$ $R_1 = 15\Omega ; R_2 = 10\Omega$ or $R_1 = 10\Omega ; R_2 = 15\Omega$	<u>2M</u>
1.3	<u>Form factor</u> for a particular waveform is defined as the ratio of the rms value to the average value. $k_f = \frac{\text{r.m.s Value}}{\text{average value}}$ <u>Peak factor</u> for a given waveform is defined as the ratio of the peak value and the rms value.	<u>1M</u>
1.4	$k_f = 1.1 = \frac{\text{RMS value}}{\text{average value}} \Rightarrow \text{RMS value} = 22A$ $k_p = 1.4 = \frac{\text{peak value}}{\text{rms value}} \Rightarrow \text{peak value} = 30.8A$ $\omega = 2\pi f = 2 \times 3.14 \times 50 = 314$ $I = I_0 \sin(\omega t + \phi) \Rightarrow 15 = 30.8 \sin(\phi)$ $\Rightarrow \sin \phi = 0.487 \Rightarrow \phi = 29.14^\circ$ $\Rightarrow I = 30.8 \sin(314t + 29.14^\circ)$	<u>2M</u>

COURSE CODE: 22ES24 | COURSE: Basics of Electrical Engg.

UG

Question No		Marks
1.5	$P_1 = 2P_2 ; \tan\phi = \sqrt{3}$ $\frac{P_1 - P_2}{P_1 + P_2} = \sqrt{3}$ $\frac{2P_2 - P_2}{2P_2 + P_2} = \frac{1}{\sqrt{3}}$ $\Rightarrow \phi = 30^\circ, \cos\phi = \cos 30^\circ = 0.866$ (lag)	<u>1</u> <u>2M</u>
1.6	Differences between a core-type and a shell type Iff (at least 4 differences)	<u>2M</u>
1.7	1. More uniform torque is produced and the noise is reduced during operation. 2. The locking tendency of the rotor is reduced.	<u>2M</u>
1.8	1. Split-phase motor 2. Capacitor-start motor 3. Capacitor-start capacitor run motor 4. Shaded-pole motor	<u>2M</u>
1.9	Characteristics of fuse	<u>2M</u>
1.10	Definition of electric shock Safety precautions to avoid electric shock	<u>1M</u> <u>1M</u>
PART-B.		
2(a)		<u>2M</u>
	$R_{th} = 10 + \frac{10 \times 10}{10 + 10} = 15\Omega$ $V_{th} = 10V$	
		$I = \frac{10}{15 + 25} = 0.25A$ Voltage across 25Ω resistor

COURSE CODE: 22ES24 COURSE: Basics of Electrical Engg.

Question No	Marks
<p>2(b)</p> $3I_1 + 6(I_1 - I_2) = 10 \Rightarrow 9I_1 - 6I_2 + 0I_3 = 10$ $4I_2 + 8(I_2 - I_3) + 6(I_2 - I_1) = 0 \quad \text{--- (1)}$ $\Rightarrow -6I_1 + 18I_2 - 8I_3 = 0 \quad \text{--- (2)}$ $5I_3 + 15 + 8(I_3 - I_2) = 0 \Rightarrow 0I_1 - 8I_2 + 13I_3 = -15 \quad \text{--- (3)}$ $\Delta = 9(18 \times 13 - 64) + 6(-6 \times 13)$ $= 9(234 - 64) + 6(-78) = 1530 - 468$ $\Delta_1 = \begin{bmatrix} 10 & -6 & 0 \\ 0 & 18 & -8 \\ -15 & -8 & 13 \end{bmatrix} = 10(18 \times 13 - 64) + 6(0 - 120)$ $= 10(234 - 64) - 720 \quad \text{2M}$ $\Delta_2 = \begin{bmatrix} 9 & 10 & 0 \\ -6 & 0 & -8 \\ 0 & -15 & 13 \end{bmatrix} = 9(0 - 120) - 10(-78)$ $= -1080 + 780 = -300$ $\Delta_3 = \begin{bmatrix} 9 & -6 & 10 \\ -6 & 18 & 0 \\ 0 & -8 & -15 \end{bmatrix} = 9(-18 \times 15) + 6(90) + 10(48)$ $= -2430 + 540 + 480$ $= -1410$ $I_1 = \frac{\Delta_1}{\Delta} = \frac{980}{1062} = 0.923 \text{ A}$ $I_2 = \frac{\Delta_2}{\Delta} = \frac{-300}{1062} = -0.282 \text{ A}$ $I_3 = \frac{-1410}{1062} = -1.290 \text{ A}$	

Question No		Marks
2(c)	Statement of maximum power transfer theorem Proof	2M 2M
3(a)	Impedance triangle Series RL Series RC Expression for the resonant frequency	2M 2M 2M 2M
	$X_L = X_C \Rightarrow 2\pi f L = \frac{1}{2\pi f C} \Rightarrow f = \frac{1}{2\pi \sqrt{LC}}$	
3(b)	(i) The instantaneous value at $t=0.0175$ s is $V = 141.48 \sin(2\pi \times 50 \times 0.0175) = -100V$ (ii) $t_1 = \frac{1}{120} s$ $t_2 = t_1 - 0.005 = \frac{1}{120} - 0.005 = 3.33 \text{ ms}$	4M 4M
4(a)	Average value of a sinusoidal waveform half-cycle average = $0.637 \times \text{maximum value}$ RMS value of a sinusoidal waveform R.M.S. value = $0.707 \times \text{maximum value}$	4M 4M
4(b)	(i) $R$ = resistance of the non-inductive resistor $R_C$ = resistance of the coil $L$ = inductance of the coil $R = \frac{140}{0.5} = 280 \Omega ; Z_C = \frac{120}{0.5} = 240 \Omega ; Z = \frac{200}{0.5} = 400 \Omega$ $R_C = 42.8 \Omega ; X_L = 236 \Omega \Rightarrow L = 0.752 H$ (ii) $P_C = 0.5^2 \times 42.8 = 10.7 W$ (iii) $\cos \phi_C = \frac{42.8}{240} = 0.178 \text{ lagging}$ (iv) $\cos \phi = \frac{280 + 42.8}{400} = 0.807 \text{ lagging}$	2M 2M 2M 2M

Question No	Marks	
5(a)	<p>(i) in Star:</p> $Z_p = \sqrt{25^2 + 20.57^2} = 32.4 \Omega$ $V_p = V_L / \sqrt{3} = 415 / \sqrt{3} = 240V$ $I_p = \frac{V_p}{Z_p} = \frac{240}{32.4} = 7.4A = I_L$ $\cos\phi = \frac{25}{32.4} = 0.772 \Rightarrow P = 3V_p I_p \cos\phi$ $= 4113 W$	4M
	(ii) in delta:	
	$Z_p = 32.4 \Omega ; V_p = V_L = 415V ; I_p = \frac{415}{32.4} = 12.8A$ $I_L = \sqrt{3} I_p = \sqrt{3} \times 12.8 = 22.2A$ $P = 3V_p I_p \cos\phi = 3 \times 415 \times 12.8 \times 0.772$ $= 12302 W.$	4M
5(b)	<p>(i) <math>P_{cu} = I^2 R ; P_i = We + Wh</math></p> <p>(ii) Reason of the rating of tlf in kVA</p> <p>(iii) Reason of tlf cannot be excited by DC supply.</p>	<p>3M</p> <p>2M</p> <p>3M</p>
6(a)	<p>Efficiency at 75% full load =</p> $\frac{500 \times 34}{500 \times \frac{3}{4} + P_i + \left(\frac{3}{4}\right)^2 P_{cu}} \times 100 = 90.5 \%$	4M
	$\text{Output at maximum efficiency} = 500 \sqrt{\frac{18.52}{37.04}}$ $= 353.55W$	
	$\text{maximum efficiency} = \frac{353.55}{353.55 + 18.52 + 18.52}$ $= 90.516 \%$	4M
6(b)	<p><math>\textcircled{1} V_L = \sqrt{3} V_{ph}</math></p> $I_L = I_{ph}$ <p>Phasor diagram - 3M</p> <p>Proof - 5M</p>	

Question No	Marks
7(a) Concept of rotating magnetic field - <u>6M</u> torque-slip characteristic - <u>2M</u>	
7(b) Diagram Description of construction	<u>3M</u> <u>5M</u>
8(a) Working principle Reasoning of no starting torque	<u>5M</u> <u>3M</u>
8(b)(i) comparison (ii) $f_1 = 50 \text{ Hz}$ $S = \frac{1500 - 1440}{1500} = 0.04 = 4\%$ . $P = \frac{120f}{N_S} = 4$	<u>4M</u> <u>4M</u>
9(a) Types of Tariff of electricity bill The total energy consumed per day Energy consumed in the month = $7.94 \text{ kWh}$ Total cost of energy = $\text{Rs. } 406.98$	<u>4M</u> <u>4M</u>
(b) Block diagram Illustration	<u>2M</u> <u>3M</u>
10(a) Types of earthing Explanation of one type of earthing	<u>2M</u> <u>6M</u>
10(b) Diagram Working of MCB Merits and demerits	<u>2M</u> <u>4M</u> <u>2M</u>
	Verted Date

.....Q.P.Code (For office use only)

Course Code: 22ES24D	Course Title: BASICS OF ELECTRICAL ENGINEERING									
----------------------	------------------------------------------------	--	--	--	--	--	--	--	--	--

## PART-A

Q.No	1.1	1.2	1.3	1.4	1.5	1.6	1.7	1.8	1.9	1.10
B T	2	2	1	2	2	1	1	1	1	1
COs	1	1	2	2	2	3	3	3	4	4
<hr/>										
Q No	1.11	1.12	1.13	1.14	1.15	1.16	1.17	1.18	1.19	1.20
B T										
COs										

## PART-B

Question No	B T Levels		Cos addressed	Question No	BT Levels		Cos addressed
2	a	3	1	3	a	2	2
	b	3	1		b	3	2
	c	2	1		c		
	d				d		
4	a	3	2	5	a	5	2
	b	3	2		b	4	3
	c				c		
	d				d		
6	a	3	2	7	a	2	3
	b	3	3		b	3	3
	c				c		
	d				d		
8	a	2	3	9	a	5	4
	b	4	3		b	2	4
	c				c		
	d				d		
10	a	2	4				
	b	2	4				
	c						
	d						

Signature of Scrutinizer:

Name: *Aldinatha Jain*

Signature of Chairperson:

Name:

