


Tutorial-1

A silicon transistor has its $I_{E0}=6\text{ nA}$ and $\alpha=0.98$. If $I_B=0$ and $V_{CE}=4\text{ V}$ then $I_C = \underline{\hspace{2cm}}$
 An NPN transistor has $I_{E0}=30\text{ nA}$, $I_B=0$, $V_{CE}=4\text{ V}$ and $I_C=30\text{ }\mu\text{A}$. The value of $\beta = \underline{\hspace{2cm}}$
 The measured terminal voltages (in Volts) of different NPN transistors are given in Table-
 For each of the transistors, find V_{BE} , V_{CE} and identify the region of operation.

VCB

0	8b
-0.7	fb
2	8b
0.3	
-0.7	

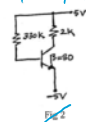8. Find the values of β that correspond to α values of 0.5, 0.8, 0.96, 0.98 and 0.996.
9. Find the values of α that correspond to β values of 40, 60, 80, 99, 149 and 249.



In the fixed base current biasing circuits of fig 1 and 2. Determine the operating point of the silicon transistor.

In the circuit of fig 3, determine V_C , V_E , V_B and I_C .




In the circuit of fig 4, find V_g , I_g , I_a , I_c and V_c .


$$I_C = \beta I_B + (\beta + 1) I_{CO}$$

$$= 50 (6n)$$


$$I_F = 0.3 \mu A$$


(b) $30\mu = (\beta + 1) 30\mu^m$
 $1000 = \beta + 1$
 $\beta = 999$

(2) (a) 

 (b) 

(c) $\begin{array}{c|c} 9b & 0 \\ \hline -2 & \\ \hline fb & 1 \\ & -2.7 \end{array}$ active

(d) 

(e) 

4) (a) $0 = (340\text{K})I_B - V_{BE} = -9$; (b) $5 = (330\text{K})I_B - V_{BE} = -5$
 $9 = (340\text{K})I_B + 0.7$; $10 - 0.7 = (330\text{K})I_B$
 $I_B = \frac{9 - 0.7}{340\text{K}}$; $I_B = \frac{9.3}{330\text{K}}$
 $I_B = 0.0213\text{mA}$; $I_B = 2.82\mu\text{A}$
 $I_B = 21.3\mu\text{A}$; $I_C = \beta I_B$
 $I_C = \beta I_B = 60 \times 21.3\mu\text{A}$; $I_C = 80 \times 2.82\mu\text{A}$
 $I_C = 1.27\text{mA}$; $I_C = 2.25\text{mA}$

$$\begin{aligned} 0 - (2.9k)(I_C) - V_{CE} &= -9 & 5 - (2k)I_C - V_{CE} &= -5 \\ V_{CE} &= 9 - (1.187m)(2.9k) & V_{CE} &= 10 - (2k)(2.25m) \\ &= 9 - 4.953 & &= 10 - 4.5 \\ V_{CE} &= 4.047V & V_{CE} &= 5.5V \end{aligned}$$

$$\textcircled{7} \quad V_{CC} = 18V \quad ; \quad I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$R_C = 2.2 \quad = \frac{18 - 0.7}{(199 + 1) + (51)(1K)}$$

$$\beta = 50 \quad = \frac{17.3}{250K}$$

$$R_E = 1k\Omega$$

$$R_B = 199k\Omega$$

$$\begin{aligned} 18 - I_C R_C &= V_C & 250\text{ K} \\ 18 - (3.46\text{ mA})(22\text{ k}) &= V_C & I_B = 69.2\text{ }\mu\text{A} \\ V_C &= \underline{10.38\text{ V}} \quad \checkmark & I_C = \beta I_B \\ & & = 50 (69.2\text{ }\mu\text{A}) \\ V_E - I_E R_E &= 0 & I_C = \underline{3.46\text{ mA}} \quad \checkmark \\ V_E &= (\underline{3.529\text{ mA}})(1\text{ k}) & I_E = (\beta + 1) I_B \\ V_E &= \underline{3.529\text{ V}} \quad \checkmark & = 51 (69.2) \\ & & = \underline{3.529\text{ mA}} \end{aligned}$$


$$18 - I_B R_B = V_B$$
$$V_B = 18 - (69.9 \mu A)(199 k)$$
$$= 18 - 13.77$$
$$V_B = 4.2 V \checkmark$$

Tutorial-1



⑥
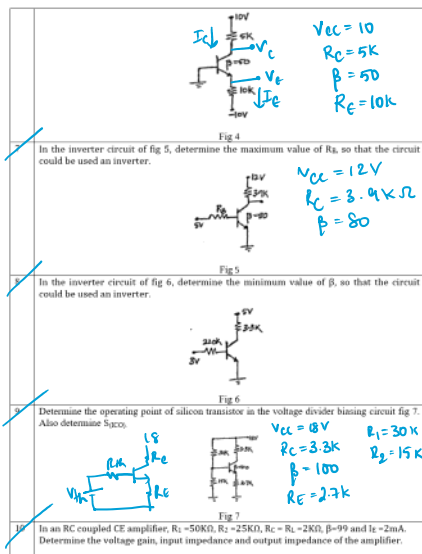
$$0 - V_{BE} - I_E R_E = -10$$
$$-0.7 - I_E (10k) = -10$$
$$I_E = \frac{9.3}{10k}$$
$$I_E = 0.93mA$$



$$I_C = \frac{9.3}{101k}$$

$$I_E = 0.93mA$$

$$I_C = (\beta + 1) I_B$$

$$I_B = \frac{0.93mA}{51}$$

$$I_B = 18.2\mu A$$

$$I_C = \beta I_B$$

$$I_C = 0.91mA$$

$$V_E - I_E R_E = -10$$

$$V_E = -10 + (0.93mA)(10k)$$

$$V_E = -0.7V$$

$$10 - I_C R_C = V_C$$

$$V_C = 10 - (0.91mA)(5k)$$

$$V_C = 5.45V$$

⑦ $12 - I_C R_C - V_{CE} = 0$

$$12 - (\beta + 1) I_B R_C - 0.3 = 0$$

(saturation)

$$12 - (80) I_B (3.9k) - 0.3 = 0$$

$$I_B = 11.7 \Rightarrow I_B = 37.5\mu A$$

$$I_B = \frac{37.5\mu A}{12k}$$

$$5 - I_B R_B - V_{BE} = 0$$

$$5 - (37.5\mu A) R_B - 0.7 = 0$$

$$R_B = 4.3$$

$$R_B = 37.5\mu A$$

$$R_B = 114.7k\Omega$$

⑧ $5 - I_C R_C - V_{CE} = 0$

$$5 - \beta I_B R_C - V_{CE} = 0$$

$$5 - \beta (10.5\mu A) (3.3k) - 0.3 = 0$$

$$\beta = 4.7$$

$$10.5 \times 10^{-6} \times 3.3 \times 10^3$$

$$\beta = 135.6$$

$$3 - I_B R_B - V_{BE} = 0$$

$$3 - I_B (220k) - 0.7 = 0$$

$$I_B = \frac{2.3}{220k}$$

$$I_B = 10.5\mu A$$

⑨ $Q_{pt}(V_{CE}, I_C) = ?$, $S_{ico} = ?$

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2} \Rightarrow V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$= \frac{6 - 0.7}{10k + 101(2.7k)}$$

$$= 5.3$$

$$R_{th} = R_1 || R_2$$

$$= \frac{30k \times 15k}{30k + 15k}$$

$$R_{th} = 10k\Omega$$

$$I_B = \frac{282.7k}{18.7k}$$

$$I_B = 18.7\mu A$$

$$I_C = \beta I_B = 100 I_B = 1.87mA$$

$$I_E = (\beta + 1) I_B = 101 I_B = 1.88mA$$

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$18 - (1.87mA)(3.3k) - V_{CE} - (1.88mA)(2.7k) = 0$$

$$V_{CE} = 18 - 6.171 - 5.076$$

$$V_{CE} = 6.753V$$

$$Q_{pt}(V_{CE}, I_C)$$

$$Q_{pt} = (6.753V, 1.87mA)$$

$$S_{ico} = \frac{1}{1 + \frac{\beta R_E}{R_{th} + R_E}}$$

$$= \frac{101}{1 + \frac{100 \times 2.7k}{10k + 2.7k}}$$

$$= \frac{101}{1 + 270}$$

$$= \frac{101}{271}$$

$$S_{ico} = 4.7529$$

⑩ $R_1 = 50k\Omega$, $R_2 = 25k\Omega$, $R_C = R_L = 2k\Omega$, $\beta = 99$, $I_E = 2mA$

$$\left\{ \begin{array}{l} Z_i = R_{th} || (\beta + 1) R_E \\ Z_o = R_C || R_L \\ A_v = \frac{-R_C || R_L}{R_E} \end{array} \right.$$

$$R_{th} = R_1 || R_2$$

$$= \frac{50k \cdot 25k}{50k + 25k}$$

$$R_{th} = 16.67k\Omega$$

$$r_e = \frac{26mV}{I_E}$$

$$= \frac{26mV}{2mA}$$

$$r_e = 13\Omega$$

$$Z_i = \frac{R_{th} (\beta + 1) r_e}{R_{th} + (\beta + 1) r_e}$$

$$= \frac{(16.67k)(100)(13)}{16.67k + 100 \times 13}$$

$$= \frac{21671}{17.97k}$$

$$= 1205.95$$

$$Z_i = 1.206k\Omega$$

$$= 1205.95$$

$$Z_i = 1.206k\Omega$$

$$Z_o = R_C || R_L$$

$$= \frac{(2k)(2k)}{2k + 2k}$$

$$Z_o = 1k\Omega$$

$$A_v = -\frac{R_C || R_L}{r_e}$$

$$= -\frac{1k}{13}$$

$$A_v = -76.9231$$

Basics Electronics (22EC13)

Tutorial-1

- 11/ Three amplifiers of voltage gains 20dB, 26dB and 32dB are cascaded to obtain an output voltage of 2V. Calculate the input voltage needed.
 12/ An amplifier having a power gain of 17dB delivers a power output of 40W to a load of 1kΩ. Calculate (i) the input power needed and (ii) the input voltage needed, if the voltage gain of the amplifier is 38dB.

- 12/ Calculate the voltage gain v_o/v_i , input impedance Z_i and output impedance Z_o for the circuits of fig 8 and 9

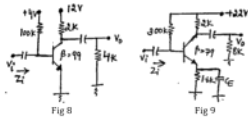


Fig 8

Fig 9

(11a) $A_{v1} = 20dB$ $V_o = 2V$
 $A_{v2} = 26dB$ $V_i = ?$
 $A_{v3} = 32dB$

$$A_{v_{tot}} = 20 \log \left(\frac{V_o}{V_i} \right)$$

$$20 + 26 + 32 = 20 \log \left(\frac{2}{V_i} \right)$$

$$\frac{78}{20} = \log \left(\frac{2}{V_i} \right)$$

$$10^{3.9} = \frac{2}{V_i}$$

$$V_i = \frac{2}{10^{3.9}} = \frac{2}{7943.28} = 0.25mV$$

(11b) $A_p = 17dB$ i) $P_i = ?$
 $P_o = 40W$ ii) $V_i = ?$ if $A_v = 38dB$
 $R = 1k\Omega$

$$\rightarrow A_p = 10 \log \left(\frac{P_o}{P_i} \right) \rightarrow A_v = 20 \log \left(\frac{V_o}{V_i} \right)$$

$$17 = 10 \log \left(\frac{40}{P_i} \right)$$

$$P_i = \frac{40}{10^{1.7}}$$

$$P_i = 0.798W \text{ (i)}$$

$$P = \frac{V^2}{R}$$

$$V_o = \sqrt{P_o R}$$

$$= \sqrt{40 \times 1k}$$

$$V_o = 200$$

$$38 = 20 \log \left(\frac{200}{V_i} \right)$$

$$\log \left(\frac{200}{V_i} \right) = 1.9$$

$$V_i = \frac{200}{10^{1.9}}$$

$$V_i = 2.5179V \text{ (ii)}$$

$$A_v, Z_i, Z_o ?$$

(12a) $Z_i = R_C || (\beta + 1) r_e$

$$= R_C (\beta + 1) r_e$$

$$R_C + (\beta + 1) r_e$$

$$= \frac{(100k)(100)(787)}{100k + (100)(787)}$$

$$= 1.206k\Omega$$

$$r_e = \frac{26mV}{I_E}$$

$$I_E$$

$$4 - I_E R_E - V_{BE} = 0$$

$$4 - I_E (100k) - 0.7 = 0$$

$$I_E = \frac{3.3}{100k}$$

$$r = 22. A$$

$$= \frac{(100k)(100)(7.87)}{100k + (100)(7.87)}$$

$$= \frac{7.87 \times 10^4}{100k + 787}$$

$$Z_i = 781 \Omega$$

$$4 - I_B(100k) - 0.7 = 0$$

$$I_B = \frac{3.3}{100k}$$

$$I_B = 33 \mu A$$

$$I_E = (\beta + 1) I_B = 3.3 \mu A$$

$$r_e = \frac{26 mV}{3.3 \mu A}$$

$$r_e = 7.87 \Omega$$

$$\rightarrow Z_o = R_c \parallel R_L$$

$$= \frac{(1k)(2k)}{1k + 2k}$$

$$Z_o = 666.67 \Omega$$

$$\rightarrow A_v = \frac{-R_c \parallel R_L}{r_e}$$

$$= \frac{-1.33k}{7.87}$$

$$A_v = -169$$

$$(2b) Z_i = R_c \parallel (\beta + 1) r_e ; r_e = \frac{26 mV}{I_E}$$

$$= \frac{R_c (\beta + 1) r_e}{R_c + (\beta + 1) r_e}$$

$$= \frac{(2k)(80)(6.5261)}{(2k) + (80)(6.5261)}$$

$$Z_i = 522 \Omega$$

$$22 - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_B = \frac{22 - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$= \frac{22 - 0.7}{300k + (80)(1.6k)}$$

$$= \frac{21.3}{428k}$$

$$I_B = 49.8 \mu A$$

$$I_C = (\beta + 1) I_B = 80 I_B$$

$$I_C = 2.984 \mu A$$

$$r_e = \frac{26 mV}{2.984 \mu A}$$

$$r_e = 6.5261 \Omega$$