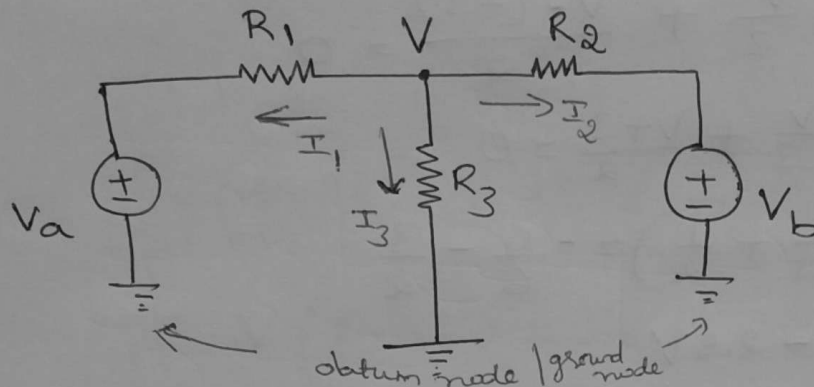


## Node voltage analysis



Applying Kcl at V

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V - V_a}{R_1} + \frac{V - V_b}{R_2} + \frac{V}{R_3} = 0$$

No of node equations =  $N - 1$


$N =$  No of principle nodes

In the above figure no of principle node = 2

ie V and ground node | datum node | Reference node

$$\therefore \text{No of eqns} = 2 - 1 = \underline{1}$$

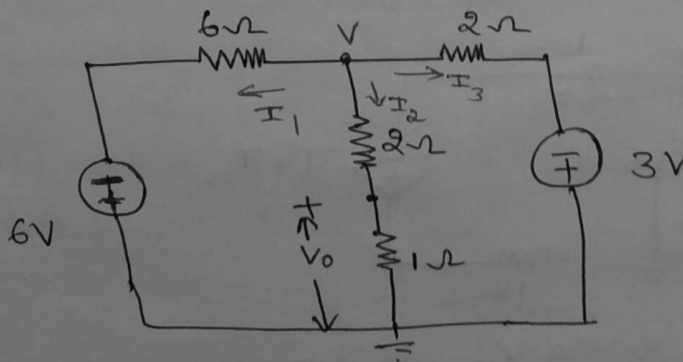Ex: use nodal analysis to find  $V_0$  in the circuit in figure



No of nodes including datum node = 2

$$\therefore \text{No of equation} = 2 - 1 = 1$$

Kcl at V

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V - (-6)}{6} + \frac{V}{3} + \frac{V - (-3)}{2} = 0$$

$$\frac{V+6}{6} + \frac{V}{3} + \frac{V+3}{2} = 0$$

$$V\left(\frac{1}{6} + \frac{1}{3} + \frac{1}{2}\right) = -\frac{6}{6} - \frac{3}{2}$$

$$V = -2.5V$$

To find  $V_0$ ,

$$V_0 = I_2 \cdot 1\Omega$$

$$I_2 = \frac{V}{3} = -\frac{2.5}{3} = -0.833A$$


$$\therefore V_0 = -0.833V$$

or using voltage division rule

$$V_0 = \frac{V(1)}{2+1} = -\frac{2.5}{3} = -0.833V$$

Ex: of nodal analysis using dependent source

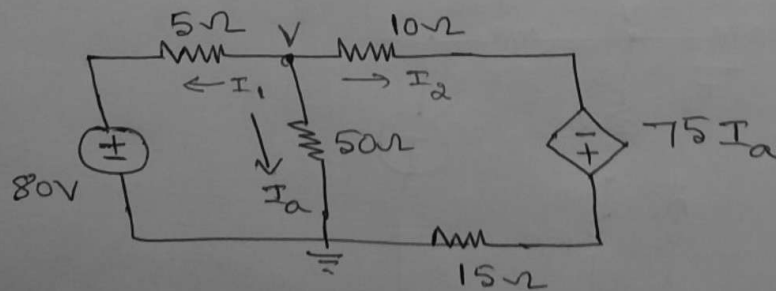Find the power delivered by the dependent  $V/g$  source in the n/w shown in the figure.



Solution: Kcl at node V,

$$I_1 + I_a + I_2 = 0$$

$$\frac{V-80}{5} + \frac{V}{50} + \frac{V+75I_a}{25} = 0$$

$$V \left( \frac{1}{5} + \frac{1}{50} + \frac{1}{25} \right) - \frac{80}{5} + \frac{75 I_a}{25} = 0$$

$$\text{But } I_a = \frac{V}{50}$$

$$V(0.26) + \frac{75}{25} \left( \frac{V}{50} \right) = 16$$

$$V(0.32) = 16$$

$$V = 50V$$

$$I_a = \frac{50}{50} = 1A$$


$$\text{Power}_{75 I_a} = V I = 75 I_a I_2$$

$$P = 75(1)(I_2)$$

$$I_2 = \frac{V + 75 I_a}{25} = \frac{50 + 75(1)}{25} = 5$$

$$P = 75(1)(5) = 375W$$

$$\boxed{P = 375W}$$

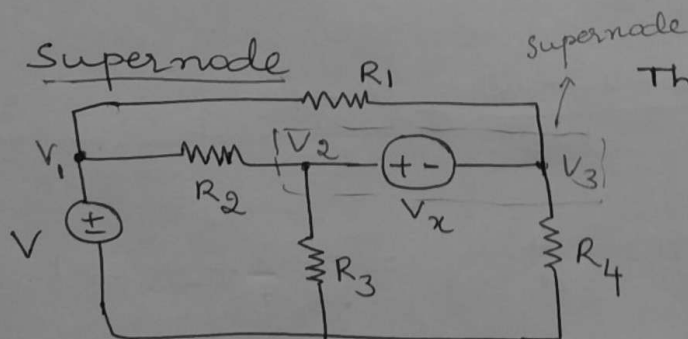

The nodes  $V_2$  and  $V_3$  are connected directly through a voltage source without any circuit element.


A voltage source which connects the two nodes directly is called supernode.

Step 1: write supernode constraint equation i.e.

$$V_x = V_2 - V_3$$

Step 2: Apply KCL at  $V_2$  and  $V_3$  simultaneously.

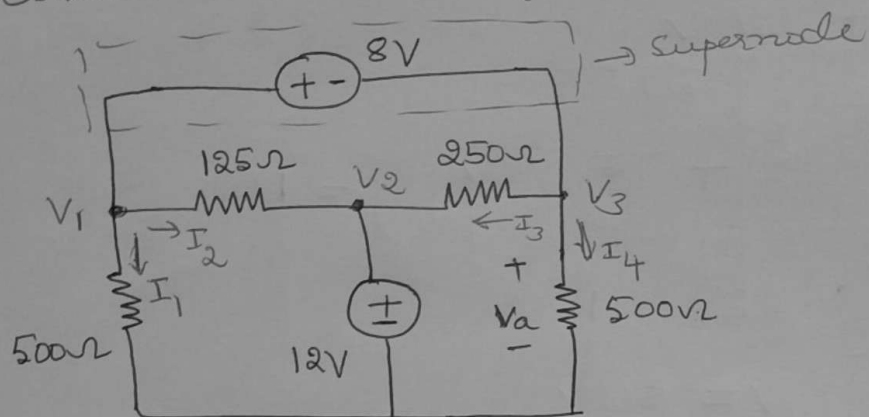Ex: using nodal analysis, find  $V_a$  for the circuit shown in figure.



Solution: The constraint equation is,

$$V_1 - V_3 = 8 \quad \text{--- (1)}$$

Apply Kcl at the supernode, ie  $V_1$  and  $V_3$

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1}{500} + \frac{V_1 - V_2}{125} + \frac{V_3 - V_2}{250} + \frac{V_3}{500} = 0$$

From equ<sup>n</sup> (1)  $V_1 = 8 + V_3$

At node  $V_2 = 12$

$$\frac{8 + V_3}{500} + \frac{8 + V_3 - 12}{125} + \frac{V_3 - 12}{250} + \frac{V_3}{500} = 0$$


$$V_3 \left( \frac{1}{500} + \frac{1}{125} + \frac{1}{250} + \frac{1}{500} \right) = -\frac{8}{500} + \frac{4}{125} + \frac{12}{250}$$

$$V_3 (0.016) = 0.064$$

$$V_3 = 4V$$

$$V_a = V_3 = 4V$$

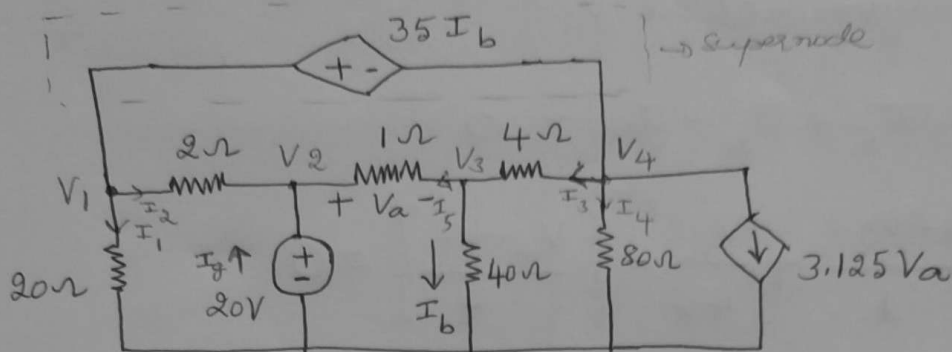Ex: use the node voltage method to find the power developed by the 20V source in the circuit shown in Fig



Solution: Constraint equations

$$V_1 - V_4 = 35I_b \quad \text{--- (1)}$$

$$I_b = \frac{V_3}{40}, \quad V_2 = 20V$$

KCL at supernode  $V_1$  and  $V_4$

$$I_1 + I_2 + I_3 + I_4 + 3.125V_a = 0$$

$$\frac{V_1}{20} + \frac{V_1 - V_2}{2} + \frac{V_4 - V_3}{4} + \frac{V_4}{80} + 3.125V_a = 0 \quad \text{--- (2)}$$

$$\text{But } V_a = V_2 - V_3 = 20 - V_3 \quad \text{--- (3)}$$

$$\text{From equation (1), } V_1 = 35I_b + V_4 = 35 \cdot \frac{V_3}{40} + V_4$$

$$V_1 = 0.875V_3 + V_4 \quad \text{--- (4)}$$

Sub equ<sup>n</sup> (3) and (4) in equ<sup>n</sup> (2)

$$\frac{0.875V_3 + V_4}{20} + \frac{0.875V_3 + V_4}{2} - \frac{20}{2} + \frac{V_4}{4} - \frac{V_3}{4} + \frac{V_4}{80} + 3.125(20 - V_3) = 0$$

$$V_3 \left( \frac{0.875}{20} + \frac{0.875}{2} - \frac{1}{4} - 3.125 \right) + V_4 \left( \frac{1}{20} + \frac{1}{2} + \frac{1}{4} + \frac{1}{80} \right) = 10 - 3.125(20)$$

$$V_3(-2.893) + V_4(0.8125) = -52.5 \quad \text{--- (5)}$$

Applying Kcl at  $V_3$

$$I_5 + I_6 - I_3 = 0$$

$$\frac{V_3 - V_2}{1} + \frac{V_3}{40} - \left\{ \frac{V_4 - V_3}{4} \right\} = 0$$

$$V_3 - 20 + \frac{V_3}{40} - \frac{V_4}{4} + \frac{V_3}{4} = 0$$

$$V_3 \left( 1 + \frac{1}{40} + \frac{1}{4} \right) - V_4 \left( \frac{1}{4} \right) = 20$$

$$V_3(1.275) - V_4(0.25) = 20 \quad \text{--- (6)}$$

Solve eqn (5) and (6)

$$\begin{bmatrix} -2.893 & 0.8125 \\ 1.275 & -0.25 \end{bmatrix} \begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} -52.5 \\ 20 \end{bmatrix}$$

$$\Delta = -0.312, \quad \Delta_3 = -3.125, \quad V_3 = \frac{\Delta_3}{\Delta} = 10V$$

$$\Delta_4 = 9.0775, \quad V_4 = \frac{\Delta_4}{\Delta} = -29.1V$$

$$\therefore V_1 = 0.875V_3 + V_4 = 0.875(10) - 29.1V$$

$$V_1 = -20.35V$$

$$\text{Power}_{20V} = VI = 20I_g$$

To find  $I_g$ , Kcl at  $V_2 \Rightarrow I_g + I_2 + I_5 = 0$


$$I_g = -I_2 - I_5 = -\left[ \frac{V_1 - V_2}{2} \right] - \left[ \frac{V_3 - V_2}{1} \right]$$

$$I_g = -\left[ \frac{-20.35 - 20}{2} \right] - \left[ \frac{10 - 20}{1} \right] = 30.175A$$

$$\boxed{P_{20V} = (20)(30.175) = 603.5W}$$

Type of the circuit	Impedance $Z$
purely resistive $\rightarrow$	$Z = R$
purely inductive $\rightarrow$	$Z = j\omega L = jX_L$
purely capacitive $\rightarrow$	$Z = \frac{-j}{\omega C} = -jX_C = \frac{1}{j\omega C}$
RL $\rightarrow$	$Z = R + j\omega L = R + jX_L$
RC $\rightarrow$	$Z = R - \frac{j}{\omega C} = R - jX_C$
RLC $\rightarrow$	$Z = R + j\omega L - \frac{j}{\omega C} = R + j(X_L - X_C)$

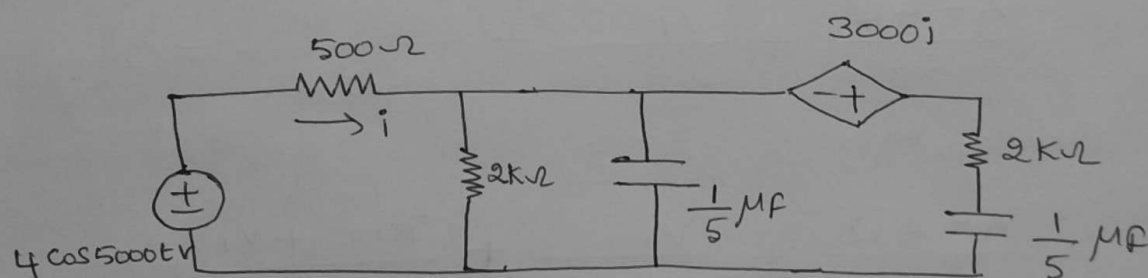
Ex: using nodal technique, find the current  $i$  in the circuit shown in figure.



$$\begin{aligned}
 \text{The reactance of the capacitor} &= \frac{1}{j\omega C} \\
 &= \frac{1}{j(5000)(\frac{1}{5} \times 10^{-6})} \\
 &= -j1K\Omega
 \end{aligned}$$

The parallel combinations of  $2K\Omega$  and  $-j1K\Omega$  is
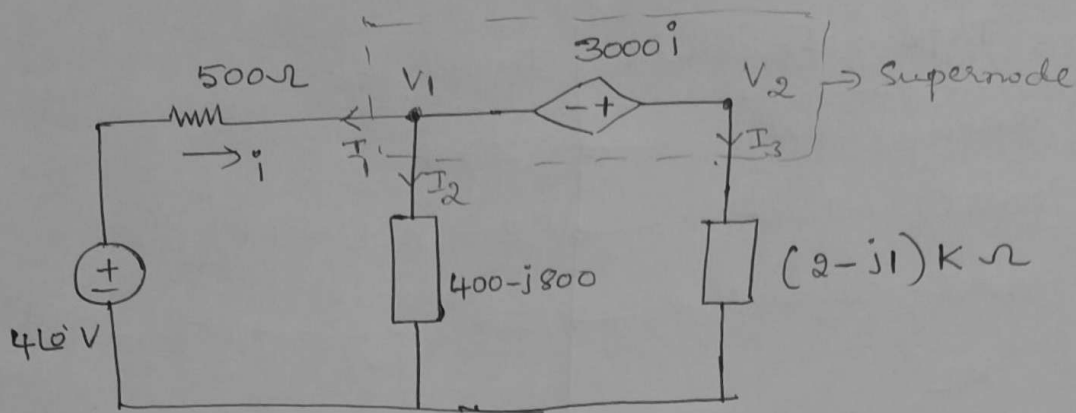
$$Z_p = \frac{2K(-jK)}{2K - jK} = 400 - j800$$



Constraint equation,

$$V_2 - V_1 = 3000i$$

$$V_2 = 3000i + V_1 \quad \text{--- (1)}$$

Kcl at Supernode

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - 4\angle 0^\circ}{500} + \frac{V_1}{400 - j800} + \frac{V_2}{(2 - j1)k} = 0 \quad \text{--- (2)}$$

Sub equ<sup>n</sup> (1) in equ<sup>n</sup> (2)

$$\frac{V_1 - 4\angle 0^\circ}{500} + \frac{V_1}{400 - j800} + \frac{3000i + V_1}{(2 - j1)k} = 0$$

$$i = \frac{4\angle 0^\circ - V_1}{500}$$

$$\therefore \frac{V_1}{500} - \frac{4\angle 0^\circ}{500} + \frac{V_1}{400 - j800} + \frac{3000\left(\frac{4\angle 0^\circ - V_1}{500}\right) + V_1}{(2 - j1)k} = 0$$

By solving  $V_1 = (-7201.04 - j9596.2) \text{ mV}$


$$\therefore i = \frac{4\angle 0^\circ - V_1}{500} = \underline{24 \angle 53.1^\circ \text{ mA}} \Rightarrow 24 \angle 126.86^\circ \text{ mA}$$

In time domain,  $\boxed{i = 24 \cos(5000t + 53.1^\circ) \text{ mA}}$



Ex: Find the node voltages in the circuit shown in

9

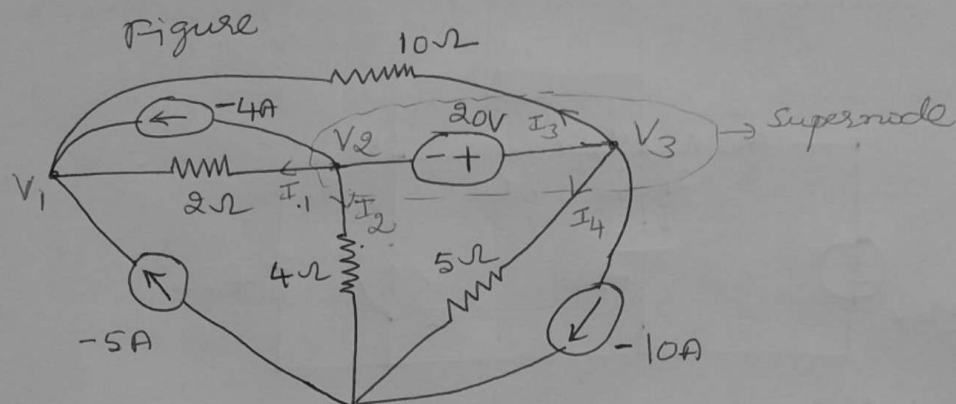

constraint equations,

$$V_3 - V_2 = 20 \quad \text{--- (1)}$$

Kcl at supernodes  $V_2$  and  $V_3$

$$I_1 + I_2 + I_3 + I_4 - 4 - 10 = 0$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_3 - V_1}{10} + \frac{V_3}{5} - 14 = 0$$

$$V_1 \left( -\frac{1}{2} - \frac{1}{10} \right) + V_2 \left( \frac{1}{2} + \frac{1}{4} \right) + V_3 \left( \frac{1}{10} + \frac{1}{5} \right) = 14$$

$$-0.6V_1 + 0.75V_2 + 0.3V_3 = 14 \quad \text{--- (2)}$$

Kcl at node 1

$$I_1 + I_3 - 4 - 5 = 0$$

$$\frac{V_2 - V_1}{2} + \frac{V_3 - V_1}{10} = 9$$


$$V_1 \left( -\frac{1}{2} - \frac{1}{10} \right) + V_2 \left( \frac{1}{2} \right) + V_3 \left( \frac{1}{10} \right) = 9$$

$$-0.6V_1 + 0.5V_2 + 0.1V_3 = 9 \quad \text{--- (3)}$$

Solving eqn (1), (2) and (3) we get

$$V_1 = -9.44V, \quad V_2 = 2.226V, \quad V_3 = 22.226V$$

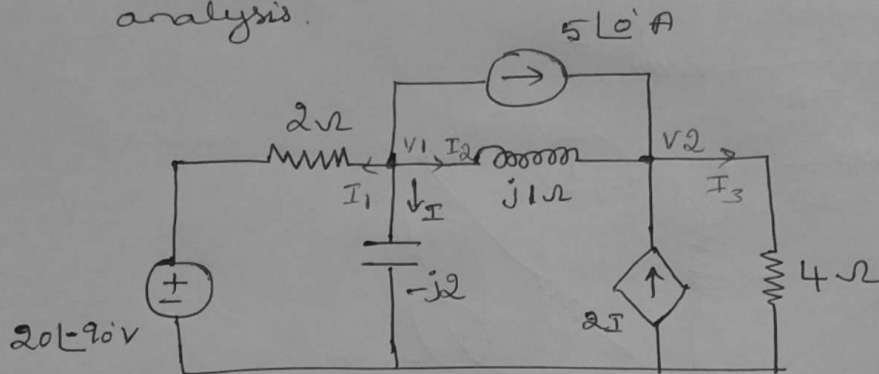Ex: Solve for current  $I$  in the circuit using nodal analysis.



Kcl at node 1

$$\frac{V_1 - 20\angle 90}{2} + \frac{V_1}{-j2} + 5\angle 0 + \frac{V_1 - V_2}{j1} = 0$$

$$(0.5 - j0.5)V_1 + jV_2 = -5 - j10 \quad (1)$$

Kcl at node 2

$$I_2 + 2I + 5\angle 0 - I_3 = 0$$

$$\frac{V_1 - V_2}{j1} + 2\left[\frac{V_1}{-j2}\right] + 5\angle 0 - \frac{V_2}{4} = 0$$

$$V_1\left(\frac{1}{j1} - \frac{2}{j2}\right) - V_2\left(\frac{1}{j1} + \frac{1}{4}\right) = -5\angle 0$$

$$V_2 = \frac{5}{0.25 - j} \quad (2)$$


sub equ<sup>n</sup> (2) in equ<sup>n</sup> (1), we get.

$$V_1 = 15.81\angle -46.5^\circ \text{ V}$$




$$\therefore I = \frac{V_1}{-j2} = \frac{15.81\angle -46.5^\circ}{2\angle -90^\circ} = 5.73 + j5.441$$

$$\boxed{I = 7.90\angle 43.5^\circ \text{ A}}$$

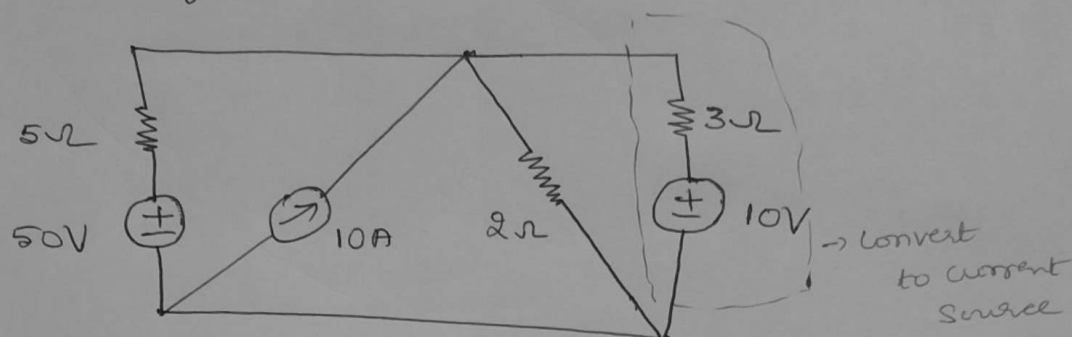Ex: using source transformation find the power delivered by the 50V voltage source in the circuit shown in figure.



Solution.

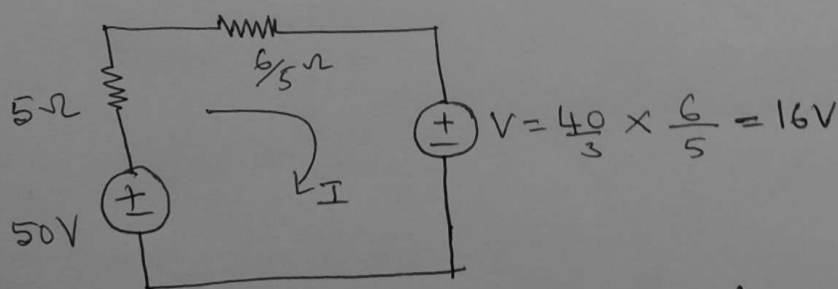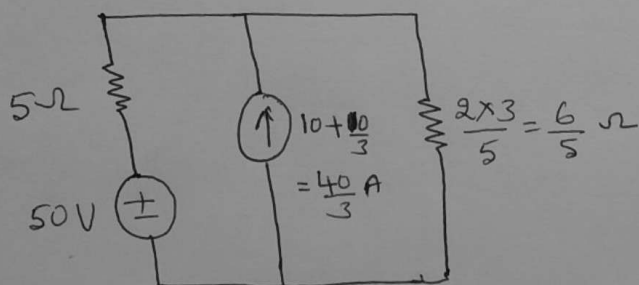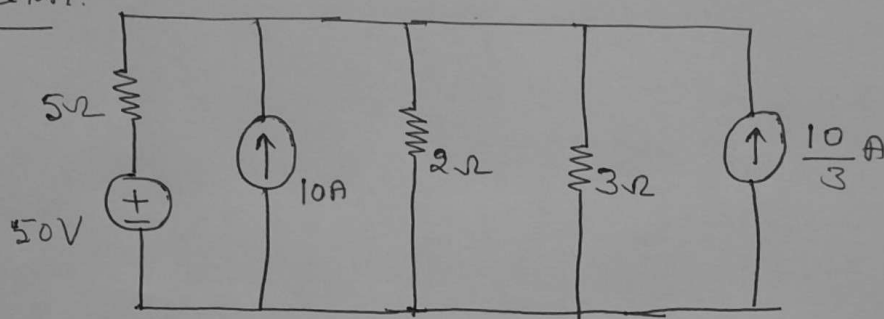

Apply KVL to mesh  $\Rightarrow 5I + \frac{6}{5}I + 16 - 50 = 0$

$$6.2I = 34$$

$$I = 5.48 \text{ A}$$

$$\therefore \text{Power}_{50V} = VI = 50I = (50)(5.48)$$

$$P = 274 \text{ W}$$