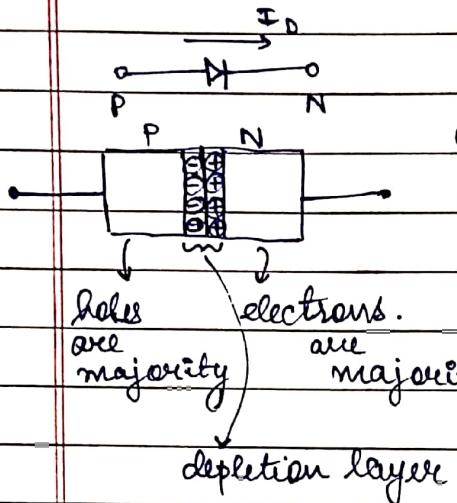


13/12/22

Date _____
Page _____

UNIT- 1

BIPOLAR JUNCTION TRANSISTORS.



unipolar device — one type of charge carriers two terminals. one junction majority

Holes electrons.
are are
majority majority

depletion layer

I_D = Diode current

$$I_D = I_S (e^{V_D/mV_T} - 1)$$

↳ for both forward
current/reverse

I_g = Reverse saturation current

V_D = Forward voltage drop

n = material constant

$$\therefore V_T \text{ at } 27^\circ C \\ \Rightarrow 26 \text{ mV}$$

V_T = Thermal voltage

$$N_T = \frac{KF}{\text{kg}} = 0.0258 \text{ V}^2 \text{ m}^2 \text{ V}$$

$$V_D = 0.1 \text{ (Si)}$$

$$v_D = 0.3 \text{ (Ge)}$$

$$k - \text{Boltzmann's const} = 8 \text{ J/K}$$


T - Temperature in Kelvin

Reverse saturation current is Temperature dependent

Q: calculate value of V_f at 57°C

$$\begin{aligned}
 & \cancel{330} \times \cancel{26} \times 10^{-3} & 273 \\
 & \cancel{1.6} \times 10^{-19} & 57 \\
 N_T \text{ at } 57^\circ C &= \frac{26}{300} \times 330 & 330 \\
 & = 11 \times \cancel{26}^6 & = 28.6 \text{ m} \\
 & & 10
 \end{aligned}$$

19/12/22

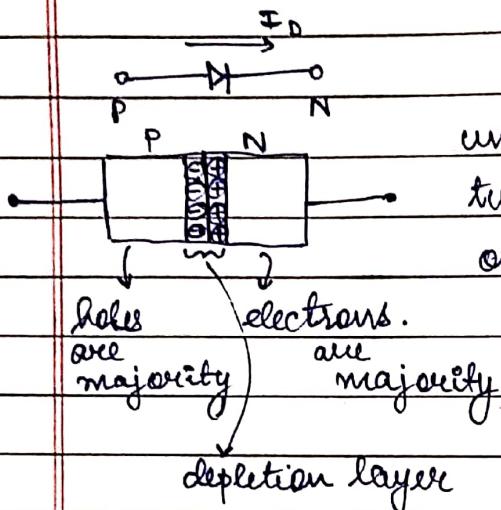Date _____
Page _____UNIT - 1BIPOLAR JUNCTION TRANSISTORS.

unipolar device — one type of charge carriers
two terminals.
one junction
majority

Holes electrons.
are are
majority majority.

I_D = Diode current

$$I_D = I_S (e^{V_D/nV_T} - 1)$$

↳ for both forward current/reverse

I_S = Reverse saturation current

V_D = Forward voltage drop

n = material constant

$\therefore V_T$ at $27^\circ C$

$$\Rightarrow 26 \text{ mV}$$

V_T = Thermal voltage

$$V_T = \frac{kT}{q} = 0.0258 \text{ V} \approx 26 \text{ mV}$$

$$V_D = 0.1 \text{ (Si)}$$

k - Boltzmann's const = $1.38 \times 10^{-23} \text{ J/K}$

$$V_D = 0.3 \text{ (Ge)}$$

T - Temperature in Kelvin

Reverse saturation current is temperature dependent

$$q = \text{Electron charge} = 1.6 \times 10^{-19} \text{ C}$$

Q: calculate value of V_T at $57^\circ C$

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} \times 26 \times 10^{-3}}{1.6 \times 10^{-19}}$$

273

57

$$V_T \text{ at } 57^\circ C = \frac{1.38 \times 10^{-23} \times 26 \times 10^{-3}}{1.6 \times 10^{-19}}$$


330

$$= \frac{1.1 \times 26}{10} = 28.6 \text{ mV.}$$

13/12/22

Date _____
Page _____



DC Resistance

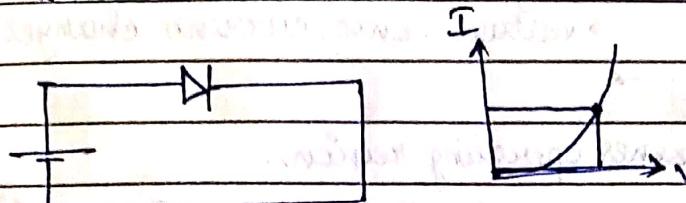

$$R_D = \frac{V}{I}$$

static resistance.

AC resistance

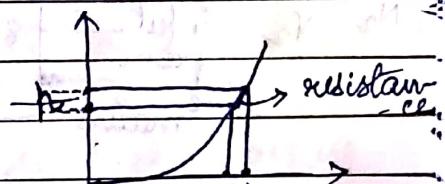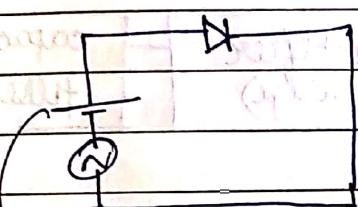for giving minimum voltage 0.7V $r_{dd} = \frac{\Delta V}{\Delta I}$

dynamic resistance

→ When we apply small AC signal diode behaves as resistance.

$$I_D = I_S (e^{V_D/mV_T} - 1)$$

diff :-

$$\frac{dI_D}{dV_D} = I_S \left(e^{V_D/mV_T} - 1 \right) \times \frac{1}{mV_T}$$

$$\frac{1}{r_{dd}} = I_D \left(\frac{1}{mV_T} \right)$$

$$\frac{1}{r_{dd}} = \frac{I_D}{mV_T}$$


$$r_{dd} = \frac{mV_T}{I_D}$$

if $m=1$


$$r_{dd} = \frac{V_T}{I_D}$$

Si: $m=2$ Ge: $m=1$

14/12/22


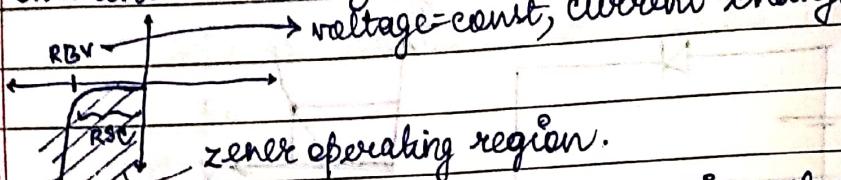
→ avalanche and zener breakdown
 → voltage=const, current changes
 • 

Regulator gives constant voltage irrespective of change in line or change in load.

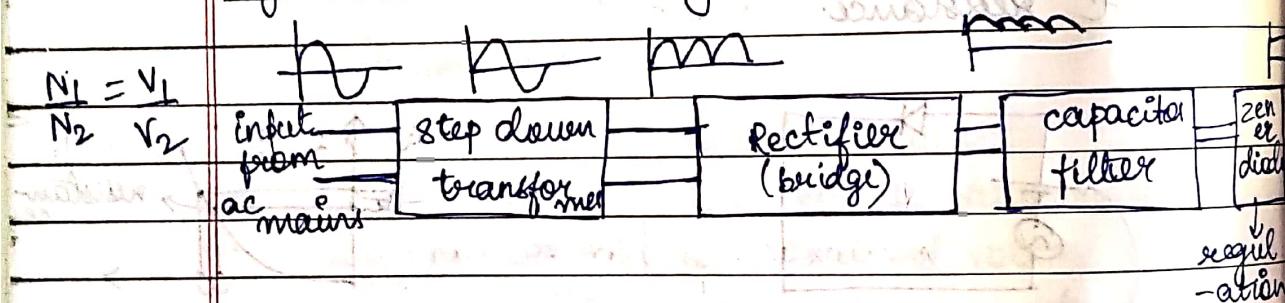
UNIT - 1Regulated Power Supply (block diagram)

Rectifier → half wave (40%)
 → full wave (80%)

→ centre tapping (2 diodes)
 → bridge rectifier (4 diodes)

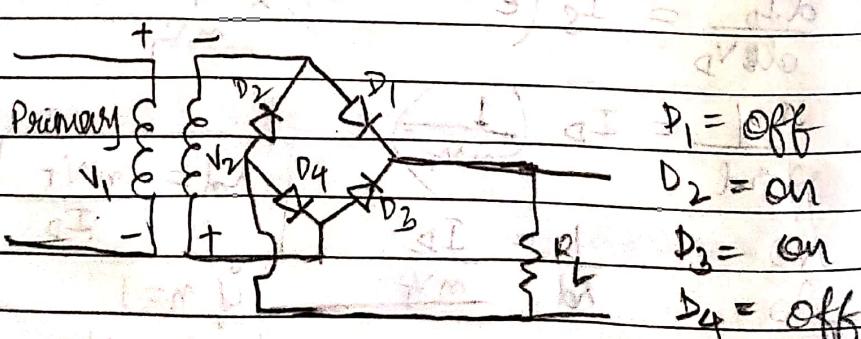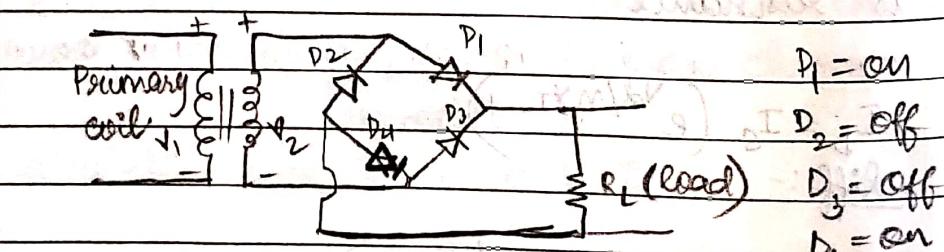NOTE:

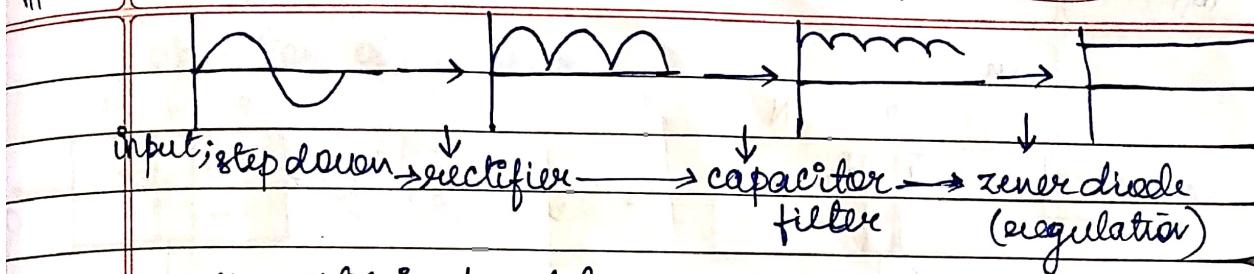The diode is not behaving as a resistor as it behaves as resistor only for small AC signals. 5V is huge AC signal.



→ zener works in breakdown region only
↓ regulation starts only after reverse breakdown.

Ripple $\gamma = 1$

(2%) $4\sqrt{3}fC_R L$
 3%) value
designed by engineer

- amount of AC content in ~~DC~~ the rectified output is called ripple factor.
- in capacitor discharging rate is more than charging rate.

V_z = zener voltage

If $V_z = 10V$, it means breakdown voltage is called zener voltage = 10V. Thus zener starts working as regulator.



IMP Qs: Explain block diagram, explain what each component is used for. with diagrams to support your answer.

Bipolar Junction Transistor.

→ 2 junction


→ 3 terminal device.

Application: used for amplification of weak signals.

Can be used as switch.

n-p-n

N P N


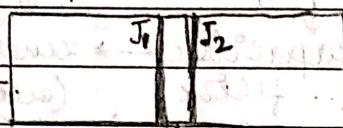


p-n-p

P N P



Base (B)

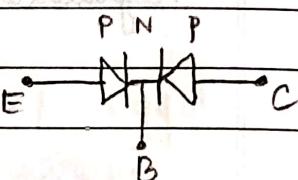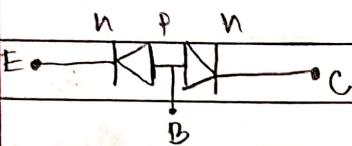

J_1 = Emitter-base junction

$C > E > B$

J_2 = collector-base junction

$E > C > B$

Regions of operation.

J_1	J_2	Region	Affiliation
FB	FB	Saturation	Closed switch
FB	RB	Active	Amplifier
RB	FB	Inverse active	Attenuator
RB	RB	Cut off	Open switch

Transistor = Transfer + Resistor.



signal is transferred from a region of low to high resistance. Thus voltage increases, hence can be used as amplifier.

$$V = IR$$

FB: $R = 0$

RB: $R = \infty$


} ideally

16/12/22

Date _____

Page _____

operation of transistor.

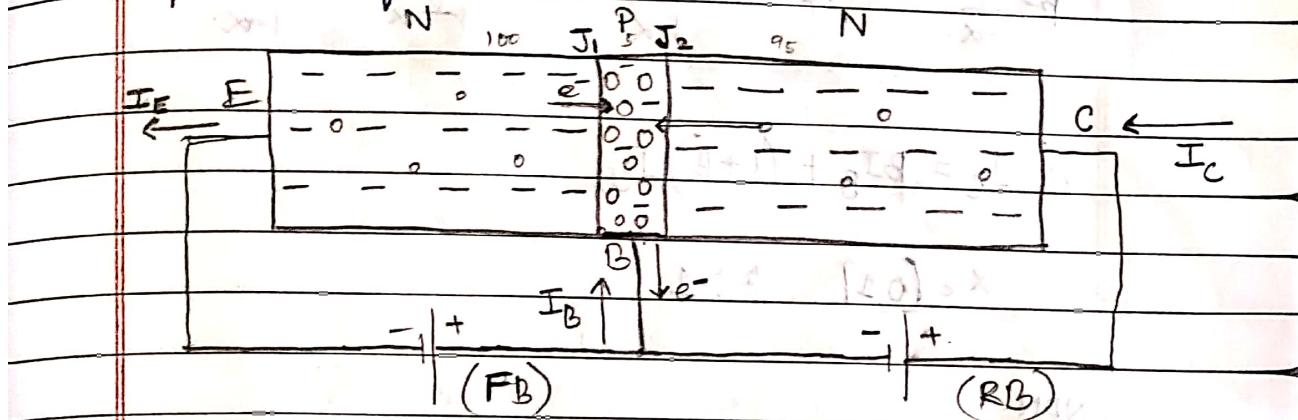

$$I_E = I_B + I_C \quad (\text{according to KCL})$$

I_E = emitter current

$$I_C \approx I_E \quad (\text{expectation})$$

I_B = base current

I_C = collector current

α = current gain

$$\alpha = \frac{I_C}{I_E}$$

Ideally $\alpha = 1$.

$$\alpha = 0.95 \text{ to } 0.98$$

$$I_C = I_{C(\text{majority})} + I_{C(\text{minority})}$$

I_{C0} = reverse saturation current / leakage current

↑
open circuit

20/12/22

$$I_E = I_B + I_C$$

$$I_C = I_{C(\text{maj.})} + I_{C0}$$

$$= \alpha I_E + I_{C0}$$

$$I_C = \alpha (I_B + I_C) \neq I_{C0}$$

$$I_C = \alpha I_B + \alpha I_C + I_{C0}$$


$$I_C [1 - \alpha] = \alpha I_B + I_{C0} \Rightarrow I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + \left(\frac{1}{1-\alpha} \right) I_{C0}$$

$$\beta = \frac{\alpha}{1-\alpha} \quad 1+\beta = 1 + \frac{\alpha}{1-\alpha} = \frac{1-\alpha+\alpha}{1-\alpha} = \frac{1}{1-\alpha}$$


$$\therefore I_C = \beta I_B + (1+\beta) I_{CO}$$

$$\alpha \in [0,1], \beta > 1$$

NPN.

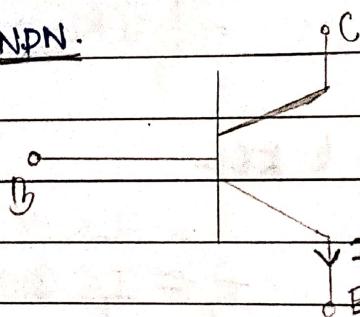

PNP.

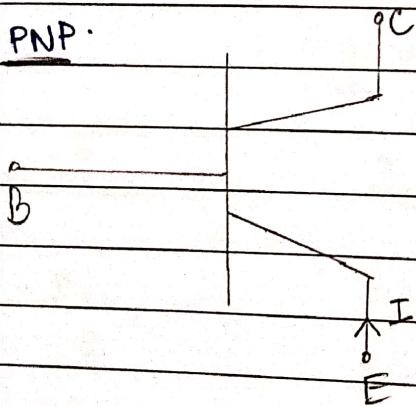


TRANSISTOR CONFIGURATION.

common base transistor configuration

common emitter transistor configuration

common collector transistor configuration

COMMON BASE CONFIGURATION (NPN)

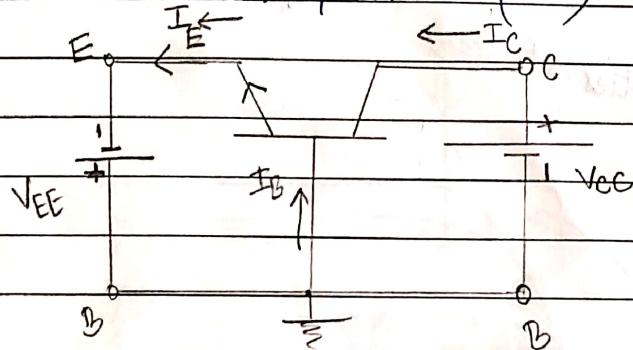


$$\text{INPUT CURRENT} = I_E$$

$$\text{INPUT VOLTAGE} = V_{BE}$$

$$\text{OUTPUT CURRENT} = I_C$$

$$\text{OUTPUT VOLTAGE} = V_{CB}$$

Input characteristics.

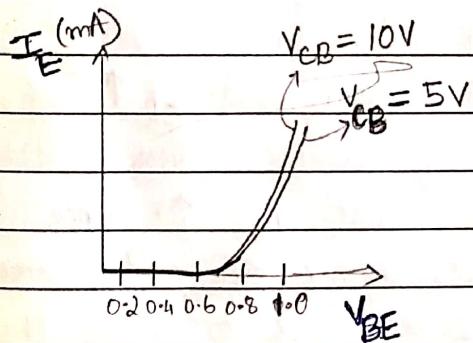

$$\text{Input resistance} = \frac{\Delta V_{BE}}{\Delta I_E}$$

For minor change in V_{BE} ,
the ΔI_E is huge. Hence
input impedance is very low
as Forward bias $\rightarrow R$ is very small.


(*) Input voltage v/s. input current for different values of output voltage

(*) As output voltage $V_{CB} \uparrow$, $I_E \uparrow$.

→ V_{CB} is the output voltage, when it is increased, the ^{emitter} current also increases.
The collector-base junction gets more reverse biased
hence collector-base junction width increases, base
width decreases hence less voltage is required for
 V_{BE} to maintain forward bias. I_E increases as
 $V_{CB} \uparrow$ ($I_C \uparrow$ and less e-h pairing in base).

20/12/22.

[Base width modulation]

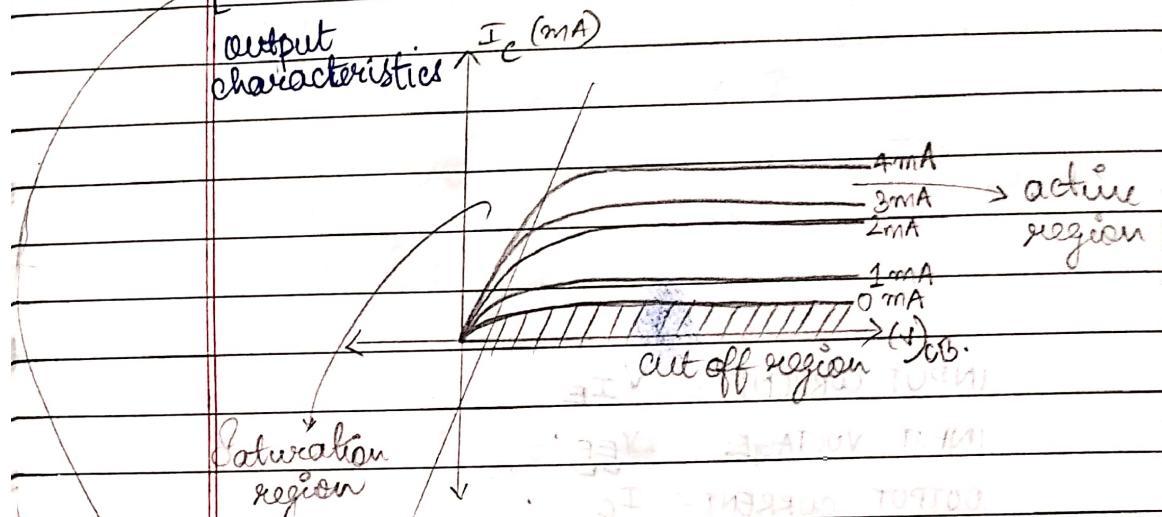


- * Output voltage vs output current for different values of input current.

FORWARD ACTIVE REGION

EARLY EFFECT :-

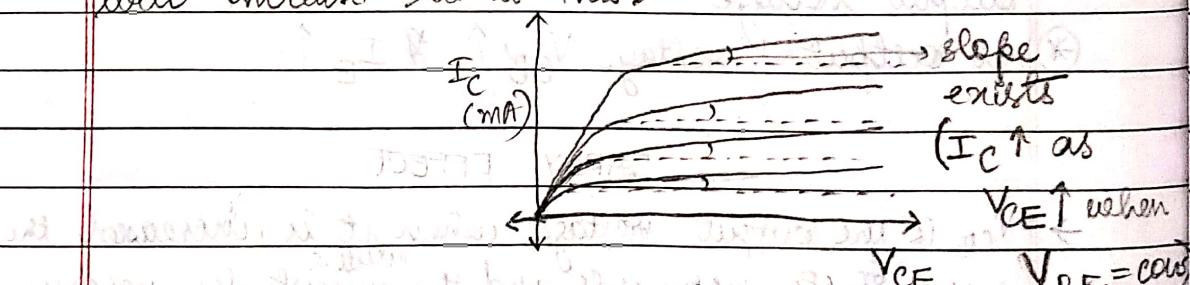When V_{BE} is kept constant and $V_{CE} \uparrow$ (effectively $V_E \uparrow$) the reverse nature of collector base increases, hence the depletion region width (w_c) \uparrow . Hence base width decreases, hence less chance of e-h recombination. More e⁻ will thus be able to cross the base without recombination. Thus collector current will increase. Due to this:-



→ about output characteristics :-

* Active region : Even if $V_{CE} \uparrow$, I_c remains almost constant. For fixed value of emitter current it is almost independent of V_{CE} . $I_c = \alpha I_e$

* Saturation region : As $V_{CE} \downarrow$, the $I_c \downarrow$ used for amplification


* Cut-off region : $I_{ct} = I_c + I_{co}$ as I_c only dependent on I_e

Reverse sat. $\propto T$
current

when $I_e = 0^\circ$, $I_{ct} \approx 0$
only due to minority charge carriers $\rightarrow I_{co}/I_{cbo}$

Reverse saturation current

common emitter configuration

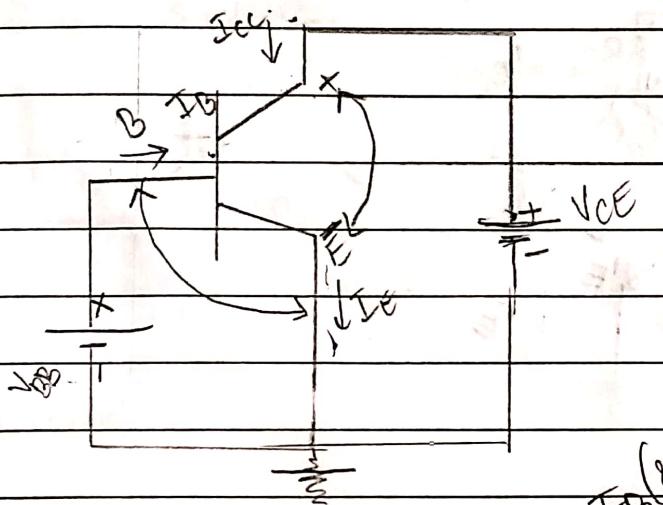

Input characteristics

$$I/P \text{ current} = I_B$$

$$I/P \text{ voltage} = V_{BE}$$


$$O/P \text{ current} = I_C$$

$$O/P \text{ voltage} = V_{CE}$$


$$I_C = \beta I_B$$

(x^A)

This form of I-V curve

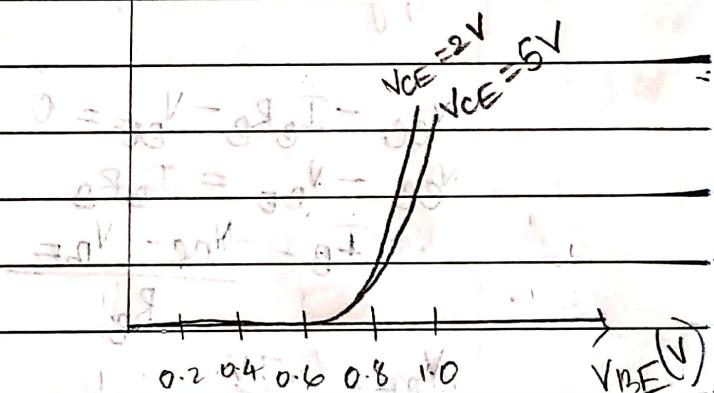

load line analysis As $V_{CE} \uparrow$,

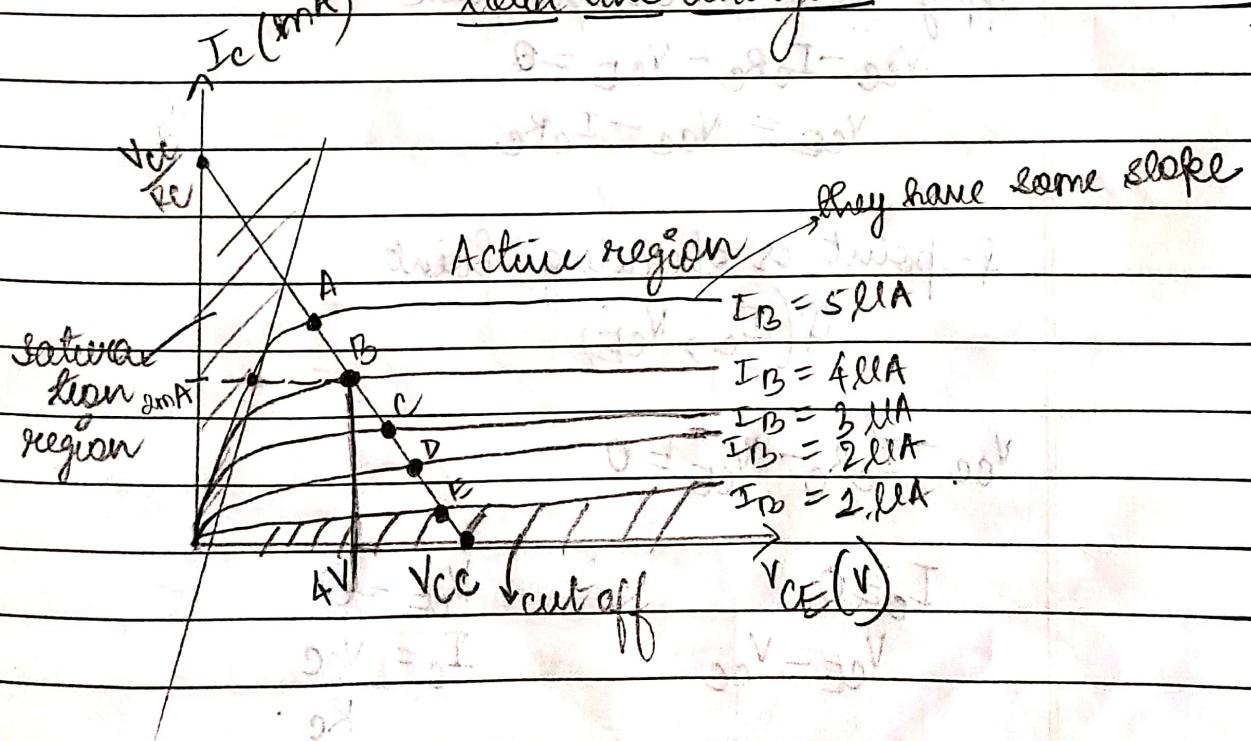


03/12/22

Date _____

Page _____

Biasing

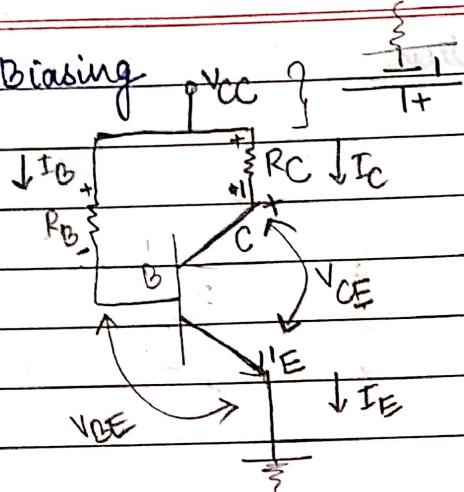

Apply KVL to input side

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$V_{CC} - V_{BE} = I_B R_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$V_{BE} = 0.7\text{V}$$

Apply KVL to output side.

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

Q-point or operating point

$$Q(I_C, V_{CE})$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$I_C = 0$$

$$V_{CE} = V_{CC}$$


$$V_{CE} = 0$$

$$I_C = \frac{V_{CC}}{R_C}$$

23/12/22

Date _____

Page _____

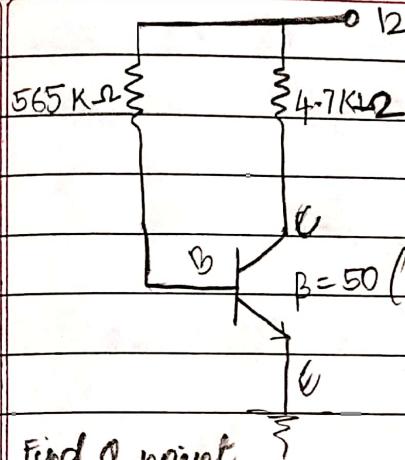

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{565}$$


$$I_C = \beta I_B = 50 \times 20 \times 10^{-6} = 1 \times 10^{-3} = 1 \text{ mA}$$

Find Q point

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C = 12 - 10^3 \times 4.7 \times 10^{-3} = 7.3 \text{ V}$$

Q point (1mA, 7.3V)

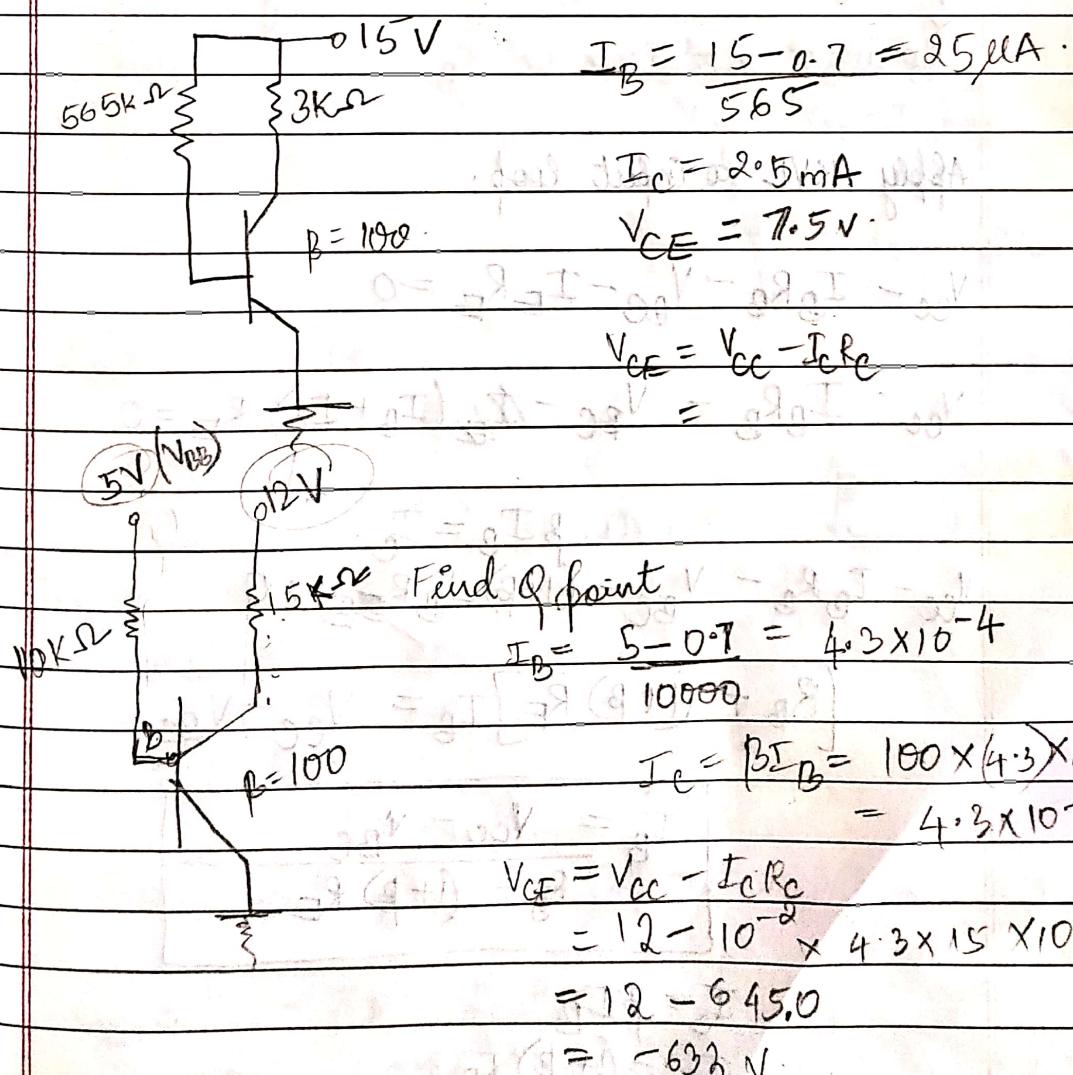

$$I_B = \frac{15 - 0.7}{565} = 25 \mu\text{A}$$

$$I_C = 2.5 \text{ mA}$$

$$V_{CE} = 7.5 \text{ V}$$

$$V_{CE} = V_{CC} - I_C R_C$$

Find Q point

$$I_B = \frac{5 - 0.7}{10000} = 4.3 \times 10^{-4}$$

$$I_C = \beta I_B = 100 \times 4.3 \times 10^{-4} = 4.3 \times 10^{-2}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 12 - 10^{-2} \times 4.3 \times 15 \times 10^3$$


$$= 12 - 645.0$$

$$= -633 \text{ V}$$

21/12/22

Date _____
Page _____

Emitter Bias configuration

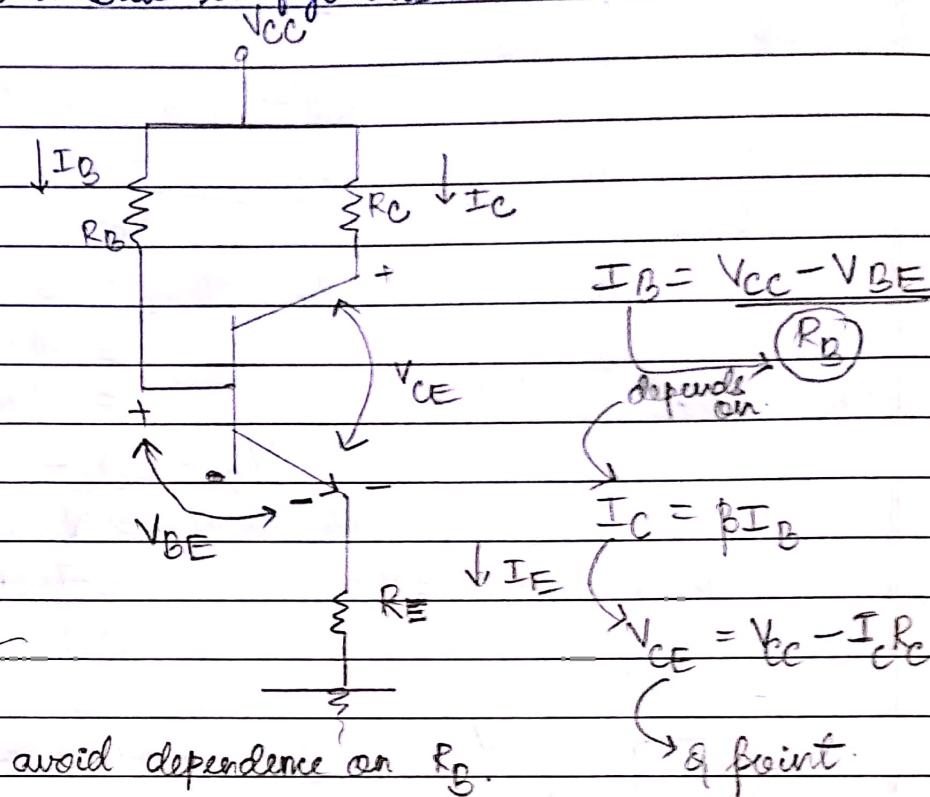

Apply KVL to input loop.

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - \beta I_B (I_B + I_C) R_E = 0$$

$$\beta I_B = I_C$$

$$V_{CC} - I_B R_B - V_{BE} - (1+\beta) I_B R_E = 0$$

$$[R_B + (1+\beta) R_E] I_B = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E}$$

$$I_C = \beta I_B$$

$$I_E = (1+\beta) I_B$$

27/12/22

Date _____

Page _____


Apply KVL to output loop.

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Q point (I_C, V_E)

$$V_{CC} = 20 \text{ V}$$

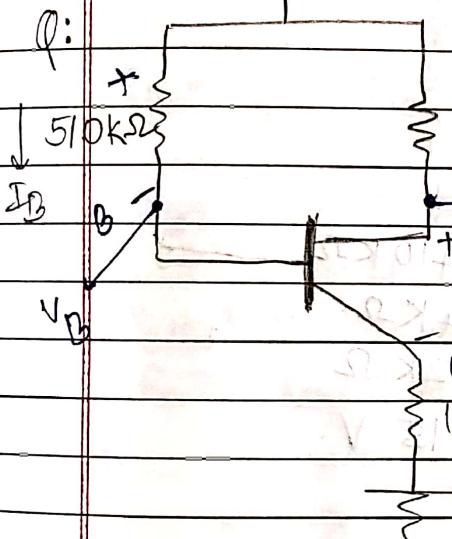

Find Q point, V_C, V_B, V_E

$$V_C = V_{CC} - I_C R_C$$

$$V_B = V_{CC} - I_B R_B$$

$$V_{CE} = V_C - V_E$$

$$\therefore V_E = V_C - V_{CE} \\ = I_E R_E$$

$$I_B = V_{CC} - V_{BE}$$

$$R_B + (1+\beta) R_E$$

$$= 20 - 0.7$$

$$V_C = 13.04 \text{ V.}$$

$$V_B = 12.04 - 5.1233$$

$$(510 \text{ k}\Omega + (1+100) 1.5 \text{ k}\Omega) \times 10^3$$

$$V_E = 4.416$$

$$I_B = 29.17 \text{ mA} \quad 0.02917 \times 10^{-3} \\ 29.17 \times 10^{-6}$$

$$I_C = 100 \times 29.17 \text{ mA} = 2917 \text{ mA}$$

$$I_C = 2917 \text{ mA}$$

$$I_C = 2.9 \text{ mA}$$

$$I_E = (1+\beta) I_B = 2.917 \text{ mA}$$



$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 20 - (2.9)(2.4 \text{ k}\Omega) - 2.917(1.5 \text{ k}\Omega)$$

$$V_{CE} = 8.66 \text{ V}$$



8/11/2022

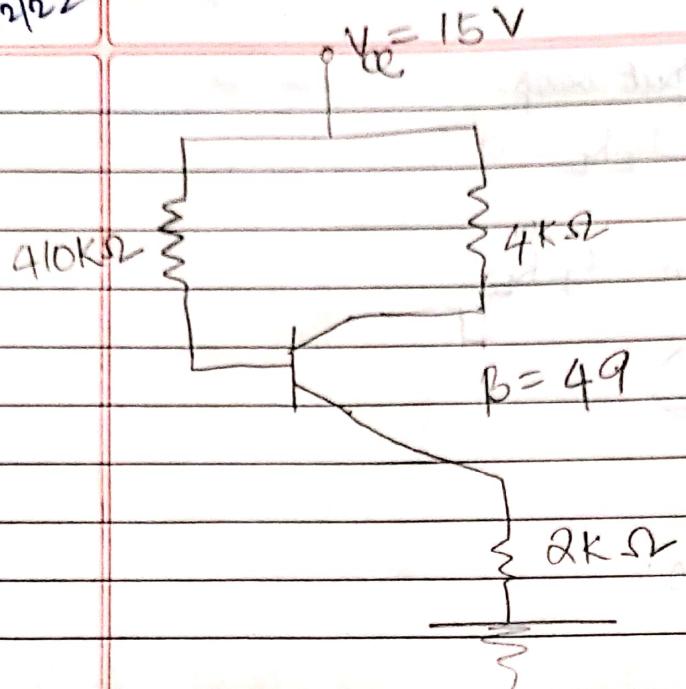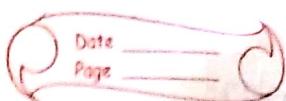

Q point = ?

$$I_C = ?$$

$$V_{CE} = ?$$

$$R_B = 410\text{ k}\Omega$$

$$R_C = 4\text{ k}\Omega$$

$$R_E = 2\text{ k}\Omega$$

$$V_{CC} = 15\text{ V}$$

Ans

$$I_C = \frac{V_{CC}}{R_C}$$

~~$$V_{CE} = V_{CC} - I_C R_C = V_{CC} - I_C R_E$$~~

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)R_E} = \frac{15 - 0.7}{410\text{ k} + (50)(2\text{ k})}$$

$$I_E = (1+\beta)I_B = 104\text{ mA} = \frac{14.3}{510\text{ k}}$$

$$= 0.028\text{ mA}$$

$$I_C = 49 \times 0.028 = 1.37\text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 15 - 1.37 \times 4 - 2 \times 1.4$$


$$V_{CE} = 6.72\text{ V}$$

27/10/22

Date _____
Page _____

Q: Design value of R_B & R_C .
 $V_{CC} = 10V$, $I_C = 5mA$ $V_{CE} = 5V$. } fixed bias.
 $B = 100$.

Sol:

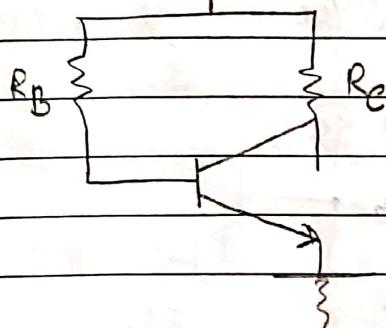

$$R_B = ? \quad R_C = ?$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$R_B = V_{CC} - V_{BE}$$

$$I_C = \beta I_B$$

$$I_B$$


$$I_B = \frac{I_C}{\beta} = \frac{0.05mA}{100} = 0.0005mA$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C}$$

$$R_B = 186K\Omega$$

$$R_C = 1K\Omega$$

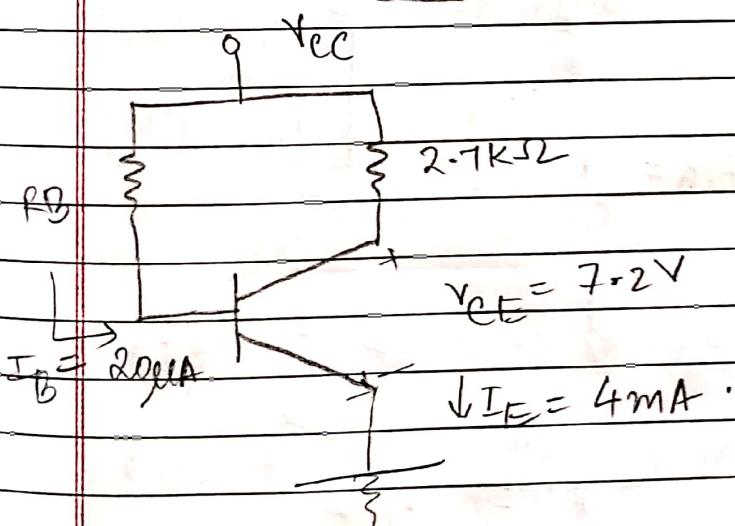

calculate I_C , V_{CC} , β , R_B .

$$I_B = \frac{\beta I_C}{\beta} \quad V_{CC} - \beta I_C R_C - V_{CE} - I_E R_E = 0.$$


$$I_C = I_E + I_B \quad N_{CC} =$$

$$= 4 + 20 \times 10^{-3}$$

$$I_C = 4.02mA$$

28/12/22

Voltage Divider biasing.

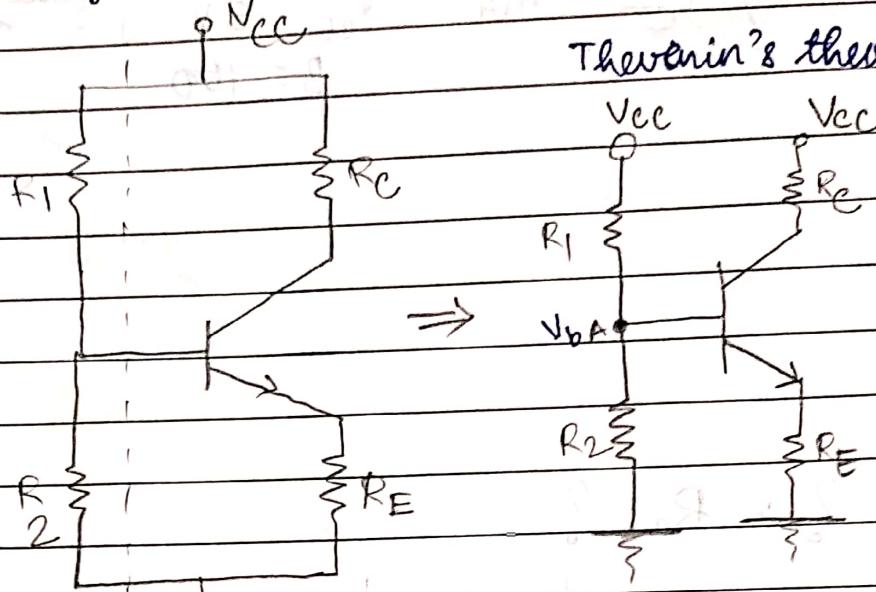


$$V_{th} = \frac{V_{cc} \times R_2}{R_1 + R_2}$$

V_{CC} is input voltage
 R_1 and R_2 are in series.

R_2 is considered, as voltage at point A is same as voltage across R_2 . $\left[V_{AB} = V_{AC} \right]$

$$V_{R_1} = \frac{V_{CC} \times R_1}{R_1 + R_2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

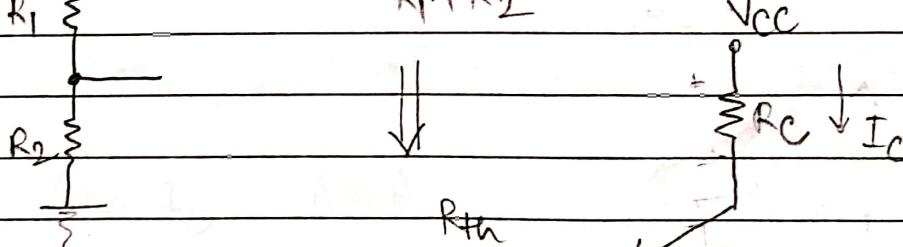

The diagram shows a common-emitter circuit configuration. A vertical input voltage source V_{in} is connected between the base terminal and ground. The output voltage V_{out} is measured across the load resistor R_L . The circuit consists of a dependent current source (emitter follower) with a gain of 1, a dependent voltage source (emitter-coupling capacitor), and a common-emitter stage. The common-emitter stage has a Thévenin resistance R_{Th} at its input and a Thévenin voltage V_{Th} at its output. The collector current I_E flows through the collector resistor R_E and is split into two paths: one through the load R_L and another through the feedback capacitor C_F back to the base. The base current I_B is indicated as flowing into the base terminal.

Apply KVL

$$V_{in} - I_D R_{in} - V_{BE} - I_F R_F = 0$$

$$V_{BE} - I_B R_{BE} - V_{BE} - (1+\beta) I_B R_E = 0$$

$$I_B = \frac{V_{BE} - V_{TH}}{R_E}$$

$$\overline{R_m + (1+\beta) R_E}$$

$$I_C = \beta R_B$$

$$I_E = (1+\beta) I_B$$

Apply KVL to collector.


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Q point (I_C , V_{CE}).

$$V_{CC} = 16V$$

Q:

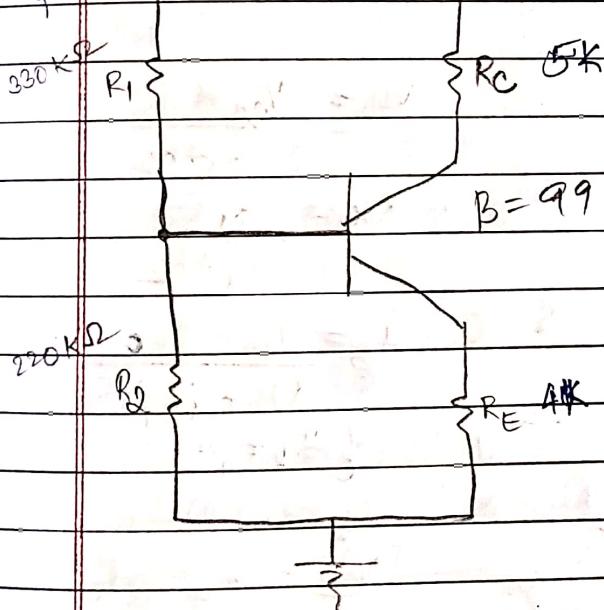

$$V_{th} = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{16 \times 220k}{220k + 330k} = 6.4V$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{330k \times 220k}{330k + 220k} = 132 \times 10^3 k\Omega$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1+\beta) R_E}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_C = \beta I_B$$

$$I_E = (1+\beta) I_B$$

$$I_B = 0.0107 mA$$


$$= 10.7 \mu A$$

$$I_C = 105.93 \mu A = 1.0593 mA$$

$$I_E = 1070 \mu A = 1.07mA$$

Qpt: (I_C, V_{CE})
: $(1.05mA, 6.47V)$


28/12/22

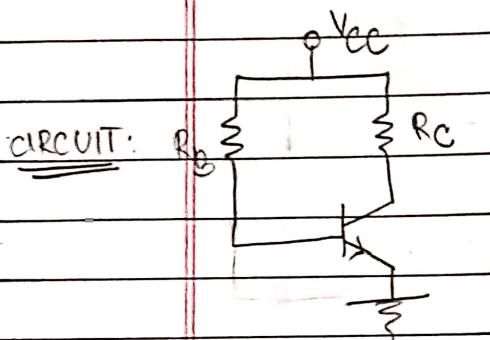Date _____
Page _____FIXED BIAS

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$


$$V_{CE} = V_{CC} - I_C R_C$$

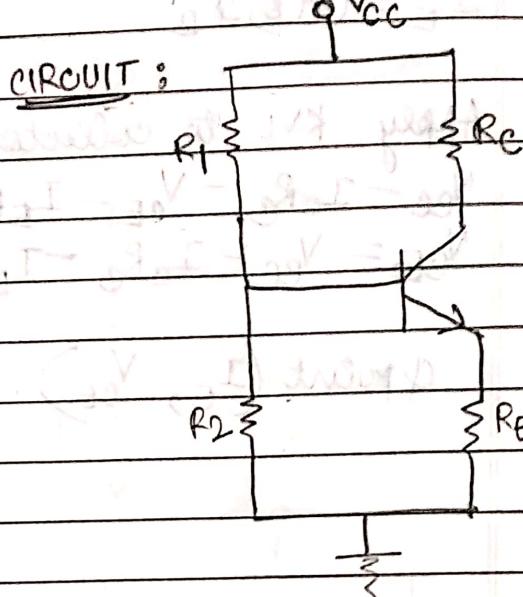VOLTAGE DIVIDER BIAS

$$V_{TH} = \frac{V_{CC} * R_2}{R_1 + R_2}$$

EMITTER BIAS

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

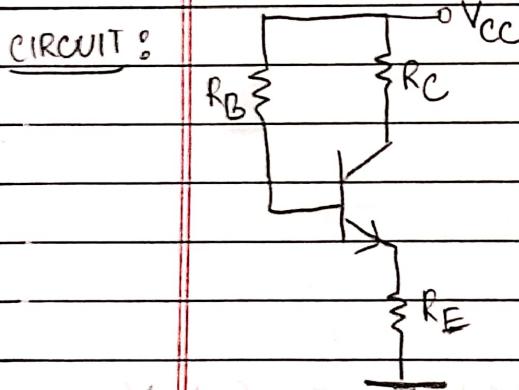

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1+\beta) R_E}$$

$$I_C = \beta I_B$$

$$I_E = (1+\beta) I_B$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E}$$

$$I_C = \beta I_B$$

$$I_E = (1+\beta) I_B$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

consider:-


$$V_{BE} = 0.7V \text{ for Si transistor.}$$

parameters of Q point

$$(I_C, V_{CE})$$

28/12/22

+12V

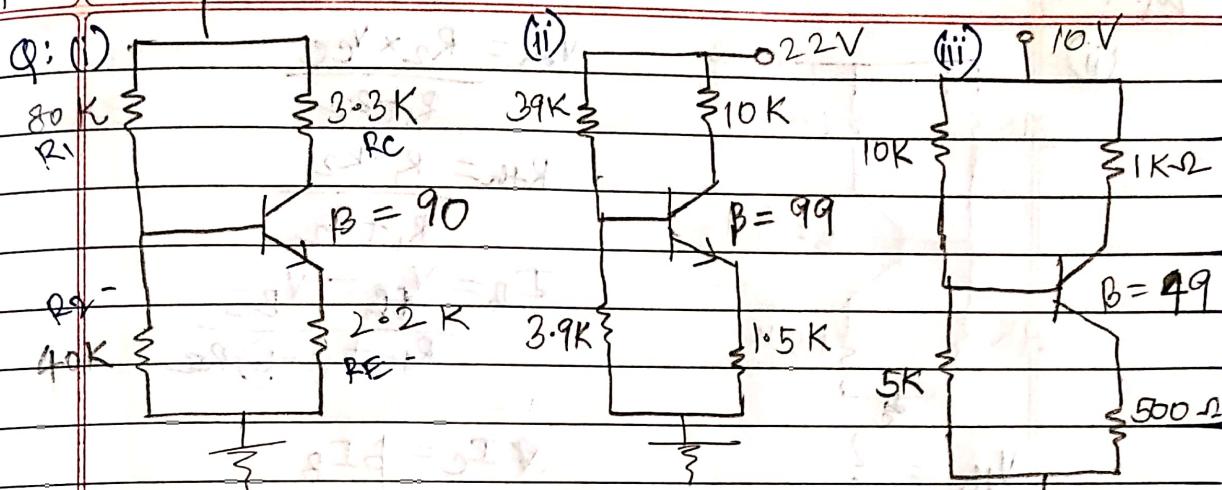 Date _____
 Page _____
Find Q point i.e. V_{BE}

$$(i) \quad V_{BE} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

$$= 4 \text{ V.}$$

$$R_{FE} = \frac{80 \times 40}{120 \times 10^{-3}} \times 10^{-6}$$

$$= 3200 \times 10^{-3}$$

$$A_{vD} = 26.6 \times 10^{-3} \Omega \cdot 5.0 = 133$$

$$\approx 26.6 \text{ k}\Omega$$

$$I_B = \frac{4 - 0.7}{(26.6 + 91 \times 2.2) \times 10^{-3}}$$

$$= 0.0145 \text{ mA}$$

$$= 14.5 \text{ mA}$$

$$I_C = 90 \times 14.5$$

$$= 1.305 \text{ mA}$$

$$I_E = 91 \times 0.0145$$


$$= 1.3195 \text{ mA}$$

$$V_{CE} = 12 - 1.305 \times 2.2 - 3.3 - 1.3195 \times 2.2$$

$$= 4.79 \text{ V.}$$

28/10/22

(ii).

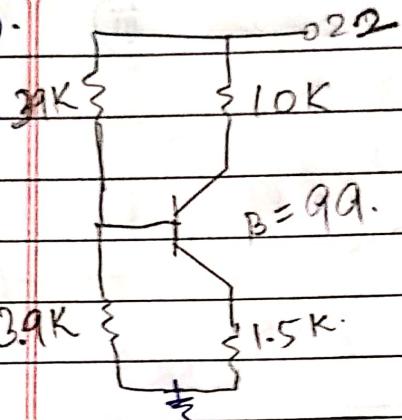

$$V_{in} = \frac{R_2 \times V_{cc}}{R_1 + R_2}$$

$$R_{in} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_{in} + (1+B)R_E}$$

$$V_{in} = ?$$

$$R_{in} = ?$$

$$I_B = ?$$

$$I_C = ?$$

$$I_E = ?$$

$$V_{CE} = ?$$

$$I_C = \beta I_B$$

$$I_E = (1+\beta) I_B$$

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$

$$V_{in} = 3.9 \times 2.2 = 8.6 \text{ V}$$

$$R_{in} = 3.54 \text{ k}\Omega$$

$$I_B = \frac{2 - 0.7}{3.54 + (100 \times 1.5)} = \frac{1.3}{3.54 + 150} = 8.4 \mu\text{A}$$

$$I_C = 8.4 \times 0.83 \text{ mA} = 6.8 \text{ mA}$$

$$I_E = 8.4 \times 0.84 \text{ mA} = 7.1 \text{ mA}$$

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$


$$= 22 - 0.83 \times 10 - 0.84 \times 1.5$$

$$= 12.44 \text{ V}$$

28/12/22

Date _____

Page _____

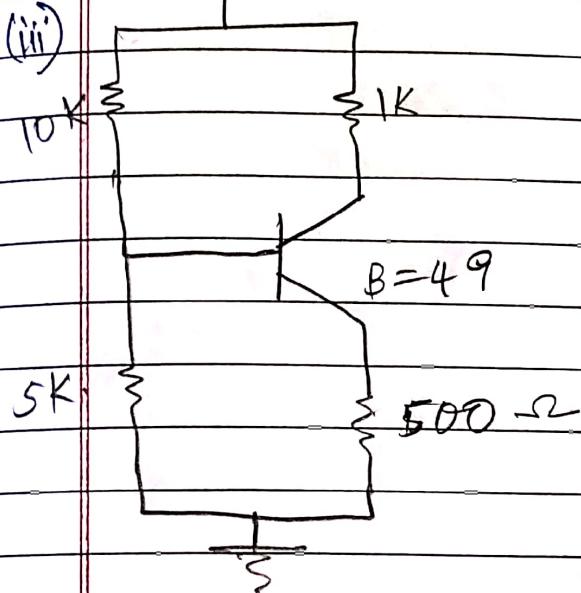

$$V_{th} = \frac{5 \times 10}{5 + 10} = \frac{50}{15} = 3.33 \text{ V.}$$

$$R_{th} = \frac{10 \times 5}{10 + 5} = \frac{50}{15} = 3.33 \text{ k}\Omega.$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1+B)R_E}$$

$$I_B = \frac{3.33 - 0.7}{10^3 \times 3.33 + (50 \times 500)} = \frac{2.63}{25900} = 2.63 \mu\text{A}$$

$$I_B = 0.0001 \times 10^{-3} = 92.8 \mu\text{A}$$



$$I_C = 49 \times 92.8 \mu\text{A} = 4.547 \text{ mA}$$

$$I_E = 50 \times 92.8 \mu\text{A} = 4640.00 \mu\text{A} = 4.64 \text{ mA}$$

$$V_{CE} = V_{CC} - 3.133 \text{ V.}$$

30/12/2022

$V_{CC} = 12V$

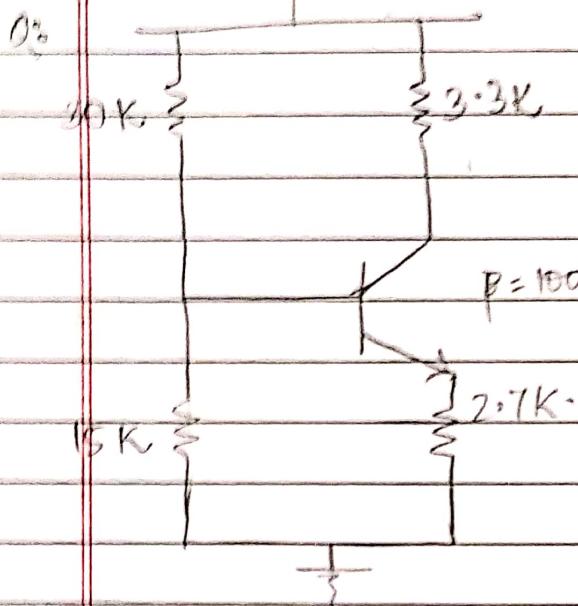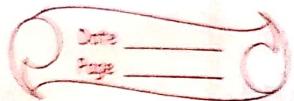

$$V_{TH} = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{12 \times 15}{15 + 30} = 4V$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{30 \times 15}{45} = 10k\Omega$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1+B)R_E} = \frac{4 - 0.7}{10 + (101 \times 2.7)} = 0.0116mA$$

~~$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1+B)R_E} = \frac{4 - 0.7}{10 + (101 \times 2.7)} = 0.0116mA$~~

$$I_C = 100 \times 1.167 = 116.7mA$$

$$I_E = 101 \times 1.167 = 1171.6mA$$

$$V_{CE} = V_C - I_C R_C - I_E R_E = 12 - 116.7 \times 3.3 - 1.1716 \times 2.7 = 5.0086V \approx 5.013V$$


$$\delta(I_{CO}) = ?$$

30/12/22

Date _____

Page _____

Q. P:

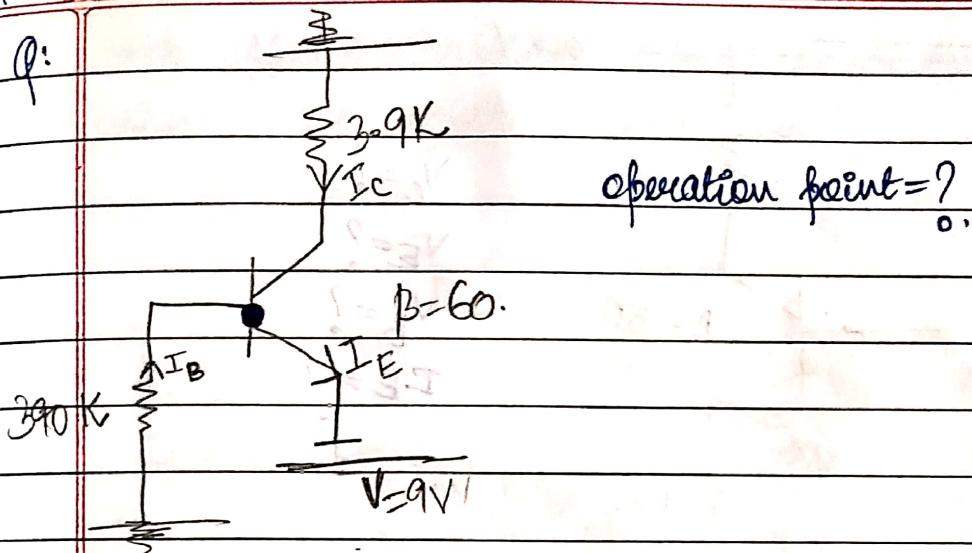

$$-I_B R_B + R_C I_C = 0 \quad \text{--- (1)}$$

$$\text{or} -I_B R_B + 9 = 0 \quad \text{--- (2)}$$

$$R_C I_C = 9$$

$$I_C = \frac{9}{R_C} = \frac{9}{3.9} \text{ mA}$$

$$V_{CE} = B - I_C R_C + 9$$

$$= -2.3 \times 3.9 + 9 = 6.03 \text{ V}$$

$$A_{vB} = \frac{V_{CE}}{V_{BE}} = \frac{6.03}{0.03} = 201$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$


$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

$$A_{vB} = A_{vD} \times A_{vE} = 201 \times 10 = 2010$$

30122.

Date _____
Page _____

3.

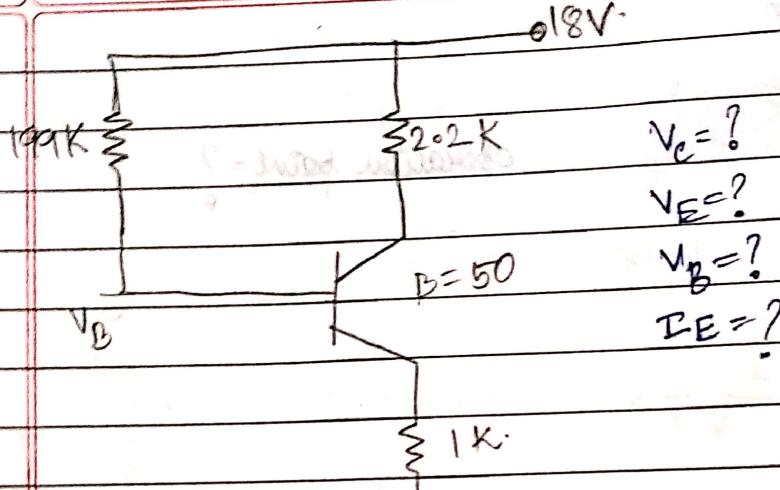

$$V_{CE} \quad I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)R_E} = \frac{18 - 0.7}{199 + 51 \times 1} = \frac{17.3}{199 + 51} = 17.3$$

$$I_C = \beta I_B = 50 \times 17.3 = 865 \text{ mA} = 865 \mu\text{A}$$

$$I_E = (1+\beta)I_B = 51 \times 17.3 = 865.2 \mu\text{A} = 865.2 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_E - I_E R_E$$

$$= 18 - 865.2 \times 51 - 865.2 \times 1$$

$$= 18 - 44162 - 865.2$$


$$V_{CE} = 6.858 \text{ V}$$

$$(I_C, V_{CE}) = (3.46, 6.858)$$

30/12/22

Page _____

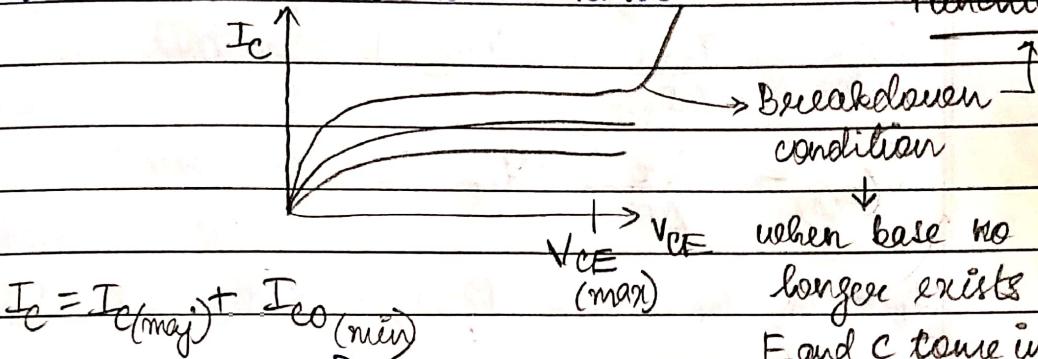Early effect \rightarrow \uparrow reverse voltage even more \rightarrow Punchthrough
 when base width doesn't exist.



\rightarrow Thermal runaway.

usually $I_{Co} = \text{constant}$



but when $T \uparrow$,

$I_{Co} \uparrow \Rightarrow I_{C,\text{Total}} \uparrow$

$$I_{S_2} = I_S \times 2^{\frac{(T_2 - T_1)}{10}}$$

\rightarrow For every 10°C rise in temp R.S.C doubles.

Thermal
runaway

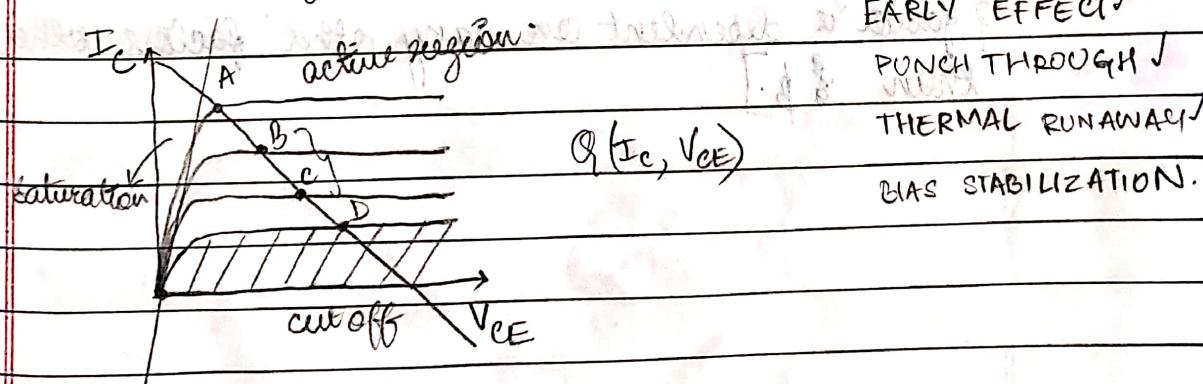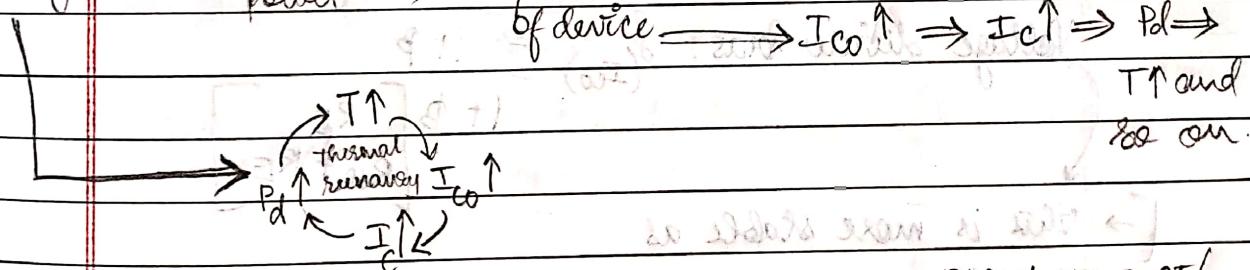

If operating point shifts, no faithful amplification as the points will not be optimum

- 1) V_{BE}
- 2) I_{Co}
- 3) β (material dependent)

3/1/23

Date _____
Page _____

$$\delta_{(I_C)} = \frac{\Delta I_C}{I_{C0}}, V_{BE}, \beta \rightarrow \text{constant}$$

$$\delta_{(I_C)} = \frac{\Delta I_C}{\Delta V_{BE}}, V_{BE}, \beta \rightarrow \text{constant}$$

$$\delta_{(I_C)} = \frac{\Delta I_C}{\Delta \beta}, V_{IE}, I_{C0} \rightarrow \text{constant}$$

$$I_0 = \frac{V_{TA} - V_{CE}}{R_H + (1+\beta)R_E}; I_C = \beta I_B; V_{CE} = V_C - I_C R_C - I_E R_E$$

→ Q point thus changes when
 V_{BE} , I_C0 and β change

→ Stability factor:-

$$\text{Fixed bias: } \delta_{(I_C)} = 1 + \beta$$


$$\text{Voltage divider bias: } \delta_{(I_C)} = \frac{1 + \beta}{1 + \beta \left[\frac{R_E}{R_H + R_E} \right]}$$

→ This is more stable as

Q factor is dependent on many other factors other than β .

4/1/23.

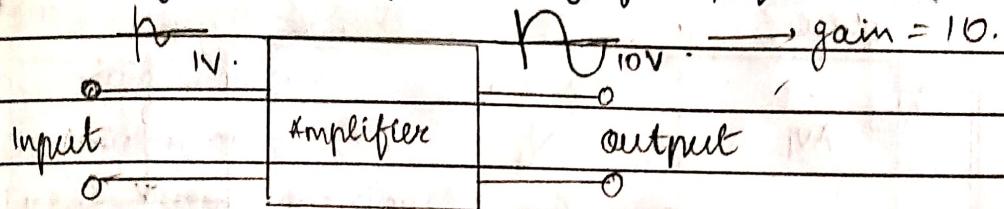→ Multistage amplifier / cascading of amplifiers.



$$\text{Gain} = \frac{\text{output}}{\text{input}}$$

$$[\text{Gain}] = \frac{V_o}{V_i} \quad \text{in units of gain}$$

$$[\text{Gain}] = \frac{V_o}{V_i} \quad \text{in dB} = 20 \log \left(\frac{V_o}{V_i} \right)$$

Actual number

Eg: $10^2 \times 10^2 \times 10^2 \times 10^2 \text{ dB}$ (not same)

$$\text{Power gain } [A_p] = \frac{\text{output power}}{\text{input power}} = \frac{P_o}{P_i}$$

$$\text{Voltage gain } [A_v] = \frac{\text{output voltage}}{\text{input voltage}} = \frac{V_o}{V_i}$$

$$\text{Current gain } [A_i] = \frac{\text{output current}}{\text{input current}} = \frac{I_o}{I_i}$$

$$\text{Power gain } [A_p]_{\text{dB}} = 10 \log \left(\frac{P_o}{P_i} \right) \quad \text{where } P = V^2/R$$

$$\text{Voltage gain } [A_v]_{\text{dB}} = 20 \log \left(\frac{V_o}{V_i} \right) \quad \text{taken } R_f = R_L$$

$$\text{Current gain } [A_i]_{\text{dB}} = 20 \log \left(\frac{I_o}{I_i} \right)$$

$$2P_f = P_o$$


∴ $A_p = A_v \cdot A_i$ and $A_p = 10^{A_v/20} \cdot 10^{A_i/20}$

\therefore $A_p = 10^{(A_v + A_i)/20}$

∴ $A_p = 10^{(A_v + A_i)/20}$

$$A_p = 10^{(A_v + A_i)/20} = 10^{(20 \log V_o/V_i + 20 \log I_o/I_i)/20}$$

∴ $A_p = 10^{(A_v + A_i)/20}$

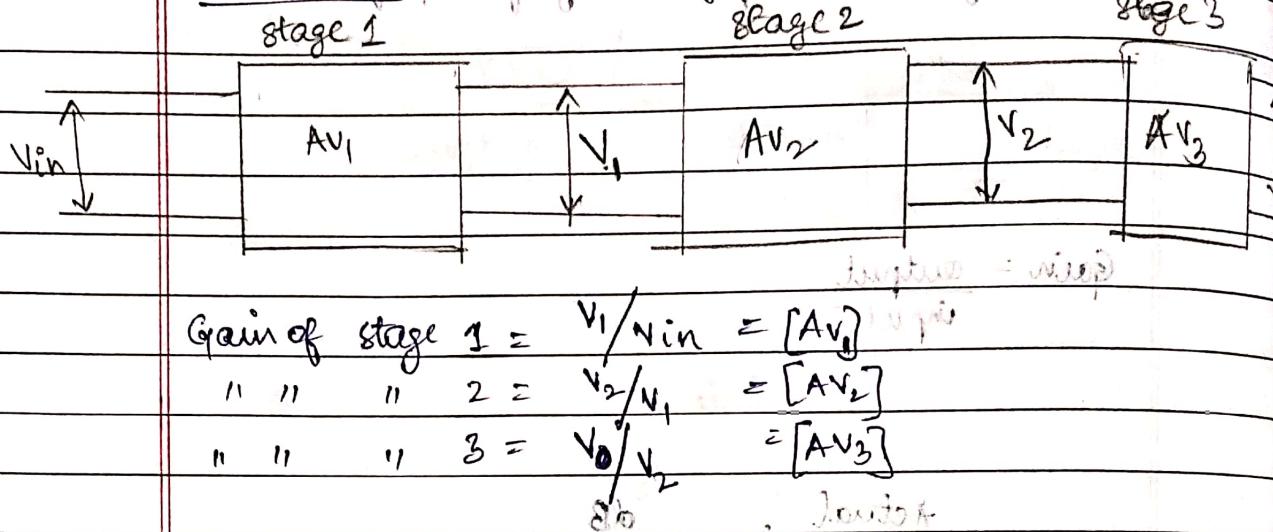

$$\text{Gain of stage 1} = \frac{V_1}{V_{\text{in}}} = [Av_1]$$

$$11 \quad 11 \quad 11 \quad 2 = \frac{v_2}{N_1} = [AV_2]$$

$$\text{II II II } \beta = \frac{V_0}{V_2} = [AV_3]$$

$$\text{overall gain } [Av] = Av_1 \times Av_2 \times Av_3$$

$$= X_1 \times \frac{X_2}{X_3} \times V_0 = V_0$$

Vinatje Vinatje

$$\text{overall gain} [A_1]_{\text{det } B} = 20 \log [A_1] + 20 \log [A_2] + 20 \log [A_3]$$

$$AV_{dB} = 20 \log \left[\frac{V_o}{V_s} \right]$$

Questions:

1. In a transistor if β changes from 99 to 199 then α changes from _____ to _____.

$$\alpha = \frac{B(\text{av})}{(1+B(\text{av}))} = \frac{199}{1+199}$$

$$= \left[\frac{99}{100} \right]_{\text{old}}^{\text{new}} = \left[+ \frac{199}{200} \right]_{\text{old}}^{\text{new}}$$

$$= 0.99 \quad = 0.995$$

2. In pnp if B-E is reverse bias and CB = forward bias
transistor is operating in inverse active region
or
reverse active

- Q3 PNP transistor has $\alpha = 0.98$ and $P_D = 40 \mu A$. calculate I_E .

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{0.02} = 49$$

$$I_E = (1 + B) I_B$$

$$= 50 \times 40$$

$$= 2000 \text{ mA}$$

4/1/23

4. A Silicon transistor has $I_{CO} = 5 \text{nA}$, $I_B = 0$, $I_C = 1 \text{mA}$.

$$\beta = ?$$

sol: $I_C = \beta I_B + (1+\beta) I_{CO}$

$$1 \text{mA} = \beta \times 0 + 5 \times 10^{-9} + \beta \times 5 \times 10^{-9}$$

$$1 \times 10^{-3} = 5 \times 10^{-9} + 5 \times 10^{-9} \times \beta$$

$$\frac{1}{5 \times 10^{-3}} = 1 + \beta$$

$$\beta = \frac{1000 - 1}{5} = \frac{995}{5} = 199$$

5. N-collector bias: $R_E = 4 \text{k}\Omega$, $R_{TH} = 60 \text{k}\Omega$.


Find stability factor: $\beta = 49$

sol: $S_{(I_{CO})} = \frac{1 + \beta}{1 + \beta} \frac{R_E}{R_E + R_E}$

$$= \frac{1 + 49}{1 + 49} \frac{4}{4 + 60}$$

$$= 50$$

$$S_{(I_{CO})} = 12.307$$

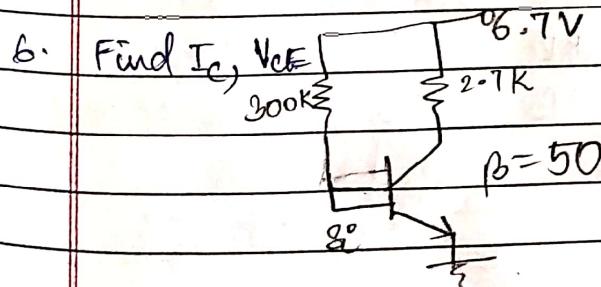

$$I_B = \frac{V_{CC} - V_B}{R_B} = \frac{6.7 - 0.7}{300 \text{k}} = \frac{6}{300 \text{k}} \times 10^3 = 20 \text{ A}$$

$$I_C = 50 \times 20 = 10^3 \text{ A}$$

$$V_{CE} = 6.7 - 1000 \times 2.7 \times 10^{-3}$$

$$V_{CE} = 4 \text{ V}$$

A/1/23

Date _____
Page _____

In the biasing circuit, design the values of R_B and R_C so that $V_{CE} = 5V$. $I_C = 1.5 \text{ mA}$ with $S_{(ce)} = 51$ and $V_{CC} = 12V$.

sol: $R_B = \frac{V_{CC} - V_{BE}}{I_B}$

$$= \frac{12 - 0.7}{1.5 \times 10^{-3}} = 7933 \Omega$$

$$R_B \rightarrow 79.33 \text{ k}\Omega$$

$$\beta = 1 + \beta$$

$$51 = 1 + \frac{\beta}{\beta + 1} = \frac{\beta + 1}{\beta + 2} = 1 + \frac{1}{\beta + 1}$$

$$\beta = 50$$

$$I_B = 1.5 = 30 \mu\text{A}$$


$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = 376.66 \text{ k}\Omega$$

$$I_C R_C = V_{CC} - V_{CE}$$

$$R_C = 12 - 5 = 4.66 \text{ k}\Omega$$

8. If a pnp transistor,

NE	N_B	N_C	J_1	J_2	Region
0	0.7	0.7	FB	RB	active
0	0.8	0.1	FB	FB	saturation
-2.7	-2.0	0	FB	RB	active
0	0	0.3	RB	RB	cut-off
0.7	0.7	0	RB	FB	reverse active

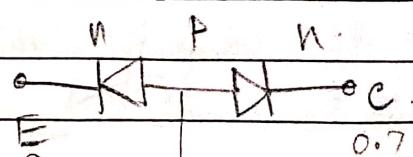

$$A_{OB} = \frac{V_{OB}}{V_{BE}} = \frac{0.7}{0.7} = 1$$



6/1/23


Q: The output characteristics of a common emitter configuration can be obtained by plotting I_C vs V_{CE} , by keeping I_B constant.

Q: Power gain of an amplifier is 20 dB, the input power required to obtain an output power of 100 watts = 1W.

$$[A_p]_{dB} = 10 \log \left[\frac{P_o}{P_{in}} \right] \quad 20 \text{ dB} = 10 \log \left[\frac{100}{P_{in}} \right]$$

$$P_{in} = \frac{100}{100} = 1 \text{ W.}$$

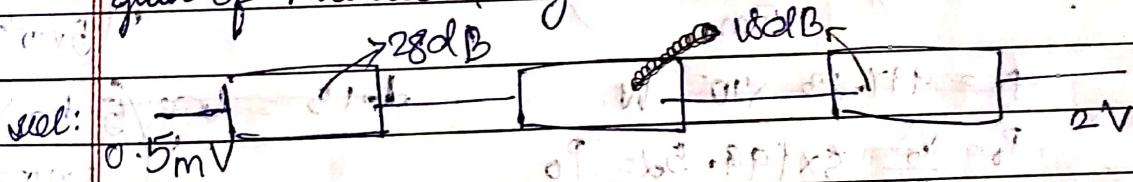Q: The output voltage of a cascaded chain of 3V amplifiers is 2V when input is 0.5 mV with 1st stage gain of 18 dB and 3rd stage are 28 dB and 18 dB. calculate the gain of middle stage.



$$\text{or } 10 \log [A_1]_{dB} = 20 \log \left[\frac{2}{0.5 \text{ mV}} \right]$$

$$= 20 \log \left[\frac{4000}{0.5 \text{ mV}} \right] = 60 \text{ dB}$$

$$= 60 \times 2 \log 2$$

$$= 72.04$$

$$72.04 = 18 + 18 + \text{middle stage gain}$$

$$\text{middle stage gain} = 26.4 \text{ dB}$$

6/1/23

Date _____
Page _____

Q: 3 voltage amplifiers are cascaded to provide an overall gain of 2000. The gains of first and last stages are 30dB & 30dB. calculate gain of middle stage.

Sol: $[A_v] = 20 \log(2000)$

$$\frac{dB}{dB} = 86.02 \text{ dB} \leftarrow 60 \text{ dB}$$

$$[A_v]_{dB} = 26.02 \text{ dB}$$

Q: The input power to an amplifier with a power gain of 23dB is 5mW. If load resistance is 100Ω calculate the output voltage.

Sol: $23 = 10 \log \left(\frac{P_o}{5 \text{ mW}} \right)$

$$23 \text{ dB} = 10 \log \left(\frac{P_o}{5 \times 10^{-3}} \right)$$

$$P_o = 997.63 \times 10^{-3} \text{ W}$$

$$115 = \log \left(\frac{P_o}{5 \times 10^{-3}} \right)$$

$$P_o = \frac{V_o^2}{R} = 5 \times 199.52 = P_o$$

$$\times 10^{-3}$$

$$P_o = 14.12 \times 5 \times 10^{-3}$$

$$V_o = 515.85 \text{ V} \quad P_o = 997.63 \quad P_o = 70.62 \times 10^{-3}$$

$$P_o = \frac{V_o^2}{R}$$

$$P_o = \frac{997.63 \times 10^{-3}}{100} \text{ W}$$

$$V_o = \sqrt{997.63 \times 10^{-3} \times 100} = 9.988 \text{ V}$$

Q: An amplifier has voltage gain of 46dB to obtain an output of 2V. The input voltage should be = 0.01V

Q: The power gain of an amplifier is 23dB and the output resistance is $10K\Omega$. If the output voltage = 100V calculate the input power to the amplifier.

$$0.005 \text{ W}$$

Q: 3 amplifier stages are cascaded with 0.05 V input providing 150 V output. If voltage gain of first stage is 20 and input to the third stage is 15V.


Find i) overall gain

ii) voltage gain of second and third stage.

iii) input voltage of the second stage.

iv) decibel voltage gain at each stage

v) overall decibel gain

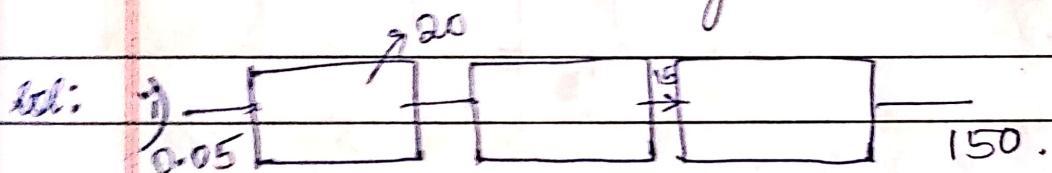

$$\text{overall gain} = \frac{150}{0.05} = 3000$$


ii) 15, 10

iii) 10, 1


iv) 26.02 dB, 23.52, 20 dB

v) 69.54 dB

10/11/22

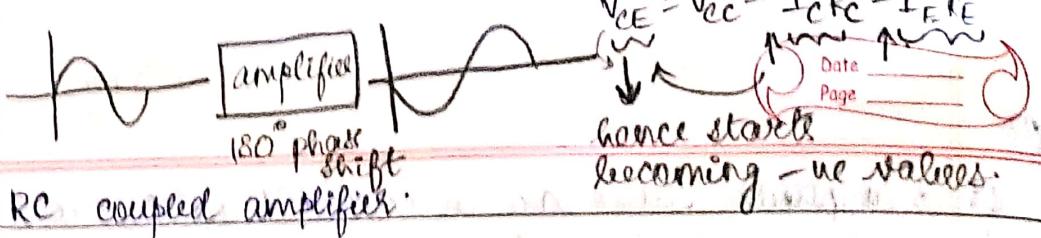

RC coupled amplifier.

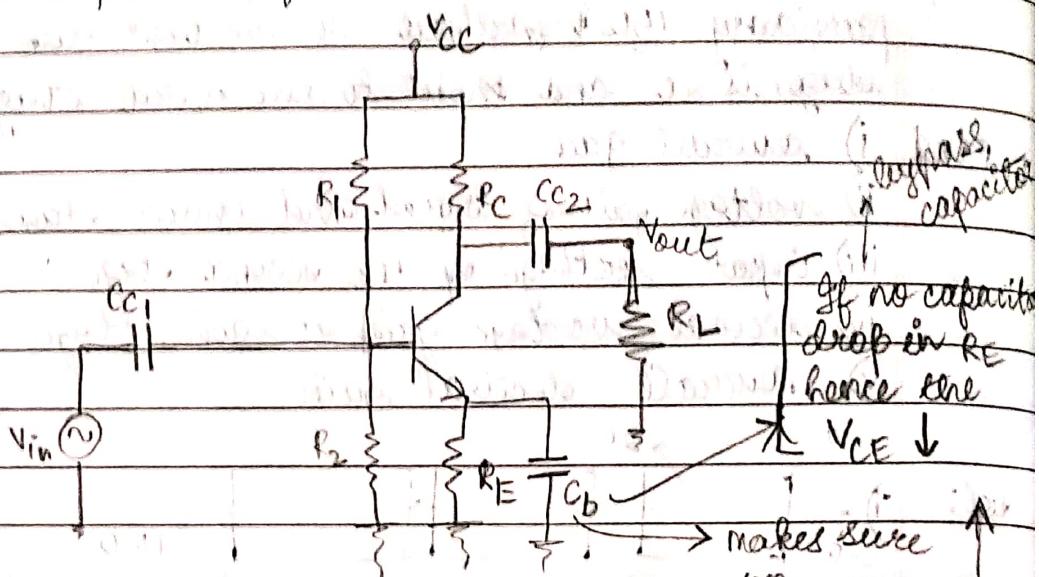

C_{C_1} and C_{C_2} - coupling capacitors
 \downarrow
 makes sure no DC component occurs across the load.

\downarrow
 makes sure that no DC component goes into transistor's base

If no capacitors drop in RE hence the $V_{CE} \downarrow$

makes sure no -ve feedback creates ac ground.

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$


DC : $f=0 \Rightarrow X_C \rightarrow \infty$
 hence open circuit

 C_{C_1} - input coupling capacitor C_{C_2} - output coupling capacitor

→ Frequency response of RC coupled amplifier.

AC analysis - capacitors → short circuited

$$DC \text{ source} = 0$$

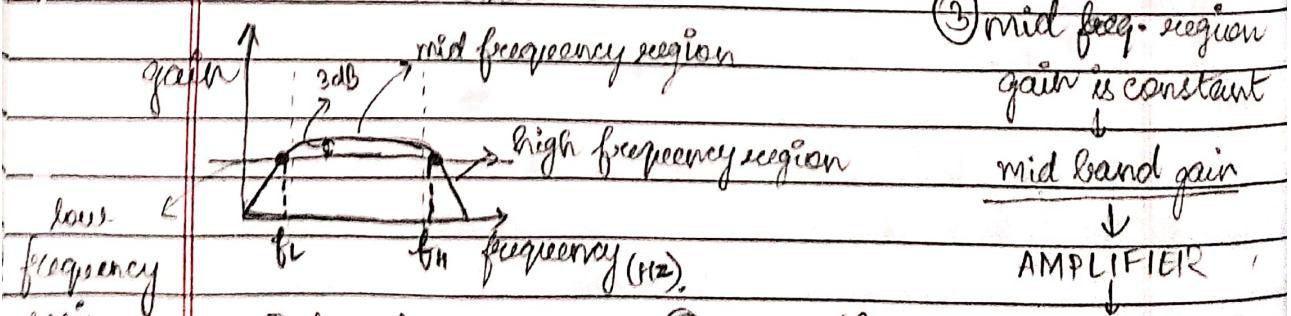

(1) low freq.

$$X_C = \frac{1}{2\pi f C}$$

$f \downarrow \quad X_C \uparrow \text{gain}$
 coupling & bypass drop in gain

(2) high freq.

$$X_C = \frac{1}{2\pi f C}$$

junction capacitances dropping gain



Scanned with OKEN Scanner

10/10/23

Band width

→ The range of frequencies over which the circuit operates as an amplifier satisfactorily.

f_L = lower cut off freq.

f_H = upper cut off freq.

$$Bw = f_H - f_L$$

→ Midband gain = V, gain at f_L $f_H = \frac{V}{\sqrt{2}}$ at half power point

Q: An amplifier has a band width of 500 KHz if the lower cut off frequency is 25 Hz. What is the higher cut off frequency. Also find voltage gain at low f_L when the midband gain is 120.

solt: $\Delta f = 500 \times 10^3 \text{ Hz}$.

$$f_L = 25 \text{ Hz}$$

$$f_H = (5 \times 10^5 + 25) \text{ Hz} = 500025 \text{ Hz}$$

$$Vg(\text{mid}) = 120$$

$$30 \log 0.707$$

$$Vg \text{ at } f_L = 120 \rightarrow 30 \text{ dB point}$$

$$= 84.85$$

Q: Gain of amplifier at $f_L = 100$ Hz. At mid-band = ?

Solt: $Vg_{mb} = \frac{Vg(f_H)}{\sqrt{2}} = \frac{120}{\sqrt{2}}$

$$\therefore Vg(\text{mb}) = 120\sqrt{2}$$

8. Mean time

$$t_{mean} = 0.11 \times 11.00 = 1.21$$



11/19/22

ideally amplifier



similar to capacitors

all positive



charging - positive
discharging - negative

(p n)

$$20 \log(0.70) = -3 \text{ dB}$$

freq. response

Ques

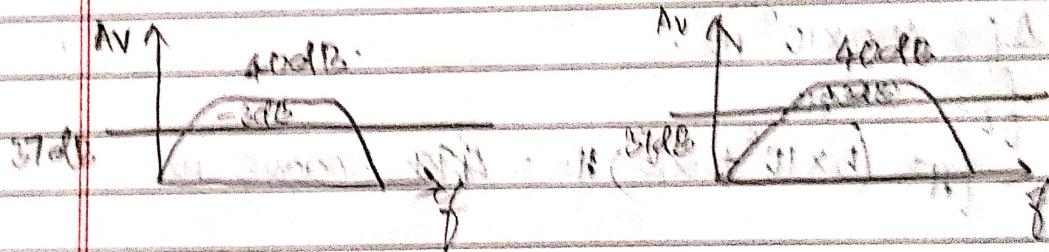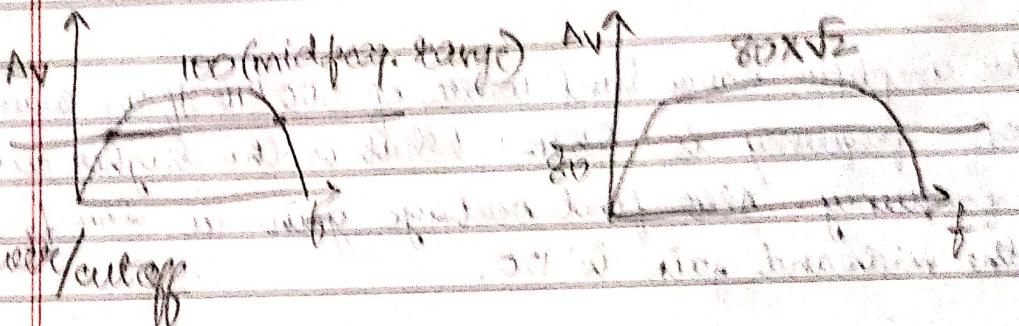

Q: The gain of an amplifier is 100 at mid frequency and the gain falls by 6 dB at cut off frequencies calculate output voltage at cut off frequencies if input is 1mV.

$$\text{Sol: } V_{in} = 1 \text{ mV} \rightarrow V_o = \frac{V_o}{V_{in}}$$

$$V_g = 100 \text{ (m-f)}$$

$$V_g \text{ at } \Delta V = 6 \text{ dB.}$$

$$V_{in}$$

$$100 \times V_{in} = V_o$$

$$V_o = 100 \text{ dB} \times V_{in} = 10 \times 10^{-3}$$

$$V_g = 40 - 6 = 34 \text{ dB}$$

$$\therefore V_g = 34 = \frac{V_o}{V_{in}}$$

$$V_o = 50.11 \text{ dB} \times 1 \text{ mV}$$

$$V_o = 50.11 \text{ mV}$$



$$\leftarrow V_o = 24 \times 34 \text{ dB} \times V_{in}$$

11/1/23


Date _____
Page _____

Q: Phase difference b/w input & output of CE amplifier
is 180° .

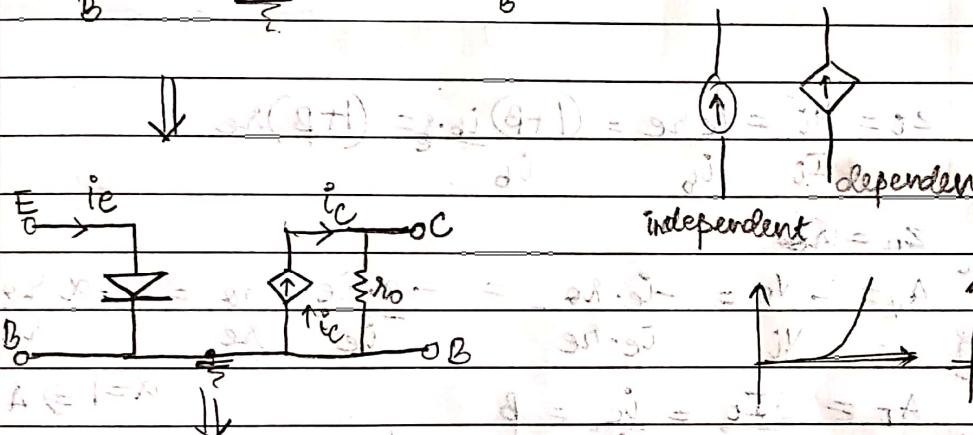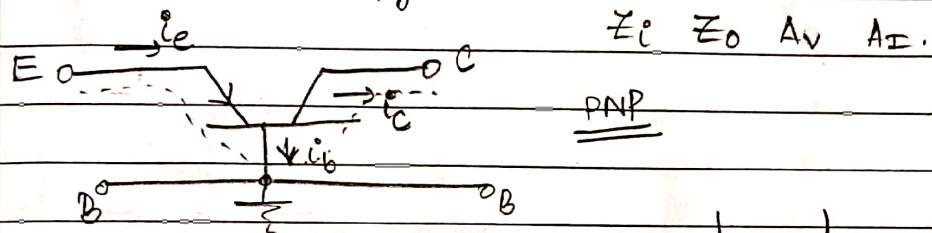Re model (small AC signals)
common base configuration



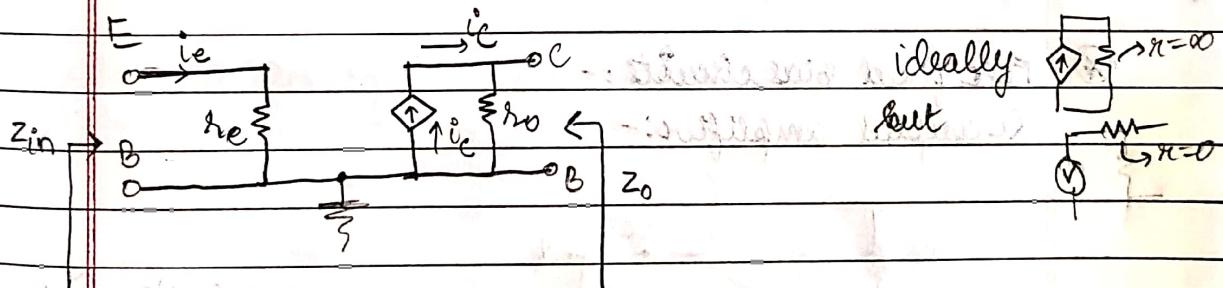small AC signals - small change \rightarrow Diode = resistance



$$\text{Input impedance} = \frac{V_{in}}{I_{in}} = \frac{i_e \cdot R_E}{i_e} = R_E = Z_{in}$$

$$\text{Output impedance} = \frac{V_o}{I_o} = \frac{i_c R_o}{i_c} = R_o = Z_o$$

$$\text{Voltage gain} = A_v = \frac{V_o}{V_{in}} = \frac{i_c R_o}{i_e R_E} = \frac{\alpha i_e R_o}{i_e R_E} = \frac{\alpha R_o}{R_E} = \frac{\alpha R_o}{R_E}$$



$$\text{Current gain} = A_I = \frac{I_o}{I_{in}} = \frac{i_c}{i_e} = \alpha \quad \text{ideally } \alpha = 1$$

$$\therefore A_v = \frac{R_o}{R_E} = \frac{\alpha R_o}{\alpha R_E} = \frac{R_o}{R_E}$$

12/1/23

Common emitter configuration

NPN.

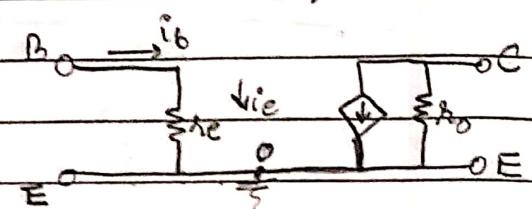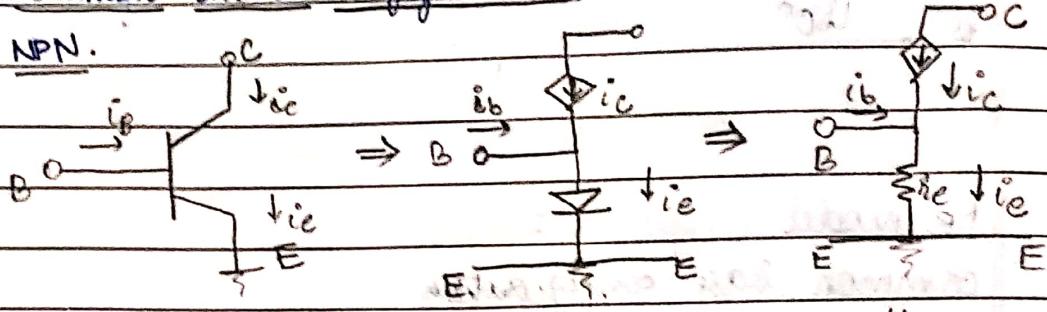

$$Z_C = \frac{V_o}{I_o} = \frac{i_c \cdot r_e}{i_c} = (1 + \beta) \frac{i_b \cdot r_e}{i_b} = (1 + \beta) r_e$$

$$Z_0 = r_o$$

\rightarrow v.c.cuz
it is flowing in opposite direction

$$A_v = -\frac{V_o}{V_i} = -\frac{i_c \cdot r_o}{i_c \cdot r_e} = -\frac{\alpha i_e \cdot r_o}{i_e \cdot r_e} = -\frac{\alpha r_o}{r_e}$$

wrt the ground


$$A_I = \frac{I_o}{I_i} = \frac{i_c}{i_b} = \beta \quad \alpha = 1 \Rightarrow A_v = -\frac{r_o}{r_e}$$

④ For fixed bias circuits :-

→ AC-capacitor -

RC coupled amplifier:-

short circuited

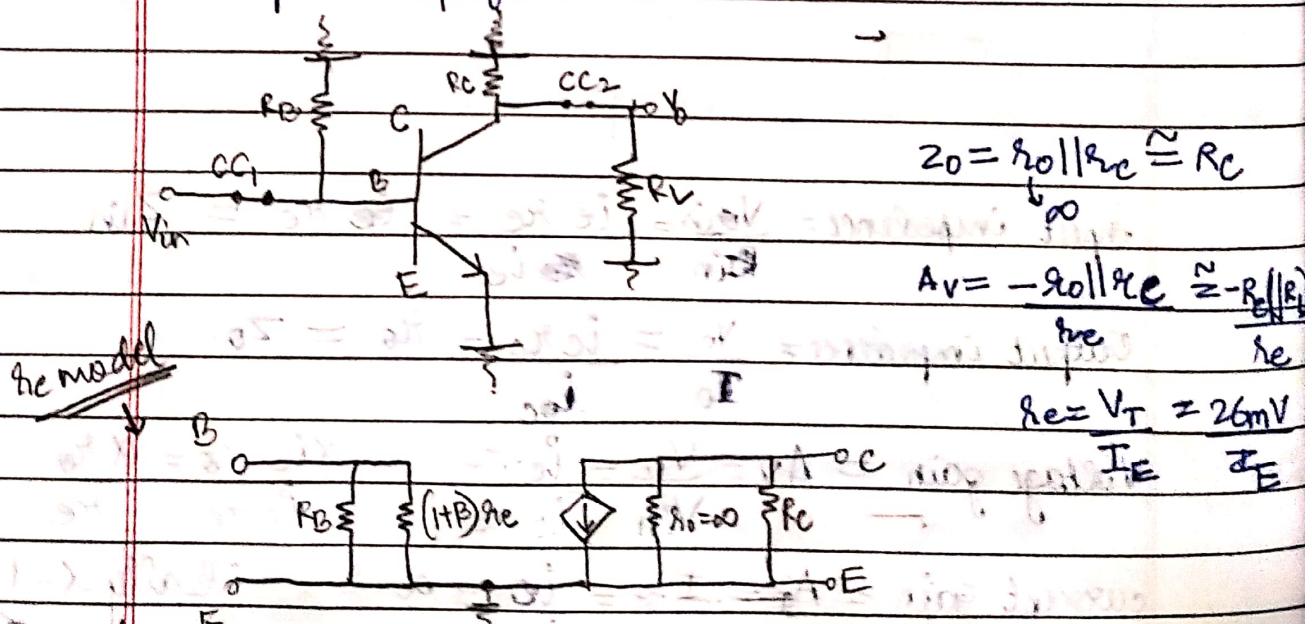


$$Z_0 = r_{o1} \| r_{c2} \approx R_C$$

$$A_v = -r_{o1} \| r_{c2} \approx -R_L / (r_e)$$


$$r_e = V_T = 26 \text{ mV}$$



Scanned with OKEN Scanner

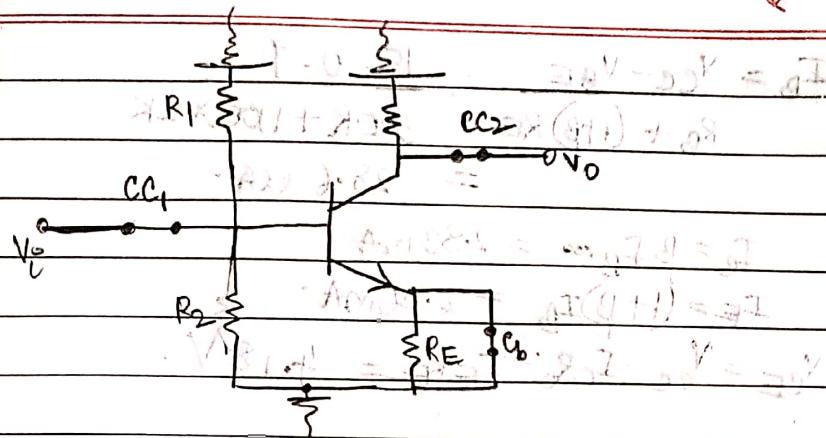

$Z_i = B \cdot (R_1 + r_e)$ (re model.)

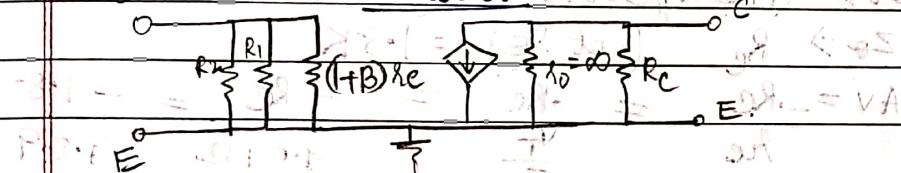

$$Z_i = (1+B)r_e \parallel R_1 \parallel R_2$$

$$Z_o = r_{oL} \parallel R_E \approx R_E$$

$$A_v = \frac{V_o}{V_{in}} = -\frac{r_{oL}}{r_e} = -\frac{R_E}{r_e}$$

$$r_e = \frac{V_T}{I_E} = \frac{26mV}{I_E}$$


Q: calculate the gain of an RC coupled amplifier given

$$R_C = 2k\Omega \text{ & } I_E = 2mA \Rightarrow A_v = ?$$

$$\text{sol: } A_v = -\frac{R_C}{r_e} = \frac{2 \times 10^3}{26 \times 10^{-3}} = -76.9 \times 10^3$$

$$= -2 \times 10^3 = -153.84$$

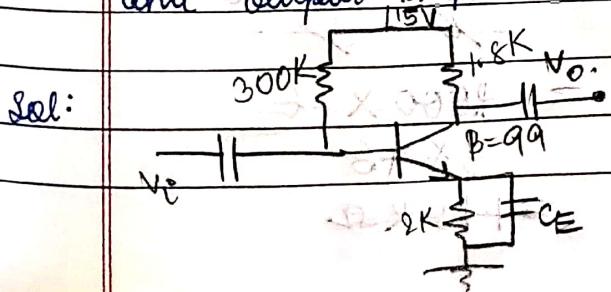Q: Find operating point of Si transistor and also determine small signal voltage gain input impedance and output impedance. Sketch re model.



Sol:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+B)R_E} = \frac{15 - 0.7}{300K + 100K \times 2K} = 28.6 \mu A$$

$$I_C = B I_B = 2.83 \text{ mA}$$

$$I_E = (1+B)I_B = 2.86 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 4.18 \text{ V}$$

$$Z_i \Rightarrow (1+B)r_e \parallel 300K = (1+99)(9.09) \parallel 300K = 2.25 \text{ K}$$

$$Z_o \Rightarrow R_C \text{ (not } R_E) = 1.8 \text{ K}$$

$$A_v = \frac{-R_C}{r_e} = \frac{-R_C}{\frac{V_T}{I_E}} = \frac{-R_C}{9.09 \Omega} = -1.8$$

$$A_v = -198$$

$$\frac{909 \times 300}{909 + 300} = 906 \Omega$$



$$R_b = 10K\Omega \quad I_E = 3 \text{ mA}$$

$$R_L = 20K\Omega \quad R_C = 2K\Omega$$

$$R_L = 4K\Omega$$

$$A_v \rightarrow Z_o, Z_i \quad R_{th} = 200 \Omega$$

$$r_e = \frac{26 \times 10^{-3}}{3 \times 10^{-3}} = 8.66 \Omega$$

$$\left| \begin{array}{l} 6.66 \times 100 \times 8.66 \\ 6.66 + 8.66 \end{array} \right.$$

$$Z_o = r_e \parallel \frac{R_L}{B} = 2 \times 10^3 \Omega = 2K\Omega = 1.33K\Omega$$

$$Z_{in} = R_b \parallel (1+B)r_e = 20 \times 100 \times \frac{26}{3} =$$

$$A_v = -\frac{2.86 \times 1.33}{3} = \frac{20 + 26 \times 100}{3} =$$

$$A_v = \frac{2.86 \times 1.33}{3} = \frac{2000 \times 26}{3 \times 46} =$$

$$= 143K\Omega$$

12/123.

Date _____
Page _____

$$R_B = \frac{20}{3} = 6.66 \text{ K} \quad \text{So choose 10k ohm unit}$$

$$\therefore Z_{in} = \frac{6.66 \times 100 \times 8.66}{6.66 + 100 \times 8.66} =$$

$$re = 8.66 \Omega = 8.66$$

$$re = (1+B) 8.66 \times 10^{-3} \text{ K}\Omega$$


$$0.866 \text{ K}\Omega$$

$$\therefore R_B \parallel re(1+B) \Rightarrow Z_{in} = 7.66$$

Saturation Region

R_B minimum B minimum

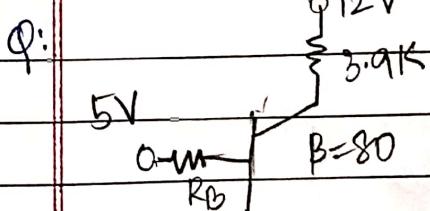$V_{CE} = 0.3 \text{ V}$ fixed [ideally = 0]



→ For inverter circuit determine

Minimum value of R_B

12/1/23

Date _____
Page _____

Q: In the inverter circuit of below figure determine minimum value of β .

Sol:

→ $V_{out} = V_{cc}$ at $V_{in} = 0$

→ $V_{out} = 0$ at $V_{in} = V_{cc}$

→ $V_{out} = V_{cc}$ & $(V_{cc})^2 / R_B \geq \beta I_{Cmax}$


→ $I_{Cmax} = \frac{V_{cc}^2}{\beta R_B}$

→ $I_{Cmax} = \frac{V_{cc}^2}{\beta R_B}$

→ $I_{Cmax} = \frac{V_{cc}^2}{\beta R_B}$


→ Transistor as a switch

(NOT GATE $\rightarrow 1 \rightarrow 0$)

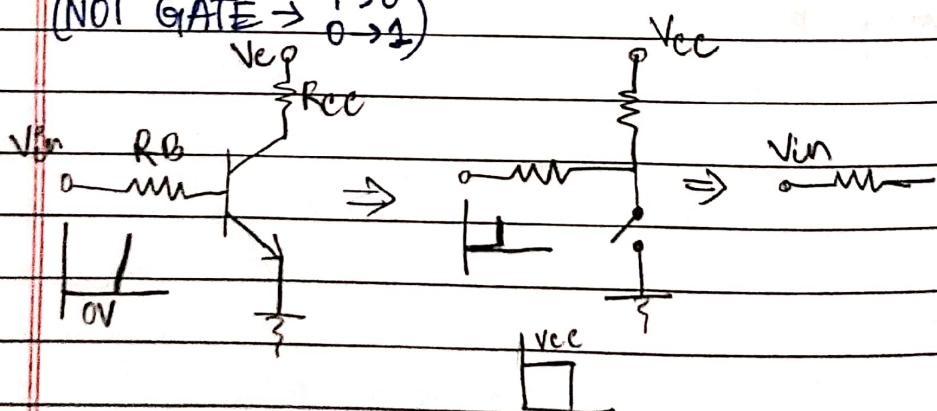

Quiz question.

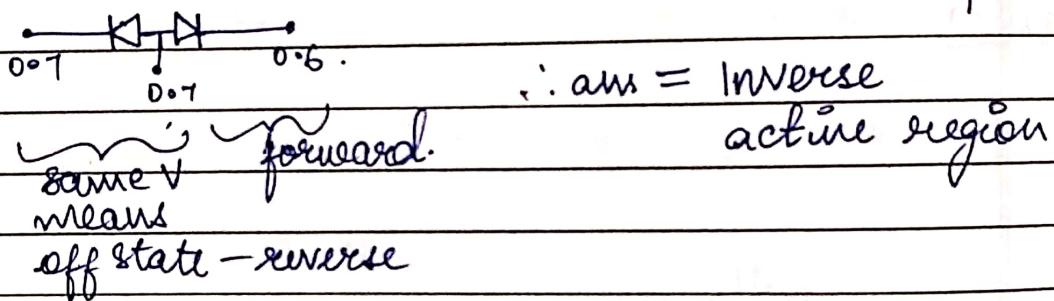1. In a pnp transistor emitter-base junction is reverse biased and collector-base junction is forward biased, the transistor is operating in inverse active region.
2. The transistor needs to be operated as amplifier it should operate in active region.
3. For the given circuit if $V_B = 0.7 \text{ V}$. Find region of operation.
- NPN
- $$V_E = 0.7 \text{ V}$$
- $$V_C = 0.6 \text{ V}$$



4. PNP $V_E = 0.8 \text{ V}$

$$V_B = 0.7 \text{ V}$$

$$V_C = 0.9 \text{ V}$$



$P \rightarrow N \quad N \rightarrow P$. \therefore It is in saturation.

WORKSHEET

Q1) $I_{CO} = 6 \text{ mA}, \alpha = 0.98, I_B = 0, V_{CE} = 4V, I_C = ?$

$$\frac{\beta}{\beta + 1} = \frac{\alpha}{\alpha + 1}$$

$$\frac{\beta}{\beta + 1} = \frac{0.98}{0.98 + 1} = \frac{0.98}{1.98} = 0.49$$

$$I_C = \beta I_B + (1 - \beta) I_{CO}$$

$$= 49 \times 0 + 50 \times 6 \times 10^{-3}$$

$$I_C = 3 \times 10^{-2} = \cancel{30} \times 10^{-6} \times 0.3 \times 10^{-3} = 0.3 \text{ mA}$$

Q2) $I_{CO} = 30 \text{ mA}, I_B = 0, V_{CE} = 4V, I_C = 30 \text{ mA}, \beta = ?$

$$I_C = (1 + \beta) I_{CO}$$

$$30 \times 10^{-3} = I_{CO} + \beta I_{CO} = 30 \times 10^{-3} + \beta \times 30 \times 10^{-3}$$

$$1 = 10^{-3} + 10^{-3} \beta$$

$$10^3 = \beta + 1$$

$$\boxed{\beta = 999}.$$

- Q3)
1. F, R : active
 2. F, F : saturation
 3. F, R : active.
 4. R, R : ~~reverse~~ cut off.
 5. R, F : reverse active



3) a) $\beta = \frac{\alpha}{1-\alpha}$ i) $\beta = \frac{0.5}{1-0.5} = 1$ v) ~~cancel~~ $\beta = 49$

ii) $\beta = \frac{0.8}{1-0.8} = 4$

iii) $\beta = \frac{0.96}{1-0.96} = 24$

iv) $\beta = \frac{0.98}{1-0.98} = 49$