
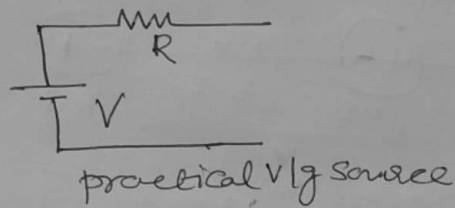




Independent Sources may be Ideal/practical voltage Sources and current Sources

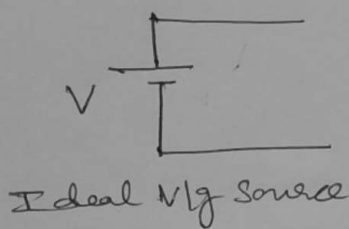An ideal voltage Source is the energy Source which delivers const voltage irrespective of network configuration
practical voltage source is the energy source which has Small resistance with voltage Source.




Ideal Current Source is the energy Source which gives const current across its terminals irrespective of the voltage connected across its terminals

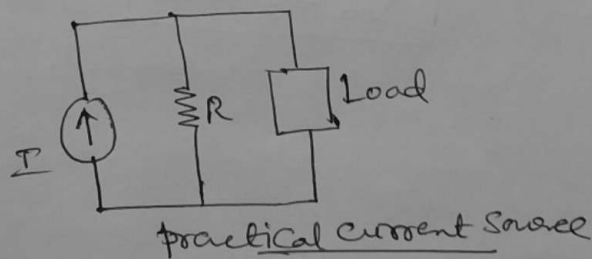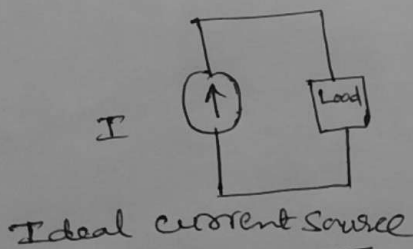
practical current source is the energy source which has Small internal resistance connected in parallel with the current source



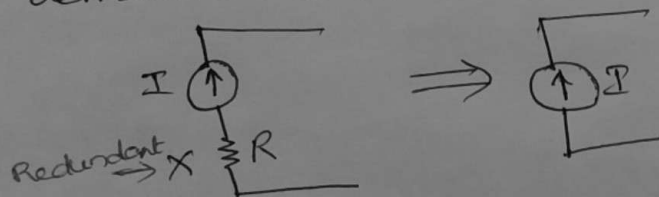
When resistance connected in series with the current Source should always be neglected (redundant) because the Current remains same in series connection.



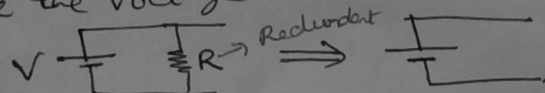
Resistance connected in parallel with the voltage Source is redundant because the voltage remains same in parallel connection.




Source transformation

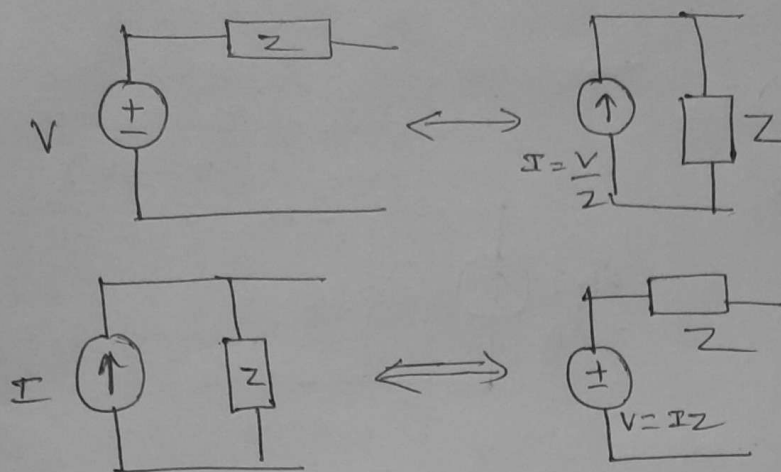

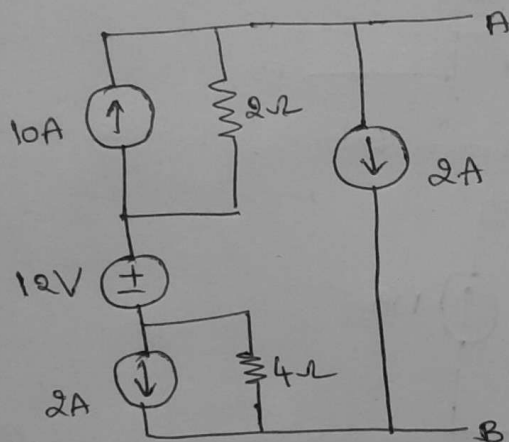Ex: Reduce the network shown in Figure into a single voltage source between A and B.




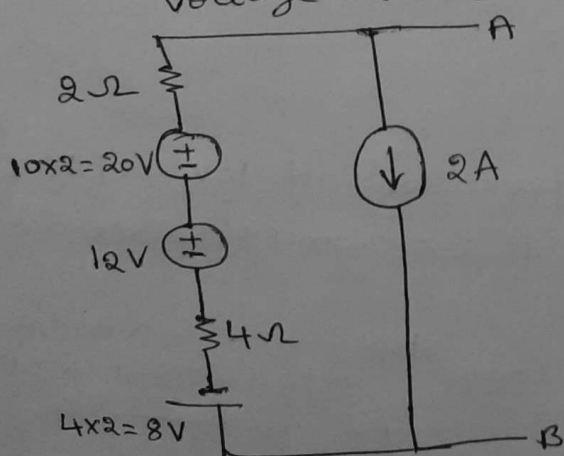Solution: current source 10A and 2A are converted into voltage source




\Rightarrow 20V, 12V and 8V voltage sources are in series and they can be reduced into a single voltage source.


$$\text{i.e. } 20 + 12 - 8 = 24$$

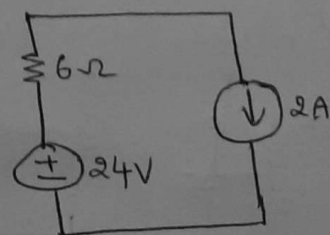


24V is converted into current source

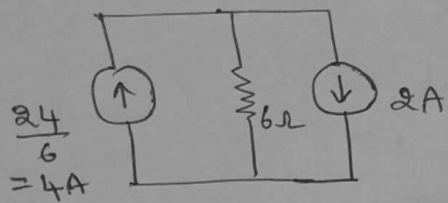

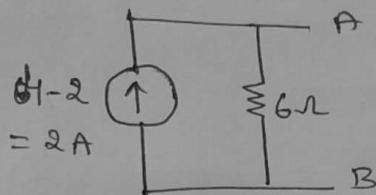
⇒ combining current source
(but direction is opposite
hence subtract)




convert into voltage source

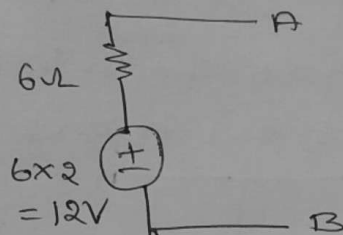

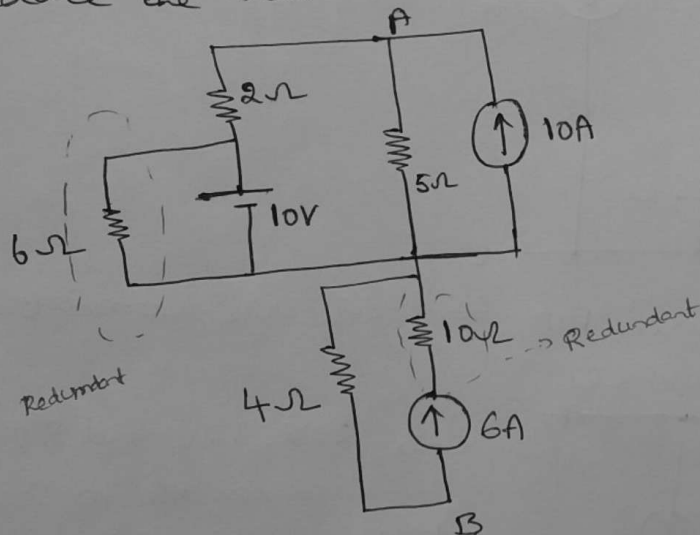
Ex: Reduce the network shown into a single source network




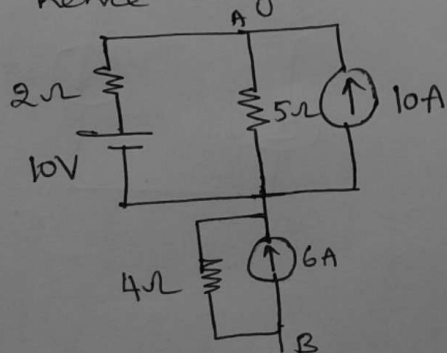Solution: 6Ω resistor in parallel with $10V$ and 10Ω resistor is in series with $6A$ current source are redundant hence neglected.




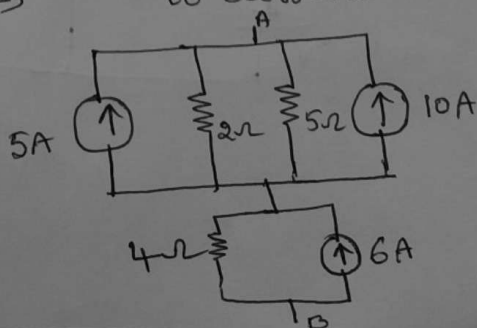⇒ 10V source can be converted to current source




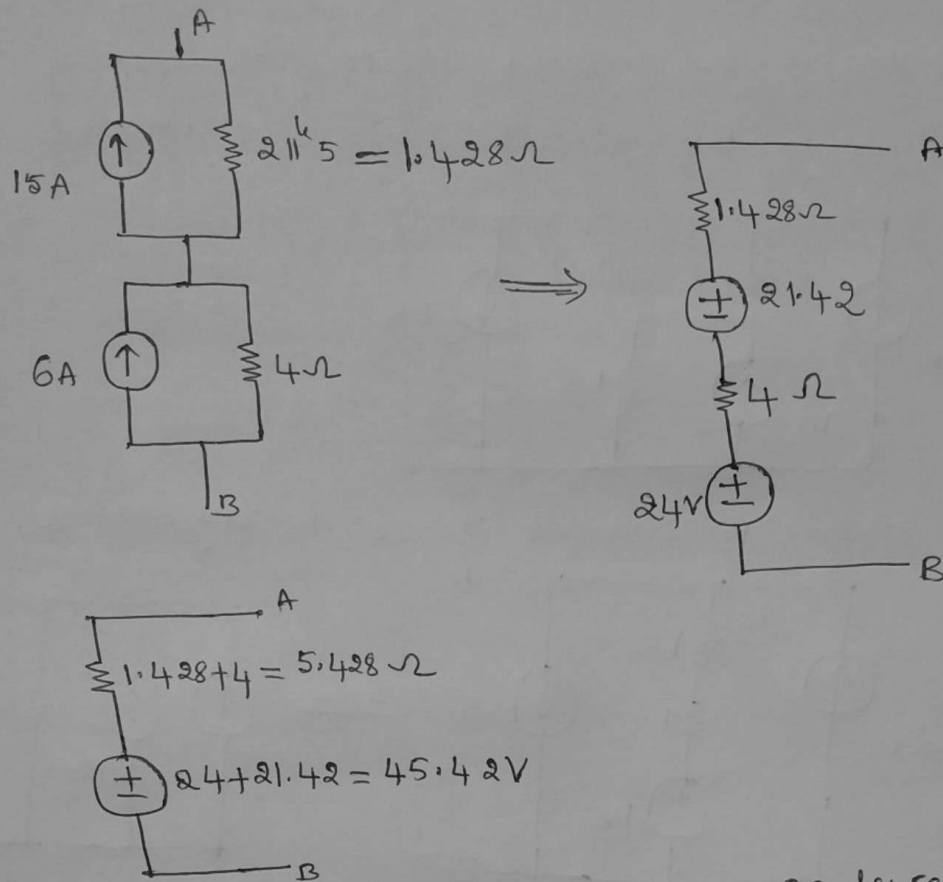

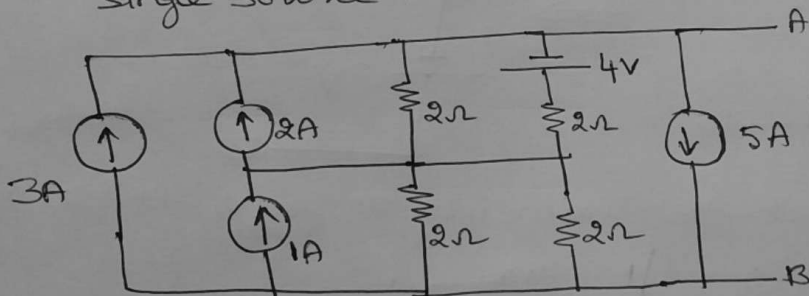
Q: Using source transformation technique reduce it into a single source network.



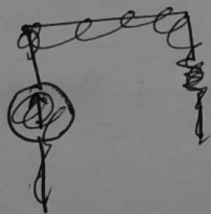
Solution: Since the $2A$ current source and the $1A$ current source are acting in opposite directions, the resultant current will be $1A$.






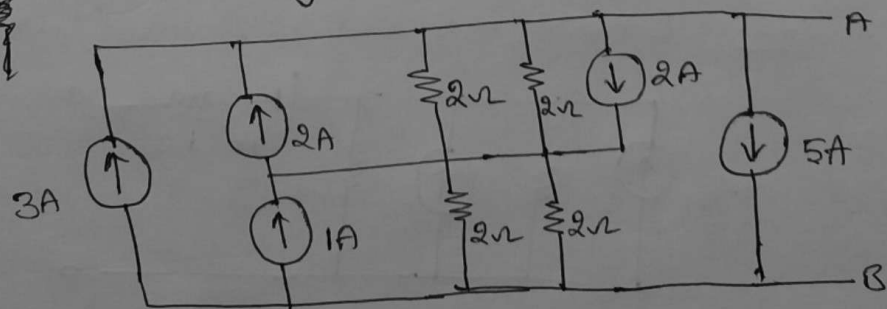
Converting $4V$ source to a current source.



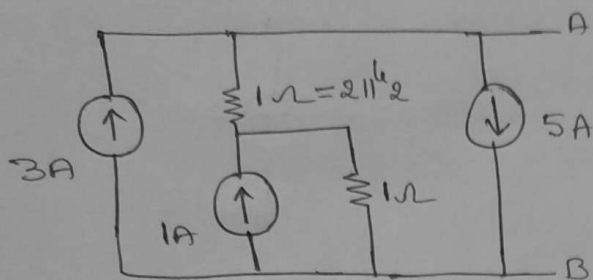
Since the 2, 2A current sources are acting in opposite direction the resultant current will be zero.



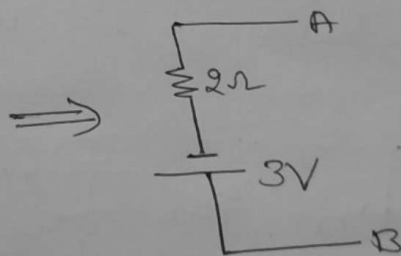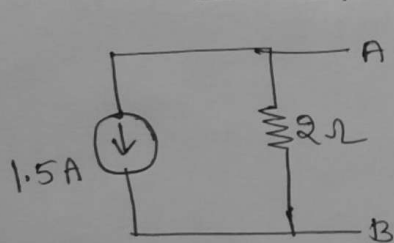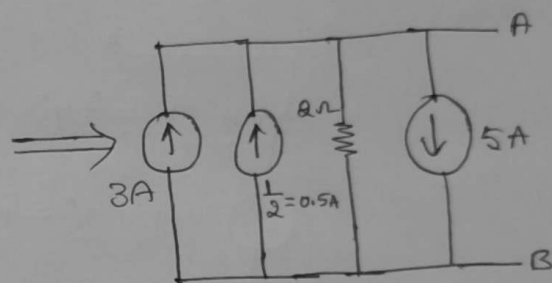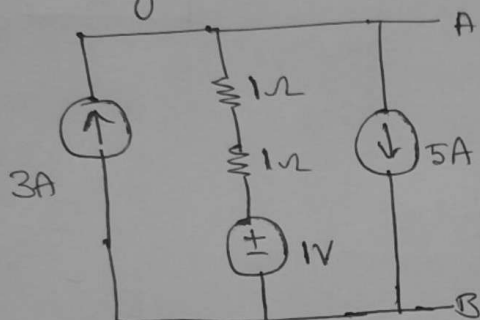
Converting 1A current source to Vg Source.



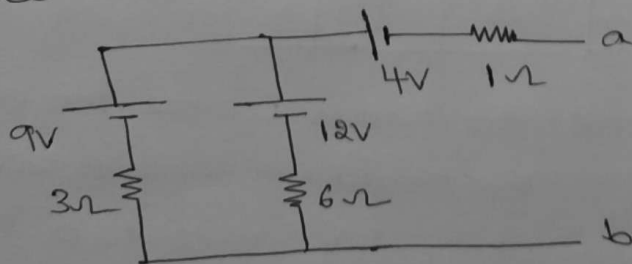
Ex: Reduce the network shown into a single source network.



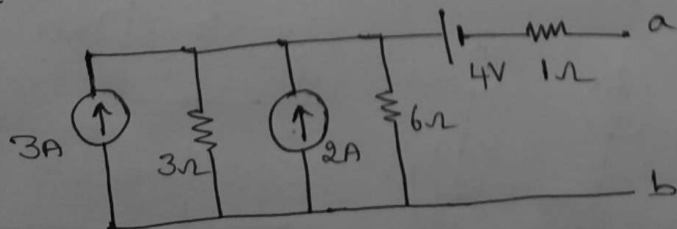
Solution: convert 9V and 12V into current source




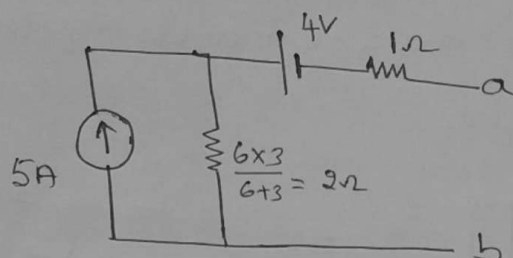
Combine 3A and 2A current source, direction is same
 \therefore perform addition.



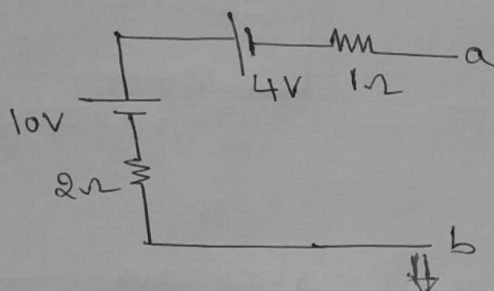
Convert 5A current source into voltage source





Combining 4V and 10V voltage source

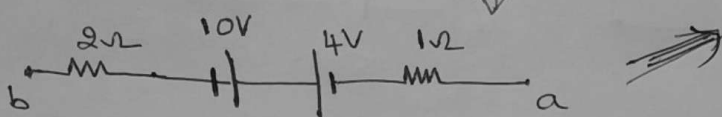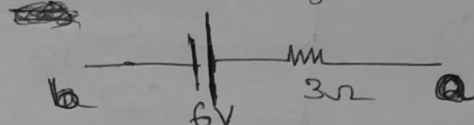

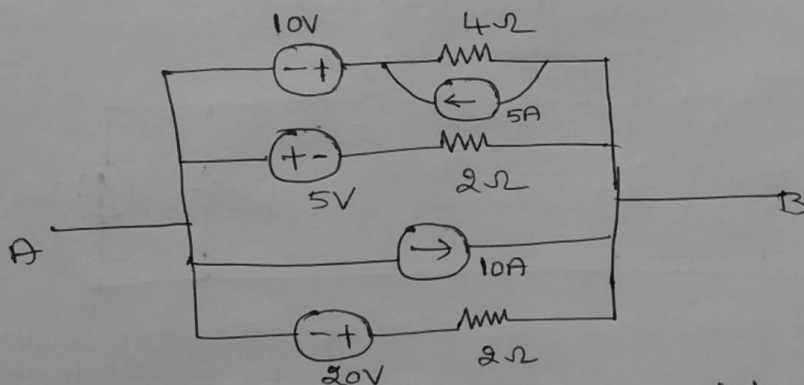
Ex: Reduce the network shown into a single source network.



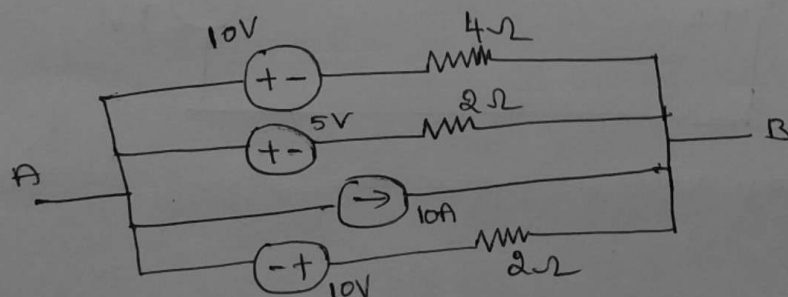
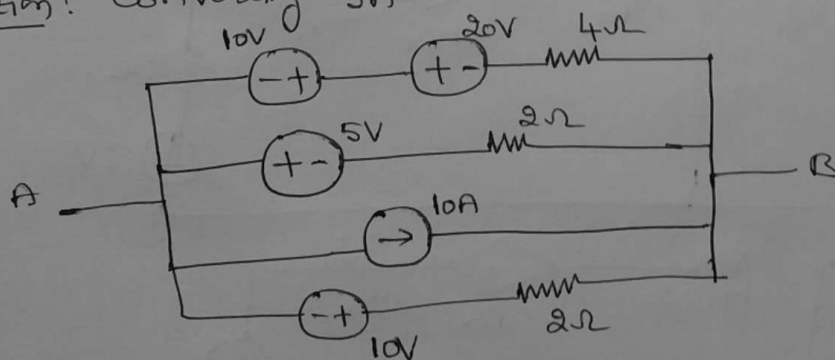
Solution: converting 5A current source into voltage source



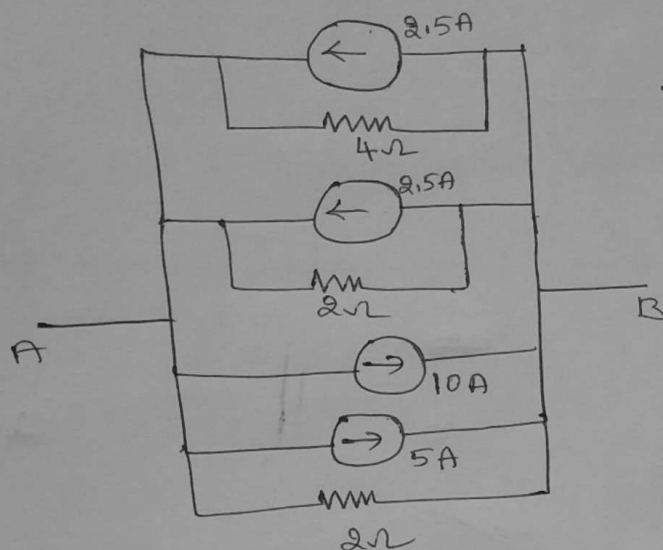
Converting all voltage sources into its equivalent current sources.





⇒ Combining current source

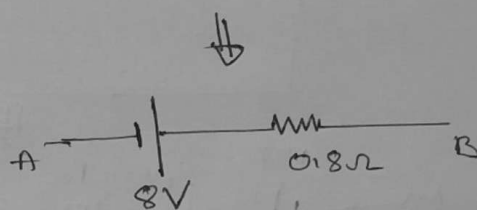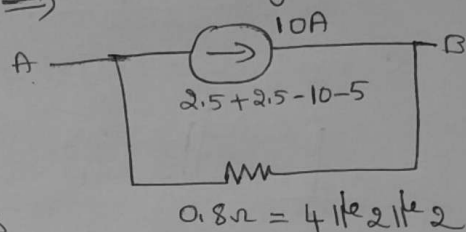

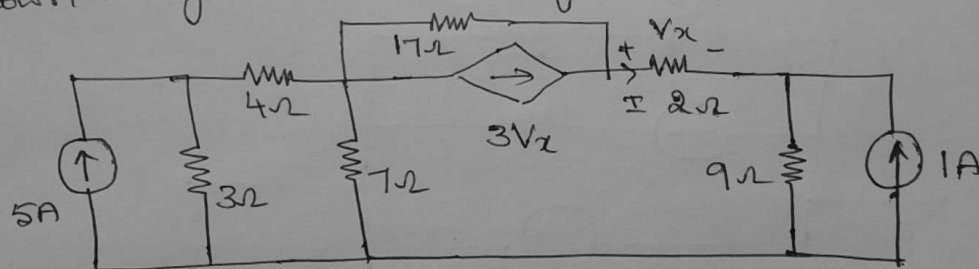
Ex: Calculate the current through 2Ω resistor for the circuit shown using source transformation.



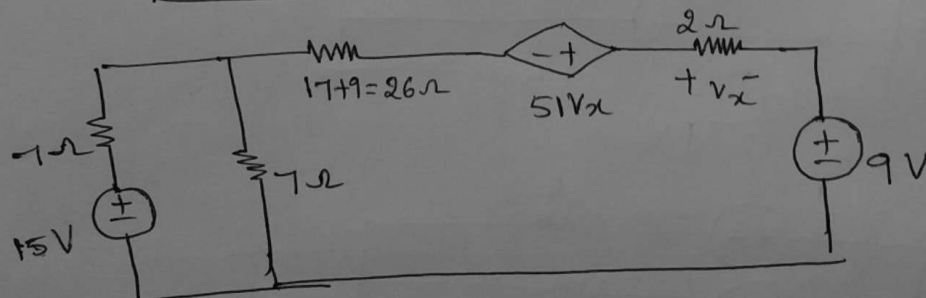
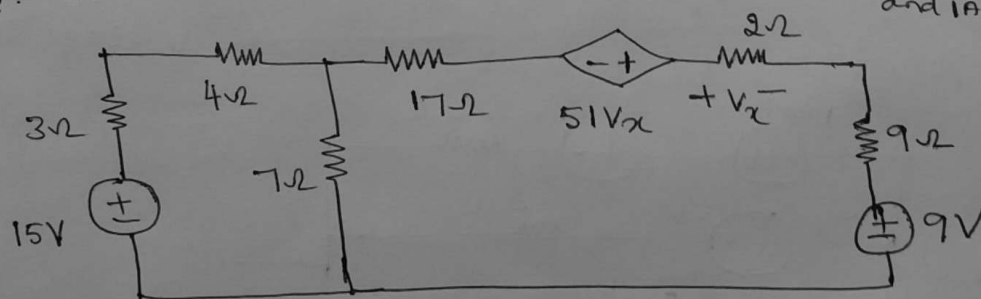
Solution: Convert $5A$ and $3V_x$ current source into voltage source and $1A$ current source into voltage source



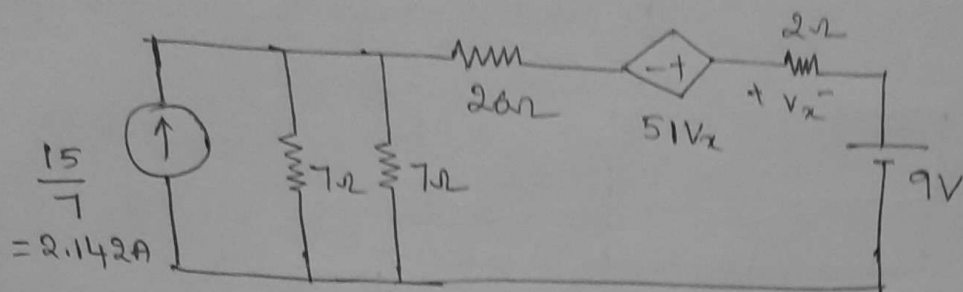Convert $15V$ voltage source into current source



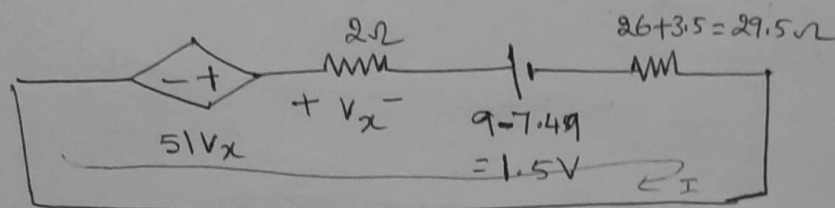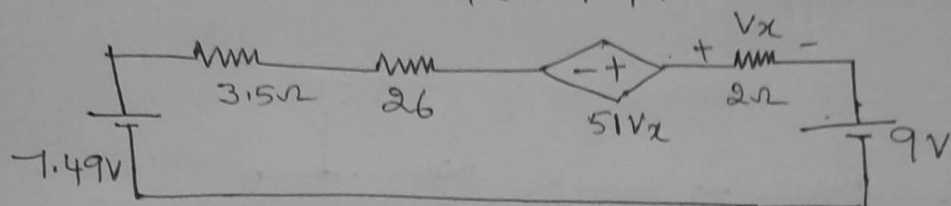Reduce parallel $\Rightarrow 7 \parallel 7 = 3.5 \Omega$
 Then convert $2.142A$ into voltage source
 ie $3.5 \times 2.142 = 7.49V$



To find V_x , $V_x = 2I$

Apply KVL to mesh 1


$$-5V_x + 2I + 1.5 + 29.5I = 0$$

$$-5(2I) + 2I + 1.5 + 29.5I = 0$$



$$-70.5I = -1.5$$

$$I = 21.27mA$$

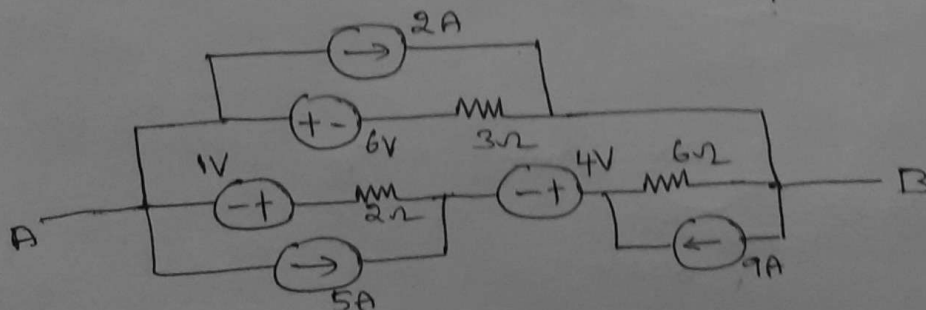Ex: Reduce the network shown into a practical voltage source



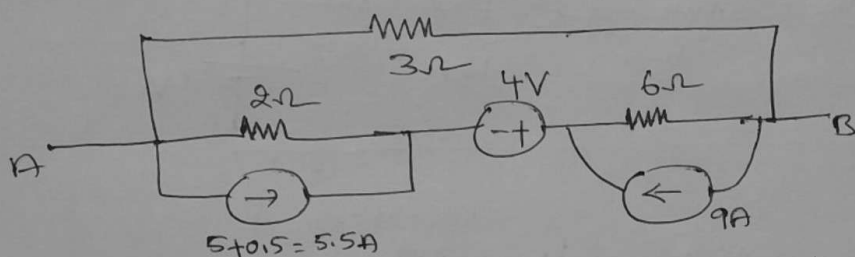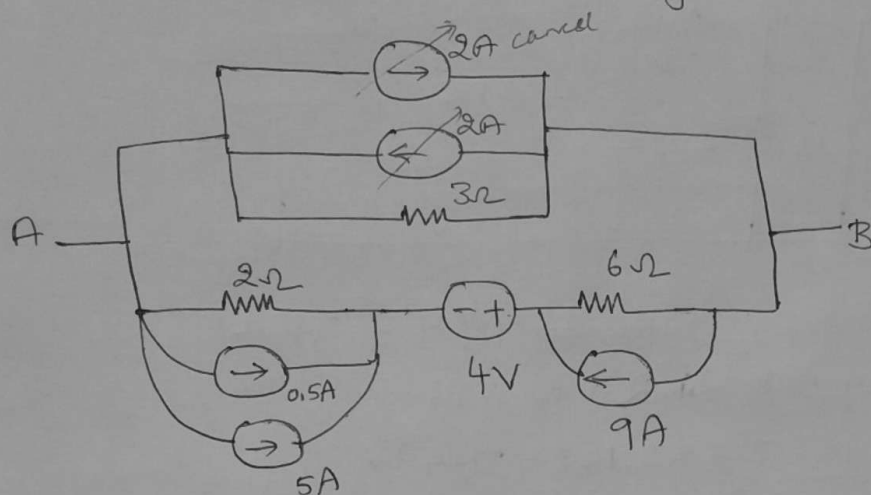Solution: Convert 6V and 1V voltage source to current source



convert $5.5A$ and $9A$ current sources to voltage source

