

USN

--	--	--	--	--	--	--	--	--	--


RV COLLEGE OF ENGINEERING®
(An Autonomous Institution affiliated to VTU)
I / II Semester B. E. Fast Track Examinations Oct-2020
Common to All Branches
ELEMENTS OF ELECTRONICS ENGINEERING

*Time: 03 Hours**Maximum Marks: 100***Instructions to candidates:**

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

PART-A

1	1.1	In a full wave bridge rectifier with capacitor filter, the value of capacitance required to get ripple factor zero is _____.	01
	1.2	With a constant forward current, if the forward voltage drop of germanium diode at 25°C is 300mv, its voltage drop at 35°C is _____.	01
	1.3	If $V_E=11V$, $V_B=2V$, $V_C=3V$ for a NPN transistor, the region of operation is _____.	01
	1.4	In a regulated DC power supply, the output voltage drops from 18V to 17.2V when the input voltage is reduced by 10%. The % line regulation is _____.	01
	1.5	For plotting the output characteristic of CE configuration using NPN transistor, the parameter in an X axis is _____.	01
	1.6	The ratio of current gain I_C / I_E is usually less than one for _____ configuration.	01
	1.7	The logic gate which has output 'low' only when all its inputs are 'high' is _____.	01
	1.8	The gain of a RC coupled amplifier decreases at higher frequency due to _____.	01
	1.9	A voltage amplifier has an open loop gain of 500 and gain stability of 12%. If 1% of negative feedback is given, the gain stability of amplifier with feedback is _____.	01
	1.10	A MOSFET is _____ controlled device.	01
	1.11	In a CMOS inverter, if the input logic is 1, then the PMOS is in _____ State.	01
	1.12	A 10V sinusoidal carrier signal is amplitude modulated by two sine waves of amplitude 6V and 8V, the resultant modulation index is _____.	01
	1.13	With negative feedback, the bandwidth of an amplifier _____ by a factor of $(1 + A\beta)$.	01
	1.14	An AM modulated signal has _____ number of sidebands.	01
	1.15	Simplify, $Y = \bar{A}B + \bar{B}C$	01
	1.16	In a 1 to 32 demultiplexer, the number of select bits are _____.	01

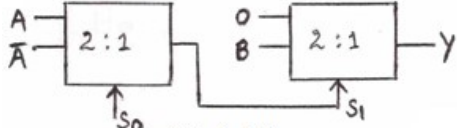1.17	Write a simplified expression for Y for the multiplexer arrangement shown in fig 1.17	
	 <p style="text-align: center;">Fig 1.17</p>	01
1.18	The minimum number of <i>NAND</i> gates required to realize Half adder is _____.	01
1.19	An Op-amp has <i>CMRR</i> of 60dB and differential gain of 1000. Determine the output voltage if $V_1 = 199\text{mV}$ and $V_2 = 201\text{mV}$	02

PART-B

2	a	Write the expression relating the current and voltage of a PN junction diode. From this obtain the expression for its dynamic resistance	04
	b	Explain the term 'Reverse recovery time' of a PN junction diode with relevant waveform	04
	c	The input to the primary of a step down transformer feeding a full wave bridge rectifier is $100 \sin 314t$. The <i>DC</i> output voltage with a resistive load of 900Ω is 10V. Assuming that each of the diodes used has a forward resistance of 50Ω , determine the transformer turns ratio.	04
	d	Explain briefly the operating principles of <i>LED</i> and photodiode. Give their applications.	04
3	a	Give the comparison between the performance of the three <i>BJT</i> amplifier configurations.	04
	b	Explain the terms briefly i) Punch through effect ii) Bias Stabilization in a <i>BJT</i>	04
	c	In <i>RC</i> coupled <i>CE</i> amplifier circuit, $V_{CC} = 12\text{V}$; $R_1 = 120\Omega$; $R_2 = 40\Omega$; $R_E = 1.5\text{K}\Omega$; $R_C = 2.7\text{K}\Omega$ and $\beta = 99$. Determine the operating point, $S_{(ICQ)}$, voltage gain, input impedance and output impedance	08
		OR	
4	a	Draw the circuit and explain the frequency response of an <i>RC</i> coupled amplifier	05
	b	List the advantages of voltage series negative feedback. Prove any one of them.	05
	c	A Voltage amplifier needs 2mV input to give a 10V output. When negative feedback is provided to this amplifier, it needs 200mV to deliver the same output. Determine the open loop gain, closed loop gain, feedback factor and amount of feedback in dB for this amplifier.	06
5	a	Draw the structure of <i>N</i> channel <i>MOSFET</i> and explain its operation along with its output characteristics. Write the necessary conditions for the different regions of operation.	06
	b	An <i>NMOS</i> having $V_t = 0.6\text{V}$, it has a drain current, $I_D = 0.4\text{mA}$ when $V_{GS} = V_{DS} = 2.6\text{V}$ i) Determine its drain current when $V_{GS} = 3.6\text{V}$ and $V_{DS} = 4\text{V}$ ii) Find the resistance between the source and drain for small values of V_{DS} when $V_{GS} = 5.6\text{V}$	06
	c	List eight differences between <i>AM</i> and <i>FM</i> .	04

OR			
6	a	With a neat circuit and truth table, explain the construction and working of two input <i>CMOS NOR</i> gate.	04
	b	List eight differences between <i>BJT</i> and <i>FET</i> .	04
	c	A modulated wave is given by, $v(t) = (10 + 16\cos 2 \times 10^4 t) \sin 4 \times 10^6 t$ Calculate: i) sideband frequencies and their amplitude ii) The Bandwidth iii) The min and max values of peak to peak voltage of the modulated signal iv) The total power, if the load is 100Ω	05
	d	What is frequency spectrum? Draw the frequency spectrum of <i>AM</i> wave	03
7	a	A logic circuit has two inputs <i>P, Q</i> and an output <i>Y</i> . The output is false when either of the two inputs are true but not both. Write the logic expression and realize using only <i>NOR</i> gate.	04
	b	Draw the truth table for 'sum' and 'carry' of a full adder. From the truth table obtain the logic expression, from these expressions realize the full adder using two half adders.	06
	c	Write the truth table of 4:1 <i>MUX</i> . Realize using <i>NAND</i> gates and obtain expression for the output <i>Y</i>	06
8	a	List the characteristics and typical values of general purpose op-amp.	04
	b	Draw the circuit of an Integrator using ideal <i>OPAMP</i> and show that output is integral of input. Write output waveform for square wave input	06
	C	Draw the summer circuit using two ideal op-amps, and calculate the different resistor values to obtain $V_0 = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$, where $+V_1, +V_2, +V_3, +V_4, +V_5, +V_6$ are the available inputs.	06

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®
(An Autonomous Institution affiliated to VTU)
I / II Semester B. E. Examinations Nov/Dec-19

Common to All Branches

BASICS OF ELECTRONICS ENGINEERING



Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

PART-A

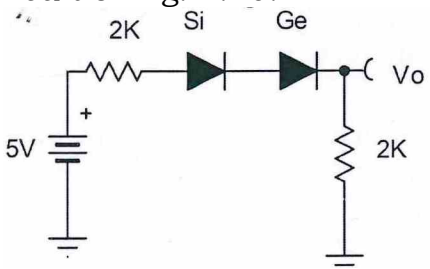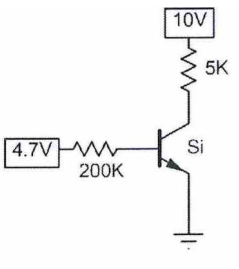1	1.1	The simplified expression of $A + AB + ACD$ is _____.	01
	1.2	Write the truth table for 1:4 Demux.	01
	1.3	The value of the dynamic resistance (r_d) of a PN junction diode at an ambient temperature of 27°C and a forward DC current of 2 mA is _____.	01
	1.4	In a transistor if α changes from 0.99 to 0.995, then β changes from _____ to _____.	01
	1.5	Three oscillators are cascaded to provide an overall voltage gain of 10,000. The first two stages have gains of 34 dB and 20 dB . Find the gain of third stage amplifier in dB .	01
	1.6	In a RC phase shift oscillator circuit, using an ideal voltage amplifier, the frequency of oscillation is 1 kHz . If $C = 0.01\mu\text{F}$, R is equal to _____.	01
	1.7	A 25 MHz carrier is frequency modulated by 400 Hz audio sine wave. The carrier voltage is 4 V and maximum deviation is 1 kHz . Write the equation of this.	02
	1.8	Realize $EX - OR$ function using basic gates.	02
	1.9	List four differences between a bipolar transistor and a field effect transistor.	02
	1.10	Determine the current, I through the diode and the output voltage V_o in the circuit of Fig. 1.10.	
		 <p style="text-align: center;">Fig. 1.10</p>	
		 <p style="text-align: center;">Fig. 1.11</p>	02
	1.11	In the inverter circuit of Fig. 1.11. Find Base Current (I_B) and Collector current (I_C) when inverter is operating in saturation.	02
	1.12	An N Channel enhancement $MOSFET$ with threshold voltage $V_T = 1\text{ V}$ has its source voltage $V_S = 2\text{ V}$. If its gate voltage $V_G = 4\text{ V}$. Find the minimum drain voltage V_D needed for the device to operate in saturation region.	02
	1.13	In the circuits of Fig. 1.13, determine the output voltage V_o . Assume the op amp to be ideal.	

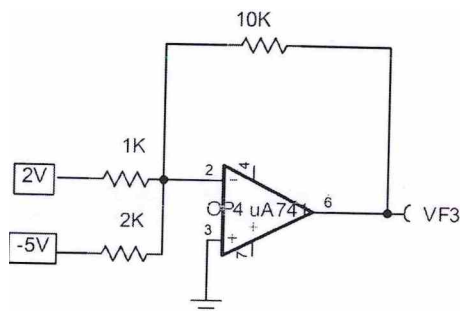


Fig. 1.13

02

PART-B

<p>2</p> <p>a</p> <p>b</p> <p>c</p>	<p>Explain the operation of a 4 – to – 1 multiplexer and write the logic expression for its output. Also draw the logic circuit to realize the multiplexer.</p> <p>Draw the truth table for '<i>SUM</i>' and '<i>CARRY OUT</i>' of a FULL ADDER. From the truth table, obtain the logic expressions for them. From these expressions, realize the FULL ADDER using logic gates.</p> <p>Write the equation that related voltage across the <i>PN</i> junction diode and current through it. Obtain the expression for the dynamic resistance r_d, of a forward biased <i>PN</i> junction diode.</p>	<p>04</p> <p>06</p> <p>06</p>
<p>3</p> <p>a</p> <p>b</p> <p>c</p>	<p>Distinguish between 'Avalanche breakdown' and 'Zener breakdown'.</p> <p>A full wave bridge rectifier using ideal diodes is supplied from a secondary of 10:1 transformer is primary is connected to 200V, 50Hz main supply. The output of the rectifier is connected to a resistance of 330Ω, in parallel with a capacitor filter $C = 1500\mu F$. Determine:</p> <ol style="list-style-type: none"> DC Output Voltage, Peak-Peak Ripple Voltage, Ripple Factor, Load regulation. <p>Determine the operating point of silicon transistor in the voltage divider biasing circuit shown in Fig. 3.c. Also, determine $S(I_{CO})$ (Take $\beta = 100$).</p>	<p>04</p> <p>06</p>
<p>Fig. 3.c</p>		
<p>OR</p>		
<p>4</p> <p>a</p> <p>b</p>	<p>Draw the circuit diagram of Full wave bridge rectifier with capacitor filter and describe its working with necessary waveforms.</p> <p>In a Zener regulator circuit of Fig. 4.b. Design the value of '<i>R</i>' so that the regulator performs satisfactorily for all given input voltage and load conditions. Given $I_{Z,min} = 10mA$ and $P_{Z,max} = 6W$.</p>	<p>03</p> <p>05</p>

		<p>Fig. 4.b</p>	
c		<p>In Fig. 4.c, determine R_C, R_1 and R_2, so that $V_{CEQ} = 4V$ and $I_{CQ} = 1mA$, with a bias stabilization factor, $S(I_{CO}) = 10$.</p> <p>Fig. 4.c</p> <p>Fig. 5.b</p>	08
5	a	State and explain the Barkhausen criterion for sustained sinusoidal oscillations.	04
	b	Calculate the voltage gain, current gain, input impedance Z_i and output impedance Z_o for the circuits in Fig. 5.b. (Take $\beta = 79$).	06
	c	An amplifier has a gain of $60dB$, bandwidth of $300kHz$, distortion of 15%, input impedance of $20k\Omega$ and an output impedance of $1k\Omega$. If voltage series negative feedback of 3.9% is given to this amplifier, calculate the gain, input impedance, output impedance, bandwidth and distortion of the amplifier with negative feedback.	06
		OR	
6	a	Draw and explain the working of following using CMOS circuits i) Inverter and ii) NAND gate.	04
	b	Draw the circuit and explain the functioning of an RC phase shift oscillator using a common emitter amplifier and write the expression for the frequency of oscillation.	06
	c	An N-channel enhancement type MOSFET with $V_{th} = 1V$ conducts a current $I_D = 100\mu A$ when $V_{GS} = V_{DS} = 1.5V$. Find the value of I_D for $V_{GS} = 2.5V$ and $V_{DS} = 4V$. Also calculate the value of r_{DS} for small value of V_{DS} , when $V_{GS} = 3V$.	06
7	a	Draw the circuit of an integrator using an ideal op-amp and prove that it works as an integrator.	04
	b	Draw the circuit and calculate the values of different resistors of a summer circuit using two ideal op-amps to obtain an output of $V_o = V_1 - 2V_2 - 4V_3 + 6V_4$, where $+V_1, +V_2, +V_3$ and $+V_4$ are the available inputs.	06
	c	Write a block diagram Data acquisition system and explain the function of each stage.	06
8	a	Write EIGHT differences between AM and FM systems.	04
	b	Draw the block diagram of a communication system and explain the function of each stage.	06
	c	A carrier of $1MHz$ with $400W$ of its power is amplitude modulated with sinusoidal signal of $2500Hz$. The depth of modulation is 75%. Calculate the side band frequencies, Bandwidth, the power in side band and total power in modulated wave.	06

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®
(An Autonomous Institution affiliated to VTU)
I Semester B. E. Examinations Nov/Dec-19

Common to All Branches

ELEMENTS OF ELECTRONICS ENGINEERING


Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

PART-A

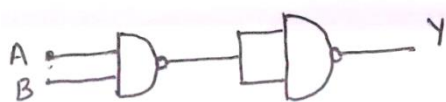
1	1.1	The current and voltage relationship of a semiconductor diode is =_____.	01												
	1.2	The reverse saturation current of a diode _____ for every $10^{\circ}C$ rise in temperature.	01												
	1.3	In a full wave bridge rectifier without any capacitor, each of the diodes used has a forward resistance of 20Ω and the load resistance is $2k\Omega$. The load regulation of the rectifier is _____.	02												
	1.4	The zener resistance of a zener diode which exhibits resistance of $50mV$ change in V_z for a $2.5mA$ change in I_z is _____.	01												
	1.5	The peak inverse voltage of a bridge rectifier without any filter is =_____.	01												
	1.6	The emitter base junction of a CE transistor is forward biased and collector base junction is reverse biased. The transistor is working in _____ region.	01												
	1.7	A voltage divider circuit has $V_{cc} = 15V$, $R_1 = 22k\Omega$, $R_2 = 12k\Omega$, $R_c = 2.7k\Omega$. The value of Thevenin voltage V_{Th} =_____.	01												
	1.8	An amplifier has an open loop gain of 1000. If 10% negative voltage series feedback is used, find the closed loop voltage gain.	01												
	1.9	An amplifier has a bandwidth of $500kHz$. If the lower cutoff frequency is $25Hz$ what is its upper cutoff frequency?	01												
	1.10	$MOSFET$ is a _____ controlled source.	01												
	1.11	Find the value of r_{ds} for the small value of V_{DS} when $V_t = 0.7V$, $V_{GS} = 3.2V$, $k = 2mA/V^2$.	02												
	1.12	Two sinusoidal signals of modulation indices 0.6 and 0.8 are transmitted over AM transmitter simultaneously. Obtain the total modulation index.	01												
	1.13	Fig 1.13 is _____.													
															
		Fig 1.13	01												
	1.14	The output of two variables k -map given in Fig 1.14 is _____.													
		<table border="1"> <tr> <td></td><td>A</td><td>0</td><td>1</td></tr> <tr> <td>B</td><td>0</td><td>0</td><td>1</td></tr> <tr> <td></td><td>1</td><td>1</td><td>1</td></tr> </table>		A	0	1	B	0	0	1		1	1	1	
	A	0	1												
B	0	0	1												
	1	1	1												
		Fig 1.14	01												

1.15	In <i>XOR</i> gate, if all the inputs are same, then output is = _____.	01
1.16	The typical value of input resistance for idea opamp is _____.	01
1.17	The output signal of an opamp with a slew rate of $2V/\mu s$ has a maximum value of $10V$. Then the maximum frequency for undistorted output voltage is _____.	01
1.18	For the truth table given in Table 1.18, identify the gate.	01

Table 1.18

A	B	y
0	0	1
0	1	1
1	0	1
1	1	0

PART-B

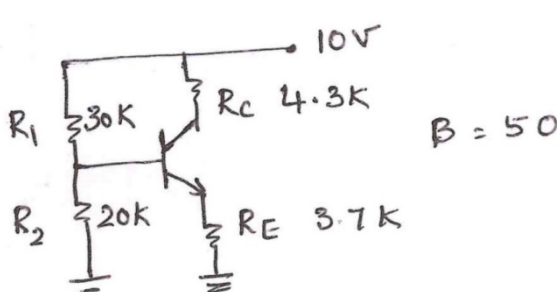2	a	Draw the circuit of full wave bridge rectifier with capacitor filter and explain its working principle with relevant waveforms. Obtain the expression for output <i>DC</i> voltage across the load.	06
	b	A $24V, 600mW$ Zener diode is used for providing a $24V$ stabilized supply to a variable load. If the input voltage is $32V$, determine: i) Value of series resistance required, ii) Diode current when the load is 1200Ω .	06
	c	Write the equation that represents the <i>VI</i> characteristic of <i>pn</i> junction diode. From this equation, obtain the expression for the dynamic resistance r_d of the diode.	04
3	a	Determine the operating point of silicon transistor in the voltage divider biasing circuit in Fig 3a. Also determine S_{ICO} .	06
		 <p>Fig 3a</p>	06
	b	Explain the following with respect to <i>BJT</i> 's: i) Thermal runaway, ii) Bias stabilization.	04
	c	List out any three advantages of negative feedback amplifier. Also prove that gain feedback decreases by a factor of $(1 + A\beta)$ compared to that of the amplifier without feedback, where ' <i>A</i> ' is the open loop gain and ' β ' is the feedback factor.	06
		OR	
4	a	Explain the working of <i>RC</i> coupled amplifier with the circuit diagram. Draw its frequency response and briefly explain 3 regions.	06
	b	An amplifier has a gain of $50dB$, bandwidth of $400kHz$, distortion of 10%, input impedance of $20k\Omega$ and an output impedance of $1k\Omega$. If voltage series negative feedback of 4% is given to the amplifier, calculate the gain, input impedance, output impedance, bandwidth and distortion of the amplifier with negative feedback.	06

c	<p>An amplifier having a power gain of $20dB$ delivers a power output of $40W$ to a load of $10k\Omega$. Calculate:</p> <p>i) Input power needed,</p> <p>ii) Input voltage needed, if the voltage gains of the amplifier is $40dB$.</p>	04
5	<p>a Draw the circuit diagram and explain the operation of a two input <i>CMOS NAND</i> gate.</p> <p>b An <i>N</i> –channel enhancement type <i>MOSFET</i> with $V_{Th} = 0.7$, $I_D = 200\mu A$ when $V_{GS} = V_{DS} = 1.2V$. Find the drain current and transconductance when $V_{GS} = 1.5V$ and $V_{DS} = 3V$.</p> <p>c With the help of neat block diagram of communication system, explain the function of each of the blocks.</p>	06 04 06
	OR	
6	<p>a Explain the operation of an <i>N</i> –channel enhancement <i>MOSFET</i> with a suitable diagram along with its output characteristics.</p> <p>b List out any eight differences between AM and FM systems.</p> <p>c If amplitude modulated transmitter radiates $20kW$ and has a modulation index of 0.6, then calculate the:</p> <p>i) Carrier power and power of each sideband,</p> <p>ii) If total antenna current is $5A$, calculate the antenna current when only the current is sent i.e. carrier current.</p>	06 05 05
7	<p>a Simplify the following expression.</p> <p>i) $Y = (A + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C})(\bar{A} + B)$ using Boolean postulates and <i>D-Morgan's</i> law,</p> <p>ii) $F(a,b,c) = \bar{a}bc + b\bar{c}a + a\bar{b}c$ using <i>K-map</i>.</p> <p>b Write the truth table for the sum and carry out of a full adder. From the truth table, obtain the logic expression and realize the logic circuit using two half adders.</p> <p>c Explain the operation of a 1:4 Demux with necessary truth table, logic expression and logic circuit.</p>	04 06 06
8	<p>a List at least eight characteristics of an ideal op-amp and indicate their typical values for a practical op-amp.</p> <p>b Design an integrator using an op-amp.</p> <p>c In the circuit shown in Figure 8c, determine the output voltage V_o, assuming op-amps to be ideal.</p>	06 06

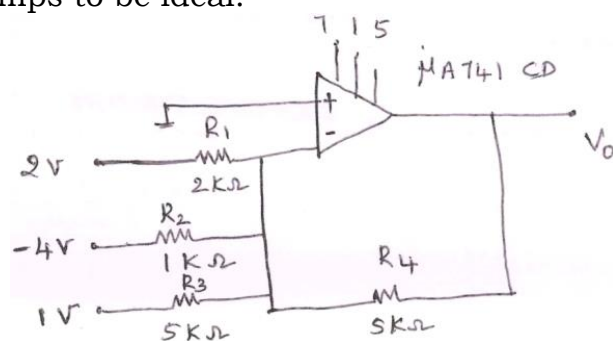


Figure 8c

04

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®
 (An Autonomous Institution affiliated to VTU)
 I / II Semester B. E. Examinations April 2021

Common to All Branches

BASICS OF ELECTRONICS ENGINEERING


Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:


1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6




PART-A

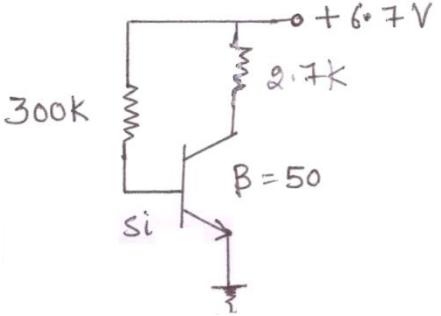
1	1.1	Simplify the following logic expression using Boolean postulates: $Y = (A + B)(\bar{A} + \bar{B})$	01
	1.2	The number of basic gates required to realize 1:4 demultiplexer is _____.	01
	1.3	The maximum power which can be dissipated at 80°C in a diode having maximum power dissipation of 1W at 25°C with a derating factor of $5\text{mW}/^{\circ}\text{C}$ is equal to _____.	01
	1.4	The dynamic resistance of a Si diode at 57°C is 14.3Ω . The dc forward current through the diode is _____.	01
	1.5	The output voltage of a DC power supply drops from 14V to 13.7V when the input voltage reduces by 10%. The line regulation is _____.	01
	1.6	The ac input to a full wave bridge rectifier is $100 \sin \omega t$. The reverse breakdown voltage capability required for diodes used in the above rectifier = _____.	01
	1.7	In a transistor, if β changes from 99 to 199, then α changes from _____ to _____.	01
	1.8	In the circuit of Fig 1.8, $I_C =$ _____ and $V_{CE} =$ _____.	
		 <p style="text-align: center;">Fig 1.8</p>	02
	1.9	In a common emitter amplifier circuit, the dc emitter current is 0.25mA and the collector resistance is $2.6\text{k}\Omega$. The voltage gain of the amplifier is _____.	01
	1.10	The gain of an RC coupled amplifier decreases at low frequencies because of _____.	01
	1.11	An n-channel enhancement MOSFET having $V_t = 0.5\text{V}$, $K = 2\text{mA}/\text{V}^2$ is biased such that $V_{gs} = 2\text{V}$ and $V_{ds} = 1\text{V}$, its $I_D =$ _____.	01

1.12	An amplifier has its open loop and closed loop voltage gains as $46dB$ and $40dB$ respectively. The feedback factor is equal to _____%.	01
1.13	In an RC phase shift oscillator using an ideal voltage amplifier, the frequency of oscillations is $41kHz$. If $R = 5.6k\Omega$, the value of capacitor is _____.	01
1.14	The slew rate of an op-amp is $6.28V/\mu sec$. If it is a voltage follower with an input of $100 \sin \omega t$, the maximum frequency of the input so that the output is not distorted = _____.	01
1.15	The $CMRR$ of an op-amp is $92dB$, if its common mode gain = 0.5 , its differential gain = _____ dB .	01
1.16	In a Schmitt trigger circuit using an op-amp with power supply voltages of $+12V$ and $-12V$ and feedback factor of 0.3 , the hysteresis voltage is equal to _____.	01
1.17	The total power delivered by an AM wave is $2640W$. If the modulation index = 0.8 , the power in each sideband = _____.	01
1.18	The output of an AM transmitter is given by $V_{AM}(t) = 200(1 + 0.4 \sin 12560 t) \sin 6.28 \times 10^6 t.$ The frequency of USB is _____.	01
1.19	In a frequency modulation scheme, $25MHz$ carrier is modulated by $400Hz$ audio sine wave, with a maximum deviation of $10kHz$. The modulation index is _____.	01

PART-B

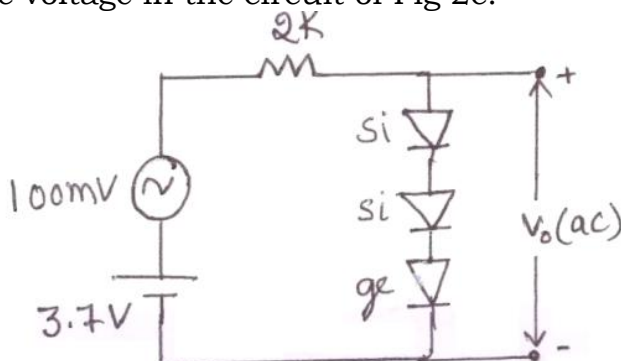2	a	Write the logic expression for exclusive-OR gate and realize it using minimum number of $NAND$ gates.	04
	b	Draw the truth table for "SUM" and "CARRYOUT" of a full adder. From the truth table, obtain the logic expression. From these expressions, realize the full adder using two half adders.	06
	c	Calculate the ac voltage in the circuit of Fig 2c.	06
		 <p style="text-align: center;">Fig 2c</p>	06
3	a	A full wave bridge rectifier without a filter capacitor is connected to a load resistance of $1.5k\Omega$. The input to the rectifier is $300 \sin 314t$, through a step down transformer. If the dc load current is $80mA$, calculate the turns ratio of the transformer. Assume all the diodes used are identical with a forward resistance of 50Ω . Also determine the load regulation.	06

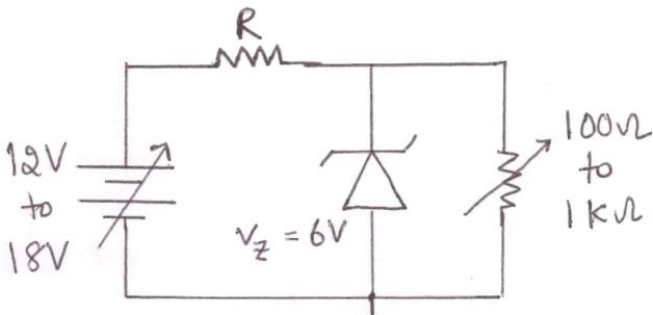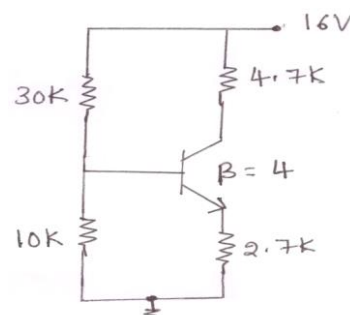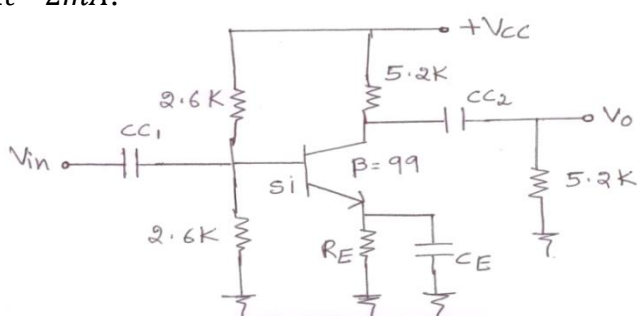b	<p>In a Zener regulator of Fig 3b, calculate the value of R, so that the circuit performs satisfactorily under all the given conditions. Given $I_{Zmin} = 6mA, P_{dmax} = 1164mW$.</p>  <p style="text-align: center;">Fig 3b</p>	06 04
c	<p>Write a note on the three regions of operation of a bipolar transistor.</p> <p style="text-align: center;">OR</p>	06 04
4	<p>a A full wave bridge rectifier drives a load resistance of 270Ω in parallel with a filter capacitor C. If the ac input to the rectifier is $150 \sin 628t$, calculate the capacitor value needed so that the ripple factor is 2%. Determine the output dc voltage, peak to peak ripple voltage and load regulation.</p> <p>b Determine the operating point (V_{CE}, I_C) of the silicon transistor in the circuit of Fig 4b. Also calculate the stabilization factor $S(I_{CO})$ for the circuit.</p>  <p style="text-align: center;">Fig 4b</p>	06 06
c	<p>Explain the working principle and application of photodiode and LEDs.</p>	06 04
5	<p>a In a common emitter amplifier of Fig 5a, find r_e, voltage gain, input and output impedance. The transistor used has a $\beta = 99$ and the dc emitter current $= 2mA$.</p>  <p style="text-align: center;">Fig 5a</p> <p>b List any four advantages of providing voltage series negative feedback to an amplifier. Prove that stability of the gain of A_f of an amplifier with negative feedback improves by a factor of $(1 + A\beta)$ compared to that of the without feedback.</p>	06 06

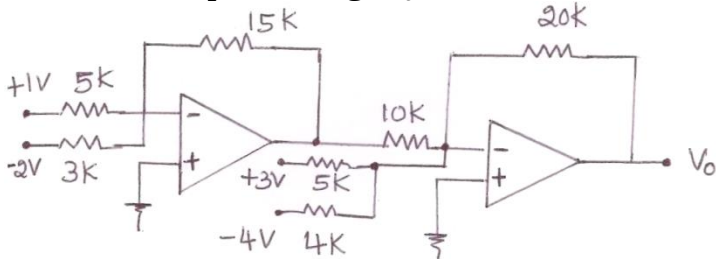c	An <i>NMOS</i> transistor where $V_t = 1V$ and $K = 2mA/V^2$ is operating in saturation with a drain current of $4mA$. Determine V_{gs} and calculate the trans-conductance g_m .	04
OR		
6 a	An amplifier requires an input of $15mV$ to produce a certain output. To get the same output with negative feedback, the required input signal is $330mV$. The closed loop voltage gain is $34dB$. Find open loop voltage gain of the amplifier and the feedback factor.	06
b	An <i>n</i> -channel <i>MOSFET</i> has a $V_t = 0.8V$ and $I_D = 0.75mA$ when $V_{gs} = V_{ds} = 2.5V$. Calculate: i) Drain current, if $V_{gs} = 4.2V$ and $V_{ds} = 4.0V$ ii) Drain to source resistance r_{ds} for small value of V_{ds} , if $V_{gs} = 4.8V$ iii) Gain A_V if $V_{gs} = 4V$ and $R_d = 10k\Omega$.	06
c	Draw the frequency response of an <i>RC</i> coupled <i>CE</i> amplifier and explain the effect of capacitor.	04
7 a	<p>Write six important specifications of an op-amp. In the circuit of Fig 7a, determine the output voltage V_o.</p>  <p style="text-align: center;">Fig 7a</p>	06
b	Draw the circuit of a Schmitt trigger using an ideal op-amp and explain its function with suitable waveform. Calculate the values of resistors R_1 and R_2 , given $V_{CC} = 12V$ and $V_H = 6V$.	06
c	Draw the block diagram of data acquisition system and explain each block.	04
8 a	<p>The output of an <i>AM</i> transmitter is given by</p> $V_{AM}(t) = 50(1 + 0.6 \cos 12560 t) \sin 628 \times 10^4 t.$ <p>Determine :</p> <ol style="list-style-type: none"> The sideband frequencies and their amplitudes Modulation index and bandwidth The minimum and maximum amplitudes of the <i>AM</i> wave The total power in the <i>AM</i> wave, if the load resistance is 10Ω. 	08
b	Write eight differences between <i>AM</i> and <i>FM</i> systems.	04
c	With a neat diagram, explain pulse code modulation system.	04

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®
(An Autonomous Institution affiliated to VTU)
I Semester B. E. Examinations April -2021

Common to All Branches

ELEMENTS OF ELECTRONICS ENGINEERING

Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:


1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6


PART-A



1	1.1	The forward voltage drop of a diode at $27^{\circ}C$ is $550mV$, the forward voltage drop at $57^{\circ}C$ is _____.	01
	1.2	The diffusion capacitance of a forward biased diode _____ with decrease in the forward current.	01
	1.3	The full wave bridge rectifier has dc load current $I_{dc} = 100mA$, input ac voltage is $220V, 50Hz$ and $C = 1000\mu F$. The peak to peak ripple voltage is _____.	01
	1.4	A dc power supply has a no load voltage of $30V$ and a full load voltage of $25V$ at a full load current of $1A$. Calculate the load regulation and its output resistance.	02
	1.5	In a voltage divider circuit for a silicon transistor having $\beta = 49$ has $R_E = 4k\Omega$ and $R_{th} = 60k\Omega$, $S_{(I_{CO})} =$ _____.	01
	1.6	A ratio of I_C/I_E is usually less than one and is defined for _____ configuration.	01
	1.7	The output of a cascaded chain of three amplifiers is $8V$, when the input voltage is $2\mu V$. If the voltage gain of first and third stages are $20dB$ and $40dB$ respectively, the voltage gain in the second stage is _____.	02
	1.8	An amplifier without feedback has a gain of 100 and a distortion of 8% . If 3% negative feedback is provided to the amplifier, the distortion is _____ %.	01
	1.9	An n -channel $MOSFET$ operating in saturation has $I_D = 4mA$ and $V_{ov} = 2V$. Its trans-conductance (g_m) is _____.	01
	1.10	A $MOSFET$ uses the electric field of a _____ to control the channel current.	01
	1.11	A $1MHz$ sinusoidal carrier is amplitude modulated by a symmetrical wave of period $100\mu sec$. Calculate the upper side band frequency.	01
	1.12	Calculate the total modulation index if an AM signal has modulation indices of 0.3 & 0.4 .	01
	1.13	The minimized form of logic expression $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + ABC$ is _____.	01
	1.14	In a 3-to-8 decoder, with $X_2X_1X_0$ as the inputs and Y_0 to Y_7 as the outputs, what should be the input code so that Y_6 is high and all other outputs are low?	01
	1.15	The total number of gates required to implement $64:1$ multiplexer is _____.	01

1.16	The minimum number of <i>NAND</i> gates required to realize <i>XOR</i> gates is _____.	01
1.17	The output signal of an op-amp with a slew rate of $2.5V/\mu\text{sec}$ has a peak to peak value of $18V$. Find the maximum frequency of undistorted output signal.	01
1.18	An op-amp has a differential gain of $86dB$ and common mode gain of $20dB$. The <i>CMRR</i> in <i>dB</i> is _____.	01



PART-B


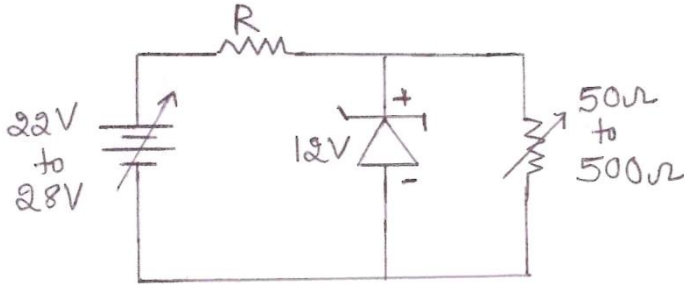
2	<p>a List any four specifications of a PN junction diode and indicate their typical values.</p> <p>b A full wave bridge rectifier using ideal diodes is supplied from the secondary of a 10:1 transformer whose primary is connected to $220V, 50Hz$ main supply. The output of the rectifier is connected to a load resistance of 220Ω in parallel with a capacitor filter C. Calculate the value of C required so that the ripple factor is 3%. Also determine:</p> <p>i) The dc output voltage</p> <p>ii) The peak to peak voltage</p> <p>iii) The load regulation.</p> <p>c In a Zener regulation circuit of Fig 2c, design the value of R, so that circuit performs satisfactorily under all the given conditions. Given $P_{d(max)} = 6W, I_{Zmin} = 10mA, V_Z = 12V$.</p>	04
	 <p style="text-align: center;">Fig 2c</p>	06
3	<p>a Explain the different operating regions of a transistor along with the applications and draw the output characteristics for transistor in common emitter configuration.</p> <p>b In a <i>RC</i> coupled <i>CE</i> amplifier, $R_1 = 120k\Omega, R_2 = 40k\Omega, R_E = 1.5k\Omega, R_C = R_L = 2.7k\Omega, V_{CC} = 12V$ and $\beta = 99$. Determine the operating point of a silicon transistor and also calculate the voltage gain.</p> <p>c Mention any six advantages of negative feedback. Prove that the stability of the gain of an amplifier with negative feedback is $(1 + A\beta)$ times better compared to that of the amplifier without feedback.</p>	04
	OR	06
4	<p>a Explain the following:</p> <p>i) Thermal runaway</p> <p>ii) Early effect.</p> <p>b A voltage amplifier needs $2mV$ input to give a $10V$ output. When negative feedback is provided to this amplifier, it needs $200mV$ to deliver the same output. Determine the open loop gain, closed loop gain, feedback factor and amount of feedback in <i>dB</i> for this amplifier.</p> <p>c Explain the working of <i>RC</i> coupled amplifier with the circuit diagram. Draw its frequency response and briefly explain three regions.</p>	04
		06

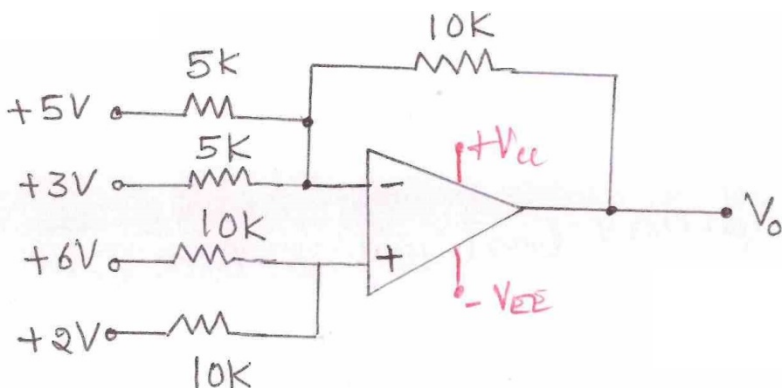5	a	Draw the circuit diagram and explain the operation of a two input <i>CMOS NOR</i> gate.	04	
	b	An <i>n</i> –channel <i>MOSFET</i> has $V_t = 0.9V$. If $V_{gs} = V_{ds} = 2.5V$, the drain current I_D is $0.75mA$, i) Find I_D , if $V_{gs} = 4.1V$ and $V_{ds} = 4V$ ii) Find the trans-conductance g_m , if $V_{gs} = 3.4V$ iii) Find r_{ds} for small value of V_{ds} if $V_{gs} = 4.9V$.		06
	c	Draw the block diagram of a communication system and explain the function of each block. List the need for modulation (any four).		
	OR			
6	a	List eight differences between amplitude modulation and frequency modulation.	04	
	b	Explain the operation of a <i>n</i> –channel enhancement <i>MOSFET</i> with a suitable diagram along with its output characteristics.	06	
	c	An amplitude modulated wave with a modulation index of 50% produces sideband frequencies of $8.824MHz$ and $8.854MHz$. The amplitude of each sideband is $50V$. Determine the amplitude and frequency of both carrier and modulating signals.	06	
7	a	Starting from the logic expression, realize <i>XNOR</i> gate using minimum number of <i>NAND</i> gates.	04	
	b	Simplify the logic expression using <i>K</i> –map and implement the logic circuit using basic gates. $f(a,b,c,d) = \sum m(0,1,2,3,4,6,8,9,10,11,12,14)$	06	
	c	Explain the operation of a 1 – to – 4 demultiplexer and write the logic expressions for its outputs. Also draw the logic circuit to realize the demultiplexer.	06	
8	a	Draw the circuit of an integrator using an op-amp. Derive the expression for the output voltage.	04	
	b	Draw the circuit and design the values of different resistors of a summer circuit using 2 ideal op-amps to get an output voltage $V_o = V_1 - 2V_2 - 4V_3 + 6V_4 + 8V_5$ where V_1, V_2, V_3, V_4 and V_5 are the available input voltages.	06	
	c	Calculate the output voltage V_o for the circuit shown in Fig 8c.		
			06	

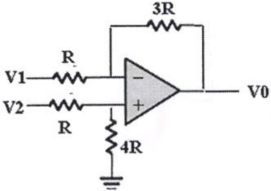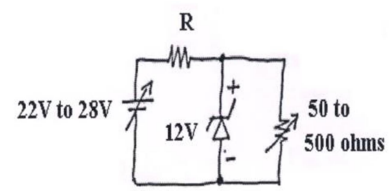1.9	Emitter current in the circuit of Fig 1.9 is = _____.	01
1.10	The lower cutoff frequency of a RC coupled amplifier is 400Hz and the corresponding gain is 80. If the bandwidth required is 30KHz , upper cutoff frequency = _____.	01
1.11	The $M1$ transistor in the circuit shown in Fig 1.11 has $V_t = 0.5\text{V}$. The region of operation of $M1$ = _____.	01
1.12	In common base configuration, phase difference between input and output = _____.	01
1.13	For the circuit shown in Fig 1.13, If $V_1 = 2\text{V}$ and $V_2 = 5\text{V}$, then output voltage = _____ V .	01
	  <p>Fig 1.13 Fig 3b</p>	02
1.14	An opamp has a differential gain of 100dB and $CMRR$ of 80dB . If the differential input is $100\mu\text{V}$ and common mode input is 100mV , output voltage = _____.	02
1.15	An amplifier modulated wave will have _____ number of sidebands.	01
1.16	Maximum efficiency of an AM wave = _____ %.	01
1.17	In a FM wave, the frequency of the carrier is varied in accordance with _____ of the message signal.	01

PART-B

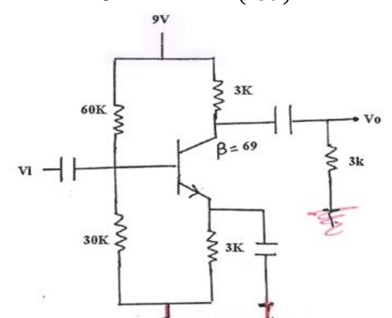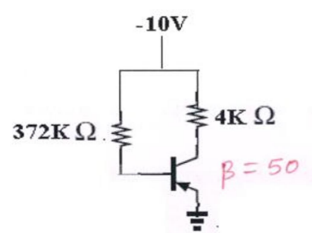2	a	Explain the operation of a 4:1 multiplexer and write the logic expression for its output. Also draw the logic circuit to realize that expression.	06
	b	Prove that the dynamic resistance of a PN junction diode depends on Thermal voltage and Diode forward current. Draw the $V-I$ characteristic of a PN junction diode indicating the different parameters. Show the effect of temperature on the characteristic.	06
	c	Prove the following postulates of Boolean logic: i) $A + \bar{A}B = A + B$ ii) $(A + B)(A + C) = A + BC$	04
3	a	Explain Thermal runaway and Bias stabilization related to Bipolar Junction Transistors (BJT).	04
	b	In the voltage regulator circuit shown in Fig 3b, design the value of R , so that the circuit performs satisfactorily for the given input voltage and load variations. For the zener, $I_{Zmin} = 10\text{mA}$ and $P_{dmax} = 6\text{W}$.	06
	c	In the voltage amplifier circuit shown in Fig 3c, find the following: i) Operating (Q) point of the transistor ii) Stability factor $S_{(ICO)}$.	
		 	

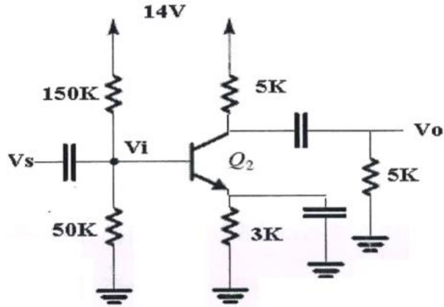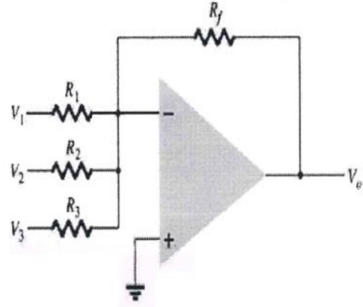		OR		
4	a	With a neat block diagram, explain different stages of <i>DC</i> power supply.	06	
	b	220V, 50Hz ac supply is connected to a full wave bridge rectifier, without a filter, through 10:1 transformer. The forward resistance of each diode used is 6Ω and the load resistance is 80Ω . Find i) dc load current ii) dc output voltage iii) <i>RMS</i> load current iv) Rectification efficiency v) Load regulation vi) Ripple factor.	06	
	c	Find the operating point for the circuit shown in Figure 4c.	04	
5	a	Draw the circuit of 2 –input <i>CMOS NAND</i> gate and explain its working.	04	
	b	A n-channel <i>MOSFET</i> has $V_t = 0.8V$ and drain current of $0.75mA$ when $V_{GS} = V_{DS} = 2.5V$. Find: i) drain current if $V_{GS} = 4.2V$ and $V_{DS} = 4V$ ii) r_{ds} if $V_{GS} = 4.8V$ assuming V_{DS} to be very small. iii) Transconductance if $V_{GS} = 3.5V$.	06	
	c	Explain Barkhausen criteria for sustained oscillations. Explain any five advantages providing negative feedback to amplifiers.	06	
		OR		
6	a	Find V_o/V_i , input impedance and output impedance for the circuit shown in Figure 6a. Assume $\beta = 50$ and $I_E = 0.5mA$.		
		 <p style="text-align: center;">Fig 6a</p>		
		 <p style="text-align: center;">Fig 7b</p>	04	
	b	Draw the circuit of <i>RC</i> phase shift oscillator and find the frequency of oscillations if the output resistance of the common emitter amplifier is $3.3K\Omega$. The phase shift network uses $2.2K\Omega$ resistors and $25nF$ capacitors.	06	
	c	With a neat diagram, explain the structure and working of N-channel enhancement type <i>MOSFET</i> . Draw the plot of I_D versus V_{GS} and I_D versus V_{DS} .	06	
7	a	Draw the circuit of a Schmitt trigger and explain its operation with necessary waveforms.	06	
	b	Explain how an Opamp can be used as a summer. If $V_1 = -2V$, $V_2 = -3V$, $V_3 = 4V$ and $R_1 = 10K\Omega$, $R_2 = 20K\Omega$, $R_3 = 30K\Omega$, $R_f = 10K\Omega$, find V_o of Opamp summer shown in Fig 7b.	04	
	c	Draw the summer circuit using two ideal op amps and calculate the different resistor values to obtain $V_o = 4V_1 - 7V_2 + 6V_3 - 7V_4$ where		

8	a	List eight differences between <i>AM</i> and <i>FM</i> .	04
	b	Draw the block diagram of a communication system and explain the function of each block. List the need for modulation (any four).	04
	c	Draw the block diagram of a digital signal processor and explain the function of each block.	04
	d	A 93.2MHz carrier is frequency modulated by a 5KHz sinusoidal signal. The resultant <i>FM</i> signal has a frequency deviation of 40KHz . What are the highest and lowest frequencies in the frequency modulated signal? Also, calculate the modulation index.	04

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®

(An Autonomous Institution affiliated to VTU)

I / II Semester B. E. Regular / Supplementary Examinations Feb-2024**Common to EC / ET /EI****BASIC ELECTRONICS****Time: 03 Hours****Maximum Marks: 100****Instructions to candidates:**

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. Question number 2 is compulsory. Choose any one full question from 3 or 4, 5 or 6, 7 or 8 and 9 or 10.

PART-A

1	1.1	A DC power supply has NO load voltage of 30V and a full load voltage of 25V at a full load current of 1A. Calculate the load regulation and its output resistance.	02
	1.2	In a NPN transistor, if the base emitter junction is reverse biased and the collector to base junction is reverse biased, the transistor is operating in the _____ region.	01
	1.3	An NPN transistor has $I_{co} = 25nA$, $I_B = 0$, $V_{CE} = 4V$ and $I_C = 20\mu A$. The value of β is _____.	01
	1.4	In a voltage divider circuit, for a silicon transistor having $\beta = 49$ has $R_E = 4K\Omega$ and $R_{th} = 60K\Omega$, $S(I_{co}) =$ _____.	01
	1.5	An amplifier has a voltage gain of 100 at 1kHz. The gain falls by 6dB at 1MHz. If the input is 3mW at 2MHz, then the output voltage is _____.	02
	1.6	The output of a cascaded chain of four amplifiers is 4V, when the input voltage is 0.5mV. If the voltage gains of the first, third and fourth stages are 28dB, 0dB and 12dB respectively, the voltage gain of the second stage in dB is _____.	01
	1.7	An N-channel MOSFET, having $V_t = 1V$, is biased such that $V_G = 4V$. The maximum value of V_D allowed, so that the device operates in ohmic region is _____.	01
	1.8	A MOSFET uses the electric field of a _____ to control the channel current.	01
	1.9	The open loop and closed loop gains of an amplifier are 66dB and 40dB respectively. The amount of negative feedback in dB is _____.	01
	1.10	An amplifier without feedback has a gain of 100 and a bandwidth of 500kHz. If 5% negative feedback is given, then the bandwidth with feedback is _____.	01
	1.11	$(AB' + AB + A'B) =$ _____.	01
	1.12	If any one of the inputs of a EX – NOR gate is always connected to LOW, then the EX – NOR gate behaves as _____.	01

1.13	The total number of gates required to implement 64:1 multiplexer is _____.	01
1.14	An operational amplifier has a differential gain of 100 and a common mode gain of 0.1. The $CMRR$ in dB is _____.	01
1.15	The slew rate of an op amp used as a voltage follower is $5V/\mu s$. If the input voltage is $20\sin 6.28wt$, the maximum frequency of the input so that the output is not distorted is _____ kHz .	01
1.16	For an AM signal, the bandwidth is $10kHz$ and the highest frequency component present is $705kHz$. The carrier frequency used for this AM signal is _____.	01
1.17	A $400W$ carrier is modulated to a depth of 75%. Assuming the modulating signal to be sinusoidal the total power in the amplitude modulated wave is _____.	01
1.18	A part of the transducer which responds to a change in the physical phenomenon is called _____.	01

PART-B

2	a	Draw the block diagram of a DC power supply and explain the function of each block.	04
	b	In a RC coupled CE amplifier, $R_1 = 90k\Omega$, $R_2 = 10k\Omega$, $R_E = 0.68k\Omega$, $R_C = 2.2k\Omega$, $V_{CC} = 16V$ and $\beta = 210$. Determine Z_i , Z_o and A_v of the transistor. Draw the re model for the same.	08
	c	Explain the different operating regions of a transistor along with the applications and draw the output characteristics for transistor in common emitter configuration.	04
3	a	With neat diagram explain the structure and working of N – channel enhancement type $MOSFET$. Draw the plot of I_D versus V_{GS} and I_D versus V_{DS} . Write the current equation at different regions of operation.	07
	b	An N – channel $MOSFET$ has a threshold voltage $V_t = 0.9V$ and $I_D = 0.75mA$, when $V_{GS} = V_{DS} = 2.5V$. Calculate: i) Drain current, if $V_{GS} = 4.1V$ and $V_{DS} = 4.0V$. ii) Drain to source resistance r_{ds} for small values of V_{DS} , if $V_{GS} = 4.9V$ iii) Trans conductance, g_m , if $V_{GS} = 4.9V$	05
	c	Explain the operation of $CMOS$ $NAND$ gate	04
OR			
4	a	Write the advantages of providing a negative series feedback to a voltage amplifier.	04
	b	An amplifier has a gain of $60dB$, bandwidth of $30kHz$, distortion of 15%, input impedance of $5k\Omega$ and an output impedance of $1k\Omega$. If voltage series negative feedback of 3.9% is given to this amplifier, calculate the gain, input impedance, output impedance, distortion, bandwidth and amount of feedback for a closed loop amplifier.	06
	c	Draw the circuit and explain the operation of a two input $CMOS$ NOR gate along with the truth table.	06

5	a	The four variable function f is given in terms of min-terms as: $f(A, B, C, D) = \sum m(0,1,2,3,4,6,8,9,10,11,12,14)$. Using the K -map minimize the function in the sum of products form and realize the expression using only $NAND$ gates.	08
	b	Write the truth table for SUM and $CARRYOUT$ of a full adder. From the truth table, obtain the logic expressions for the same and then realize the full adder using two half adders.	08
OR			
6	a	A logic circuit has 3 inputs A, B and C and 2 outputs X and Y . Output X is 1, only when any two of the inputs are at 1 and Y is 1, only when any one of the inputs is at 1. Write the truth table and the logic expressions for X and Y . Also realize the logic circuit using basic gates.	08
	b	Explain the operation of 8:1 multiplexer along with the truth table and logic expression. Also draw the logic circuit to realise the multiplexer.	08
7	a	List at least eight important characteristics of ideal op-amp and indicate their typical practical values.	04
	b	Draw the circuit and design the values of different resistors of a summer circuit using 2 ideal op amps to get an output voltage $V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$ where V_1, V_2, V_3, V_4, V_5 and V_6 are available input voltages.	06
	c	Draw the circuit of a Schmitt trigger using an ideal op amp and explain its operation with necessary waveforms.	06
OR			
8	a	Draw the circuit of a differentiator using an ideal op amp and derive the expression for the output voltage.	06
	b	Calculate the output voltage for the circuit in Fig. 8.b	
<p style="text-align: center;">Fig. 8.b</p>			
9	a	What is the need for modulation? Write eight differences between AM and FM.	08
	b	Explain the working of a piezoelectric transducer with relevant equations.	08
OR			

10	a	A carrier signal of 1MHz with 400W of its power amplitude modulated with a sinusoidal signal of 2500Hz . The depth of modulation is 75% . Calculate the sideband frequencies, the bandwidth, the power of the sidebands and total power in the modulated wave and sketch the frequency spectrum when amplitude of the carrier signal is 3V .	08
	b	With the help of a neat diagram, discuss the working principle of <i>LVDT</i> .	08

USN


--	--	--	--	--	--	--	--	--	--

R. V. COLLEGE OF ENGINEERING
Autonomous Institution affiliated to VTU
I Semester B. E. Examinations Nov/Dec-18
Common to All Branches
ELEMENTS OF ELECTRONICS ENGINEERING

Time: 03 Hours**Maximum Marks: 100****Instructions to candidates:**



1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

PART-A

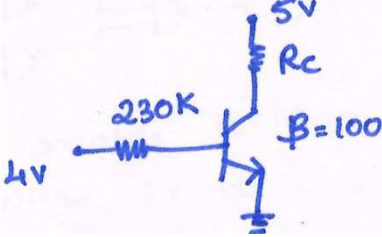1	1.1	The maximum frequency at which a PN junction diode could be used as a switch is limited by its _____.	01
	1.2	For small signal ac operation, a practical forward biased diode can be modeled as _____.	01
	1.3	The input to a full wave bridge rectifier with a capacitor filter is $200V, 50Hz$ supply. If the load resistance is $1K\Omega$, calculate the minimum value of filter capacitor required to keep the ripple factor below 2%.	01
	1.4	For an NPN transistor, if I_{CO} is $4\mu A$, $I_B = 0$, $V_{CE} = 4V$ and $I_C = 100\mu A$, then the value of β is _____.	01
	1.5	In the inverter circuit of fig 1.5, determine the minimum value of R_C .	01
		 <p style="text-align: center;">Fig 1.5</p>	01
	1.6	In a BJT , if the forward voltage V_{BE} is maintained constant, the base current _____ with increase in the reverse bias voltage across CB junction.	01
	1.7	The bandwidth of an amplifier with negative feedback increases by a factor of _____.	01
	1.8	An $NMOS$ transistor with $V_t = 1V$ is biased such that $V_S = 2V$ and $V_G = 5V$. The maximum value of V_D allowed so that transistor operates in ohmic region = _____.	01
	1.9	A $MOSFET$ is a _____ controlled device.	01
	1.10	A carrier signal of $20V$ amplitude is modulated by two sinusoidal modulating signals of amplitudes $6V$ and $8V$. The effective modulation index is _____.	01
	1.11	Three amplifiers with voltage gains 10, 200 and 400 are connected in cascade. Find the overall voltage gain in decibels.	01
	1.12	In a comparator using an ideal op-amp, if the input voltage is $5 \sin \omega t$ and the reference voltage is zero, the output waveform is _____.	01

1.13	The differential gain of an op-amp is 94dB and the common mode gain is 2. Then $CMRR$ in dB is _____.	01
1.14	If an op-amp with an open loop gain of 499 is used as a voltage follower, the error in the gain from its ideal value = _____.	01
1.15	In an n -variable K -map, combining 8-adjacent cells containing 1's as a single group will eliminate _____ variables.	01
1.16	Simplify the following expression $y = \overline{AB} + \overline{A} + AB$.	02
1.17	An ideal op-amp is an ideal _____ controlled _____ source.	01
1.18	Avalanche breakdown in a semiconductor diode occurs due to _____.	01
1.19	The two inputs to an $XNOR$ gate are A and \overline{A} . The output is _____.	01

PART-B

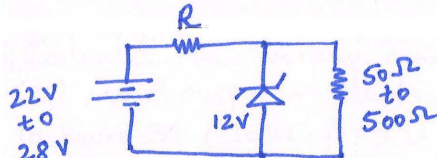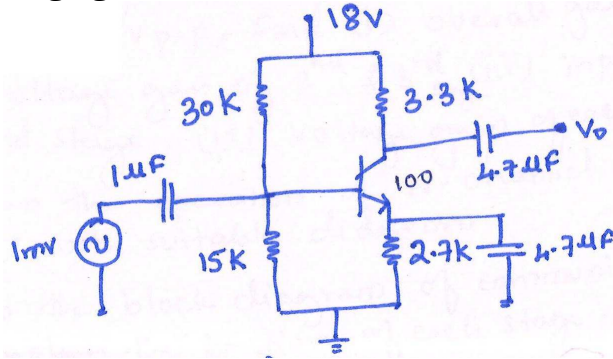2	a	Draw the circuit diagram of a full wave bridge rectifier with capacitor filter along with input and output waveforms. The rectifier drives a load resistance in parallel with a capacitor. Given the ripple factor is equal to 1.5% and the ac input to the rectifier is 150V at 100Hz , calculate the output DC voltage, peak to peak ripple voltage and load regulation.	06
	b	In a Zener regulator of fig 2b, calculate the value of R , so that the circuit performs satisfactorily under all the given conditions.	
		 <p style="text-align: center;">Fig 2b</p>	06
	c	Draw the VI characteristics of a PN junction diode at two different temperatures and explain the changes in the characteristics with temperature.	04
3	a	With respect to $BJTs$, explain the following: i) Bias stabilization ii) Thermal runaway iii) Early effect.	06
	b	Determine the operating point of the silicon transistor in fig 3b. Also calculate the voltage gain.	
		 <p style="text-align: center;">Fig 3b</p>	06
	c	Prove that the gain stability of an amplifier with negative feedback improves by a factor of $(1 + A\beta)$ compared to that of the amplifier without feedback, where A is the open loop gain and β is the feedback factor.	04
OR			

4	a	Briefly explain the three regions of operation of a <i>BJT</i> . Draw and explain the input and output characteristics of a <i>BJT</i> .	06
	b	An amplifier in the open loop has a gain of 80 dB, bandwidth of 300 KHz, distortion of 10%, input impedance of 20 K Ω and output impedance of 2 K Ω . If 2% voltage series negative feedback is given to this amplifier, calculate the gain, BW, input & output impedances and distortion of the closed loop amplifier.	05
	c	Three amplifier stages are cascaded with 0.05 V_{p-p} input providing 150 V_{p-p} output. If the voltage gain of first stage is 20 and the input to the third stage is 15 V_{p-p} , find:	05
		i) Overall gain in dB	
		ii) Voltage gains of 2 nd and 3 rd stages	
		iii) Input voltage to the second stage	
		iv) Voltage gain of each stage in dB.	05
5	a	Explain the operation of an N-channel enhancement <i>MOSFET</i> with a suitable diagram along with its output characteristics.	06
	b	Draw the block diagram of communication system and explain the function of each of the blocks.	05
	c	A carrier of 1 MHz with 1 KW power is amplitude modulated with a sinusoidal signal of 2 KHz. The depth of modulation is 60%. Calculate the sideband frequencies, bandwidth, power in each sideband and the total power in the modulated wave.	05
		OR	
6	a	Draw the circuit diagram and explain the operation of a two input <i>CMOS NOR</i> gate.	06
	b	An N-channel <i>MOSFET</i> has a threshold voltage $V_t = 0.8V$ and $I_D = 0.75mA$, when $V_{GS} = V_{DS} = 2.5V$. Calculate:	06
		i) Drain current, if $V_{GS} = 4.2V$ and $V_{DS} = 4.0V$.	
		ii) Drain to source resistance r_{DS} for small values of V_{DS} , if $V_{GS} = 4.8V$.	
		iii) Trans conductance g_m , if $V_{GS} = 4.8V$.	
	c	List out eight differences between <i>AM</i> and <i>FM</i> systems.	04
7	a	Simplify the following expression using 4-variable <i>K-map</i> :	05
		$f(a,b,c,d) = \sum (1,3,4,5,7,8,9,11,15)$	
	b	Explain the operation of an 8:3 encoder with necessary truth table, logic expression and logic circuit.	
	c	Write the truth table for the sum and carry out of a full adder. From the truth table, obtain the logic expressions. From the logic expressions, realize the logic circuit using <i>NAND</i> gates only.	06
8	a	List atleast eight characteristics of an ideal op-amp and indicate their typical values for a practical op-amp.	04
	b	Draw the circuit of a summer, using two ideal op-amps and design the different resistance values to obtain an output $V_0 = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5$, where $+V_1, +V_2, +V_3, +V_4$ and $+V_5$ are the only available inputs.	06

c

In the circuit of fig 8c, show that the differential gain is equal to R_2/R_1 , if $R_1/R_2 = R_3/R_4$. Assume the op-amp used is ideal.

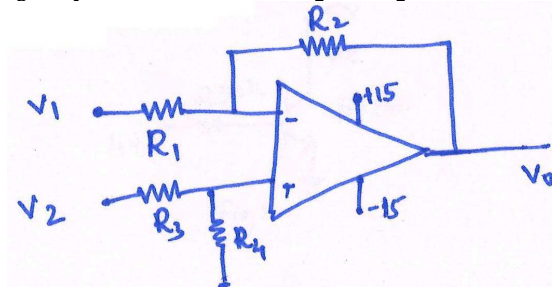


Fig 8c

USN



--	--	--	--	--	--	--	--	--	--

R. V. COLLEGE OF ENGINEERING
Autonomous Institution affiliated to VTU
I Semester B. E. Examinations Nov/Dec-18
Common to All Branches
BASICS OF ELECTRONICS ENGINEERING

Time: 03 Hours**Maximum Marks: 100****Instructions to candidates:**


1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

PART-A

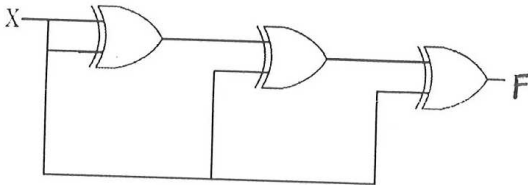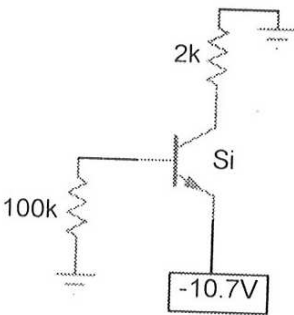1	1.1	What are the minimum number of 2-to-1 multiplexers required to generate a 2-input <i>AND</i> gate.	01
	1.2	The Boolean function $Y = AB + CD$ is to be realized using only 2 input <i>NAND</i> gates. The minimum number of gates required is _____.	01
	1.3	For the circuit of fig 1.3, the output <i>F</i> is given by	
			
		Fig 1.3	01
	1.4	A S_i diode has its maximum power dissipation as 3W at 27°C with a de-rating factor of 20 mW/°C. Determine the power dissipation of the diode at 37°C.	01
	1.5	If a full wave bridge rectifier uses a capacitor filter with $C = 1000\mu F$ and $R_L = 1k\Omega$, $f = 100Hz$, then the ripple factor is _____.	01
	1.6	In a full wave rectifier, without any filter, using diodes with a forward resistance of 10Ω each, the load resistance is equal to $20K\Omega$. The % load regulation of the rectifier= _____.	01
	1.7	A bipolar junction transistor has its $I_C = 2mA$ and $\beta = 199$, if $I_B = 0$, its $I_{C0} =$ _____.	01
	1.8	For the circuit of fig 1.8, $\beta = 30$. The value of $I_C =$ _____.	
			
		Fig 1.8	01

1.9	The lower cut off frequency of an RC coupled amplifier is 500Hz , it has a voltage gain of 50 at 500Hz and has a bandwidth of 50KHz . The upper cut off frequency = _____.	01
1.10	Three voltage amplifiers are cascaded to provide an overall gain of 10000. The first and the last stages have gains of 16dB and 22dB , then the gain of the middle stage is _____.	01
1.11	For an N -channel $MOSFET$, threshold voltage $V_t = 1\text{V}$. The device is biased such that $V_S = 3\text{V}$, $V_G = 6\text{V}$ and $V_D = 4\text{V}$. The device is operating in _____ region.	01
1.12	An open loop amplifier gain is 1000 and 2.9% negative feedback is provided to this amplifier. The gain of the open loop amplifier changes by 15% due to temperature variations. The change in gain with feedback is = _____.	01
1.13	The slew rate of an op amp is $2\text{V}/\mu\text{s}$. If it is used as a voltage follower with an input signal of $5\sin\omega t$, the maximum frequency of the input so that the output is not distorted= _____.	01
1.14	An op-amp has a common mode gain of 10 and a $CMRR$ of 100dB . If the differential input is $10\mu\text{V}$ and common mode voltage is 1mV , the output voltage is = _____.	01
1.15	In a voltage follower circuit, the op-amp used is ideal in all respects except that it has a finite gain of 100. The gain of the voltage follower is = _____.	01
1.16	A Schmitt trigger circuit with an op-amp is connected to a power supply voltages $+15\text{V}$ and -12V and has a feedback factor $\beta = 0.3$. The value of resistors in a Schmitt trigger circuit, $R_1 =$ _____ and $R_2 =$ _____.	01
1.17	The current drawn by the antenna of an AM transmitter is 5A when only carrier is present and this increases to 6A when the carrier is modulated by a sine wave. The percentage modulation is = _____.	01
1.18	AM signal and FM signal frequency ranges are _____ and _____ respectively.	01
1.19	Given an FM wave, $V_{FM} = 10\sin[2\pi \times 10^8 t + 5\sin(2\pi \times 15 \times 10^3 t)]$, the bandwidth is = _____.	01
1.20	Mention two advantages of digital communication over analog communication.	01

PART-B

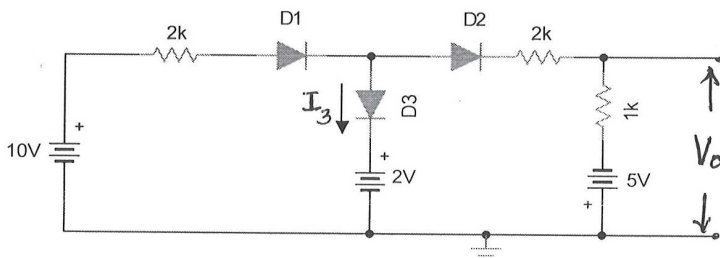2	a	Write the logic expression for $EX - NOR$ function and realize it using minimum number of NOR gates only.	04
	b	Explain the operation of 8 to 3 encoder. Write the logic expressions for the outputs and realize it using basic gates.	06
	c	Determine the current I_3 through the diode D_3 and the output voltage V_o in the circuit of fig 2c. All the diodes are silicon diodes.	
		 <p style="text-align: center;">Fig 2c</p>	06

<p>3</p> <p>a</p> <p>b</p>	<p>A full wave bridge rectifier using ideal diodes is supplied from a secondary of a 10:1 transformer whose primary is connected to 240V, 50Hz main supply. The output of the rectifier is connected to a resistance of 1000Ω, in parallel with a capacitor filter C. Calculate:</p> <ol style="list-style-type: none"> The value of 'C' required so that the ripple factor is 1% DC output voltage Peak-peak ripple voltage Load regulation. <p>In a Zener circuit of fig 3b, design the value of 'R' so that the regulator performs satisfactorily for all the given input voltage and load conditions. Load resistance varies from 30Ω to 300Ω.</p>	<p>04</p>
<p>c</p>	<div data-bbox="544 533 1145 880" data-label="Diagram"> </div> <p>Fig 3b</p> <p>For the voltage divider bias circuit of fig 3c, find the operating point.</p> <div data-bbox="687 1003 997 1473" data-label="Diagram"> </div> <p>Fig 3c</p>	<p>06</p>
OR		
<p>4</p> <p>a</p> <p>b</p> <p>c</p>	<p>Draw the circuit of a full wave bridge rectifier along with input and output waveforms. Explain the principle of operation. Derive the expression for efficiency of a practical full wave bridge rectifier.</p> <p>Explain the principle of operation of LED and photodiode. Mention their typical applications.</p> <p>Determine the values of R_C, R_1 and R_2 for the voltage divider bias network with a silicon transistor given the following DC operating conditions. $V_{CC} = 20V$, $V_{CEQ} = 8V$, $I_{CQ} = 10mA$, $S(I_{CO}) = 3$, $R_E = 200\Omega$ and $\beta = 80$.</p>	<p>04</p> <p>04</p> <p>08</p>
<p>5</p> <p>a</p>	<p>Draw the circuit of an RC coupled amplifier in common emitter configuration. Explain the principle of operation by drawing the frequency response.</p>	<p>06</p>

6	b	An amplifier has a voltage gain of $40dB$, bandwidth of $600KHz$, input impedance of $15K\Omega$, distortion of 10% and an output impedance of $2K\Omega$. If voltage series negative feedback of 1.9% is given to this amplifier, calculate the gain, input impedance, output impedance, bandwidth and distortion of the amplifier with negative feedback. Also find the amount of feedback in dB .	06
	c	An N-channel enhancement type <i>MOSFET</i> with $V_t = 1V$ conducts a current $I_D = 100\mu A$ when $V_{GS} = V_{DS} = 1.5V$. Find the value of I_D for $V_{GS} = V_{DS} = 2.5V$. Also calculate the value of r_{DS} for small values of V_{DS} , when $V_{GS} = 3V$.	04
	OR		
	a	Draw the circuit and explain the operation of an <i>RC</i> phase shift oscillator using a common emitter amplifier. Determine the frequency of oscillation, if the output resistance of the common emitter amplifier is $3K\Omega$, the phase shift network uses $1.5K\Omega$ resistors and $10nF$ capacitors.	07
	b	Draw the circuit of a <i>CMOS</i> Inverter. With the truth table, explain the operation of the circuit.	04
	c	Draw the ac equivalent circuit of a <i>CE</i> configuration. Give a comparison of the three configurations in which a <i>BJT</i> could be used as an amplifier.	05
7	a	Draw the summer circuit, using two ideal op amps, and calculate the different resistor values to obtain an output voltage of $V_0 = V_1 - 4V_2 + 5V_3 - 8V_4$.	05
	b	Draw the circuit of an Instrumentation amplifier, using three ideal amplifiers, and calculate the values of the different resistors to obtain a differential gain of $80dB$ with an infinite <i>CMRR</i> .	06
	c	Explain the principle of operation of data converters.	05
8	a	Write eight differences between <i>AM</i> and <i>FM</i> systems.	06
	b	A carrier wave with amplitude $10V$ and frequency $10MHz$ is amplitude modulated to 70% level with a modulating frequency $2KHz$, write the equation of <i>AM</i> signal and sketch the frequency spectrum.	04
	c	Draw the block diagram of a digital signal processor and explain function of each block.	06