

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®

(An Autonomous Institution affiliated to VTU)

I / II Semester B. E. Regular / Supplementary Examinations Feb-2024**Common to EC / ET /EI****BASIC ELECTRONICS****Time: 03 Hours****Maximum Marks: 100****Instructions to candidates:**

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. Question number 2 is compulsory. Choose any one full question from 3 or 4, 5 or 6, 7 or 8 and 9 or 10.

PART-A

1	1.1	A DC power supply has NO load voltage of 30V and a full load voltage of 25V at a full load current of 1A. Calculate the load regulation and its output resistance.	02
	1.2	In a NPN transistor, if the base emitter junction is reverse biased and the collector to base junction is reverse biased, the transistor is operating in the _____ region.	01
	1.3	An NPN transistor has $I_{co} = 25nA$, $I_B = 0$, $V_{CE} = 4V$ and $I_C = 20\mu A$. The value of β is _____.	01
	1.4	In a voltage divider circuit, for a silicon transistor having $\beta = 49$ has $R_E = 4K\Omega$ and $R_{th} = 60K\Omega$, $S(I_{co}) =$ _____.	01
	1.5	An amplifier has a voltage gain of 100 at 1kHz. The gain falls by 6dB at 1MHz. If the input is 3mW at 2MHz, then the output voltage is _____.	02
	1.6	The output of a cascaded chain of four amplifiers is 4V, when the input voltage is 0.5mV. If the voltage gains of the first, third and fourth stages are 28dB, 0dB and 12dB respectively, the voltage gain of the second stage in dB is _____.	01
	1.7	An N-channel MOSFET, having $V_t = 1V$, is biased such that $V_G = 4V$. The maximum value of V_D allowed, so that the device operates in ohmic region is _____.	01
	1.8	A MOSFET uses the electric field of a _____ to control the channel current.	01
	1.9	The open loop and closed loop gains of an amplifier are 66dB and 40dB respectively. The amount of negative feedback in dB is _____.	01
	1.10	An amplifier without feedback has a gain of 100 and a bandwidth of 500kHz. If 5% negative feedback is given, then the bandwidth with feedback is _____.	01
	1.11	$(AB' + AB + A'B) =$ _____.	01
	1.12	If any one of the inputs of a EX – NOR gate is always connected to LOW, then the EX – NOR gate behaves as _____.	01

1.13	The total number of gates required to implement 64:1 multiplexer is _____.	01
1.14	An operational amplifier has a differential gain of 100 and a common mode gain of 0.1. The $CMRR$ in dB is _____.	01
1.15	The slew rate of an op amp used as a voltage follower is $5V/\mu s$. If the input voltage is $20\sin 6.28wt$, the maximum frequency of the input so that the output is not distorted is _____ kHz .	01
1.16	For an AM signal, the bandwidth is $10kHz$ and the highest frequency component present is $705kHz$. The carrier frequency used for this AM signal is _____.	01
1.17	A $400W$ carrier is modulated to a depth of 75%. Assuming the modulating signal to be sinusoidal the total power in the amplitude modulated wave is _____.	01
1.18	A part of the transducer which responds to a change in the physical phenomenon is called _____.	01

PART-B

2	a	Draw the block diagram of a DC power supply and explain the function of each block.	04
	b	In a RC coupled CE amplifier, $R_1 = 90k\Omega$, $R_2 = 10k\Omega$, $R_E = 0.68k\Omega$, $R_C = 2.2k\Omega$, $V_{CC} = 16V$ and $\beta = 210$. Determine Z_i , Z_o and A_v of the transistor. Draw the re model for the same.	08
	c	Explain the different operating regions of a transistor along with the applications and draw the output characteristics for transistor in common emitter configuration.	04
3	a	With neat diagram explain the structure and working of N – channel enhancement type $MOSFET$. Draw the plot of I_D versus V_{GS} and I_D versus V_{DS} . Write the current equation at different regions of operation.	07
	b	An N – channel $MOSFET$ has a threshold voltage $V_t = 0.9V$ and $I_D = 0.75mA$, when $V_{GS} = V_{DS} = 2.5V$. Calculate: i) Drain current, if $V_{GS} = 4.1V$ and $V_{DS} = 4.0V$. ii) Drain to source resistance r_{ds} for small values of V_{DS} , if $V_{GS} = 4.9V$ iii) Trans conductance, g_m , if $V_{GS} = 4.9V$	05
	c	Explain the operation of $CMOS$ $NAND$ gate	04
OR			
4	a	Write the advantages of providing a negative series feedback to a voltage amplifier.	04
	b	An amplifier has a gain of $60dB$, bandwidth of $30kHz$, distortion of 15%, input impedance of $5k\Omega$ and an output impedance of $1k\Omega$. If voltage series negative feedback of 3.9% is given to this amplifier, calculate the gain, input impedance, output impedance, distortion, bandwidth and amount of feedback for a closed loop amplifier.	06
	c	Draw the circuit and explain the operation of a two input $CMOS$ NOR gate along with the truth table.	06

5	a	The four variable function f is given in terms of min-terms as: $f(A, B, C, D) = \sum m(0,1,2,3,4,6,8,9,10,11,12,14)$. Using the K -map minimize the function in the sum of products form and realize the expression using only $NAND$ gates.	08
	b	Write the truth table for SUM and $CARRYOUT$ of a full adder. From the truth table, obtain the logic expressions for the same and then realize the full adder using two half adders.	08
OR			
6	a	A logic circuit has 3 inputs A, B and C and 2 outputs X and Y . Output X is 1, only when any two of the inputs are at 1 and Y is 1, only when any one of the inputs is at 1. Write the truth table and the logic expressions for X and Y . Also realize the logic circuit using basic gates.	08
	b	Explain the operation of 8:1 multiplexer along with the truth table and logic expression. Also draw the logic circuit to realise the multiplexer.	08
7	a	List at least eight important characteristics of ideal op-amp and indicate their typical practical values.	04
	b	Draw the circuit and design the values of different resistors of a summer circuit using 2 ideal op amps to get an output voltage $V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$ where V_1, V_2, V_3, V_4, V_5 and V_6 are available input voltages.	06
	c	Draw the circuit of a Schmitt trigger using an ideal op amp and explain its operation with necessary waveforms.	06
OR			
8	a	Draw the circuit of a differentiator using an ideal op amp and derive the expression for the output voltage.	06
	b	Calculate the output voltage for the circuit in Fig. 8.b	
<p style="text-align: center;">Fig. 8.b</p>			
9	a	What is the need for modulation? Write eight differences between AM and FM.	08
	b	Explain the working of a piezoelectric transducer with relevant equations.	08
OR			

10	a	A carrier signal of 1MHz with 400W of its power amplitude modulated with a sinusoidal signal of 2500Hz . The depth of modulation is 75% . Calculate the sideband frequencies, the bandwidth, the power of the sidebands and total power in the modulated wave and sketch the frequency spectrum when amplitude of the carrier signal is 3V .	08
	b	With the help of a neat diagram, discuss the working principle of <i>LVDT</i> .	08