

## Basics Electronics (22EC13)

## Tutorial-1

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{0.02} = 49$$

$$I_E = \beta I_B + (1+\beta) I_{CO}$$


$$I_E = 50(6n) = 0.3\mu A$$

1. Silicon transistor has its  $I_{CO}=6nA$  and  $\alpha=0.98$ . If  $V_{BE}=0$  and  $V_{CE}=4V$  then  $I_C = \dots$   
 2. An NPN transistor has  $I_{CO}=30nA$ ,  $I_{BQ}=0$ ,  $V_{CEQ}=4V$  and  $I_{CQ}=30nA$ . The value of  $\beta = \dots$   
 3. The measured terminal voltages (in Volts) of different NPN transistors are given in Table-1. For each of the transistors, find  $V_{BE}$  and identify the region of operation.

	$V_{BE}$	$V_{CE}$	$V_{CB}$
Q1	0	0.7	0.7
Q2	0	0.8	0.1
Q3	-2.7	-2.0	0
Q4	0	0	0.3
Q5	0.7	0.7	0

Table 1.4.29.49.49.49

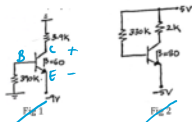Find the values of  $\beta$  that correspond to  $\alpha$  values of 0.5, 0.6, 0.8, 0.9, 0.98 and 0.99.  
 Find the values of  $\alpha$  that correspond to  $\beta$  values of 40, 60, 80, 99, 149 and 249.



In the fixed base current biasing circuit of Fig 1 and 2 determine the operating point of the silicon transistor.

In the circuit of Fig 3, determine  $V_C$ ,  $V_E$ ,  $V_{CE}$  and  $I_C$ .


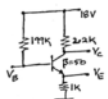


Fig 3

In the circuit of Fig 4, find  $V_C$ ,  $I_C$ ,  $I_B$ ,  $I_E$  and  $V_{CE}$ .

## Basics Electronics (22EC13)

## Tutorial-1

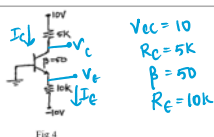

In the inverter circuit of Fig 5, determine the maximum value of  $R_B$  so that the circuit could be used as an inverter.

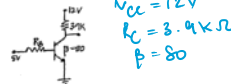


Fig 5

In the inverter circuit of Fig 6, determine the minimum value of  $\beta$ , so that the circuit could be used as an inverter.

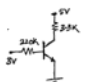


Fig 6

Determine the operating point of silicon transistor in the voltage divider biasing circuit Fig 7. Also determine  $\beta_{DC}$ .

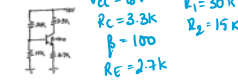


Fig 7

In an RC coupled CE amplifier,  $R_1 = 50k\Omega$ ,  $R_2 = 25k\Omega$ ,  $R_C = 2k\Omega$ ,  $\beta = 99$  and  $I_C = 2mA$ . Determine the voltage gain, input impedance and output impedance of the amplifier.

$$\beta = \alpha = 0.98 = 49$$

$$1 - \alpha = 0.02$$

$$I_E = \beta I_B + (1 + \beta) I_{CO}$$

$$I_E = 50(6n)$$

$$I_E = 0.3\mu A$$

$$30\mu A = (\beta + 1) 30\mu A$$

$$1000 = \beta + 1$$

$$\beta = 999$$

$$(a) \quad \begin{array}{c} 10V \\ | \\ R_B \\ | \\ B \\ | \\ E \\ | \\ 0 \end{array}$$

active

$$(b) \quad \begin{array}{c} 10V \\ | \\ R_B \\ | \\ B \\ | \\ E \\ | \\ 0 \end{array}$$

saturation

$$(c) \quad \begin{array}{c} 10V \\ | \\ R_B \\ | \\ B \\ | \\ E \\ | \\ 0 \end{array}$$

active

$$(d) \quad \begin{array}{c} 10V \\ | \\ R_B \\ | \\ B \\ | \\ E \\ | \\ 0 \end{array}$$

active

$$(e) \quad \begin{array}{c} 10V \\ | \\ R_B \\ | \\ B \\ | \\ E \\ | \\ 0 \end{array}$$

active

$$(f) \quad \begin{array}{c} 10V \\ | \\ R_B \\ | \\ B \\ | \\ E \\ | \\ 0 \end{array}$$

active

$$0 - V_{BE} - I_E R_E = 0$$

$$-0.7 - I_E (10k) = 0$$

$$I_E = \frac{0.7}{10k}$$

$$I_E = 0.07mA$$

$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{0.07mA}{51}$$

$$I_B = 1.37\mu A$$

$$I_C = \beta I_B$$

$$I_C = 0.91mA$$

$$V_E = I_E R_E = 0.7V$$

$$V_E = 10 + (0.91mA)(10k)$$

$$V_E = 9.1V$$

$$V_C = 10 - I_C R_C$$

$$V_C = 10 - (0.91mA)(5k)$$

$$V_C = 5.45V$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = 5.45V - 9.1V$$

$$V_{CE} = -3.65V$$

$$V_{CE} = 10 - I_C R_C - V_{BE} - I_E R_E = 0$$

$$10 - (1.37\mu A)(25k) - 0.7 - (1.37\mu A)(10k) = 0$$

$$10 - 3.425 - 0.7 - 13.7 = 0$$

$$10 - 17.825 = 0$$

$$-7.825 = 0$$

$$V_{CE} = 10 - I_C R_C - V_{BE} - I_E R_E = 0$$

$$10 - (1.37\mu A)(25k) - 0.7 - (1.37\mu A)(10k) = 0$$

$$10 - 3.425 - 0.7 - 13.7 = 0$$

$$10 - 17.825 = 0$$

$$-7.825 = 0$$

$$(a) \quad 0 - (390k) I_B - V_{BE} = -9$$

$$9 = (390k) I_B + 0.7$$

$$I_B = \frac{9 - 0.7}{390k}$$

$$I_B = 0.0213mA$$

$$I_B = 21.3\mu A$$

$$I_C = \beta I_B = 60 \times 21.3\mu A$$

$$I_C = 1.278mA$$

$$(b) \quad 5 - (30k) I_B - V_{BE} = -5$$

$$10 - 0.7 = (30k) I_B$$

$$I_B = \frac{9.3}{30k}$$

$$I_B = 0.31mA$$

$$I_C = \beta I_B = 80 \times 0.31mA$$

$$I_C = 24.8mA$$

$$(c) \quad 0 - (3.9k) I_C - V_{CE} = -9$$

$$V_{CE} = 9 - (1.87mA)(3.9k)$$

$$V_{CE} = 9 - 7.393$$

$$V_{CE} = 1.607V$$

$$(d) \quad V_{CE} = 18V$$

$$R_C = 2.2k\Omega$$

$$\beta = 50$$

$$R_E = 1k\Omega$$

$$R_B = 199k\Omega$$

$$I_B = \frac{V_{CE} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$I_B = \frac{18 - 0.7}{(199k) + (51)(1k)}$$

$$I_B = \frac{17.3}{250k}$$

$$I_B = 69.2\mu A$$

$$I_C = \beta I_B = 50(69.2\mu A)$$

$$I_C = 3.46mA$$

$$I_E = (\beta + 1) I_B$$

$$I_E = 51(69.2\mu A)$$

$$I_E = 3.529mA$$

$$18 - I_C R_C = V_C$$

$$18 - (3.46mA)(2.2k) = V_C$$

$$V_C = 10.38V$$

$$V_E = I_E R_E = 0$$

$$V_E = (3.529mA)(1k)$$

$$V_E = 3.529V$$

$$18 - I_B R_B = V_B$$

$$V_B = 18 - (69.2\mu A)(199k)$$

$$V_B = 18 - 13.77$$

$$V_B = 4.23V$$

$$(f) \quad R_1 = 50k\Omega$$

$$R_2 = 25k\Omega$$

$$R_C = R_L = 2k\Omega$$

$$\beta = 99$$

$$I_E = 2mA$$

$$Z_i = R_{th} \parallel (\beta + 1) Z_o$$

$$Z_o = R_L \parallel R_C$$

$$A_v = \frac{-R_C \parallel R_L}{Z_o}$$

$$V_E = I_E R_E = 0$$

$$V_E = 10 + (0.91mA)(10k)$$

$$V_E = 9.1V$$

$$V_C = 10 - I_C R_C$$

$$V_C = 10 - (0.91mA)(5k)$$

$$V_C = 5.45V$$

$$R_{th} = R_1 \parallel R_2$$

$$R_{th} = \frac{50k \cdot 25k}{50k + 25k}$$

$$R_{th} = 16.67k\Omega$$

$$Z_o = R_L \parallel R_C$$

$$Z_o = \frac{2k \cdot 2k}{2k + 2k}$$

$$Z_o = 1k\Omega$$

$$A_v = \frac{-R_C \parallel R_L}{Z_o}$$

$$A_v = \frac{-2k \parallel 2k}{1k}$$

$$A_v = -1$$

$$(g) \rightarrow 12 - I_C R_C - V_{CE} = 0$$

$$12 - (\beta + 1) I_B R_C - 0.3 = 0$$

$$12 - (80) I_B (3.9k) - 0.3 = 0$$

$$I_B = \frac{11.7}{312k}$$

$$I_B = 37.5\mu A$$

$$I_C = \beta I_B = 100 I_B = 3.75mA$$

$$I_E = (\beta + 1) I_B = 101 I_B = 3.7875mA$$

$$(g) \quad 0 - V_{CE} - I_C R_C = 0$$

$$V_{CE} = -I_C R_C$$

$$V_{CE} = -3.75mA \cdot 3.9k$$

$$V_{CE} = -14.625V$$

$$\rightarrow V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$V_{th} = \frac{10V \cdot 15k}{30k + 15k}$$

$$V_{th} = 6.67V$$

$$R_{th} = R_1 \parallel R_2$$

$$R_{th} = \frac{30k \cdot 15k}{30k + 15k}$$

$$R_{th} = 10k\Omega$$

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$V_{th} = \frac{10V \cdot 15k}{30k + 15k}$$

$$V_{th} = 6.67V$$

$$R_{th} = R_1 \parallel R_2$$

$$R_{th} = \frac{30k \cdot 15k}{30k + 15k}$$

$$R_{th} = 10k\Omega$$

$$\rightarrow V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$10 - (1.37\mu A)(25k) - 0.7 - (1.37\mu A)(10k) = 0$$

$$10 - 3.425 - 0.7 - 13.7 = 0$$

$$10 - 17.825 = 0$$

$$-7.825 = 0$$

$$R_{th} = 10k\Omega$$

$$I_C = (\beta + 1)I_B = 101I_B = 1.88mA \rightarrow 5 - I_B R_B - V_{BE} = 0$$

$$5 - (37.5\mu A) R_B - 0.7 = 0$$

$$R_B = 4.3k\Omega$$

$$K_B = 114.7k\Omega$$

$$V_{CE} = 18 - 6.171 - 5.076$$

$$V_{CE} = 6.753V$$

$$S_{ICO} = \frac{1}{1 + \frac{\beta R_E}{R_{th} + R_E}}$$

$$S_{ICO} = \frac{101}{1 + \frac{100 \times 2.7k}{10k + 2.7k}}$$

$$S_{ICO} = 4.7529$$

$$P = 10 \dots$$


$$3 = I_B R_B - V_{BE} = 0$$

$$3 = I_B (220k) - 0.7 = 0$$

$$I_B = \frac{2.3}{220k}$$

$$I_B = 10.5\mu A$$

# Basics Electronics (22EC13) Tutorial-1

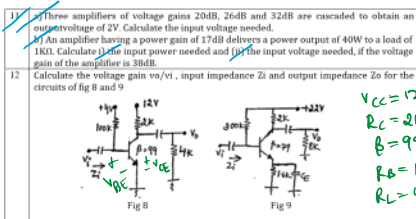

11a) Three amplifiers of voltage gains 20dB, 26dB and 32dB are cascaded to obtain an output voltage of 2V. Calculate the input voltage needed.

12) Calculate the voltage gain  $v_o/v_i$ , input impedance  $Z_i$  and output impedance  $Z_o$  for the circuits of Fig 8 and 9.

$V_{CC} = 12V$   
 $R_C = 2k\Omega$   
 $\beta = 99$   
 $R_B = 100k\Omega$   
 $R_E = 1k\Omega$

$Z_i = R_B \parallel (\beta + 1)r_e$   
 $12 - I_C(2k) - V_{CE} = 0$   
 $4 - (100k)(I_B) - 0.7 = 0$   
 $I_B = 33\mu A$   
 $I_C = \beta I_B$   
 $I_C = (99)(33\mu A)$   
 $I_C = 3.27mA$

$V_o = 2V$   
 $V_i = ?$   
 $A_{v_{tot}} = 20 \log \left( \frac{V_o}{V_i} \right)$   
 $20 + 26 + 32 = 20 \log \left( \frac{2}{V_i} \right)$   
 $78 = 20 \log \left( \frac{2}{V_i} \right)$   
 $10^{3.9} = \frac{2}{V_i}$   
 $V_i = \frac{2}{10^{3.9}} = 0.3mV$

11b)  $A_T = 17dB$  i)  $P_i = ?$   
 $P_o = 40W$  ii)  $V_i = ?$  if  $A_v = 38dB$   
 $R = 1k\Omega$

$A_p = 10 \log \left( \frac{P_o}{P_i} \right)$   
 $17 = 10 \log \left( \frac{40}{P_i} \right)$   
 $P_i = \frac{40}{10^{1.7}}$   
 $P_i = 0.798W$

$A_v = 20 \log \left( \frac{V_o}{V_i} \right)$   
 $38 = 20 \log \left( \frac{200}{V_i} \right)$   
 $\log \left( \frac{200}{V_i} \right) = 1.9$   
 $V_i = \frac{200}{10^{1.9}}$   
 $V_i = 2.579V$

$$38 = 20 \log \left[ \frac{200}{V_i} \right]$$

$$P = \frac{V^2}{R}$$

$$40 = \frac{V^2}{1000}$$

$$Z_i = \frac{R_B (\beta + 1) r_e}{R_B + (\beta + 1) r_e}$$

$$Z_o = R_C \parallel R_L$$

$$Z_o = \frac{(2k)(4k)}{2k + 4k}$$

$$Z_o = 1.33k\Omega$$

$$r_e = \frac{26mV}{I_E}$$

$$r_e = \frac{26mV}{3.27mA}$$

$$r_e = 7.87\Omega$$

$A_v, Z_i, Z_o$

12a)  $Z_i = R_B \parallel (\beta + 1) r_e$   
 $Z_i = \frac{R_B (\beta + 1) r_e}{R_B + (\beta + 1) r_e}$   
 $Z_i = \frac{(100k)(100)(7.87)}{100k + (100)(7.87)}$   
 $Z_i = 7.87 \times 10^4 \Omega$   
 $Z_i = 78.7k\Omega$

$r_e = \frac{26mV}{I_E}$   
 $4 - I_B R_B - V_{BE} = 0$   
 $4 - I_B (100k) - 0.7 = 0$   
 $I_B = \frac{3.3}{100k}$   
 $I_B = 33\mu A$   
 $I_C = (\beta + 1) I_B = 3.3mA$

$r_e = \frac{26mV}{3.3mA}$   
 $r_e = 7.87\Omega$

$Z_o = R_C \parallel R_L$   
 $Z_o = \frac{(4k)(2k)}{4k + 2k}$   
 $Z_o = 1.33k\Omega$

$A_v = \frac{-R_C \parallel R_L}{r_e}$   
 $A_v = \frac{-1.33k}{7.87m}$   
 $A_v = -169$

12b)  $Z_i = R_B \parallel (\beta + 1) r_e$   
 $Z_i = \frac{R_B (\beta + 1) r_e}{R_B + (\beta + 1) r_e}$   
 $Z_i = \frac{(300k)(80)(6.5261)}{(300k) + (80)(6.5261)}$   
 $Z_i = 521.18\Omega$

$Z_o = R_C \parallel R_L$   
 $Z_o = \frac{(4k)(8k)}{4k + 8k}$   
 $Z_o = 1.6k\Omega$

$A_v = \frac{-Z_o}{r_e} = \frac{-1.6k}{6.5261}$   
 $A_v = -245.16$

$r_e = \frac{26mV}{3.984mA}$   
 $r_e = 6.5261\Omega$