

unit 4  
tutorial s...

Subject:

## Tutorial 4

1. In the voltage follower circuit, op amp used is ideal in all respects, except it has a finite gain, A. Determine  $v_o/v_a$ . If A is equal to 1000, calculate the error of the gain from that of the voltage follower with an ideal op amp.
2. Draw the summer circuit, using two ideal op amps, and calculate the different resistor values to obtain  $v_o = 2v_1 - 4v_2 + 6v_3$ . Let  $v_o = v_1 + 3v_2 + 5v_3 - 7v_4 - 9v_5 - 11v_6$ , where  $v_1, v_2, v_3, v_4, v_5$  and  $v_6$  are the available inputs.
3. The output signal of an op amp with a slew rate of  $2.5V/\mu s$ , has a peak to peak value of  $18V$ . Find the maximum frequency for undistorted output voltage.
4. An op amp has a differential gain of  $2 \times 10^4$  and a CMRR of  $86dB$ . Determine the output, if the differential input is  $10\mu V$  and the common mode input is  $10mV$ .
5. In the circuits of Figs 7, 8 and 9, determine the output voltage,  $v_o$ . Assume the op amps to be ideal.

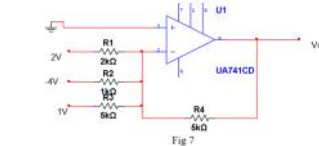


Fig 7

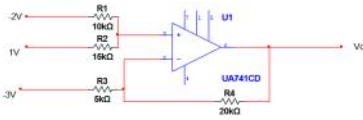


Fig 8

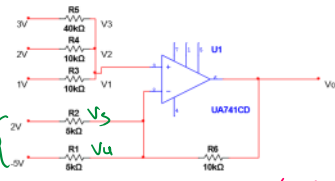


Fig 9

$$V_{o1} = -R_f \left( \frac{V_4}{R_1} + \frac{V_5}{R_2} \right)$$

$$= -10k \left( \frac{2}{5k} + \frac{2}{5k} \right)$$

$$V_{o1} = -6V$$

$$V_o = V_{o1} + V_{o2}$$

$$V_{o2} = \left( 1 + \frac{R_f}{R_1 || R_2} \right) V^+$$

$$V^+ = \frac{R_4 || R_5 \times V_1}{R_4 || R_5 + R_3} + \frac{R_3 || R_5 \times V_2}{R_3 || R_5 + R_4} + \frac{R_3 || R_4 \times V_3}{R_3 || R_4 + R_5}$$

①  $A = 1000$

$$\frac{v_o}{v_{in}} = A_v = \frac{A}{1+A}$$


$$= \frac{1000}{1+1000}$$

$$A_v = 0.99$$

$$e_{\%} = 1 - A_v$$

$$= 0.01$$

② a)  $V_o = 2V_1 - 4V_2 + 6V_3$

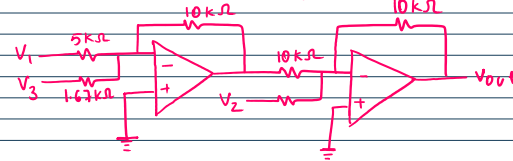Assuming  $R_f = 10k\Omega$ ,

$$V_o = - \left[ \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right] \quad V_o = - \left[ \frac{R_f}{R_2} V_2 \right]$$

$$\frac{R_f}{R_1} = 2$$

$$R_1 = \frac{10k}{2} = 5k\Omega$$


$$\frac{R_f}{R_2} = 4$$

$$R_2 = \frac{10k}{4} = 2.5k\Omega$$

$$\frac{R_f}{R_3} = 6$$

$$R_3 = \frac{10k}{6} = 1.67k\Omega$$

b)  $V_o = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$

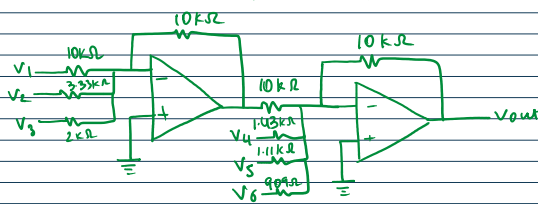Assuming  $R_f = 10k\Omega$ 

$$V_o = - \left[ \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] \quad V_o = - \left[ \frac{R_f}{R_4} V_4 + \frac{R_f}{R_5} V_5 + \frac{R_f}{R_6} V_6 \right]$$

$$\frac{R_f}{R_1} = 1 \Rightarrow R_1 = \frac{10k}{1} = 10k\Omega$$

$$\frac{R_f}{R_2} = 3 \Rightarrow R_2 = \frac{10k}{3} = 3.33k\Omega$$

$$\frac{R_f}{R_3} = 5 \Rightarrow R_3 = \frac{10k}{5} = 2k\Omega$$

$$\frac{R_f}{R_4} = 7 \Rightarrow R_4 = \frac{10k}{7} = 1.43k\Omega$$

$$\frac{R_f}{R_5} = 9 \Rightarrow R_5 = \frac{10k}{9} = 1.11k\Omega$$

$$\frac{R_f}{R_6} = 11 \Rightarrow R_6 = \frac{10k}{11} \approx 909\Omega$$

③  $S_R = 2.5V/\mu s$

$$2V_m = 18V \Rightarrow V_m = 9V$$

$$f_m = 9$$

$$f_m = \frac{S_R}{2\pi V_m}$$

$$= \frac{2.5/10^{-6}}{2(3.14)(9)}$$

$$f_m = 44.23 KHz$$

④  $A_d = 20k$

$$CMRR(p) = 86dB ; 86 = 20 \log f$$

$$V_d = 10\mu V$$

$$V_c = 10mV$$

$$\rightarrow f = \frac{A_d}{A_c}$$

$$A_c = \frac{A_d}{f} = \frac{20k}{19.95k}$$

$$A_c = 1.0025$$

$$\rightarrow V_{oc} = A_c V_c$$

$$= 1.0025 \times 10^{-2}$$

$$V_{oc} \approx 0.01002V$$

$$\rightarrow V_{od} = A_d V_d$$

$$= 20k \times 10\mu$$

$$= 0.2V$$

$$\rightarrow V_o = V_{od} + V_{oc}$$

$$V_o = 0.21002V$$

⑤