
Elements of Electronics Engineering [22EC13]

Tutorial-2

1. An enhancement type NMOS transistor with $V_t=0.8\text{V}$ and $k=2\text{mA/V}^2$, find the drain current for each of the following cases:
 - a. $V_{GS}=5\text{V}$ and $V_{DS}=1\text{V}$.
 - b. $V_{GS}=0.6\text{V}$ and $V_{DS}=0.2\text{V}$.
 - c. $V_{GS}=2\text{V}$ and $V_{DS}=1.2\text{V}$.
 - d. $V_{GS}=V_{DS}=3\text{V}$.
2. An N-channel enhancement type MOSFET with $V_{th}=1\text{V}$ conducts a current $I_D=100\mu\text{A}$ when $V_{GS}=V_{DS}=1.5\text{V}$. Find the value of I_D for $V_{GS}=2.5\text{V}$ and $V_{DS}=4\text{V}$. Also calculate the value of r_{DS} for small values of V_{DS} , when $V_{GS}=3\text{V}$.
3. An n-channel MOSFET is used as an amplifier with a drain resistance of $20\text{K}\Omega$. It is biased such that $V_{GS}=4\text{V}$ and $V_{DS}=5\text{V}$. If $V_{th}=0.8\text{V}$ and $k=1.5\text{mA/V}^2$ for the MOSFET, determine the transconductance, g_m , and the voltage gain.
4. An N-channel enhancement type MOSFET with $V_{th}=0.7$, $I_D=100\mu\text{A}$ when $V_{GS}=V_{DS}=1.2\text{V}$. Find I_D and g_m when $V_{GS}=1.5\text{V}$ and $V_{DS}=3\text{V}$.
5. Find r_{ds} for the small value of V_{DS} when $V_{th}=0.7$, $V_{GS}=3.2\text{V}$ and $k=2\text{mA/V}^2$.
6. A voltage amplifier needs 10mV input to give a certain output. When negative feedback is provided to this amplifier, it needs 4V to deliver the same output. If the closed loop gain of the amplifier is 40dB , determine the open loop gain of the amplifier and the feedback factor.
7. An amplifier with an open loop gain of 1000 delivers a certain output power at 10% harmonic distortion when the input signal is 10mV . If 40dB negative voltage series feedback is provided to this amplifier, determine the required input signal so that the output power remains the same and also find the new % harmonic distortion.
8. An amplifier has a gain of 40dB , bandwidth of 300KHz , distortion of 15% , input impedance of $10\text{K}\Omega$ and an output impedance of $1\text{K}\Omega$. If voltage series negative feedback of 3.9% is given to this amplifier, calculate the gain, input impedance, output impedance, bandwidth and distortion of the amplifier with negative feedback.

Course Co-ordinator Name

Course Co-ordinator Signature
