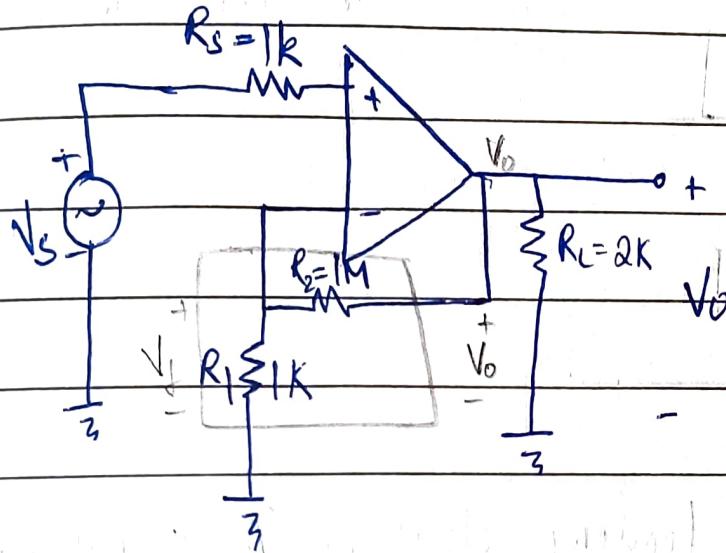



In the given, non-inverting voltage series Negative feedback amplifier circuit, if $R_i = 100k\Omega$, $R_o = 1k\Omega$, $A_v = 10^4 \times V_o$. Find R_{if} , R_{of} , A_f and the actual R_{in} and R_{out} .



Non-inverting amp
is ex. for
Voltage Series am

[Non-inverting Amp].

b. Network:

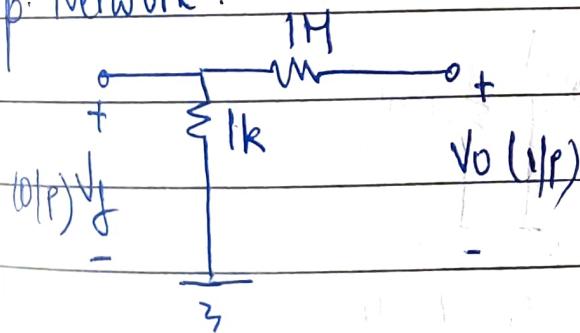

$$B = \frac{V_f}{V_o}$$

$$V_f = 1 \times 1k = \frac{V_o \times 1k}{1M + 1k}$$

$$\Rightarrow \frac{V_f}{V_o} = \frac{1k}{1M + 1k} = 0.999m \text{ (or) } 999\mu$$


- Looking from left if any β pno is connected to A'
- β pno is connected to A' then shunt between the β and A'
- Shunt has to be shunted

- O/p is connected to $(A' \text{ in series} \rightarrow \text{Open})$

R_{sh}
then shunt of β pno is connected to $'A'$ amp o/p as shunt

- If β pno is connected to A' amp, β pno as series
then open it.

\Rightarrow

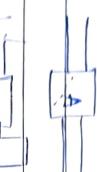

$$1k || 1M \approx 999\Omega$$

$$1k + 1M = 1.001 M\Omega$$

$$\Rightarrow R_{\text{sh}} = \frac{1}{1 + \beta}$$

$$R_{\text{sh}} = \frac{R_o}{1 + \beta}$$

$$R_o = 1k || 1.99k = 665.5\Omega //$$

$$7.5\Omega$$

$$R_{\text{sh}} = R_o / (1 + \beta)$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$



Considering the β 's loading effect on ' A' amplifier, the new open loop transimpedance circuit will be as below:



$$A = \frac{V_o}{V_i} = \frac{V_o}{V_i} \times \frac{V_i}{V_s}$$

$$V_o = 10^3 \times 1.99k = 6.655k V_i$$

$$\frac{V_o}{V_i} = 6.655k$$

$$V_i = \frac{V_s \times 100k}{1k + 0.99k + 100k} = 0.99V_s$$

$$\Rightarrow \frac{V_i}{V_s} = 0.99$$

$$\boxed{\frac{V_i}{V_s}}$$

$$A = 0.99 \times 6.655k = 6.525k$$

$$R_{\text{sh}} = R_o (1 + \beta)$$

$$\Rightarrow R_{\text{sh}} = \frac{R_o}{1 + \beta}$$

With loading effect

$$R_{\text{sh}} = 10\Omega$$

$$[1k + 1k + 100k]$$

$$R_{\text{sh}} = (10\Omega) (7.5\Omega) = 75.1\Omega //$$

$$R_{\text{sh}} = \frac{R_o}{1 + \beta}$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$


$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$R_{\text{sh}} = R_o / (1 + 6.525k) \approx 100\Omega$$

$$\boxed{R_{\text{sh}} = 100\Omega}$$

Power Amplifiers

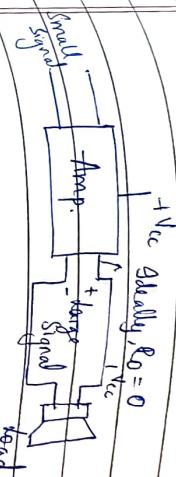

Q.2 A voltage amplifier needs 50mV input to give a certain opf. If the amplifier, it needs open loop feedback is provided to the amplifier, it needs 2.5V to deliver the same opf. If the closed loop gain of the amplifier is 50 dB. Find the open loop gain (A_v) of the amplifier and amount of feedback.

$$38 = 20 \log(A_v/10^2)$$

$$1.9 = \log(A_v/10^2) \Rightarrow A_v = 10^{1.9} = 19.43 //$$

$$V_i = 50 \text{ mV} \Rightarrow V_o = 2.5 \text{ V}$$

$$V_o = V_b \quad V_b = V_o$$

$$(A_v)_{OL} = \frac{(AV)_{OL}}{1 + A_f \beta}$$

$$\frac{V_o}{V_b} = \frac{V_o}{\frac{V_b}{(1+A_f \beta)}} \Rightarrow (1+A_f \beta) = \frac{V_o}{V_b} = \frac{2.5}{0.5} = 5.0$$

$$(1+A_f \beta = 5.0)$$


$$(A_v)_{OL} = (19.43)(5.0) = 97.2 //$$

$$1 + A_f \beta = 5.0$$

$$A_f \beta = 4.9$$

$$\beta = 4.9 = 0.0103 //$$
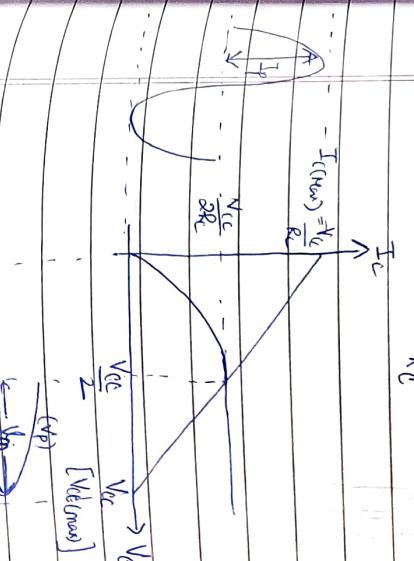
$$\text{Opf. dropt } \eta: \\ V_{ce} - I_c R_c - V_{be} = 0 \\ V_{ce}(\max) = V_{cc} \quad [\text{when } I_c = 0] \\ I_c(\max) = V_{cc} \quad [\text{when } V_{ce} = 0]$$



$$-I_{C(\text{Max})} = \frac{V_{cc}}{R_C}$$

$$V_{in} = \frac{V_{cc}}{2}$$


$$\rho_{OL} = \text{diss} \quad [\text{dissipation should be low}]$$

$$A \rightarrow \eta = 0.51$$

$$B \rightarrow \eta = 0.81$$

$$C \rightarrow \eta = 50//$$

Draw A Power Amplifier

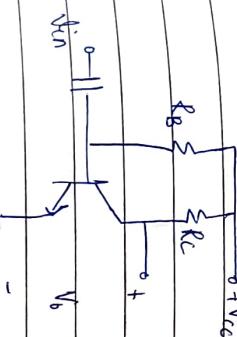

Class B Power Amplifier



$$\frac{V_{AC}}{\sqrt{2}} \times \frac{\pi R_L}{\sqrt{2} V_{AC}} = \frac{\pi R_L}{4}$$

Q.1 For a class-A power amp. $V_C = 30V$, $R_C = 20\Omega$. Find P_e if the current varies by $\pm 50mA$ for the applied input. Find the circuit efficiency.

$$I_{BQ} = I_{S(BE)} - \sqrt{V_{BE}} =$$

$$\text{for Class-A amp., } I_{CQ} = \frac{V_{CC}}{2R_C}$$

$$\beta = \frac{I_c}{I_B} \Rightarrow I_B = \frac{0.15}{20} = 25mA$$

$$w_{\text{use}} = 25 \text{ cm}$$

$$\eta = \frac{P_{\text{el,des}}}{P_{\text{in,dc}}} = \frac{V_{\text{rms}} \times I_{\text{rms}}}{N_{\text{DC}} \times I_{\text{DC}}} = 0$$

$$V_{\text{rms}} \times I_{\text{rms}} = I_{\text{rms}} \times R_C = \left(\frac{1}{\sqrt{2}} V_m\right) \times R_C = \left(\frac{B_2 R_1}{\sqrt{2}} V_m\right) \times R_C = B_2 R_1 R_C V_m$$

$$V_{in(d)} = \sqrt{B_C} \times I_{AC} = \sqrt{B_C \times I_Q} = \sqrt{B_C \times V_{DC}} \dots$$

Q.2 If the current ratio is 2:1 and $R_L = 45\Omega$ what is the V_{CC} min to get $4W$ of power [Polar] a) What is the I_{CS} for $V_{CC} = 11.5V$ b) When $V_{CC} = 18V$ and $R_L = 45\Omega$,

$$= \frac{V_{cc} \times I_c}{\sqrt{L_2}} \times \frac{V_u}{B_R}$$

二
七

$$\eta = \frac{P_0}{P_{in}} = \frac{6.05}{14.228} = 43.9\%$$

To understand better, $P_{o(ac)} = \frac{18^2}{2 \times 8} = 20.25$

$$P_{o(ac)} = \frac{V_{ce}^2}{2R_L}$$

$$R_L' = \frac{(18)^2}{2R_L} \times 4 = 11.32$$

$$AV = \frac{V_{ce}}{R_L'} \Rightarrow (AV)^2 = A \times 362$$

$$V_{ce} = 11.31V$$


$$a) \quad I_{Q2} = \frac{V_{ce}}{R_L} = 11.31 = 0.907A$$

$$I_Q = \frac{1}{16}$$

$$b) \quad V_{ce} = 18V \quad R = 4\Omega$$

$$P_{o(ac)} = \frac{V_{ce}^2}{2R_L} = \frac{18^2}{2 \times 6} = 10.125W$$
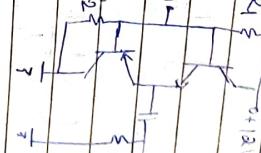
$$c) \quad \text{If } G_F \text{ is given at } 1/f_p \text{ what is } P_{o(ac)}? \\ P_o = \frac{V_{ce}^2}{2R_L} = \frac{3^2}{2 \times 4} = \frac{9}{8} = 1.125W$$



Q.3 A class-B power amplifier is given. What is the Vce min to

get 80% of power to 8Ω load

$$\text{thus } P_{o(ac)} = \frac{V_{ce}^2}{2R_L}$$

$$V_{ce}^2 = \partial R_L P_{o(ac)}$$

$$V_{ce} = 17.88V$$

Q) If the input peak voltage $P_{in(AC)}, P_{o(ac)}$, η , V_{ce}
 $V_m = 18V$

$$P_{in(AC)} = V_{ce} \times \frac{V_m}{2R_L}$$

$$= 17.88 \times \frac{18 \times 10}{2 \times 8} = 14.228W$$

Particularly, $V_{ce} = V_m = V_p$
 $P_{o(ac)} = \frac{V_p^2}{2R_L} = 6.25W$

$$P_{o(ac)} = \frac{V_{ce}^2}{2R_L} = 11.66W = 2.43W$$

$$\eta = \frac{P_{in(AC)}}{P_{in(AC)}} = \frac{6}{11.66} = 52.356\%$$

Power dissipation in each transistor:


$$P_{transistor} = P_{ce} - P_{ac} = \frac{11.66 - 6}{2} = 2.83W$$

Unit 5 : Operational Amplifier

Draw → transistor always in active
Draw is → high efficiency
Draw is → combines with

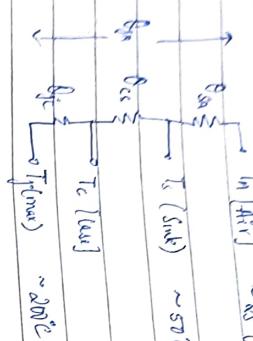1) Draw

Heat Sink → Material used to dissipate heat generated → to the ambient q_0 .



$$T_j = T_h + \frac{\theta_{ja}}{P_b} = C/W$$

$$R = \frac{V_1 - V_2}{I}$$

$$-CHRR \text{ is } \infty \quad CHRR = \frac{A_d}{A_m}$$

Characteristics of Op-Amp

- Gain is ∞
- β_{in} is ∞
- γ_{o} is 0
- B_W is ∞

$$T_j = T_h + \theta_{ja} + \theta_{jc}$$

+ve feedback is given \rightarrow oscillation
-ve feedback is given \rightarrow amplifier

Q.1 A power transistor for which $T_j(\max) = 200^\circ\text{C}$ can dissipate $P(\max) = 50\text{W}$. Find θ_{ja} at Ambient temperature $T_a = 25^\circ\text{C}$.

Find P_b at $T_h = 50^\circ\text{C}$

$$\theta_{ja} = \frac{T_j(\max) - T_h}{P_b(\max)} = \frac{200 - 50}{50} = 3.5^\circ\text{C/W}$$

$$P_b = T_j - T_h = 200 - 50 = 150 \text{ W}$$

$$P_b = \frac{150}{3.5} = 42.857 \text{ W}$$

$$T_j = T_h + \theta_{ja} = 50 + 3.5^\circ\text{C}$$

$$T_j = 53.5^\circ\text{C}$$


$$P_b = \frac{T_j(\max) - T_h}{\theta_{ja}} = \frac{180 - 50}{3.5} = 40 \text{ W}$$

$$P_b = \frac{180 - 50}{25} = 6 \text{ W}$$

$$P_b = 40 \text{ W and } P_b = 50 \text{ W.}$$

$$P_b = \frac{T_j(\max) - T_c}{\theta_{jc}} = \frac{180 - 70}{50} = 2.0^\circ\text{C/W}$$

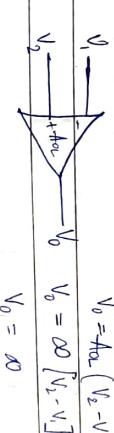$V_1 = V_2 = 0 \Rightarrow V_o = A_{OL} [V_2 - V_1]$
 $V_1 = V_2 \neq 0 \Rightarrow V_o = 0$ [Virtual short]



$$V_o = A_{OL} (V_2 - V_1)$$

$$V_o = 0$$

$$V_2 - V_1 \text{ is } +V, \quad V_o = +\infty$$

$$V_2 - V_1 \text{ is } -V, \quad V_o = -\infty$$



$$V_o = A_{OL} (V_2 - V_1)$$

$$V_o = 0$$

Limitations of -Amplifier (BJT, H-bridge)

- Gain is less (A_{OL})
- Bandwidth is low
- R_{in} is not high (g_m needed is high)
- R_{out} is not low

* No wound gap $\Rightarrow N_1 = N_2$, $N_1 \neq 0$

$$* V_{Q1} \Rightarrow V_1 - \frac{N_1}{N_2} V_{A1} - V_1 = 0, N_1 \neq 0$$

$$* N_2 V_2 \Rightarrow N_2 A_2 \cdot V_2 = 0, N_2 \neq 0$$

i) Inverting Amplifier [Ideal]

$$A_{V1} = N^2, I_{in} = \infty, N_2 = N_1$$



$$V_{in} - V_2 - V_1 = 0$$

$$V_1 = V_2$$

$$V_2 = -\frac{V_1}{R_2}$$

$$\frac{V_1}{R_1} = -R_2 - A_{V1}$$

$$V_1 = -R_2 (V_{in})$$


i) Inverting Amplifier [Non-Ideal] $\rightarrow A_{V1} \neq \infty, R_{in} = \infty, N_2 \neq N_1$

$$R_{in} = \frac{N_1}{R_1}$$

$$\frac{V_{in}}{R_{in}} = R_1$$

Input Impedance of Inverting Amplifier
 $R_{in} = \frac{V_{in}}{I_1}$

thus, $X_{in} = R_1 || \infty = R_1$
 the \therefore if $R_1 \uparrow$, then gain reduces.
 Thus, R_2 is increased.

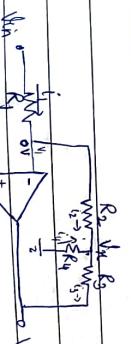

thus, $I_1 = I_2$ [$R_{in} = \infty$]

$$\frac{V_1 - V_2}{R_1} = V_1 - V_2$$

$$\frac{V_1 + V_0/A_{V1}}{R_1} = -\frac{V_0/A_{V1}}{R_2} - V_2 = -\left(\frac{V_0 + V_0/A_{V1}}{A_{V1}}\right)$$

$$R_2 \left[\frac{V_0 + V_0}{A_{V1}} \right] = -R_1 \left[\frac{V_0 + V_0}{A_{V1}} \right]$$

$$V_{in} R_2 = -R_1 V_0 - \frac{R_1 V_0}{A_{V1}} - \frac{R_2 V_0}{A_{V1}}$$

$$\Rightarrow I_3 = \frac{V_{in}}{R_1} + \frac{V_{in} R_2}{R_1 R_2}$$

$$V_{in} R_2 = -R_1 V_0 \left[1 + \frac{1}{A_{V1}} \left(1 + \frac{R_2}{R_1} \right) \right]$$

$$= -R_2$$

$$\frac{V_0}{V_{in}} = \frac{-R_2/R_1}{1 + \left(\frac{1 + R_2/R_1}{A_{V1}} \right)}$$

$$A_{V1}$$

ii) a) Non-Inverting Amplifier [Bridg] [$R_{in} = \infty$, $A_{out} = \infty$]

$$\text{V}_x - \text{V}_o = \text{i}_2 R_2$$

$$\text{V}_o = \text{V}_x + \text{i}_2 R_2$$

$$\text{V}_o = \frac{\text{R}_2 \text{R}_4}{\text{R}_1} - \text{i}_2 \left[\frac{\text{V}_o}{\text{R}_2} + \frac{\text{V}_o + \text{V}_{in}}{\text{R}_1 \text{R}_2} \right]$$

$$\text{V}_o = \text{R}_2 \left[\frac{\text{R}_1}{\text{R}_2} + \frac{\text{R}_2 + \text{R}_1}{\text{R}_1 \text{R}_2} \right] \text{V}_{in}$$

$$\text{V}_o = -\frac{\text{R}_2}{\text{R}_1} \left[1 + \frac{\text{R}_2 + \text{R}_1}{\text{R}_1 \text{R}_2} \right] \text{V}_{in}$$

The input impedance is increased.


$$\text{I}_2 = \text{i}_1 \quad [\text{R}_{in} = \infty]$$

$$\frac{\text{V}_o - \text{V}_{in}}{\text{R}_2} = \frac{\text{V}_{in}}{\text{R}_1}$$

$$\frac{\text{V}_o}{\text{R}_2} = \frac{\text{V}_{in}}{\text{R}_1 + \text{R}_2}$$

$$\frac{\text{V}_o}{\text{R}_2} = \frac{\text{V}_{in}}{\text{R}_1 + \text{R}_2} = 1 + \frac{\text{R}_2}{\text{R}_1}$$

$$\frac{\text{V}_o}{\text{V}_{in}} = A_{CL} = 1 + \frac{\text{R}_2}{\text{R}_1}$$

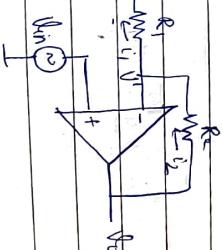ii) b) Non-Inverting Amplifier [Non-bridg] [$\text{R}_{in} = \infty$, $A_{out} \neq \infty$]

$$\text{V}_o = A_{OL} \left[\text{V}_{in} - \text{V}' \right]$$

$$\text{V}' = \text{i}_1 \text{R}_1$$

$$\text{i}_1 = \text{i}_2$$


$$\frac{\text{V}'}{\text{R}_1} = \frac{\text{V}_o - \text{V}'}{\text{R}_2}$$

$$\frac{\text{V}_o - \text{V}_o}{\text{A}_{OL}} = \frac{\text{V}_o - \text{V}_{in} + \text{V}_o}{\text{A}_{OL}}$$

$$\frac{\text{R}_1}{\text{R}_1 + \text{R}_2} = \frac{\text{V}_o - \text{V}_{in}}{\text{A}_{OL}}$$

$\frac{V_o}{V_{in}} = \frac{A_{OL}}{1 + A_{OL}}$
At when $1 + A_{OL} \gg 1$,
 $V_o = A_{OL} V_{in}$

(ii) Voltage follower [Non-Invert]

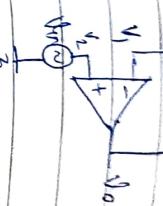

$$R_2 \left(\frac{V_{in}}{A_{OL}} - \frac{V_0}{A_{OL}} \right) + V_0 \left(\frac{V_0 - V_{in}}{R_1} + \frac{V_0}{A_{OL}} \right)$$

$$\frac{V_{in}}{A_{OL}} - \frac{V_0}{A_{OL}} = R_2 \frac{V_0}{A_{OL}} - A_{OL} \frac{V_0}{A_{OL}} + \frac{V_0}{A_{OL}}$$

$$A_{OL}$$

$$V_{in} (R_2 + R_1) = V_0 \left(R_1 + \frac{V_0}{A_{OL}} + \frac{V_0}{R_1} \right)$$

$$\frac{V_0}{R_1} = \frac{R_2 + R_1}{A_{OL}} \quad \Rightarrow \quad R_2 + R_1 = A_{OL} \frac{V_0}{R_1}$$

$$\frac{V_0}{R_1} = \frac{R_2 + R_1}{A_{OL}} + \frac{V_0}{A_{OL}} \left(R_2 + R_1 \right)$$

$$\frac{V_0}{R_1} = \frac{V_0 \left[1 + \frac{R_2}{R_1} \right]}{R_1 \left[1 + \frac{1}{A_{OL}} (R_2 + R_1) \right]}$$


$$\frac{V_0}{R_1} = \frac{1 + R_2 / R_1}{1 + \frac{1}{A_{OL}} (R_2 + R_1)}$$

$$\frac{V_0}{R_1} = \frac{1 + R_2 / R_1}{1 + \frac{1 + R_2 / R_1}{A_{OL}}}$$

From independent:

$$\frac{V_0}{R_1} = R_{in} = \infty \quad [\text{Practically a short}]$$

(iii) a. Voltage Follower [Invert]

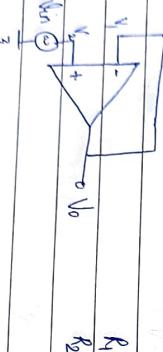

$$R_2 = \infty$$

$$R_1 = 0$$

$$\text{ideally, } V_0 = A_{OL} (V_2 - V_1)$$

$$V_0 = A_{OL} V_{in} \quad \rightarrow A$$

Practically, $V_0 = A_{OL} V_{in} + A_{in} V_{in} \rightarrow B$

- 1. Differential Op
- Applying superposition theorem
- Consider, $V_1 = V_{in}, V_2 = 0V$.


$$V_0 = A_{OL} [V_{in} - 0V]$$

$$V_0 = \left(1 + \frac{R_2}{R_1} \right) V_{in} \Rightarrow V_0 = \left[1 + \frac{R_2}{R_1} \right] V_{in}$$

$$V_0 = V_{in}$$

$$AV = 1$$

(iii) b. Difference Amplifier

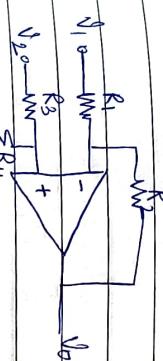

$$\frac{V_1}{R_1}$$

$$\frac{V_2}{R_2}$$

$$\frac{V_0}{R_3}$$

$$\frac{V_0}{R_4}$$

$$\text{ideally, } V_0 = A [V_2 - V_1]$$

$$V_0 = A_{OL} V_{in} \quad \rightarrow A$$

Practically, $V_0 = A_{OL} V_{in} + A_{in} V_{in} \rightarrow B$

$$\frac{V_0}{R_3} = A_{OL} \left[\frac{V_2}{R_2} - \frac{V_1}{R_1} \right] + A_{in} \left[\frac{V_2}{R_2} - \frac{V_1}{R_1} \right]$$


$$\frac{V_0}{R_3} = \left(1 + \frac{R_3}{R_4} \right) V_{in} \Rightarrow V_0 = \left[1 + \frac{R_3}{R_4} \right] V_{in}$$

$$V_0 = V_{in}$$

$$AV = 1$$

$$V_o = -\left(\frac{R_2}{R_1}\right)V_i$$

\rightarrow

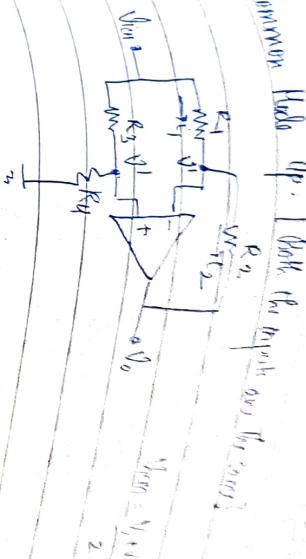

Case II $V_o = iR_4$

$$\begin{aligned} V' &= iR_4 \\ V' &= \frac{V_{CM} \times R_4}{R_3 + R_4} \end{aligned}$$

By V_s , V_o at Non-inverting Terminal,

$$i_1 = i_2$$

[$i_{in} = \infty$]

$$\frac{V_{CM} - V'}{R_1} = \frac{V' - V_o}{R_2}$$

$$i' = \frac{V_{CM} - V_{CM} R_4}{R_3 + R_4} = \frac{V_{CM}(R_3 + R_4) - V_{CM} R_4}{R_3(R_3 + R_4)}$$

[Voltage division]

$$R_1$$

$$i_1 = \frac{V_{CM}}{R_1} \left[\frac{R_3}{R_3 + R_4} \right] = i_o$$

$$V_o = V'$$

$$V' - V_o = i_2 R_2$$

$$= 0$$

$$= \frac{V_{CM} R_4 R_1 - V_{CM} \left[\frac{R_3 R_2}{R_3 + R_4} \right]}{R_1 (R_3 + R_4)}$$

$$V_o = \frac{V_{CM}}{R_1} \left[\frac{R_4 R_1 - R_3 R_2}{R_3 + R_4} \right]$$

$$R_1$$

$$V_o = \frac{V_{CM} (R_4 R_1 - R_3 R_2)}{R_1 (R_3 + R_4)}$$

$$V_o = \frac{V_{CM} R_4 \left(1 - \frac{R_2}{R_1} \right)}{R_3 + R_4} \rightarrow ②$$

$$V_o = V_{o1} + V_{o2}$$

$$V_o = -\left(\frac{R_2}{R_1} \right) V_{o1} + \frac{V_{CM} R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \right) \rightarrow ③$$

$$\frac{R_2 R_3}{R_1 R_4} = 1 \rightarrow \text{Then } ③ \text{ tends to } ②.$$

$$\frac{R_2 R_3}{R_1 R_4} \rightarrow (R_2 R_3 = K_{kl}) \rightarrow ③$$

$\frac{R_o}{R_1} = \frac{R_4}{R_3}$) condition won't be satisfied due to tolerance, thus condition won't be satisfied

Applying (5) on (7) \rightarrow for min [minimum load signal]

$$\text{Applying (5) on (7)} \rightarrow \text{for min } V_{in}$$

input impedance of diff-amp:
if $V_p = V_{in} = R_s + R_u \parallel \left(\frac{R_1(R_3+R_4)}{R_3} \right)$

i)

$$V_{in} = (R_s + R_u) \parallel \left(\frac{R_1(R_3+R_4)}{R_3} \right)$$

Applying (5) on (3)
 $V_o = -\left(\frac{R_4}{R_3}\right)V_1 + \frac{V_2 R_u}{R_3 + R_u} \left(1 + \frac{R_2}{R_1}\right)$

$$= -\left(\frac{R_4}{R_3}\right)V_1 + \frac{V_2 R_u}{R_3 + R_u} \left(1 + \frac{R_2}{R_1}\right)$$

$$= -\left(\frac{R_4}{R_3}\right)V_1 + V_2 \frac{R_u}{R_3 + R_u} \left(\frac{R_2 + R_4}{R_3}\right)$$

$$= V_2 \left(\frac{R_u}{R_3}\right) - V_1 \left(\frac{R_u}{R_3}\right)$$

$$V_o = \frac{R_u}{R_3} (V_2 - V_1)$$

$$V_o = \frac{R_u}{R_3} (V_2 - V_1) = \frac{R_u}{R_1} (V_{dH})$$

$$\text{Hence, } \frac{R_2}{R_1} = \frac{R_u}{R_3}$$

$$\frac{50k}{1k} = \frac{100k}{2k} = 50$$

$$A_{CH} = 0, \text{ CMRR} = \frac{Ad}{A_{CH}} = \infty, Ad = R_2 = 50k$$

When the conditions are not satisfied, substitute $V = V_{CH} - V_{dH}$,
 $V_d = V_{CH} + V_{dH}$ in (3)

$$\text{Hence, } A_{CH} = -R_2 + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right)$$

$$A_{dH} = \frac{1}{2} \left[\frac{R_2}{R_1} + \frac{R_4}{R_3 + R_4} \left[1 + \frac{R_2}{R_1} \right] \right]$$

$$V_d = V_2 - V_1$$

$$V_d = -V_1 + V_2$$

$$V_{CH} = \frac{V_1 + V_2}{2} \Rightarrow 2V_{CH} = V_1 + V_2$$

$$V_2 = V_{CH} + \frac{V_d}{2} ; V_1 = V_{CH} - \frac{V_d}{2}$$

$$Z_{in} = R_1 + R_2$$

(Input Impedance).


$$A_{CH} = -50.5 + 99 \left[1 + \frac{50.5}{0.99} \right] = 50.99$$

$$Ad = \frac{1}{2} \left[\frac{50.5}{0.99} + \frac{99}{101.02} \left[1 + \frac{50.5}{0.99} \right] \right] = 50.99$$

$$\text{CMRR} = \frac{|Ad|}{|A_{CH}|} = 10^{244.75}$$

$$|A_{CH}|$$

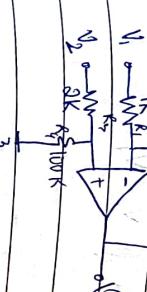for a given difference amplifier find Ad, A_{CH}, CMRR. This is done by this and other when further have to do.
Radical



Date _____
Page _____
Uttamchand

$$Q_4 = -\nabla V, \quad LTr = -W$$

15
3/24


523
Q. 1. Please explain in relation to how a gain of -100 and input voltage of 5V using an op-amp which is ideal in all respects. The gain of KDP

op-amp is required to have a gain of -10 and input impedance of $10^6 \Omega$ using an Op-amp which is ideal in all aspects except that it has a finite gain of 600.

b) In the following circuit, what would be the gain of the

the feedback voltage across the op-amp would be the modulation needed to obtain original gain with some input impedance with an ideal op-amp.


The - It is an inverting amplifier.

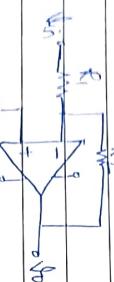

Move -N here.

$$R_2 = 2\pi \cdot 14 \text{ k}\Omega //$$
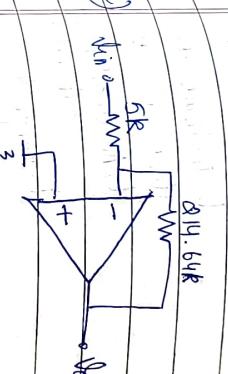
$$b) A_{CL} = \frac{4V_0}{V_{in}} = \frac{-R_2}{R_1} = \frac{-214.64k}{5k} = -42.93$$



$$R = 5k$$

$$A_{OL} = -40$$

$$-A_{OL} = \frac{-R_2}{5R} \Rightarrow R_2 = 200k\Omega \rightarrow \text{Hence the required load resistance.}$$

$$\frac{1}{\text{Dil. tuk}} = \frac{1}{R} + \frac{1}{L}$$

$$R = 2932.24 \text{ kJ/m}^3$$

Hence the new draft is


$$\begin{aligned} k &= 5R : A_{KL} = -40 \\ \Rightarrow V_0 &= A_{KL} = - \\ \text{Vis} &= \end{aligned}$$

$$\Rightarrow \frac{R_1}{\frac{R_1 + R_2 + R_3}{R_3}} = \frac{R_1}{R_3}$$

$$\frac{601 + R_2}{6k} = \frac{3R_2}{1000}$$

$$\frac{3R_3}{1600} - \frac{R_1}{5000} = R_2 \left[\frac{3}{1600} - \frac{1}{Q_{\text{crit}}} \right] = R_3 R_4$$
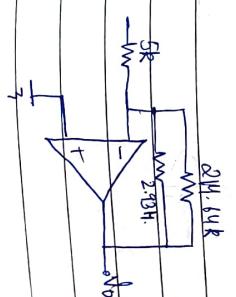
$$R_2 = \frac{601}{0.0089} = 674.6 \text{ kS}$$




Diode Rectifiers

$$\text{d/p of } A_2 = \left(-\frac{R}{R_L} \right) V_{01}$$

$$V_{02} = -(-V_{in}) = V_{in}$$

Half-Wave Rectifier Super Diode

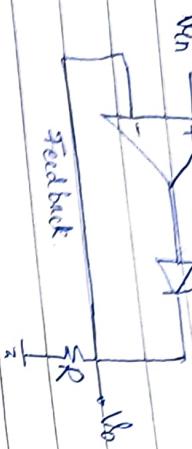

$$V_{in} < 0$$

$$\text{d/p} \rightarrow -V_R ; D_1 \text{ is off}$$

L, Feedback doesn't exist

L, acts as Comparator


L, At $V_{in} > 0$, it gets saturated.

L, Larger switching time

$$V_{02} = \left(i_1 + \frac{R}{2R} \right) V = \frac{3}{2} \left[-\frac{2}{3} V_{in} \right] = -V_{in}$$

$$\text{Hence, } V_{in} < 0 \text{, } V_{02} = -(-V_{in}) = V_{in} //$$

Full-Wave Rectifier

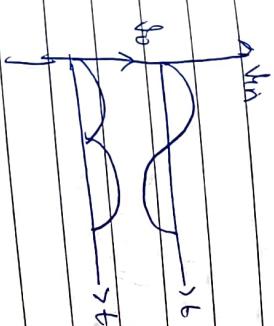

Case 1 $V_{in} > 0$



$$A_1 = -V_R$$

$$D_1 = \text{ON} \Rightarrow D_2 = \text{OFF}$$

$$V_{01} = (-R_F) V_{in} = -V_{in}$$

