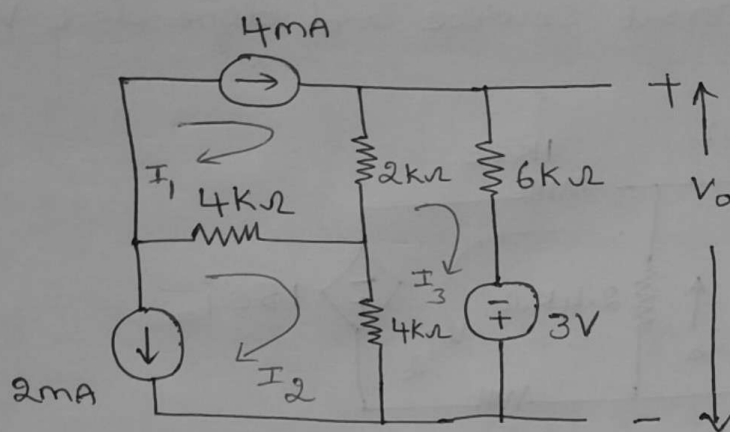


## Mesh Analysis with independent current source

2.

Ex: Find the voltage  $V_0$  in the circuit shown in Figure using mesh analysis method.



Solution:  $V_0 = 6K I_3 - 3$

Apply KVL for the mesh 3, we get

$$2K(I_3 - I_1) + 6KI_3 - 3 + 4K(I_3 - I_2) = 0$$
$$-2KI_1 - 4KI_2 + 12KI_3 = 3 \quad \text{--- (1)}$$

From mesh 1, we get

$$I_1 = 4mA \quad \text{--- (2)}$$

From mesh 2, we get,  $I_2 = -2mA$  --- (3)

substitute (2) and (3) in equ<sup>n</sup> (1)

$$-2K(4m) - 4K(-2m) + 12KI_3 = 3$$


$$I_3 = 0.25mA$$

$$V_0 = 6KI_3 - 3 = 6K(0.25m) - 3$$

$$\boxed{V_0 = -1.5V}$$

Ex: Mesh analysis using dependent source

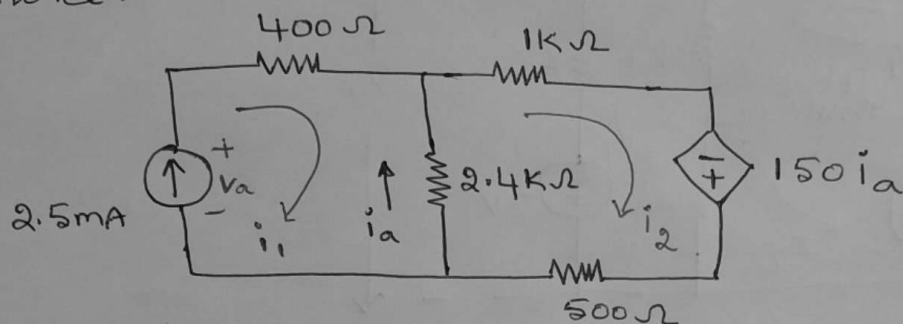using mesh analysis method to solve for  $i_a$  in the circuit. Also find the power delivered by the independent current source and dependent voltage source.



Solution:  $i_a = i_2 - i_1$  — (1)

From mesh 1  $\Rightarrow i_1 = 2.5\text{mA}$

Apply KVL to mesh 2,

$$1\text{k}i_2 - 150i_a + 500i_2 + 2.4\text{k}(i_2 - i_1) = 0 \quad \text{--- (2)}$$

From equ<sup>n</sup> (1)  $i_2 = i_a + i_1 = i_a + 2.5\text{mA}$  — (3)

Sub equ<sup>n</sup> (3) in equ<sup>n</sup> (2)

$$1\text{k}(i_a + 2.5\text{mA}) - 150i_a + 500(i_a + 2.5\text{mA}) + 2.4\text{k}(i_a + 2.5\text{mA} - 2.5\text{mA}) = 0$$

$$1\text{k}i_a + 2.5 - 150i_a + 500i_a + 500 \times 2.5\text{m} + 2.4\text{k}i_a = 0$$

$$i_a = -1.0\text{mA}$$

$$i_2 = -1\text{m} + 2.5\text{m} = 1.5\text{mA}$$

Apply KVL to mesh 1

$$400i_1 + 2.4\text{k}(i_1 - i_2) - V_a = 0$$


$$V_a = 3.4\text{V}$$

Power independent source  $= VI = V_a i_1 = (3.4)(2.5\text{m}) = 8.5\text{mW}$

Power dependent source  $= VI = 150i_a i_2 = (150)(-1\text{m})(1.5\text{m}) = -0.225\text{mW}$

Ex: Mesh analysis using AC source.

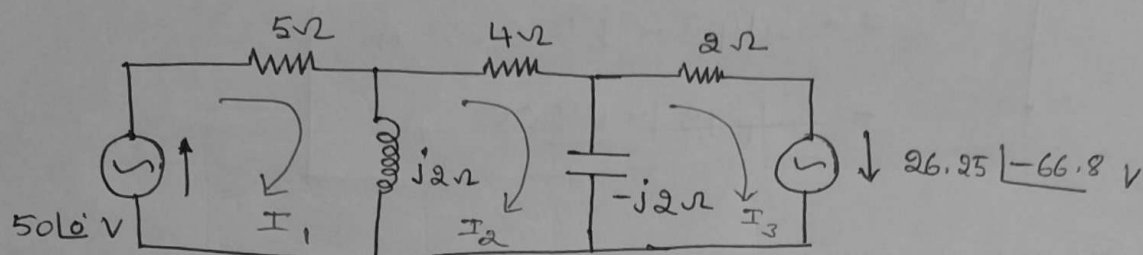Find the current through  $4\Omega$  resistor by using loop current method as shown in network.



Solution: Current through  $4\Omega$  resistor is  $I_2$

$$\begin{bmatrix} (5+j2) & -j2 & 0 \\ -j2 & 4 & j2 \\ 0 & j2 & (2-j2) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50\angle 0^\circ \\ 0 \\ 26.25\angle -66.8^\circ \end{bmatrix}$$

$$\Delta = \begin{vmatrix} (5+j2) & -j2 & 0 \\ -j2 & 4 & j2 \\ 0 & j2 & (2-j2) \end{vmatrix}$$

In calculator  
write  
2j

$$\Delta = (5+j2) \{ 4(2-j2) + 4 \} + j2 \{ -j2(2-j2) \}$$

$$\Delta = 76 - 16j + 8 - 8j$$

$$\Delta = 84 - j24$$

$$\Delta_2 = \begin{vmatrix} (5+j2) & 50\angle 0^\circ & 0 \\ -j2 & 0 & j2 \\ 0 & 26.25\angle -66.8^\circ & (2-j2) \end{vmatrix}$$

$$26.25\angle -66.8^\circ = 10.34 - j24.12$$

$$\Delta_2 = (5+j2) \{ -j2(26.25\angle -66.8^\circ) \} - 50\angle 0^\circ \{ -j2(2-j2) \}$$

$$\Delta_2 = -199.84 - 199.88j - 200 - 200j$$

$$\Delta_2 = -399.84 - 399.88j$$


$$\therefore I_2 = \frac{\Delta_2}{\Delta} = \frac{-399.84 - 399.88j}{84 - j24}$$

$$\boxed{I_2 = -3.143 - j5.658 \text{ A}} \\ \boxed{= 6.472 \angle -119.05^\circ \text{ A}}$$

### Supermesh


- (\*) When a current source is common to two meshes, involves the concept of a supermesh.
- (\*) Supermesh is created from two meshes that have a current source as a common element.
- (\*) Thus reduce the number of meshes by one for each current source present.

Ex:

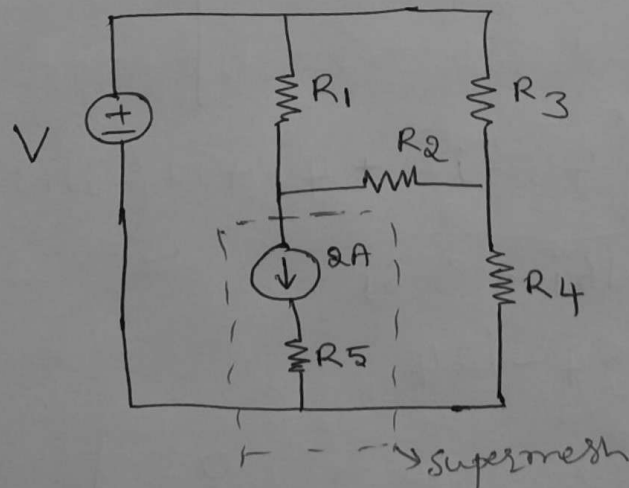
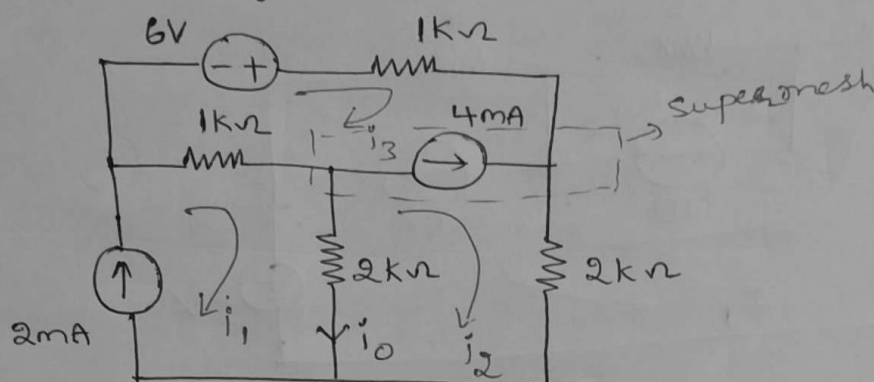
# Example 9 Supermesh

Ex: Find the current  $i_o$  in the circuit shown in Figure using mesh analysis.




\* Step 1: Specify the mesh currents.

\* Step 2: Write supermesh constrained equation by the current source

$$\text{i.e., } i_2 - i_3 = 4\text{mA} \quad (1)$$

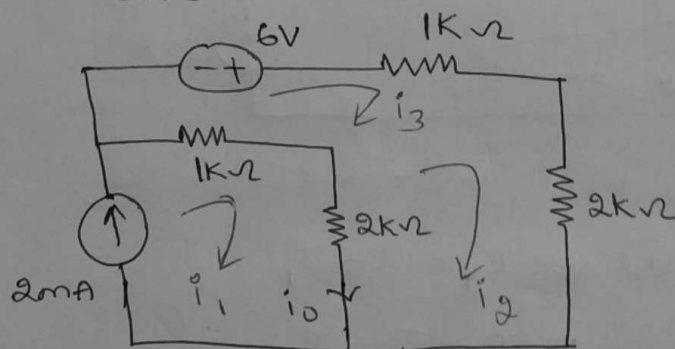\* Remove the current source and redraw the circuit.



Apply KVL to mesh 1,  $i_1 = 2\text{mA}$

Apply KVL to mesh 2 and 3 together,

$$-6 + 1k i_3 + 2k i_2 + 2k(i_2 - i_1) + 1k(i_3 - i_1) = 0$$


Substituting  $i_1 = 2\text{mA}$ ,  $i_3 = i_2 - 4\text{mA} \rightarrow$  From equ (1)

solving  $i_2 = 10/3 \text{mA} = 3.33\text{mA}$

$$i_o = i_1 - i_2 = 2\text{mA} - 3.33\text{mA} = -1.33\text{mA}$$

$$\boxed{i_o = -1.33\text{mA}}$$

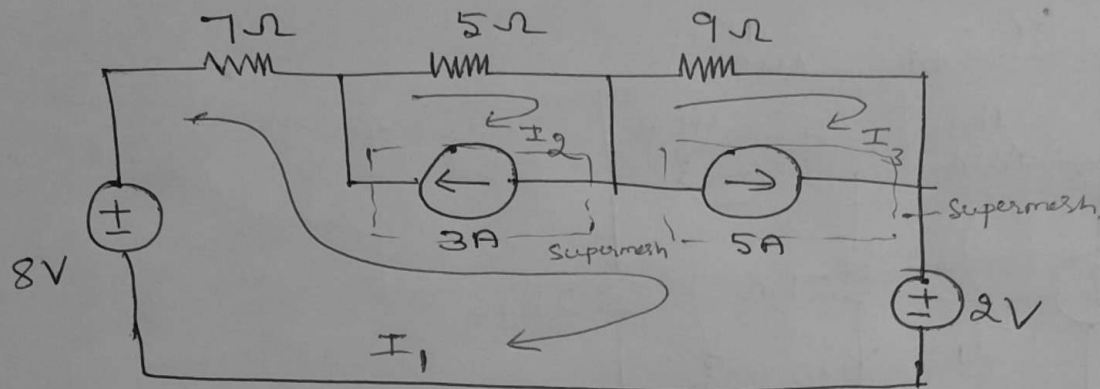Ex: using mesh analysis, calculate the current  $I_1$  shown in the figure.




Solution: Supermesh constrained equations.

$$I_2 - I_1 = 3 \quad \text{--- (1)}$$

$$I_1 - I_3 = 5 \quad \text{--- (2)}$$

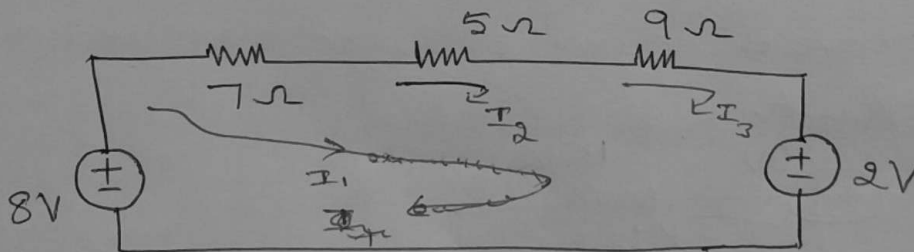Remove the current source, redraw the circuit



$$7I_1 + 5I_2 + 9I_3 + 2 - 8 = 0 \quad \text{--- (3)}$$

From equ<sup>n</sup> (1)  $\Rightarrow I_2 = 3 + I_1$

From equ<sup>n</sup> (2)  $\Rightarrow I_1 - 5 = I_3$

Substituting in equ<sup>n</sup> (3)

$$7I_1 + 5(3 + I_1) + 9(I_1 - 5) = 6$$

$$7I_1 + 15 + 5I_1 + 9I_1 - 45 = 6$$

$$21I_1 = 36$$

$$I_1 = \frac{36}{21} = 1.7142 \text{ A}$$