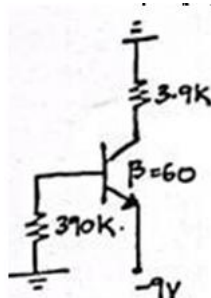
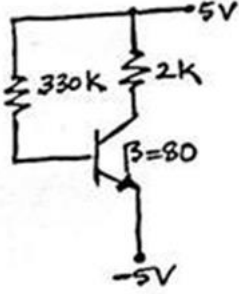
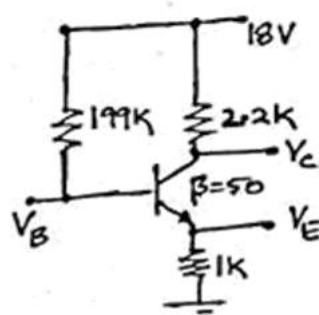






Basics Electronics (22EC13)

Tutorial-1

1	a.A silicon transistor has its $I_{co}=6nA$ and $\alpha=0.98$. If $I_B=0$ and $V_{CE}=4V$ then $I_C = \underline{\hspace{2cm}}$. b.An NPN transistor has $I_{co}=30nA$, $I_B=0$, $V_{CE}=4V$ and $I_C=30uA$. The value of $\beta = \underline{\hspace{2cm}}$.																								
2	<p>The measured terminal voltages (in Volts) of different NPN transistors are given in Table-1. For each of the transistors, find V_{BE}, V_{CB} and identify the region of operation.</p> <table><tr><td></td><td>V_E</td><td>V_B</td><td>V_C</td></tr><tr><td>Q1</td><td>0</td><td>0.7</td><td>0.7</td></tr><tr><td>Q2</td><td>0</td><td>0.8</td><td>0.1</td></tr><tr><td>Q3</td><td>-2.7</td><td>-2.0</td><td>0</td></tr><tr><td>Q4</td><td>0</td><td>0</td><td>0.3</td></tr><tr><td>Q5</td><td>0.7</td><td>0.7</td><td>0</td></tr></table> <p style="text-align: center;">Table-1</p>		V_E	V_B	V_C	Q1	0	0.7	0.7	Q2	0	0.8	0.1	Q3	-2.7	-2.0	0	Q4	0	0	0.3	Q5	0.7	0.7	0
	V_E	V_B	V_C																						
Q1	0	0.7	0.7																						
Q2	0	0.8	0.1																						
Q3	-2.7	-2.0	0																						
Q4	0	0	0.3																						
Q5	0.7	0.7	0																						
3	a. Find the values of β that correspond to α value of 0.5, 0.8, 0.96, 0.98 and 0.996. b. Find the values of α that correspond to β value of 40, 60, 80, 99, 149 and 249.																								
4	<div><div></div><div></div></div> <p style="text-align: center;">Fig 1Fig 2</p> <p>In the fixed base current biasing circuits of fig 1 and 2.Determine the operating point of the silicon transistor.</p>																								
5	<p>In the circuit of fig 3, determine V_C, V_E, V_B and I_C.</p> <div></div> <p style="text-align: center;">Fig 3</p>																								
6	<p>In the circuit of fig 4, find V_E, I_E, I_B, I_C and V_C.</p>																								



Basics Electronics (22EC13)

Tutorial-1

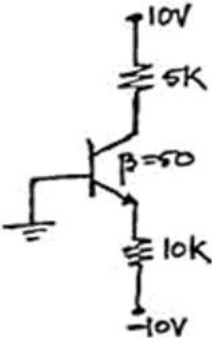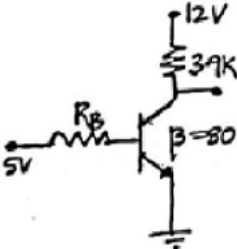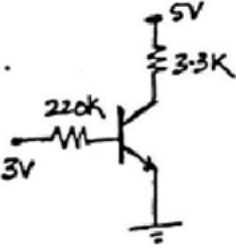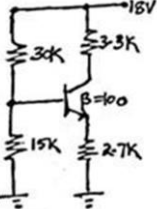	 <p>Fig 4</p>
7	<p>In the inverter circuit of fig 5, determine the maximum value of R_B, so that the circuit could be used as an inverter.</p>  <p>Fig 5</p>
8	<p>In the inverter circuit of fig 6, determine the minimum value of β, so that the circuit could be used as an inverter.</p>  <p>Fig 6</p>
9	<p>Determine the operating point of silicon transistor in the voltage divider biasing circuit fig 7. Also determine $S_{(ICQ)}$.</p>  <p>Fig 7</p>
10	<p>In an RC coupled CE amplifier, $R_1 = 50K\Omega$, $R_2 = 25K\Omega$, $R_C = R_L = 2K\Omega$, $\beta = 99$ and $I_E = 2mA$. Determine the voltage gain, input impedance and output impedance of the amplifier.</p>

Basics Electronics (22EC13)

Tutorial-1

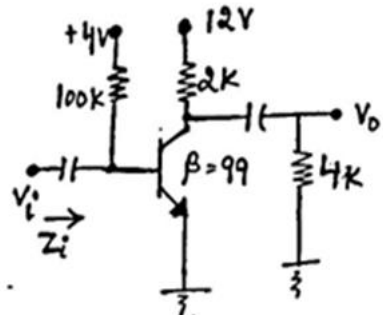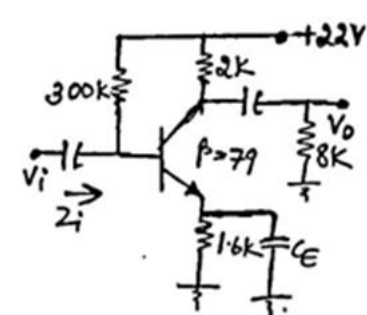11	<p>a) Three amplifiers of voltage gains 20dB, 26dB and 32dB are cascaded to obtain an output voltage of 2V. Calculate the input voltage needed.</p> <p>b) An amplifier having a power gain of 17dB delivers a power output of 40W to a load of 1KΩ. Calculate i) the input power needed and (ii) the input voltage needed, if the voltage gain of the amplifier is 38dB.</p>
12	<p>Calculate the voltage gain v_o/v_i, input impedance Z_i and output impedance Z_o for the circuits of fig 8 and 9</p> <div style="display: flex; justify-content: space-around; align-items: flex-end;"> <div style="text-align: center;">  <p>Fig 8</p> </div> <div style="text-align: center;">  <p>Fig 9</p> </div> </div>