



RV Educational Institutions[®]
RV College of Engineering[®]

Autonomous
 Institution Affiliated
 to Visvesvaraya
 Technological
 University, Belagavi






Approved by AICTE,
 New Delhi

Go, change the world

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

www.rvce.edu.in; hod.ec@rvce.edu.in; (O) 080 - 6818 8178

Tutorial 1B: Theorems

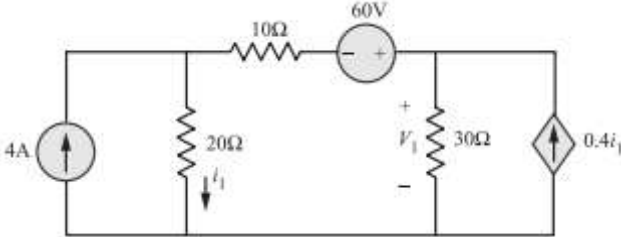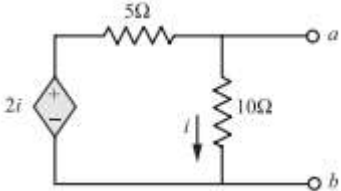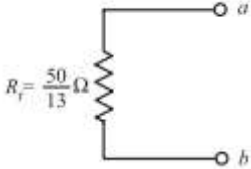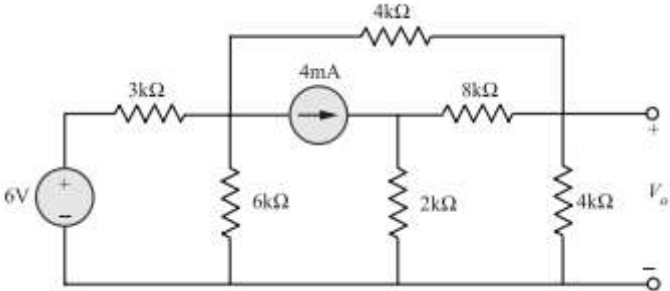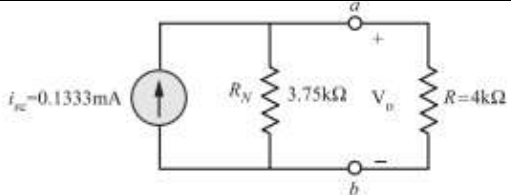Sl. No.	Problems	Ans
1	Find the voltage V_1 using the superposition principle. Refer the circuit shown in Fig. 	$22.5 + 60 = 82.5$
2	Find the Thevenin equivalent circuit as seen from the terminals a-b. Refer the circuit diagram shown in Fig. 	
3	Find V_o in the circuit of Fig. 	
4	Find the value of R_L for maximum power transfer. Also find the maximum power transferred to R_L	$2K\Omega, 12.5mW$



RV Educational Institutions[®]
RV College of Engineering[®]

Autonomous
 Institution Affiliated
 to Visvesvaraya
 Technological
 University, Belagavi


Approved by AICTE,
 New Delhi

Go, change the world

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

www.rvce.edu.in; hod.ec@rvce.edu.in; (O) 080 - 6818 8178

5	<p>Find the Thevenin and Norton equivalent circuits for the circuit shown in Fig.</p>	$V_t = 158.11 \angle 108.43^\circ$ $I_N = \frac{V_t}{Z_t} = \frac{158.11 \angle 108.43^\circ}{150 \angle 90^\circ} = 1.054 \angle 18.43^\circ \text{ A}$ $Z_N = Z_t = j150 \Omega$
6	<p>For the circuit, (a) what is the value of Z_L that will absorb the maximum average power? (b) what is the value of maximum power?</p>	$V_t = 107.33 \angle 116.57^\circ \text{ V}$ $Z_t = 8 - j14 \Omega$ $Z_L = 8 + j14 \Omega$ <p>180 Watts</p>
7	<p>Refer the circuit shown in Fig. Find current through the ammeter, and hence verify reciprocity theorem</p>	0.8 A

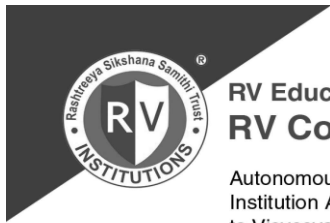

RV Educational Institutions[®]
RV College of Engineering[®]




Autonomous
 Institution Affiliated
 to Visvesvaraya
 Technological
 University, Belagavi

Approved by AICTE,
 New Delhi

Go, change the world

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

www.rvce.edu.in; hod.ec@rvce.edu.in; (O) 080 - 6818 8178

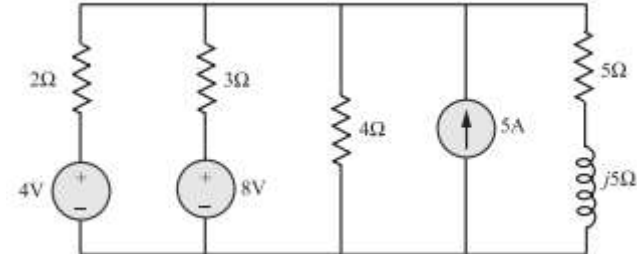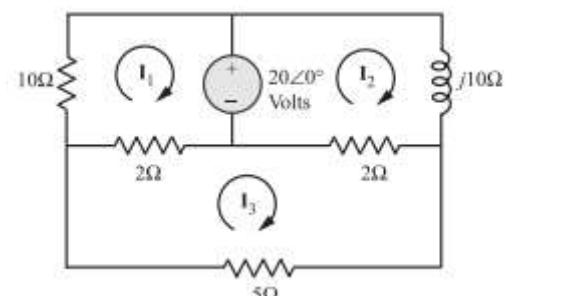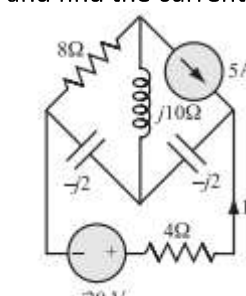8	<p>Refer the circuit shown in Fig. Use Millman's theorem to find the current through $(5+5j) \Omega$ impedance</p> 	<p>8.9231V, 0.9231Ω, $1.15 / -40.2^\circ$ A</p>
9	<p>Find current through 5 ohm resistor shown in Fig. and hence verify reciprocity theorem.</p> 	<p>$0.5376 / -126.25^\circ$ A</p>
10	<p>For the network shown in Fig., apply superposition theorem and find the current I</p> 	<p>$6.1121 / 144.78^\circ$ A</p>