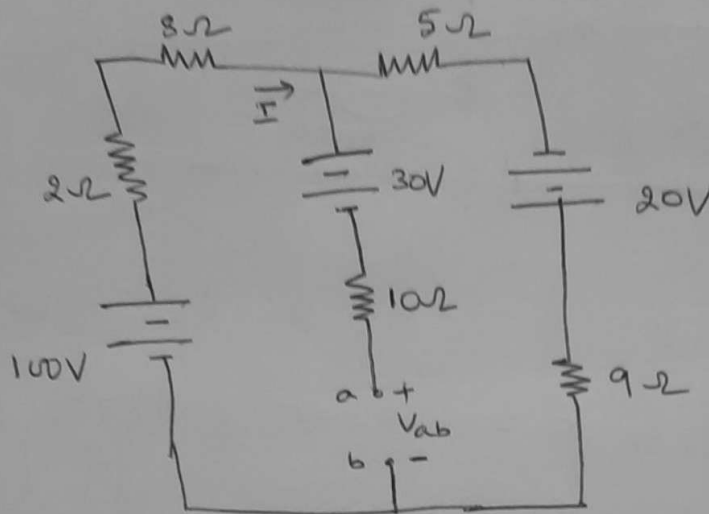


Tutorials


#1

Ex Calculate I and V_{ab} in the circuit of Fig




Ans: $I = 5A$, $V_{ab} = 20V$

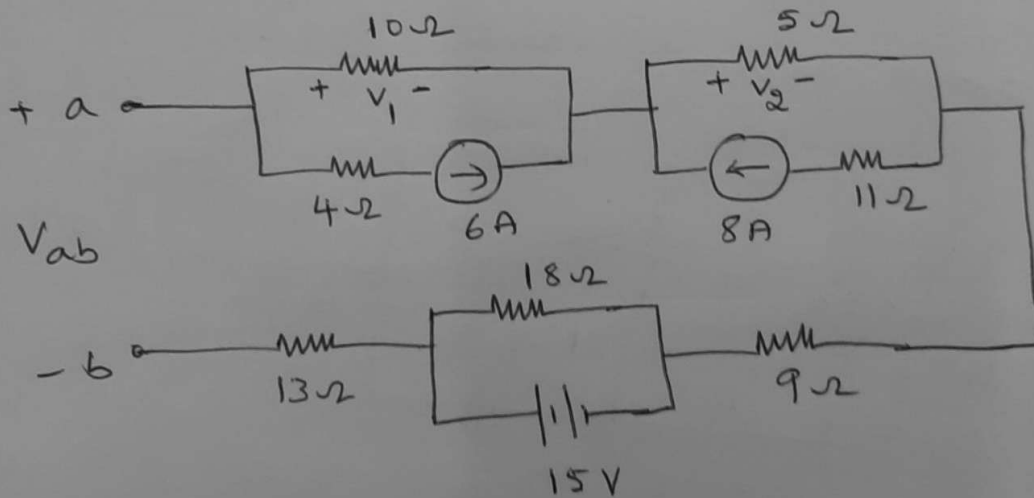Ex: Determine the voltage drop V_{ab} across the open circuit in the circuit shown in Fig.




Solution: $V_1 = -60V$, $V_2 = 40V$
 $V_{ab} = -35V$

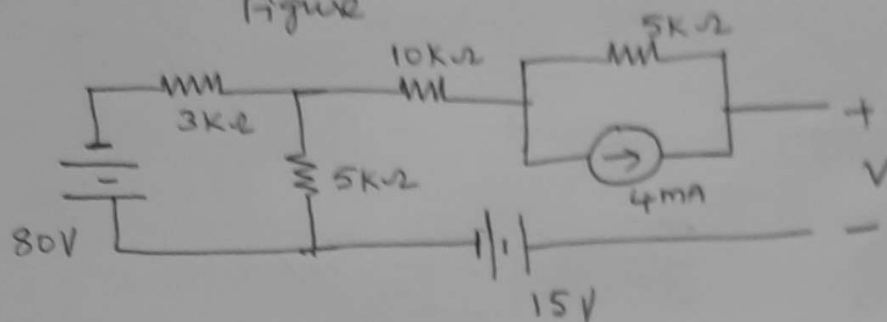Ex: Find V across the open circuit in the circuit of Figure




Ans: $V = -45V$

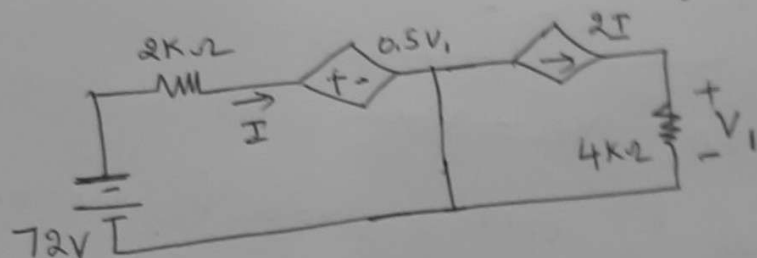Ex: Calculate V_1 in the circuit of Figure




Ans: $V_1 = 96V$

Ex: obtain the mesh currents

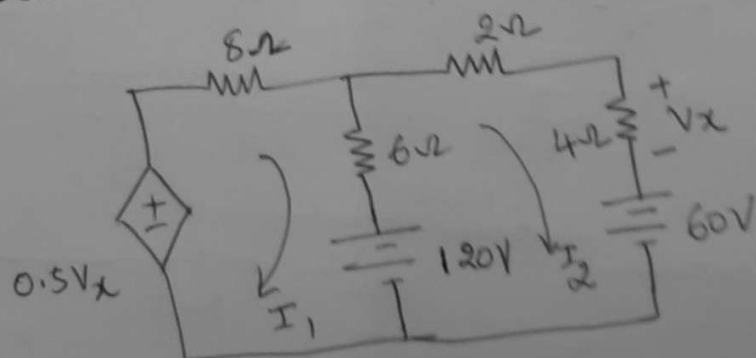


Ans: $I_1 = -8A$, $I_2 = 1A$

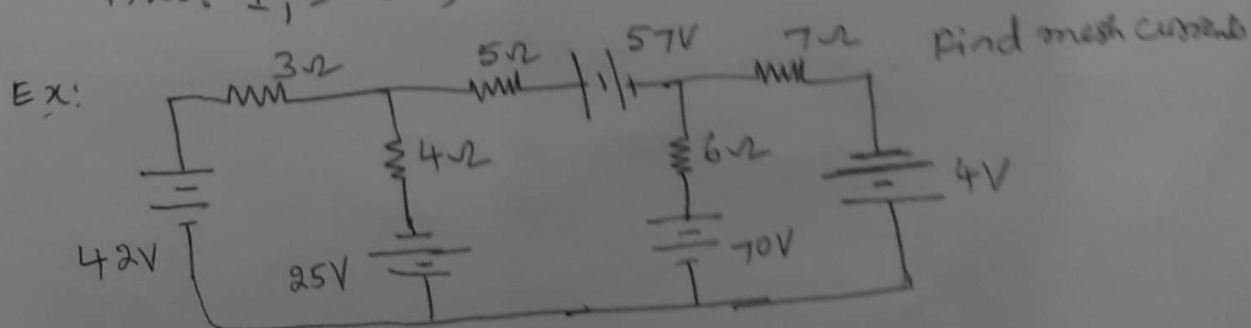

Ans: $I_1 = 5A$, $I_2 = -8A$, $I_3 = 2A$


Ex: Find the mesh currents shown in Figure

*2

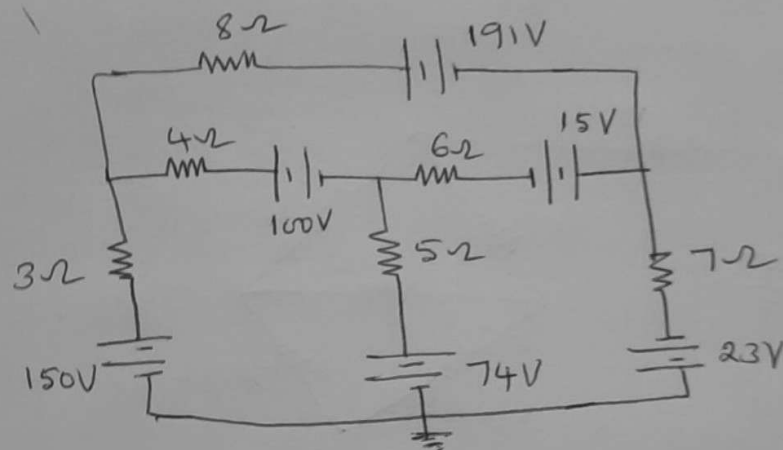

Solution: $I_1 = -2A$, $I_2 = 4A$, $I_3 = -5A$

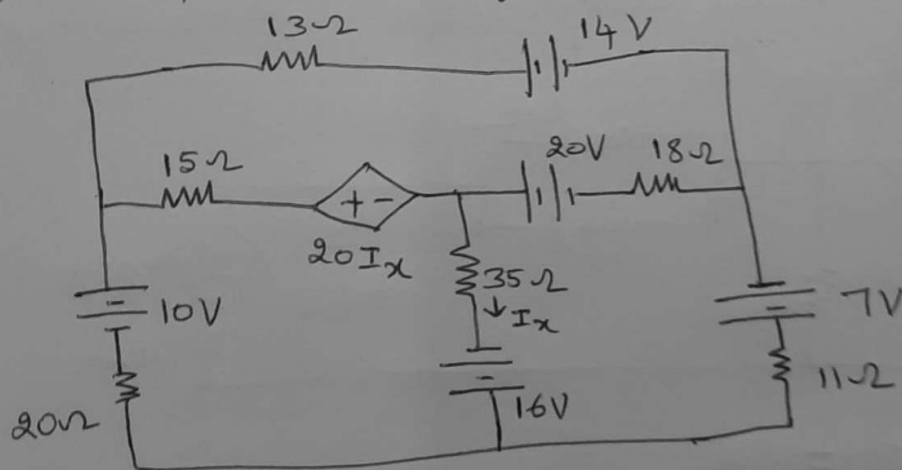
Ex: Use mesh analysis determine the power absorbed by the dependent voltage source in the circuit.



Solution: $I_1 = 0.148A$, $I_2 = -0.3A$, $I_3 = 0.256A$


$P = -0.968W$

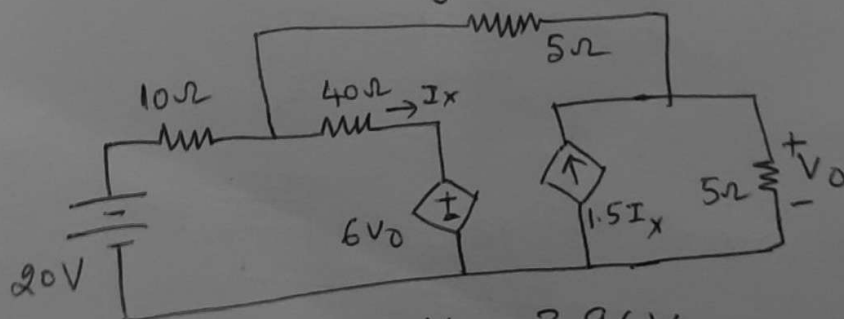Ex: Use mesh analysis in finding V_0 in the circuit shown




Ans: $V_0 = 3.96V$

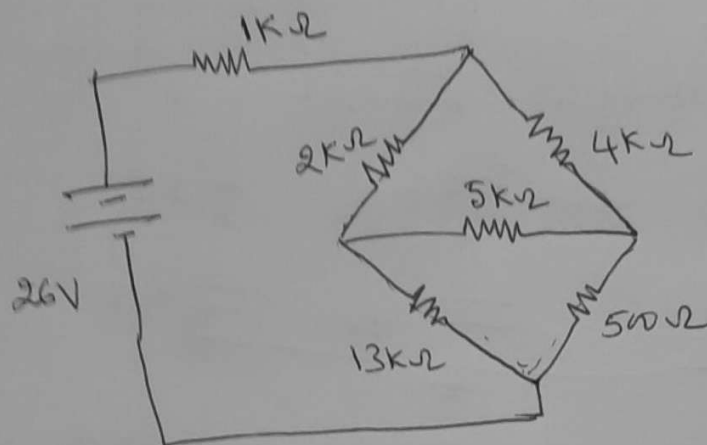Ex: use loop analysis to find the current flowing to through $5K\Omega$ resistor in the circuit shown in fig




Ans: $I = 2mA$

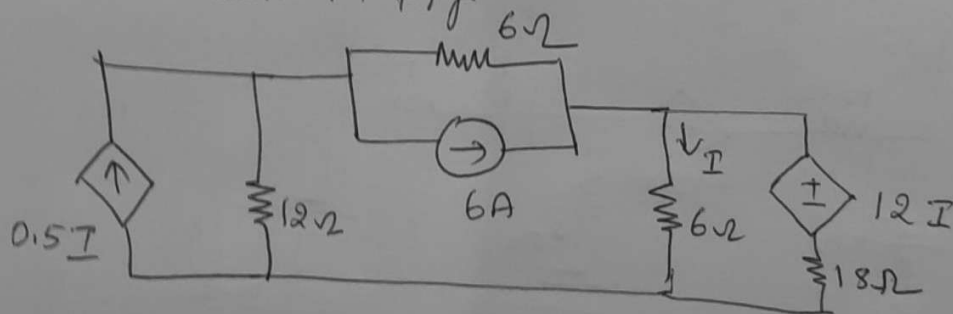Ex: use nodal analysis find I in the circuit shown in fig



Ans: $I = 3A$

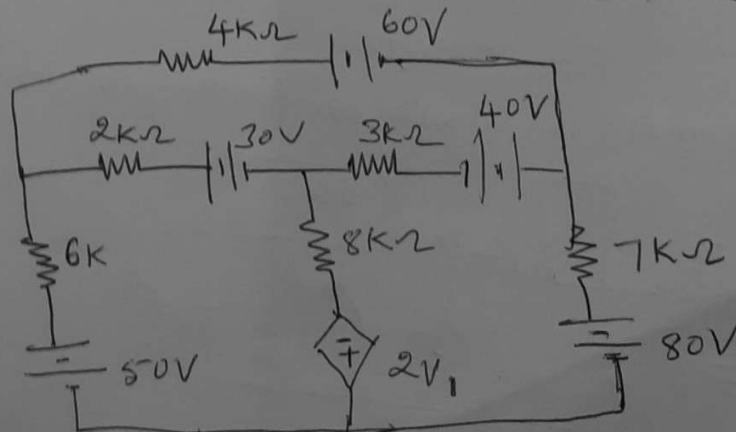
Ex: obtain the mesh currents in the circuit shown in fig



Ans: $I_1 = -0.879mA$, $I_2 = -6.34mA$, $I_3 = -10.1mA$


AC source problems

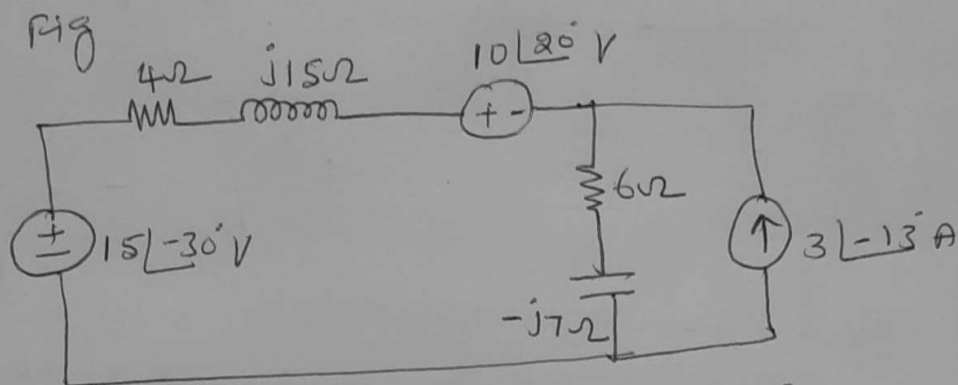Ex: Find the mesh currents for the circuit shown in Fig




Ans: $I_1 = 1.28 \angle 85.5^\circ \text{ A}$, $I_2 = -3 \angle -13^\circ$

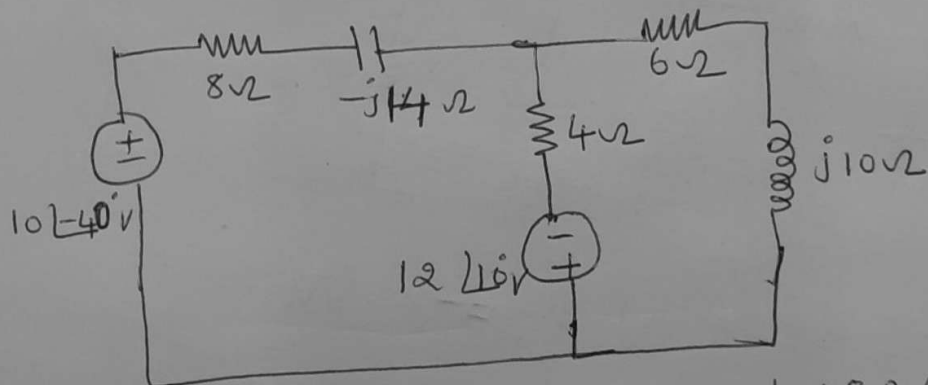Ex: Solve mesh currents for the circuit shown in Fig




Ans: $I_1 = 0.97 \angle 41.5^\circ \text{ A}$, $I_2 = -0.63 \angle -48.2^\circ \text{ A}$

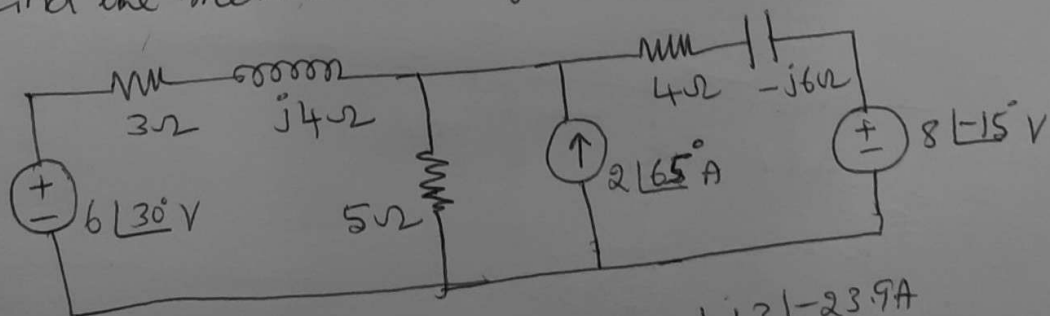Ex: Find the mesh currents for the circuit shown in Fig



Ans: $I_1 = -0.63 \angle 15.6^\circ \text{ A}$, $I_2 = -1.13 \angle -23.9^\circ$
 $I_3 = -2.31 \angle 35.9^\circ \text{ A}$

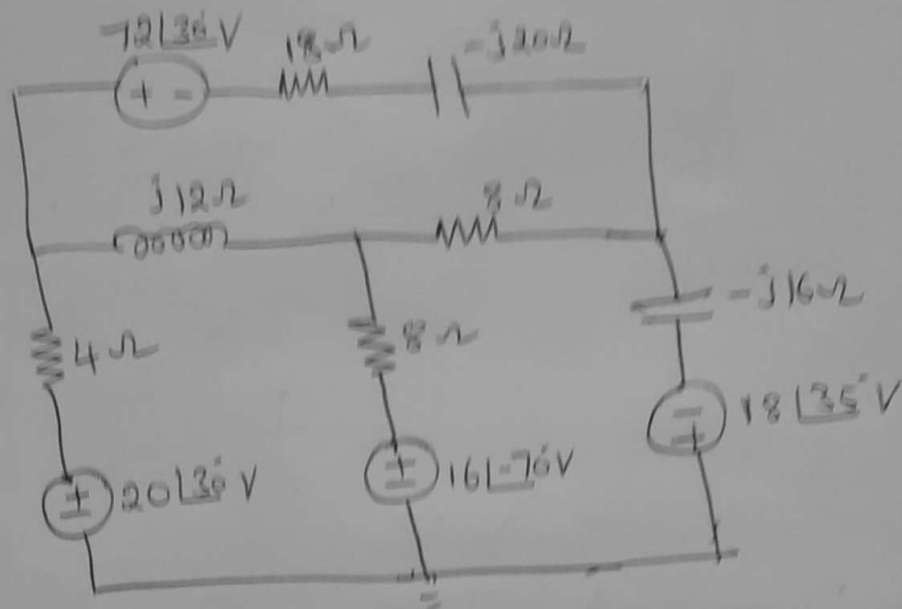Ex: Use mesh analysis to solve for the currents i_1 and i_2 in the circuit shown in Fig.




Ans: $I_1 = 2.07 \angle -26.6^\circ \text{ A}$, $I_2 = 1.38 \angle 7.36^\circ \text{ A}$
 $I_3 = 1.53 \angle -14.6^\circ \text{ A}$

Ex: Show a circuit that corresponds to the following mesh equations.


$$(17 - j4)I_1 - (11 + j5)I_2 = 6 \angle 30^\circ$$

$$-(11 + j5)I_1 + (18 + j7)I_2 = -8 \angle 30^\circ$$

Ans.

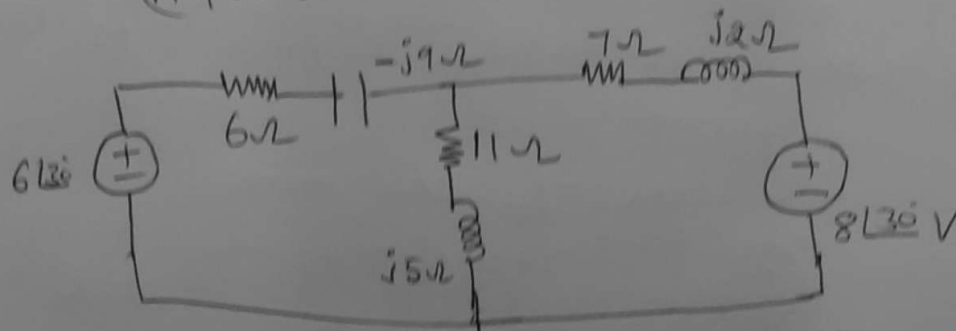


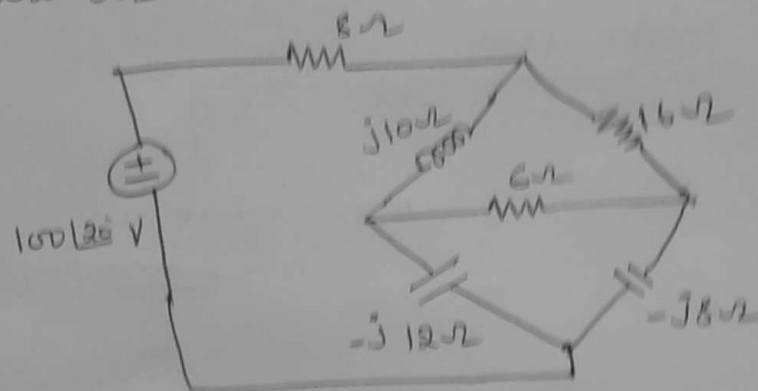Ex: use loop analysis to solve for the current flowing thro' 6Ω resistor in the ckt




Ans: $I = 3.62 \angle -45.8^\circ \text{ A}$

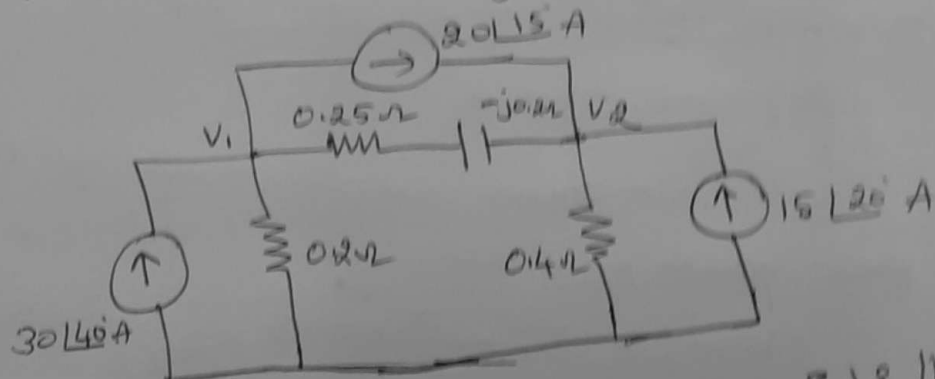Ex: Find the node voltages in the circuit shown in fig



Ans: $V_1 = 5.13 \angle 47.3^\circ \text{ V}$ and $V_2 = 8.18 \angle 15.7^\circ \text{ V}$


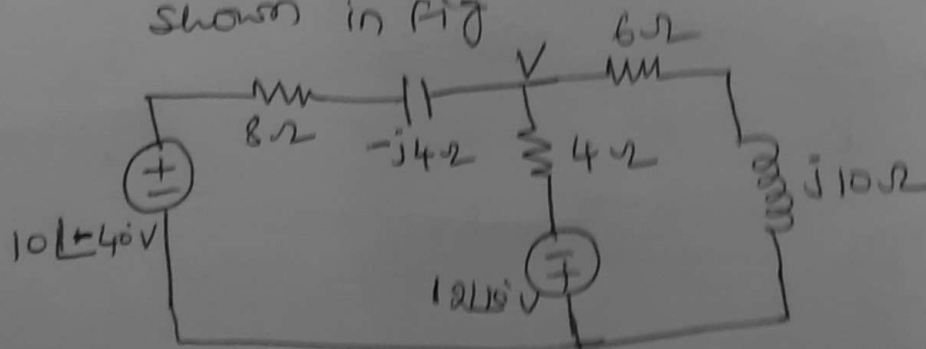
Ex: use nodal analysis to find V for the circuit shown in fig



Ans: $V = -7.35 \angle 10.8^\circ \text{ V}$

Ex.

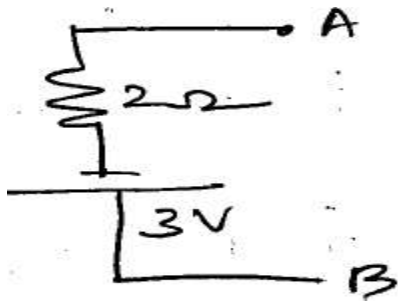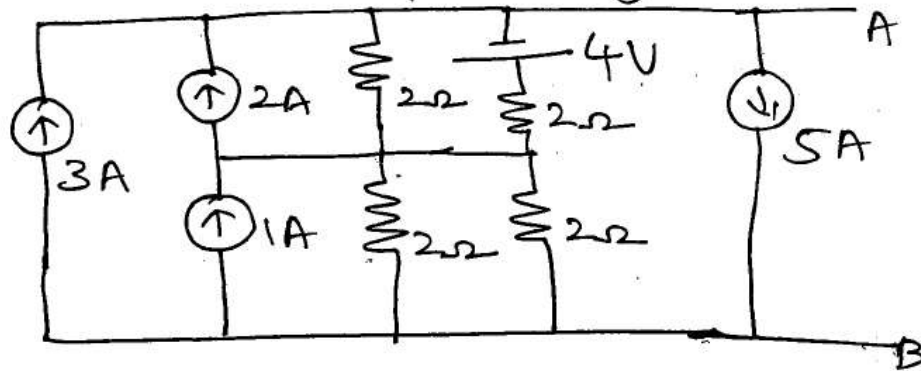
using source transformation technique
reduce it in to a single source network



Ans:

Ex.

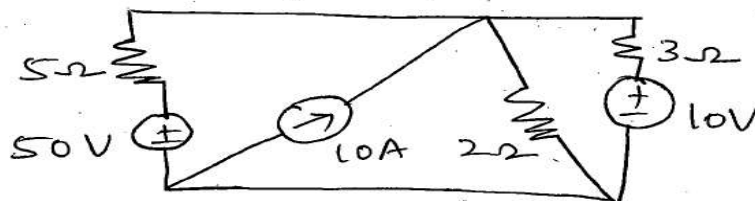
using source transformation technique
find the power delivered by 50V source
for the figure shown.



Ans: $P = 274.19 \text{ W}$

Ex.

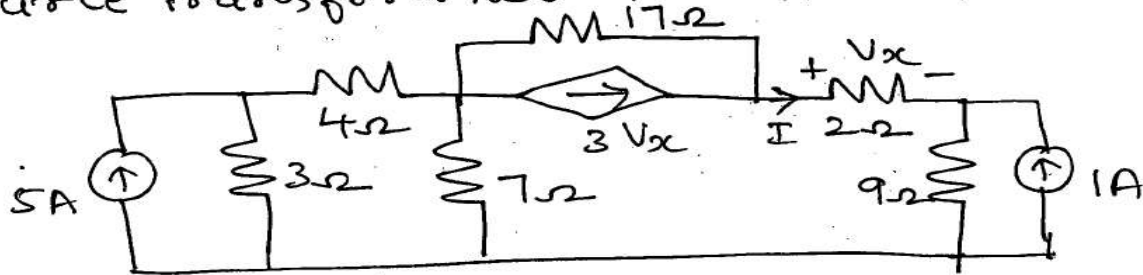calculate the current through 2Ω resistor for the circuit shown using source transformation




Ans:



Ex.

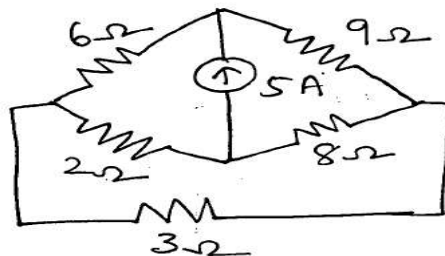Reduce the network shown into a single source network using source shifting technique




Ans:



Ex.

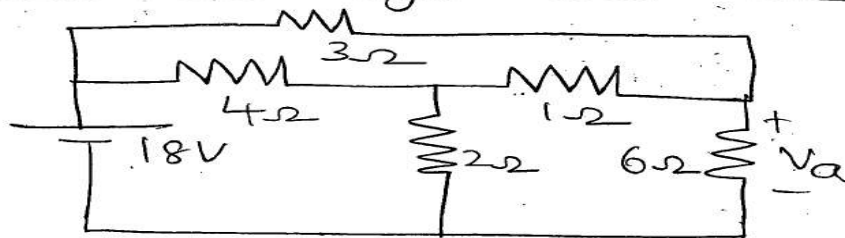Calculate the voltage across 6Ω resistor using source shifting technique



Ans:

$$V_a = 9.23V$$