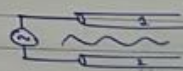


Transmission lines


- 2 conducting system with finite gap.
- Source is applied b/w 2 conduct.




2 wire Tx line.




Coaxial Tx line.

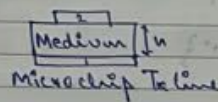

Microstrip Tx line

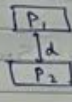


Planar or Parallel plate Tx line.

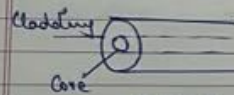

Optical fibre


Equivalent Circuit

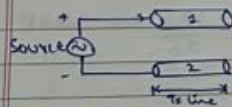

- Due to current through Tx line,
 - mag field is produced
 - " flux is produced. $\rightarrow$ flux linkage
 - represented by inductance $\text{---} \mu\text{H}$
- Conductors are not perfect.
 - Ohmic losses.
 - represented by resistance $\text{---} \text{m}\Omega$

- Conductors separated by medium
 - dielectric losses
 - represented by conductance (G)

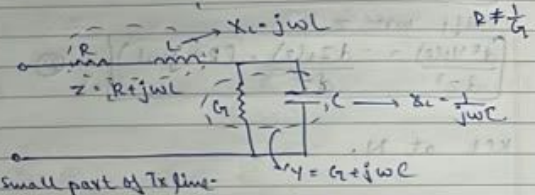- Conductors separated by distance
 - dielectric is paral.
 - capacitance $\text{---} \mu\text{F}$



Primary Constants: R, L, G, C .


Transmission line Equation

Considering small length,

Δz = small length

R = res. per unit length

L = inductance per unit length

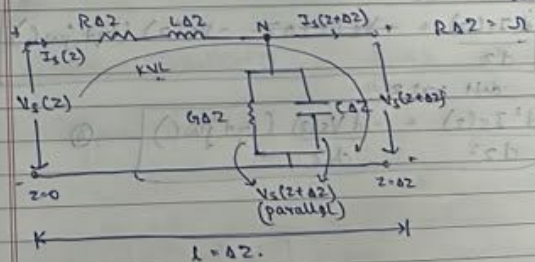

$$V_s(z) = I_s(z)RAZ + I_s(z)j\omega LAZ + V_s(z+\Delta z)$$

$$V_s(z+\Delta z) - V_s(z) = -I_s(z)\Delta z(R+j\omega L)$$

$$\lim_{\Delta z \rightarrow 0} \frac{V_s(z+\Delta z) - V_s(z)}{\Delta z} = \lim_{\Delta z \rightarrow 0} -I_s(z)(R+j\omega L)$$

$$\frac{dV_s(z)}{dz} = -I_s(z)(R+j\omega L) \quad (1)$$

$$\text{diff wrt } z$$

$$\frac{d^2 V_s(z)}{dz^2} = -\frac{dI_s(z)}{dz}(R+j\omega L) \quad (2)$$

KCL at N,

$$I_s(z) = I_s(z+\Delta z) + V_s(z+\Delta z)G\Delta z + V_s(z+\Delta z)$$

$$I_s(z) = I_s(z+\Delta z) + V_s(z+\Delta z)G\Delta z + V_s(z+\Delta z)G\Delta z j\omega C$$

$$-V_s(z+\Delta z)G\Delta z - V_s(z+\Delta z)G\Delta z j\omega C = I_s(z+\Delta z) - I_s(z)$$

$$I_s(z+\Delta z) - I_s(z) = -V_s(z+\Delta z)\Delta z(G+j\omega C)$$

$$\lim_{\Delta z \rightarrow 0} \frac{I_s(z+\Delta z) - I_s(z)}{\Delta z} = \lim_{\Delta z \rightarrow 0} -V_s(z+\Delta z)(G+j\omega C)$$

$$\frac{dI_s(z)}{dz} = -V_s(z)(G+j\omega C) \quad (3)$$

$$\text{diff wrt } z$$

$$\frac{d^2 I_s(z)}{dz^2} = -\frac{dV_s(z)}{dz}(G+j\omega C) \quad (4)$$

in (2),

$$\frac{d^2 V_s(z)}{dz^2} = +V_s(z)(G+j\omega C)(R+j\omega L)$$

$$\frac{d^2 V_s(z)}{dz^2} = -\underbrace{(G+j\omega C)(R+j\omega L)}_{\gamma^2} V_s(z) = 0$$

$$\frac{d^2 V_s(z)}{dz^2} - \gamma^2 V_s(z) = 0 \quad \text{Tx line eqn. (Voltage wave)}$$

$$\gamma = \sqrt{R+j\omega L} \sqrt{G+j\omega C} \quad \gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

Propagation constant.

in (4), in (3),

$$\frac{d^2 I_s(z)}{dz^2} = +I_s(z)(R+j\omega L)(G+j\omega C)$$

$$\frac{d^2 I_s(z)}{dz^2} - \gamma^2 I_s(z) = 0$$

$$\frac{d^2 I_s(z)}{dz^2} - \gamma^2 I_s(z) = 0 \quad \text{Tx line eqn. (Current wave)}$$

Solution of Equation

$$\frac{d^2 V_s(z)}{dz^2} - \gamma^2 V_s(z) = 0 \quad \frac{d}{dz} \rightarrow \lambda \quad \frac{d^2}{dz^2} \rightarrow \lambda^2$$

$$(\lambda^2 - \gamma^2) V_s(z) = 0$$

$$\lambda^2 - \gamma^2 = 0$$

$$\lambda^2 = \gamma^2$$

$$\lambda = \pm \gamma$$

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

Forward travelling vltg (+z axis).

m_1, m_2 roots

$$y(t) = C_1 e^{m_1 t} + C_2 e^{m_2 t}$$

* Imp mismatch (constant)

Reverse travelling vltg. (-z axis)

load

$$d^2 I_2(z) - \gamma^2 I_2(z) = 0$$

$$(D^2 - \gamma^2) I_2(z) = 0$$


$$D^2 = \gamma^2$$

$$D = \pm \gamma$$

$$I_2(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

Characteristic Impedance (Z_0)

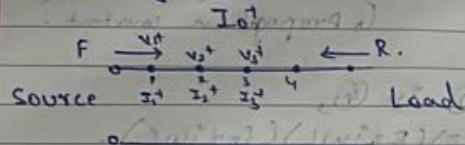ratio of $\frac{V_0^+}{I_0^+} = Z_0$ (ohm).



$$Z_0 = \frac{V_1^+}{I_1^+} = \frac{V_2^+}{I_2^+} = \frac{V_3^+}{I_3^+}$$

$V = \text{exponential decay}$

$$Z_0 = \frac{V_0^+}{I_0^+} = - \frac{V_0^-}{I_0^-}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Lossless Tx line

Condition: $R=0, G=0$.

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\alpha + j\beta = \sqrt{(j\omega L)(j\omega C)} = j\omega\sqrt{LC}$$

Comparing,
 $\alpha = 0$; $\beta = \omega\sqrt{LC}$
 attenuation constant phase constant.

Phase velocity, $V_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$

Characteristic Imp, $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \Rightarrow Z_0 = \sqrt{\frac{L}{C}}$

$$\beta Z_0 = \omega\sqrt{LC} \cdot \sqrt{\frac{L}{C}}$$

$$\beta Z_0 = \omega L$$

$$L = \frac{\beta Z_0}{\omega}$$

$$\beta \times V_p = \omega\sqrt{LC} \times \frac{1}{\sqrt{LC}}$$

$$\beta V_p = \omega$$

$$\frac{\beta}{Z_0} = \omega\sqrt{LC} \times \sqrt{\frac{C}{L}}$$

$$C = \frac{\beta \omega}{Z_0 \omega}$$

Distortionless Tx line

signals with diff
freqs reach load
at same time.

Condition: $\boxed{\frac{R}{L} = \frac{G}{C}}$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\alpha + j\beta = \sqrt{RG(1 + j\omega L/R)(1 + j\omega C/G)}$$

use $\frac{C}{G} = \frac{L}{R}$

$$\begin{aligned} \alpha + j\beta &= \sqrt{RG(1 + j\omega L/R)^2} = \sqrt{RG} \times (1 + j\omega L/R) \\ &= \sqrt{RG} + j\omega \frac{L}{R} \sqrt{RG} = \sqrt{RG} + j\omega \sqrt{RG \times \frac{L^2}{R^2}} \\ &= \sqrt{RG} + j\omega \sqrt{\frac{L}{R} \times C^2} \end{aligned}$$

$$\boxed{\alpha + j\beta = \sqrt{RG} + j\omega \sqrt{LC}}$$

$$\boxed{\alpha = \sqrt{RG} \quad \beta = \omega \sqrt{LC}}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{R(1 + j\omega L/R)}{G(1 + j\omega C/G)}}$$

use $\frac{C}{G} = \frac{L}{R}$

$$\boxed{Z_0 = \sqrt{\frac{R}{G}}}$$

$$\frac{R}{G} = \frac{L}{C}$$

$$\boxed{Z_0 = \sqrt{\frac{L}{C}}}$$

$$V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \boxed{\frac{1}{\sqrt{LC}}} = V_p$$

$$\alpha Z_0 = \sqrt{RG} \times \sqrt{\frac{L}{C}} = \sqrt{RG} \times \sqrt{\frac{R}{G}}$$

$$\boxed{\alpha Z_0 = R}$$

$$\frac{\alpha}{Z_0} = \sqrt{RG} \times \sqrt{\frac{C}{L}} = \sqrt{RG} \times \sqrt{\frac{G}{R}} = G$$

$$\boxed{\frac{\alpha}{Z_0} = G}$$

$$\beta Z_0 = \omega \sqrt{LC} \times \sqrt{\frac{L}{C}} = \omega L = \beta Z_0$$

$$\boxed{1 = \frac{\beta Z_0}{\omega L}}$$

$$\frac{\beta}{Z_0} = \omega \sqrt{LC} \times \sqrt{\frac{C}{L}} = \omega C$$

$$\boxed{C = \frac{\beta}{Z_0 \omega}}$$

lossless

$$\alpha = 0$$

distortionless

$$\alpha = \sqrt{RG}$$

Low-loss Tx line

Condition: $R \ll j\omega L$
 $G \ll j\omega C$

$$\Rightarrow RG \ll j^2 \omega^2 LC$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\begin{aligned} \alpha + j\beta &= \sqrt{j\omega L (1 + R/j\omega L)} \sqrt{j\omega C (1 + G/j\omega C)} \\ &= j\omega \sqrt{LC} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{1/2} \\ &= j\omega \sqrt{LC} \left(1 - \frac{R}{\omega L}\right)^{1/2} \left(1 - \frac{G}{\omega C}\right)^{1/2} \end{aligned}$$

use $\boxed{(1+x)^n = 1+nx}$ $x \ll 1$

$$\begin{aligned} \alpha + j\beta &= j\omega \sqrt{LC} \left(1 - \frac{jR}{2\omega L}\right) \left(1 - \frac{jG}{2\omega C}\right) \\ \alpha + j\beta &= j\omega \sqrt{LC} \left(1 - \frac{jR}{2\omega L} - \frac{jG}{2\omega C} - \frac{RG}{4\omega^2 LC}\right) \end{aligned}$$

$$\begin{aligned} \alpha + j\beta &= j\omega \sqrt{LC} \left(1 - \frac{jR}{2\omega L} - \frac{jG}{2\omega C}\right) \\ &= j\omega \sqrt{LC} + \frac{R\sqrt{LC}}{2\omega L} + \frac{G\sqrt{LC}}{2\omega C} \\ &= j\omega \sqrt{LC} + \frac{R}{2}\sqrt{\frac{C}{L}} + \frac{G}{2}\sqrt{\frac{L}{C}} \end{aligned}$$

Comparing $\boxed{\alpha = \frac{R}{2}\sqrt{\frac{C}{L}} + \frac{G}{2}\sqrt{\frac{L}{C}}}$ $\boxed{\beta = \omega \sqrt{LC}}$

$$V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} \quad \boxed{V_p = \frac{1}{\sqrt{LC}}}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{j\omega L (1 + R/j\omega L)}{j\omega C (1 + G/j\omega C)}}$$

$$Z_0 = \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{1/2}$$

$$= \sqrt{\frac{L}{C}} \left(1 - \frac{Rj}{\omega L}\right)^{1/2} \left(1 - \frac{Gj}{\omega C}\right)^{1/2}$$

$$= \sqrt{\frac{L}{C}} \left(1 - \frac{Rj}{2\omega L}\right) \left(1 - \frac{Gj}{2\omega C}\right)$$

$$= \sqrt{\frac{L}{C}} \left(1 - \frac{Rj}{2\omega L} - \frac{Gj}{2\omega C} + \frac{RG}{4\omega^2 LC}\right) \approx 0$$

$$Z_0 = \underbrace{\sqrt{\frac{L}{C}}}_{\text{real}} - \underbrace{\frac{R}{2\omega L}\sqrt{\frac{L}{C}} + \frac{G}{2\omega C}\sqrt{\frac{L}{C}}}_{\text{img.}}$$

if Z_0 is real, $\text{img}(Z_0) = 0$.

$$\frac{G}{2\omega C}\sqrt{\frac{L}{C}} = \frac{R}{2\omega L}\sqrt{\frac{L}{C}}$$

$$\boxed{\frac{G}{C} = \frac{R}{L}} \Rightarrow \text{Distortionless.}$$

Z_0 is given & real $\Rightarrow T_x$ is $\frac{1}{2}$

Problem 1

$L, C = ?$

1. Air medium, $Z_0 = 50 \Omega$, $\beta = 3 \text{ rad/m}$ at 150 MHz .

Ans $\hookrightarrow$ lossless

$$R = G = 0.$$

$$Z_0 = 50$$

$$\beta = 3 \text{ rad/m}^{-1}$$

$$f = 150 \text{ MHz} \Rightarrow \omega = 2\pi f$$

$$L = \frac{\beta Z_0}{\omega} = \frac{3 \times 50}{2\pi \times 150 \times 10^6} = \frac{1}{2\pi} \times 10^{-6} \text{ H/m}$$

$$C = \frac{\omega}{\beta Z_0} = \frac{2\pi \times 150 \times 10^6}{3 \times 50} = \frac{10^{-6}}{2500\pi} \text{ F/m}$$

② $f = 600 \text{ MHz}$ $Z_0 = 50 \Omega$ $\alpha = 0.04$
 $\rho = 2 \text{ rad/m}$ find R, L, C .

Ans $Z_0 = 50 \Omega$ (Real)

$\Rightarrow$ Distortionless.

$$\frac{R}{L} = \frac{G}{C}$$

$$\alpha = \sqrt{RG} \quad Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$$

$$R = \alpha^2 Z_0 = 0.04 \times 50$$


$$R = 2 \Omega/\text{m}$$

$$G = \frac{\alpha}{Z_0} = \frac{0.04}{50} = 0.0008 \text{ S/m}$$

$$L = \frac{R Z_0}{\omega} = \frac{2 \times 50}{2\pi \times 600 \times 10^6} \text{ H/m}$$

$$C = \frac{G}{\omega} = \frac{0.0008}{2\pi \times 600 \times 10^6} \text{ F/m}$$

Reflection Co-eff

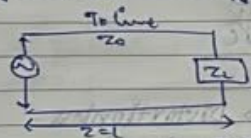

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I_s(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

at $z=0$,

$$V_s(0) = V_0^+ + V_0^-$$

$$I_s(0) = I_0^+ + I_0^-$$

$$Z_L = \frac{V(z=0)}{I(z=0)} = \frac{V_0^+ + V_0^-}{I_0^+ + I_0^-}$$

$$\text{use } Z_0 = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-}$$

$$I_0^+ = \frac{V_0^+}{Z_0}, \quad I_0^- = -\frac{V_0^-}{Z_0}$$

$$Z_L = \frac{V_0^+ + V_0^-}{\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}} = \frac{(V_0^+ + V_0^-) \cdot Z_0}{(V_0^+ - V_0^-)}$$

$$= \frac{V_0^+ (1 + V_0^-/V_0^+)}{V_0^+ (1 - V_0^-/V_0^+)} = \frac{1 + \Gamma}{1 - \Gamma} Z_0$$

where $\Gamma = \frac{V_0^-}{V_0^+}$ ← ref. coeff

$$Z_L = \left(\frac{1 + \Gamma}{1 - \Gamma} \right) Z_0$$

$$Z_L - Z_0 = \Gamma (Z_0 + Z_L)$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

if $Z_L = Z_0$
 $\Rightarrow \Gamma = 0$
 else $0 \leq \Gamma \leq 1$

Transmission Co-eff (T)

$$T = \frac{V_0^-}{V_0^+}$$

$$T + \Gamma = 1$$

$$T = \frac{2 Z_L}{Z_L + Z_0}$$

Voltage Standing Wave Ratio (VSWR)

VSWR $\rightarrow$ S.

$$S = \frac{V_{\max}}{V_{\min}} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} = \frac{1 + \Gamma}{1 - \Gamma}$$

$$S = \frac{V_0^+ (1 + \Gamma/V)}{V_0^+ (1 - \Gamma/V)}$$

WKT, $\frac{V}{V_0} = \Gamma$

$S = \frac{1+\Gamma}{1-\Gamma}$

if $\Gamma = 0$, $S = 1$.

if $\Gamma = 1$, $S = \infty$

$1 \leq S < \infty$

$Z_{max} = \frac{V_{max}}{I_{min}}$

$= \frac{V_{max}}{I_{min}} \times \frac{V_{min}}{V_{min}}$


$Z_{max} = S Z_0$

$Z_{min} = \frac{V_{min}}{I_{max}}$

$= \frac{V_{min}}{I_{max}} \times \frac{V_{max}}{V_{max}}$

$Z_{min} = \frac{1}{S} Z_0$

Input Impedance

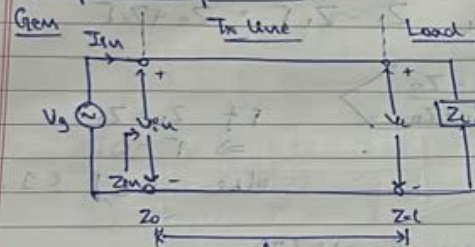

$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$

$I_s(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$

$V_0^+ = Z_0 I_0^+ \quad -V_0^- = Z_0 I_0^-$

$\frac{V_0^+}{Z_0} = I_0^+ \quad \frac{-V_0^-}{Z_0} = I_0^-$

At $z=l$

$V_l(z=l) = V_0^+ e^{-\gamma l} + V_0^- e^{\gamma l} = V_L$

$I_l(z=l) = I_0^+ e^{-\gamma l} + I_0^- e^{\gamma l} = I_L$
 $= \frac{V_0^+}{Z_0} e^{-\gamma l} - \frac{V_0^-}{Z_0} e^{\gamma l} = I_L$

$I_L Z_0 = V_0^+ e^{-\gamma l} - V_0^- e^{\gamma l}$

① + ②

$2V_0^+ e^{-\gamma l} = V_L + I_L Z_0$

$2V_0^+ e^{-\gamma l} = I_L Z_L + I_L Z_0$

$V_0^+ = \frac{(I_L Z_L + I_L Z_0) e^{\gamma l}}{2}$

① - ②

$2V_0^- e^{\gamma l} = V_L - I_L Z_0$

$2V_0^- e^{\gamma l} = I_L Z_L - I_L Z_0$

$V_0^- = \frac{(I_L Z_L - I_L Z_0) e^{-\gamma l}}{2}$

At $z=0$,

$V_s(0) = V_0^+ + V_0^-$

$I_s(0) = I_0^+ + I_0^- = \frac{V_0^+ - V_0^-}{Z_0}$

$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_s(0)}{I_s(0)} = \frac{(V_0^+ + V_0^-) \cdot Z_0}{(V_0^+ - V_0^-)}$
 $= Z_0 \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right)$

$Z_{in} = Z_0 \left\{ \frac{\left(\frac{I_L Z_L + I_L Z_0}{2} \right) e^{\gamma l} + \left(\frac{I_L Z_L - I_L Z_0}{2} \right) e^{-\gamma l}}{\left(\frac{I_L Z_L + I_L Z_0}{2} \right) e^{\gamma l} - \left(\frac{I_L Z_L - I_L Z_0}{2} \right) e^{-\gamma l}} \right\}$

$Z_{in} = \left\{ \frac{Z_L e^{\gamma l} + Z_0 e^{\gamma l} + Z_L e^{-\gamma l} - Z_0 e^{-\gamma l}}{Z_L e^{\gamma l} + Z_0 e^{\gamma l} - Z_L e^{-\gamma l} + Z_0 e^{-\gamma l}} \right\} Z_0$
 (Common terms cancel)

$Z_{in} = Z_0 \left\{ \frac{Z_L \left(\frac{e^{\gamma l} + e^{-\gamma l}}{2} \right) + Z_0 \left(\frac{e^{\gamma l} - e^{-\gamma l}}{2} \right)}{Z_L \left(\frac{e^{\gamma l} - e^{-\gamma l}}{2} \right) + Z_0 \left(\frac{e^{\gamma l} + e^{-\gamma l}}{2} \right)} \right\}$

$Z_{in} = Z_0 \left\{ \frac{Z_L \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_L \sinh \gamma l} \right\}$
 Take $\cosh \gamma l$ common

$$Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \right]$$

For lossless,

$$\gamma = \alpha + j\beta$$

$$\gamma = j\beta$$

$$\alpha = 0$$

$$\tanh \gamma l = \frac{(e^{\gamma l} - e^{-\gamma l})}{2}$$

$$\frac{(e^{\gamma l} + e^{-\gamma l})}{2}$$

$$= j \frac{(e^{j\beta l} - e^{-j\beta l})}{2j}$$

$$\frac{(e^{j\beta l} + e^{-j\beta l})}{2}$$

$$= j \frac{\sin \beta l}{\cos \beta l} = j \tan \beta l$$

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

βl = Electrical length. (rad).

(i) If $l = \frac{\lambda}{8}$, $Z_{in} = ?$

$$\beta = \frac{2\pi}{\lambda} \Rightarrow \frac{2\pi}{\lambda} \times \frac{\lambda}{8} = \frac{\pi}{4}$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{8} = \frac{\pi}{4}$$

$$\tan \beta l = 1$$

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0}{Z_0 + j Z_L} \right]$$

$$x = a + jb$$

$$|x| = \sqrt{a^2 + b^2}$$

$$|Z_{in}| = Z_0 \left[\frac{\sqrt{Z_L^2 + Z_0^2}}{\sqrt{Z_0^2 + Z_L^2}} \right]$$

$$|Z_{in}| = Z_0$$

$$l = \frac{\lambda}{4}$$

(ii) $l = \lambda/4$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} = \frac{\pi}{2}$$

$$\tan \beta l = \infty$$

$$Z_{in} = Z_0 \left[\frac{\tan \beta l \left(\frac{Z_L}{\tan \beta l} + j Z_0 \right)}{\tan \beta l \left(\frac{Z_0}{\tan \beta l} + j Z_L \right)} \right]$$

$$Z_{in} = Z_0 \left[\frac{j Z_0}{j Z_L} \right] = \frac{Z_0^2}{Z_L}$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_{in} \propto \frac{1}{Z_L}$$

if $Z_L = \infty \Rightarrow Z_{in} = 0$
(open circuit)

if $Z_L = 0 \Rightarrow Z_{in} = \infty$
(short circuit).

(iii) $l = \lambda/2 \Rightarrow \beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{2} = \pi \Rightarrow \tan \pi = 0$

$$Z_{in} = Z_0 \left[\frac{Z_L}{Z_0} \right]$$

$$Z_{in} = Z_L$$

iv for matched load
 $Z_L = Z_0$

$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$$

$$Z_{in} = Z_0 \Rightarrow \Gamma = 0$$

SWR = absent.

v load imp is short circuit
 $Z_L = 0 \Omega$

$$Z_{in} = Z_0 \left[\frac{0 + jZ_0 \tan \beta l}{Z_0 + 0} \right]$$

$$Z_{in} = jZ_0 \tan \beta l$$

$$Z_{sc} = jZ_0 \tan \beta l$$

$$\rightarrow 0 < l < \lambda/4$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4}$$

$$0 < \beta l < \frac{\pi}{2}$$

$$\tan \beta l = +ve.$$

$$\tan \beta l = +k.$$

$$Z_{sc} = jZ_0 k \rightarrow \text{purely inductive. } (\because j \text{ is present})$$

$$\rightarrow \lambda/4 < l < \lambda/2$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{2}$$

$$\frac{\pi}{2} < \beta l < \pi$$

$$\tan \beta l = -ve \quad \tan \beta l = -k.$$

$$Z_{sc} = -jZ_0 k \rightarrow \text{purely capacitive } (\because j \text{ is present})$$

$$\rightarrow \lambda/2 < l < 3\lambda/4$$

$$\pi < \beta l < 3\pi/2$$

$$\tan \beta l = +ve$$

$$Z_{sc} = jZ_0 k \rightarrow \text{Inductive}$$

$$\rightarrow \text{ully } 3\lambda/4 < l < \lambda$$

capacitive.

vi load imp is open circuit.

$$Z_L = \infty \Omega$$


$$Z_{in} = Z_0 \left[\frac{Z_L (1 + jZ_0 \tan \beta l)}{Z_0 + jZ_L \tan \beta l} \right]$$

$$= \frac{Z_0}{j \tan \beta l}$$

$$Z_{in} = -jZ_0 \cot \beta l$$

$$Z_{oc} = -jZ_0 \cot \beta l$$


Same cases as before.

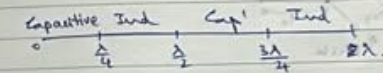

$$\% \text{ attenuation } d = \frac{up}{km} \text{ to dB, } d \times 8.686$$

Stub Matching

It is SC or OC in line.

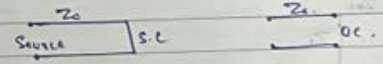

Why stub?


$$Z_L \neq Z_0 \rightarrow \text{reflection occurs.}$$

If $\Gamma > 0$, max power will not be transferred to load.


To match Z_L & Z_0 , we use stub in the line

- Series connection (2)
- Parallel connection (3).


→ Open ckt series stub

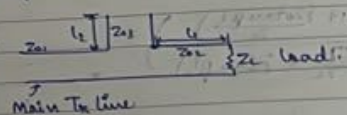


→ Open ckt parallel stub

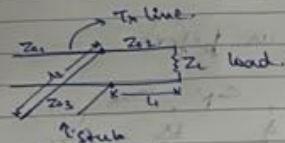

→ Short ckt series stub

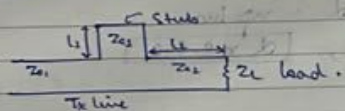


→ Short ckt parallel stub

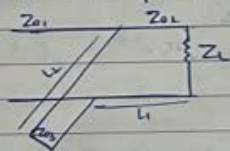


Short circuit stubs are better than open.

Types

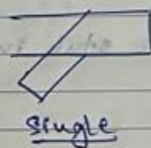

Single

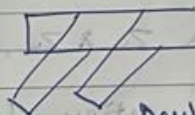

Double

Normalised load imp


$$\bar{Z}_L = \frac{Z_L}{Z_0}$$

Normalised input imp

$$\bar{Z}_{in} = \frac{Z_{in}}{Z_0}$$

SMITH CHART

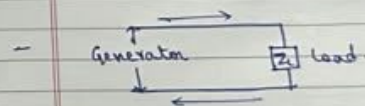- Graphical method.
- To find Γ , Z_{in} , VSWR, stub matching.
- Types: Constant resistance circle
Constant reactance circle
- Works on normalised imp.
- One complete circle = $\lambda/2$ distance.



load to generator: move clockwise.
generator to load: move anti-clock

